

# UESTC 3003: Electronic System Design

*Static Errors*

## Lecture 2.3: Bias Current Blues (1)


Dr Duncan Bremner

WORLD  
CHANGING  
GLASGOW


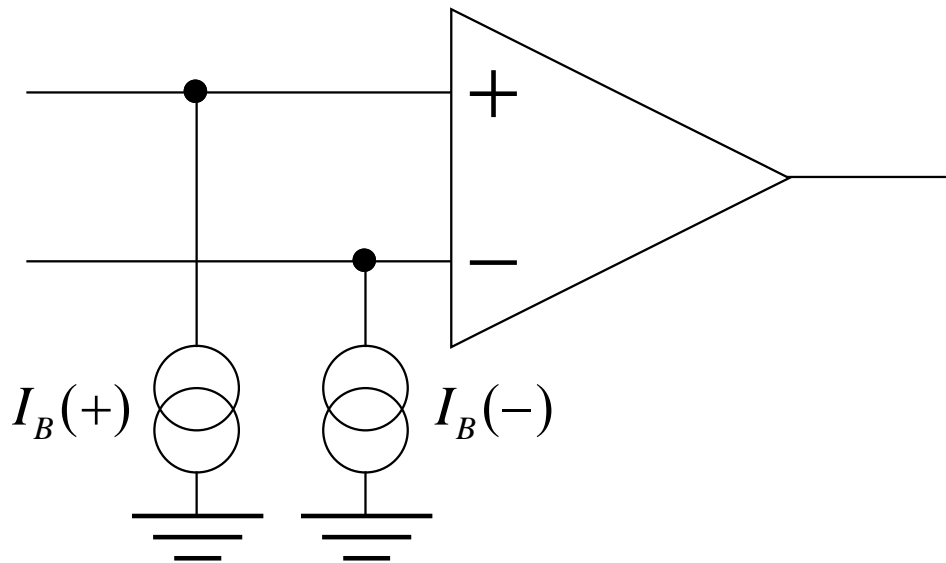
## Revision of previous section...

Perfect Opamp + Current sources  
= **model** of a real opamp




$$I_B(+)\approx I_B(-)$$

For **simple** opamp. (Not always)

$$I_B\equiv\frac{I_B(+)+I_B(-)}{2}\text{ (i.e. the average current)}$$


## Bias Current Blues

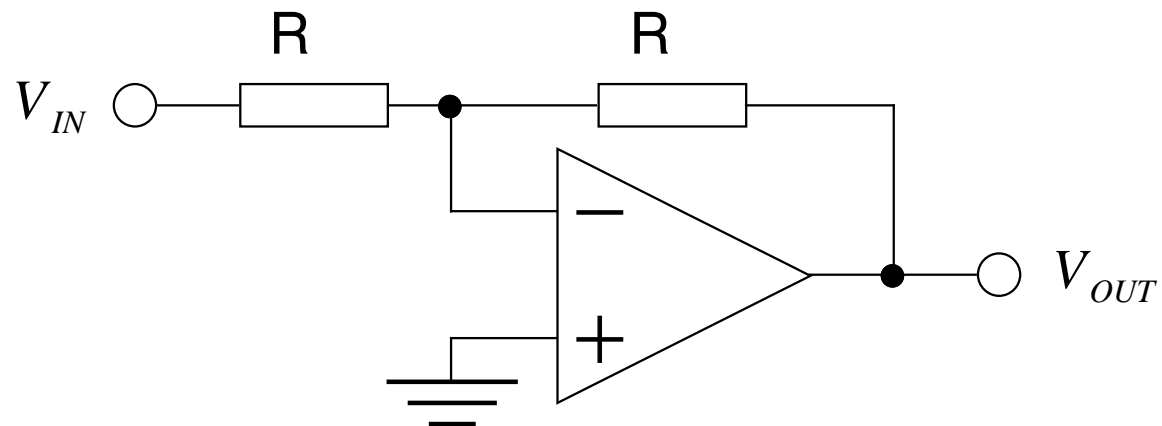

Perfect opamp  $V_{OUT} = -(V_{IN})$

Independent of the value of  $R$


## Bias current blues (2)

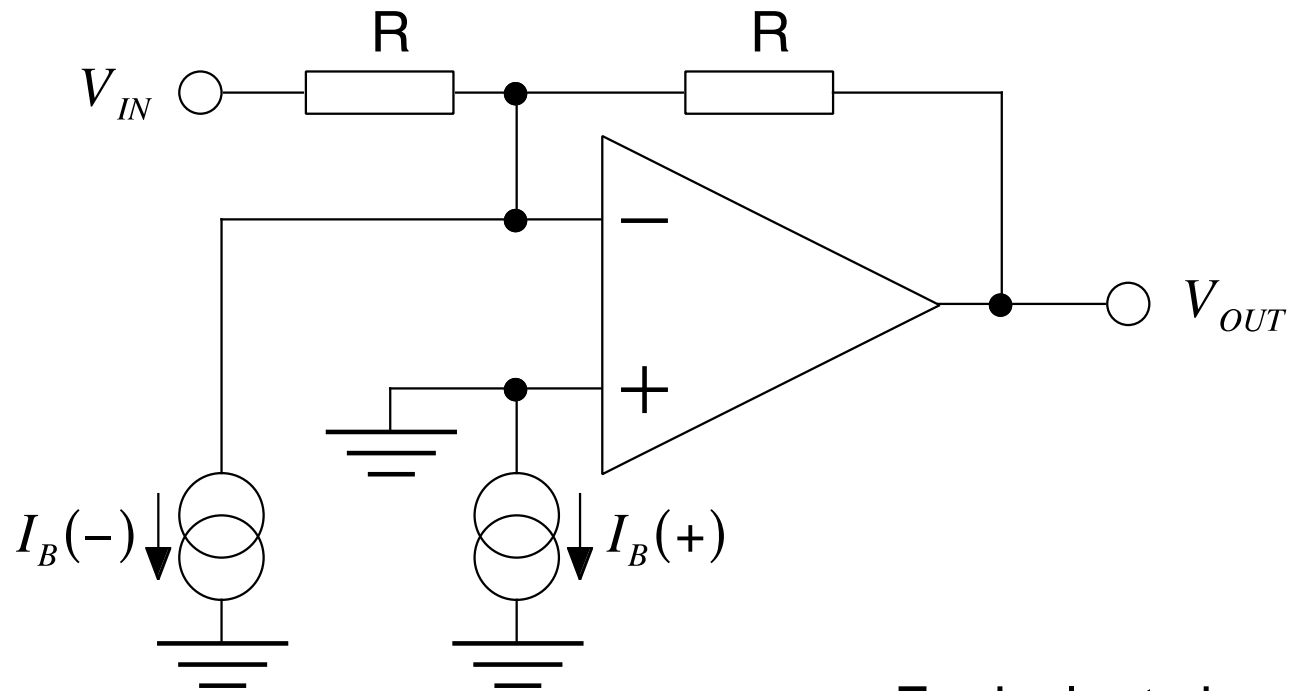

Equivalent circuit

NB: The triangular thing is still a **PERFECT OPAMP!**


## Bias Current Blues (3)

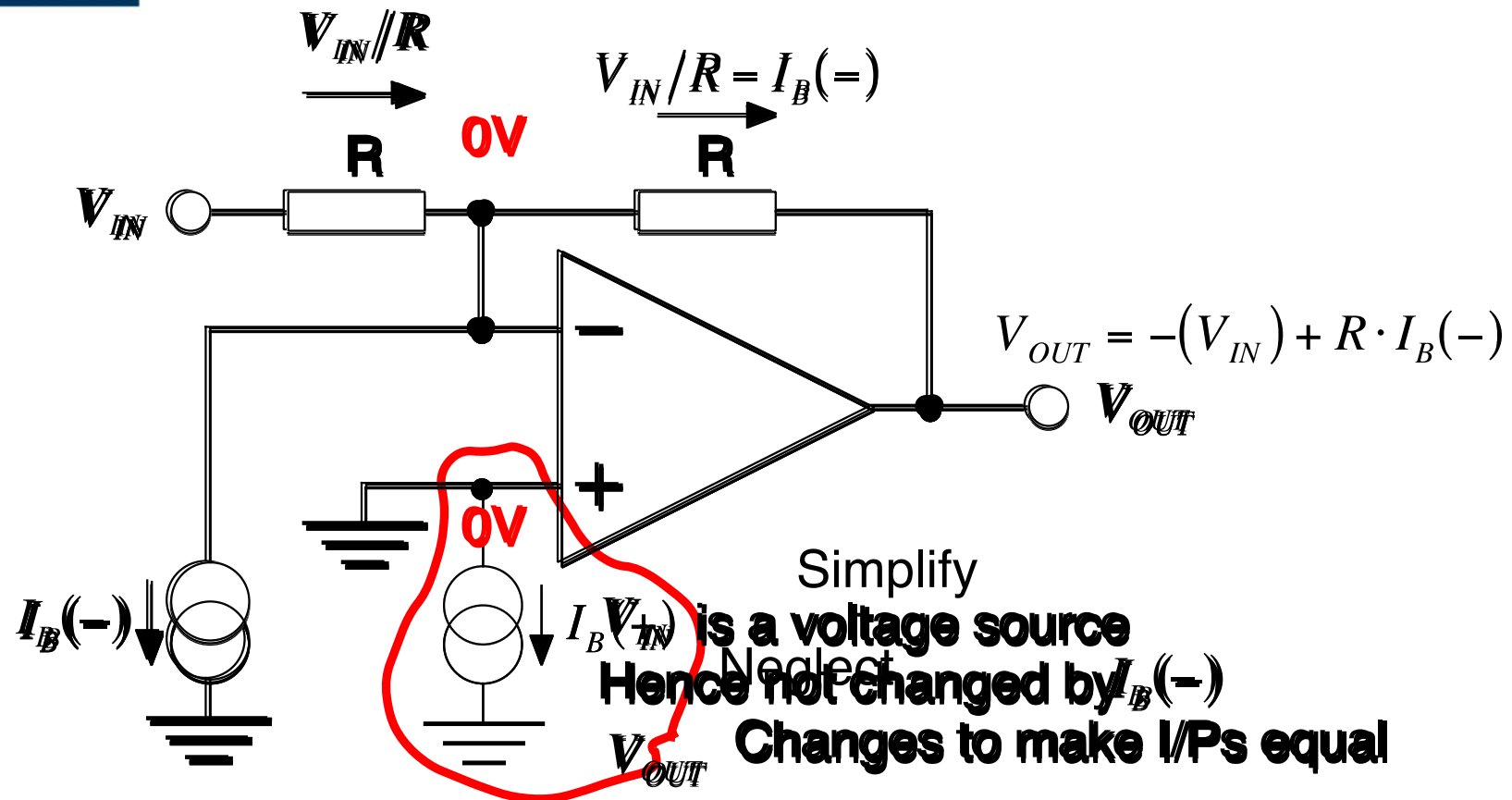

Bias current adds error V of  $R \cdot I_B(-)$  to O/P
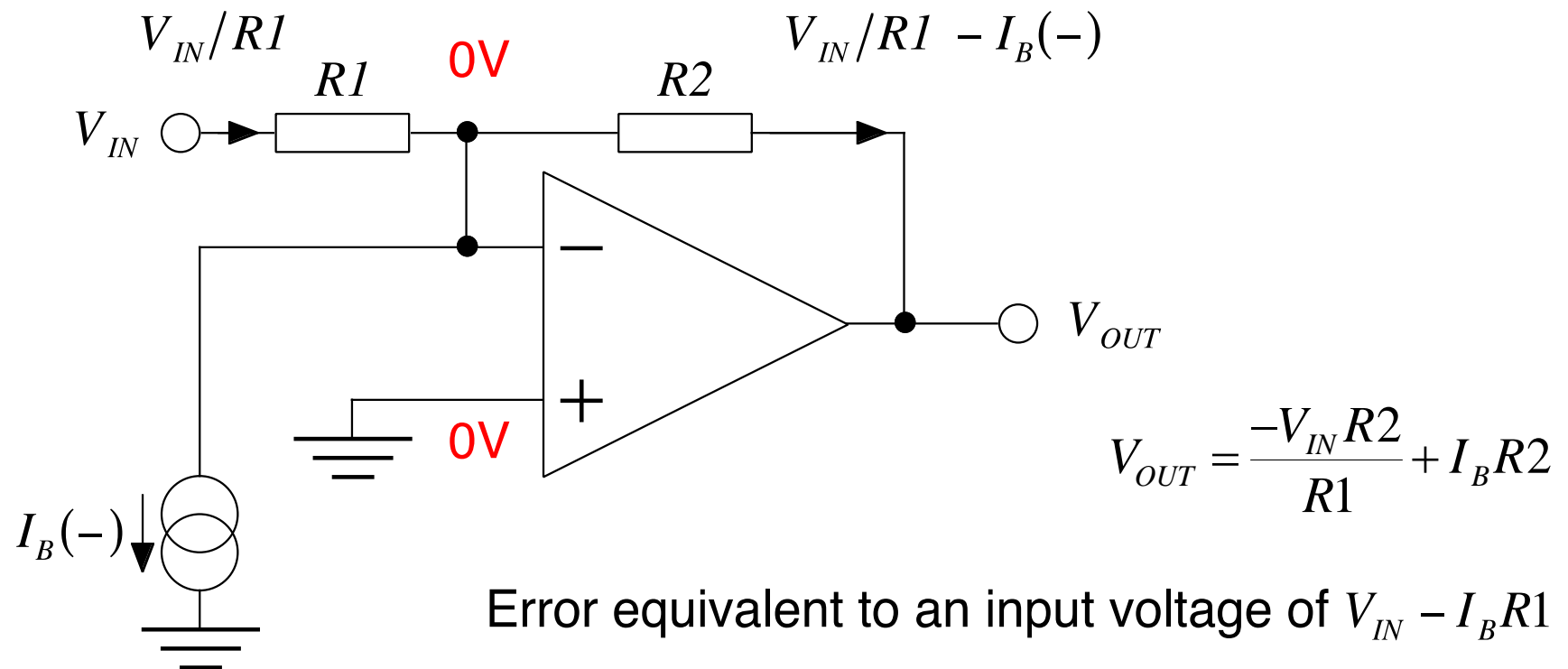
## Bias Current Blues (4)

In the case of an inverting amplifier with gain:




Errors may be quoted as “Referred To Output” (RTO)  $I_B R2$   
 or “Referred To Input” (RTI)  $-I_B R1$




## Bias Current Blues (5)


Circuit is equivalent to...

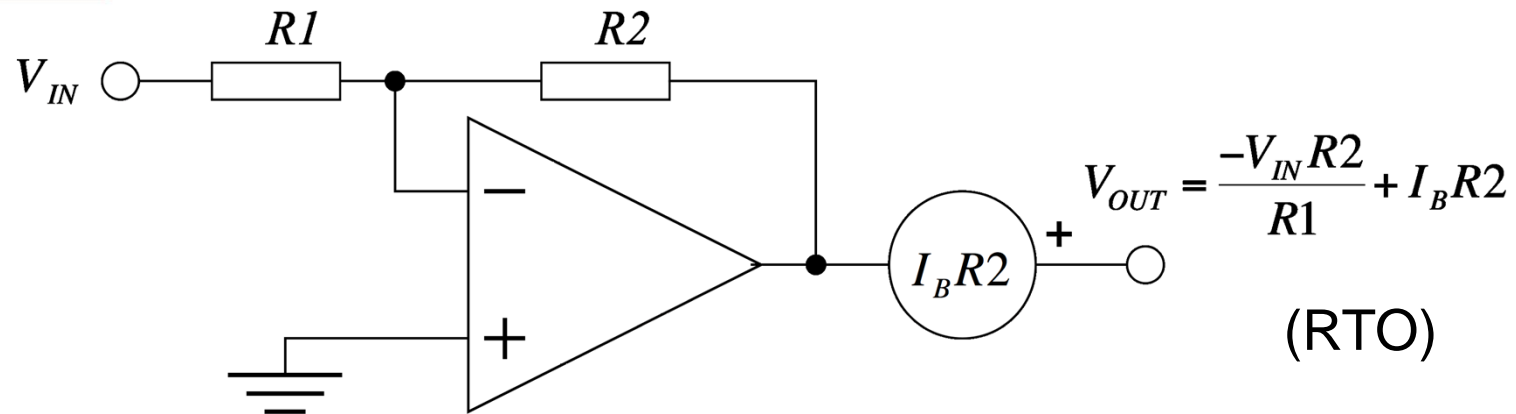

Also equivalent to...

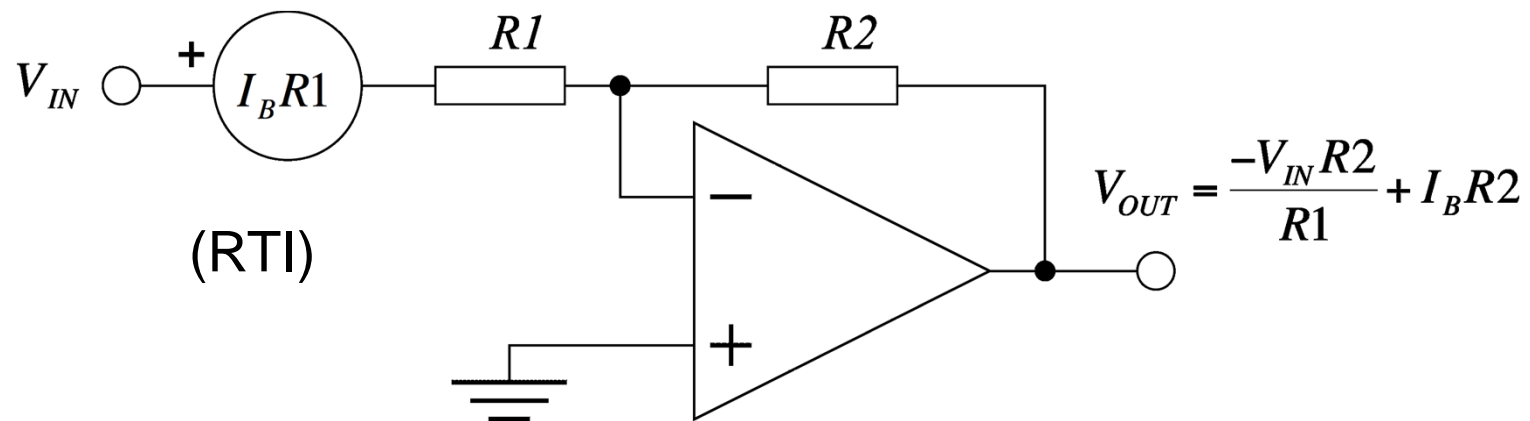
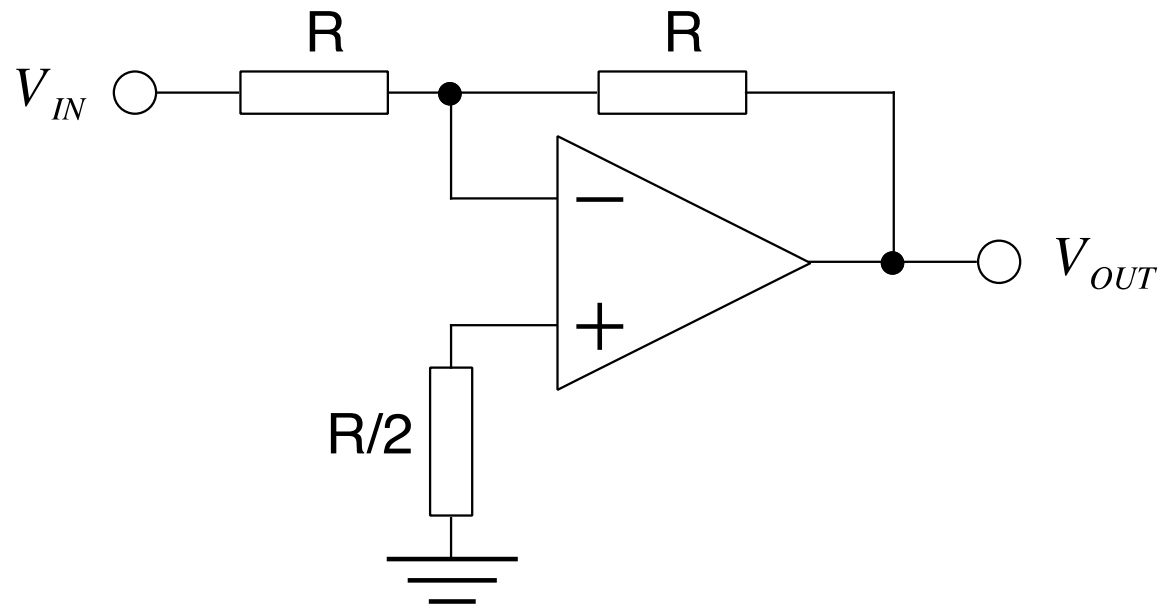
## A Cool Fix (If currents are **Equal**)



Make **DC** resistances equal at both inputs

(NOTE: Take care if there are inductors or capacitors about!)





University  
of Glasgow

Thank you  
谢谢

INSPIRING  
PEOPLE

#UofGWorldChangers



@UofGlasgow