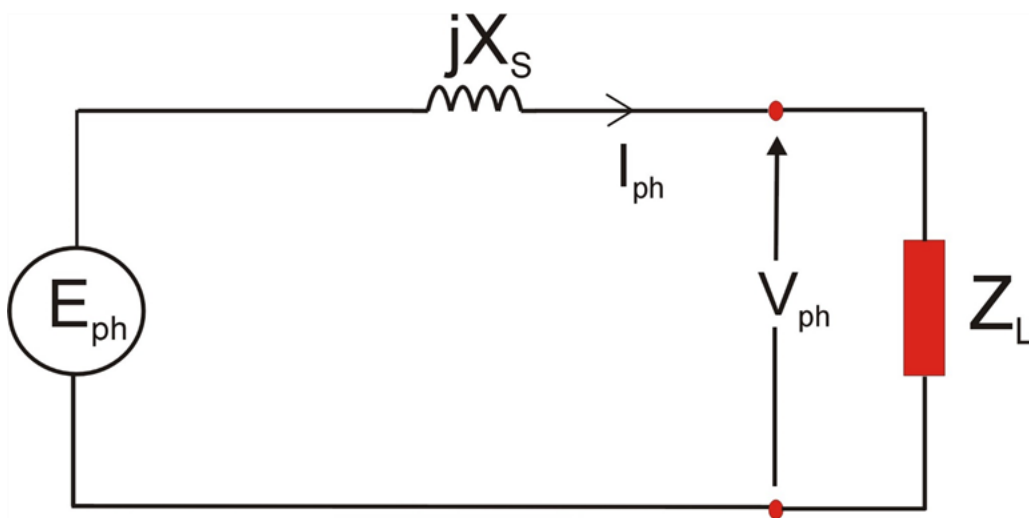


Examples Synchronous Generators


1. A star connected 3-phase wound field synchronous generator with a synchronous reactance X_s of 25Ω is connected to a 9kV (line) grid and supplies 1MW at 0.863 lagging power factor at its terminals. Evaluate the following:
 - a. The phase current.
 - b. The resultant voltage V_{xs} across the synchronous reactance.
 - c. The required excitation voltage (E_{ph}).
 - d. The load angle (δ).

Solution



For this question we need to consider the equivalent circuit

$$\begin{aligned}
 P_{out} &= 3 \times \frac{V_L}{\sqrt{3}} \times I_{ph} \times \text{power factor} \\
 &= \sqrt{3} \times |V_L| \times |I_{ph}| \times \text{power factor} \\
 \text{a. } \therefore |I_{ph}| &= \frac{1 \times 10^6}{\sqrt{3} \times 9000 \times 0.863} = 74.33 \text{ A} \\
 \text{so: } I_{ph} &= 74.33 \angle \cos^{-1} 0.863 = 74.33 \angle -30.34^\circ \text{ A} \\
 \text{b. } V_{xs} &= I_{ph} \times jX_s = 74.33 \angle -30.38^\circ \times 25 \angle 90^\circ \\
 &= 1858 \angle 59.66^\circ \text{ V}
 \end{aligned}$$

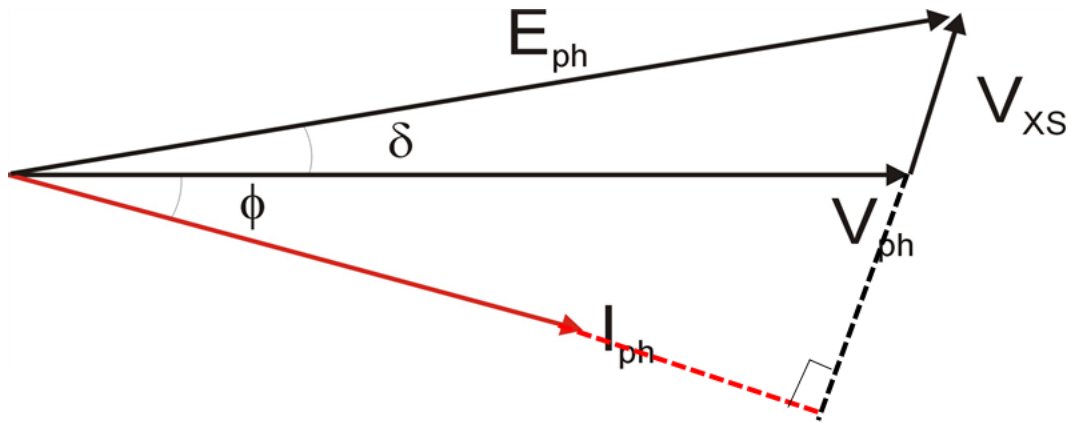

c.

$$\begin{aligned}
 E_{ph} &= V_{ph} + V_{xs} \\
 &= \frac{9000}{\sqrt{3}} + 1858 \angle 59.66^\circ = 6341 \angle 14.68^\circ V
 \end{aligned}$$

d. $\delta = 14.645^\circ$