



POWER ENGINEERING

#03 THREE-PHASE AC POWER SYSTEMS (1)

Semester 1 – 2021/2022



University
of Glasgow



电子科技大学

University of Electronic Science and Technology of China

Outline

- ❑ Benefits of three-phase power systems
- ❑ 3-phase generator: phase voltages and line voltages
- ❑ 3 Phase Transmission Lines
- ❑ **Balanced STAR** connected 3 phase RCL load
 - ❑ 3-phase 3-wire system
 - ❑ 3-phase 4-wire systems
- ❑ **Balanced DELTA** connected 3 phase RCL load
- ❑ Power Measurement
 - ❑ 3 Wattmeter Method
 - ❑ 2 Wattmeter Method
- ❑ Modern Digital Sampling Power Meters


BENEFITS OF THREE-PHASE POWER SYSTEMS

Three-phase power systems are the de facto standard in the industry.

- The 'workhorse' of industry; the 3 phase induction motor requires a 3 phase AC power supply
- A balanced 3 phase system will lead to **constant instantaneous power demand** on the generator – results in a smoother running generator
- A 3 phase generator has far better energy density compared to a single phase machine, hence it is smaller for a given output power (see next slides)
- The weight of the conductors and other components in a three-phase system is much lower than in a single-phase system delivering the same amount of power.



SINGLE PHASE AC GENERATOR

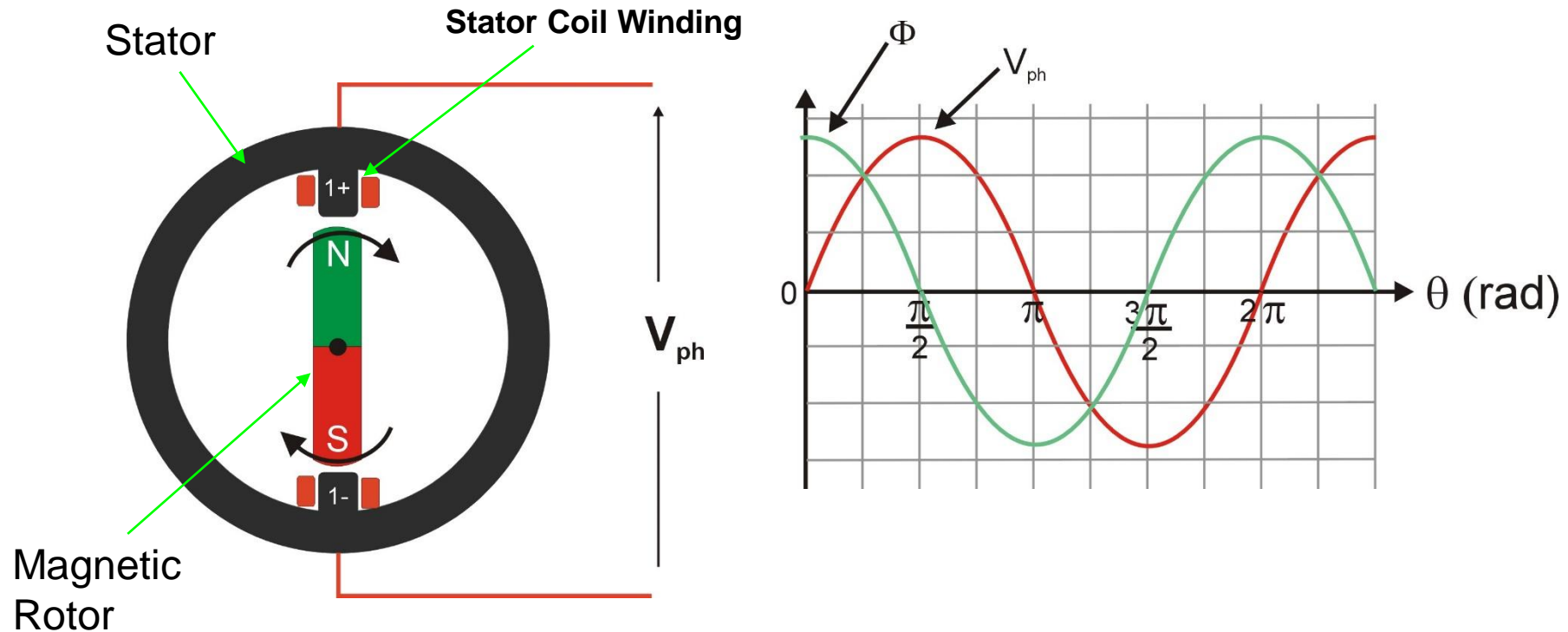


Voltage (V_{ph}) induced in Stator Winding Coils (1+, 1-) :


$$v_{ph} = \frac{N \cdot d\phi}{dt}$$

where N is the number of the stator coils turns and ϕ is the rotor magnet flux.

THREE PHASE AC GENERATOR

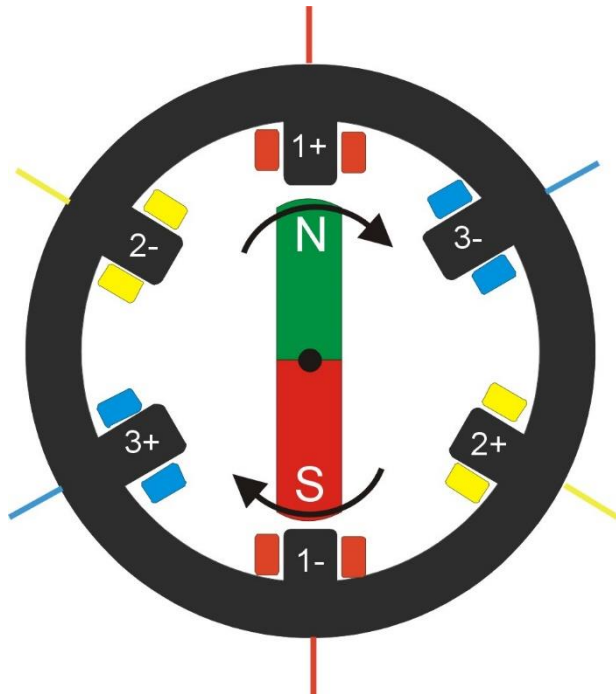


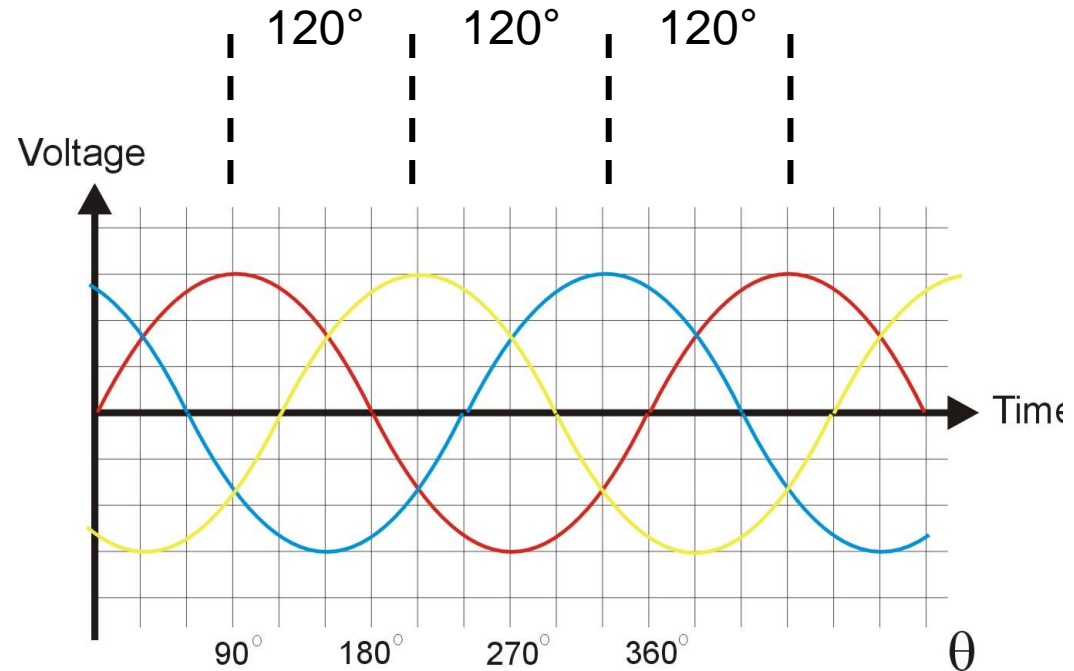**Now have 3 Phase windings
on the Stator 120° apart**



Countries use different conventions for naming the 3 PHASE voltages. We will adopt the (old!) UK convention of RED, YELLOW & BLUE PHASES

3-PHASE AC GENERATOR: PHASE VOLTAGES

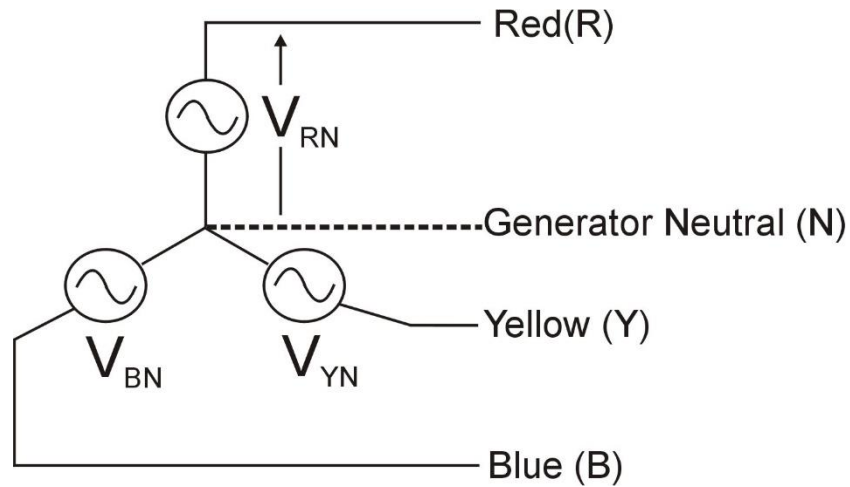


Phase Voltages

$$V_{RN} = V_{pk} \cos \theta$$

$$V_{YN} = V_{pk} \cos(\theta - 2\pi / 3)$$

$$V_{BN} = V_{pk} \cos(\theta + 2\pi / 3)$$

$$V_{RN} + V_{YN} + V_{BN} = 0$$

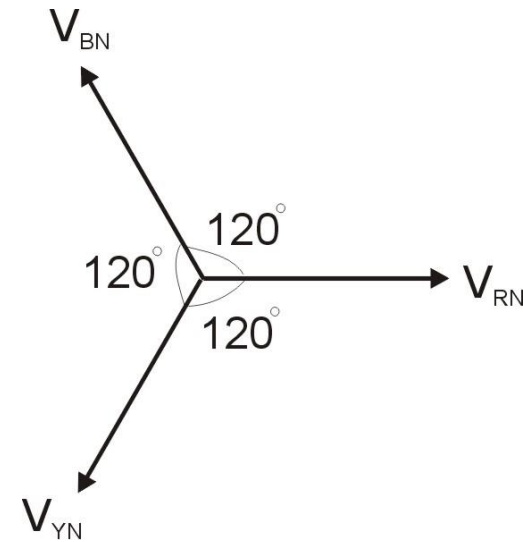

Phasor Diagram

Complex Form (Polar):


$$V_{RN} = V_{ph} \angle 0^\circ$$

$$V_{YN} = V_{ph} \angle -120^\circ$$

$$V_{BN} = V_{ph} \angle 120^\circ$$

Note: all 3 Phase Voltages have the same rms magnitude V_{ph}

3-PHASE AC GENERATOR: LINE VOLTAGES

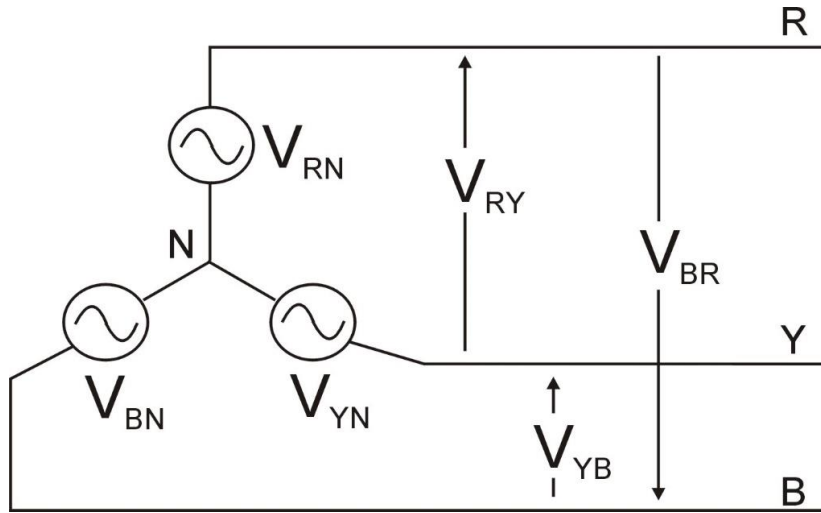


Phase and Line Voltages

$$V_{RY} = V_{RN} + V_{NY} = V_{RN} - V_{YN}$$

$$V_{BR} = V_{RN} + V_{NB} = V_{RN} - V_{BN}$$
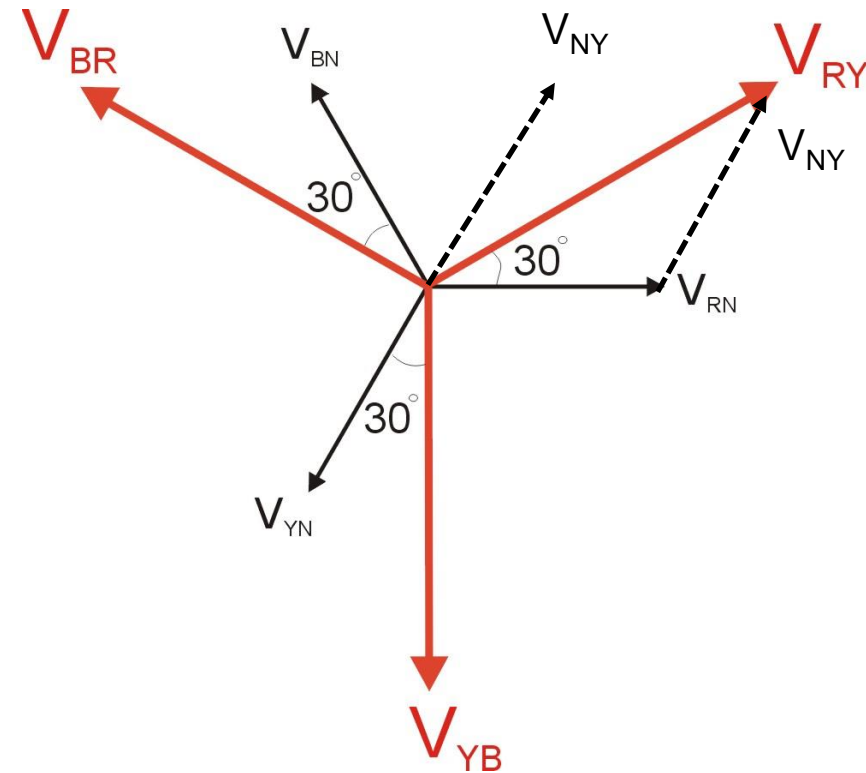
$$V_{YB} = V_{YN} + V_{NB} = V_{YN} - V_{BN}$$




Phasor Diagram

$$V_{RY} = \sqrt{3} \cdot V_{ph} \angle 30^\circ \quad V_{BR} = \sqrt{3} \cdot V_{ph} \angle 150^\circ \quad V_{YB} = \sqrt{3} \cdot V_{ph} \angle -90^\circ$$

3-PHASE TRANSMISSION LINES

ANATOMY OF A PYLON

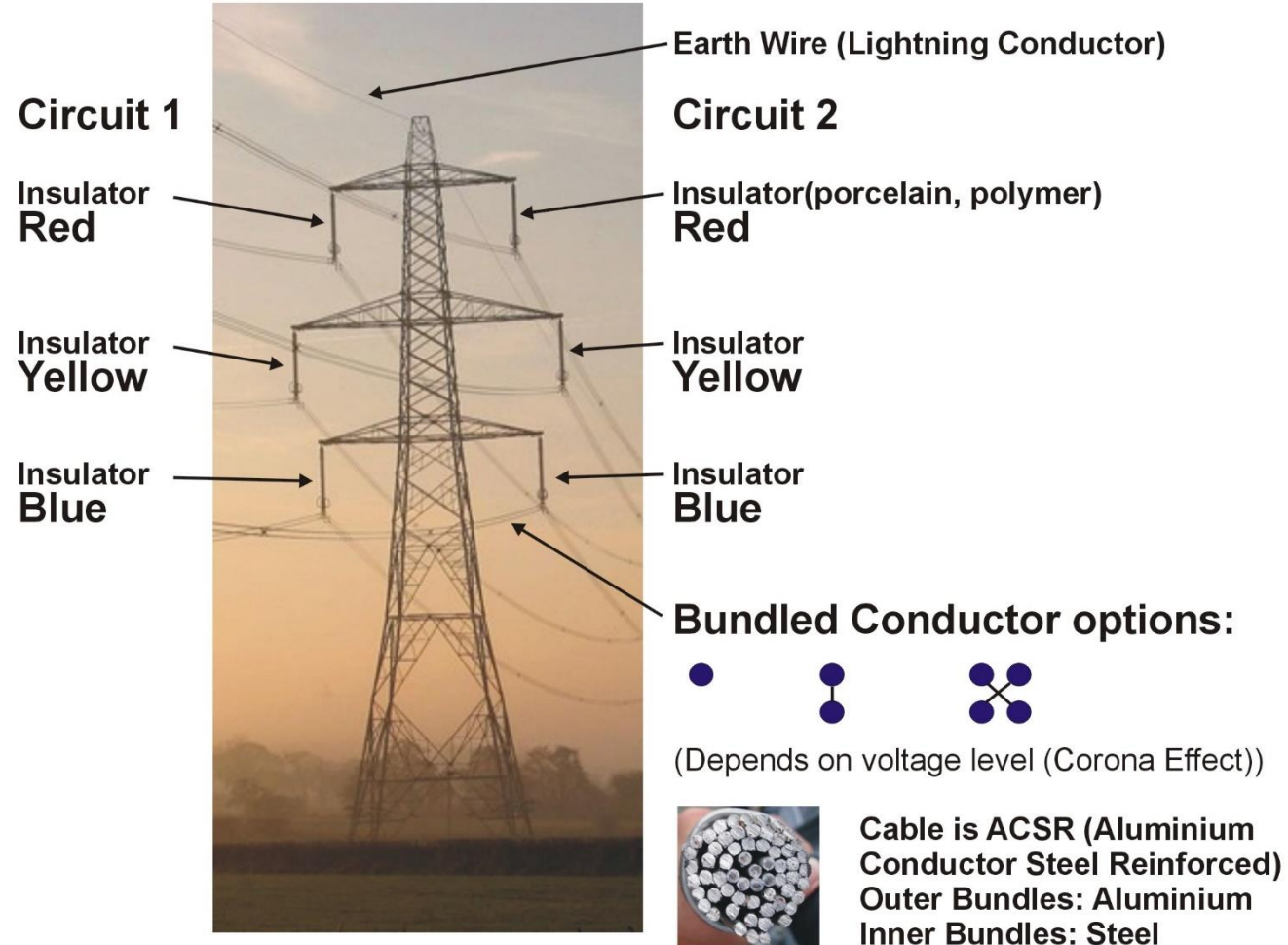


If you want to find out more about pylons then check out the Pylon Appreciation Society at <http://www.pylons.org/>

3-PHASE TRANSMISSION LINES

Some interesting facts!


- The 'standard' UK pylon was chosen by Sir Reginald Blomfield (a leading architect) in 1928
- The tallest pylon in the world is in China. The Yangtze River crossing pylon is 346.5m high
- The Beauly-Denny transmission line upgrade in Scotland consists of 600 towers with an average height of 53m
- The UK National Grid is made up of 440kV, 275kV, 132kV, 110kV, 33kV and 11kV transmission lines

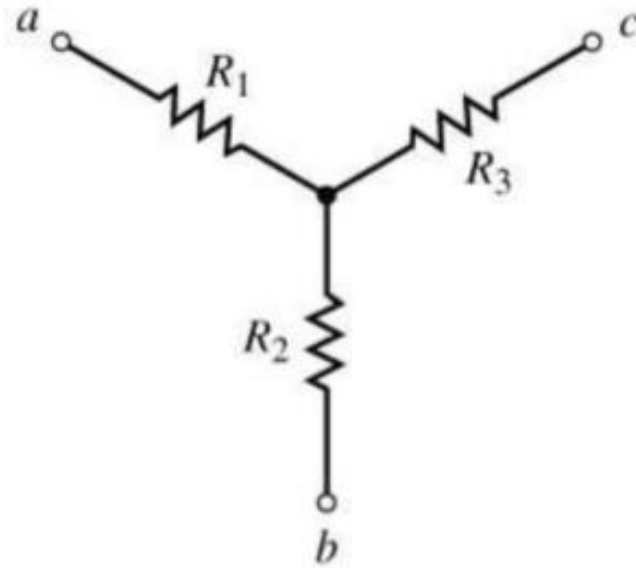- AC three-phase generators can be connected in multiple configurations. The first we will discuss is the **Y-Connected Generator**...



Wye (Y)

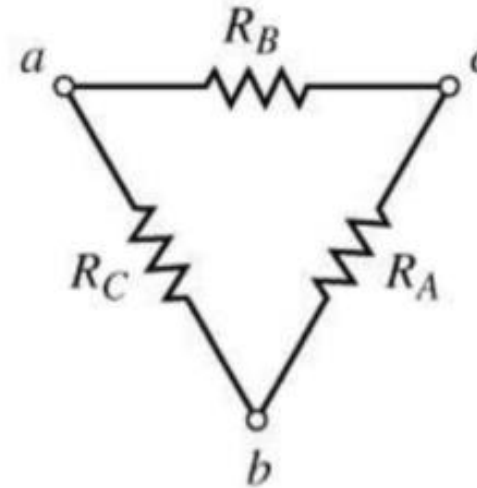
Has a grounding advantage
for varying loads




Delta (Δ)

Advantage for dedicated loads
where grounding not as important

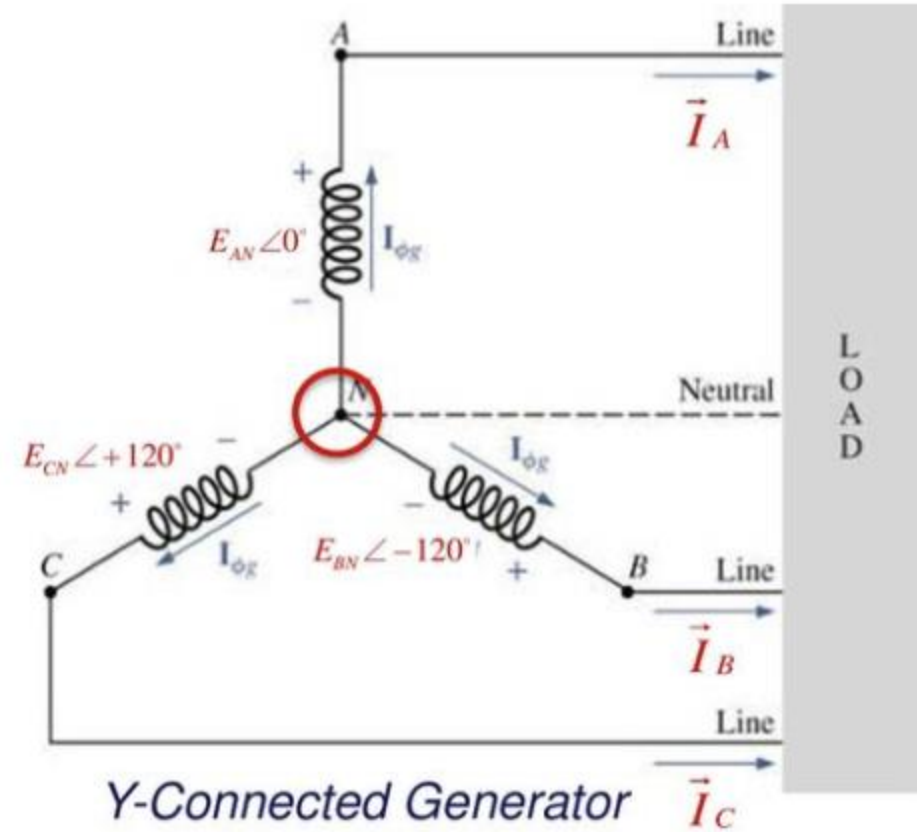- If the three phase terminals are connected together at N , the generator is referred to as a **Y-connected three-phase generator**.
- Note that the negative (-) terminals are connected together at N , which is the *neutral*.
- The three phase Y generator is connected to the load via the three lines labeled with a corresponding phasor current (I_A , I_B and I_C).



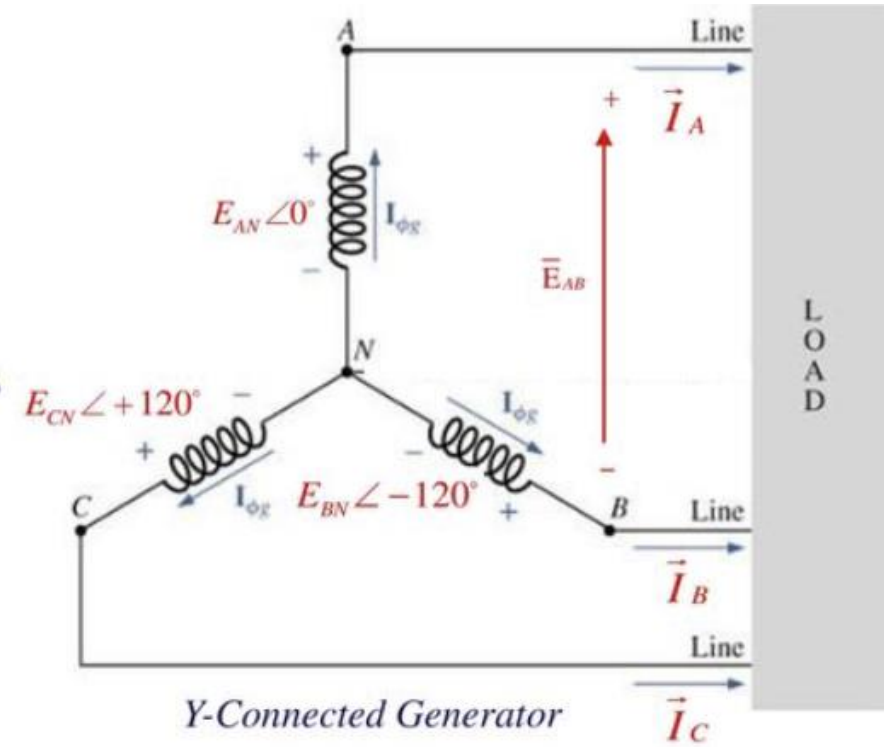- However, the phase for E_{AN} is rarely fixed at zero. So for any θ relationship it can be shown that for a balanced Y-Connected Generator the magnitude of line-to-line voltage is $1.732 (\sqrt{3})$ times the magnitude of the phase voltage.
- Line to line voltage leads the phase voltage by 30° .



Phase Voltages

$$\bar{E}_{AN} = E \angle (\theta + 0^\circ)$$

$$\bar{E}_{BN} = E \angle (\theta - 120^\circ)$$

$$\bar{E}_{CN} = E \angle (\theta + 120^\circ)$$

Line Voltages


$$\bar{E}_{AB} = \sqrt{3}E \angle (30^\circ + \theta)$$

$$\bar{E}_{BC} = \sqrt{3}E \angle (-90^\circ + \theta)$$

$$\bar{E}_{CA} = \sqrt{3}E \angle (150^\circ + \theta)$$

BALANCED STAR connected load:

3-PHASE 3-WIRE SYSTEM

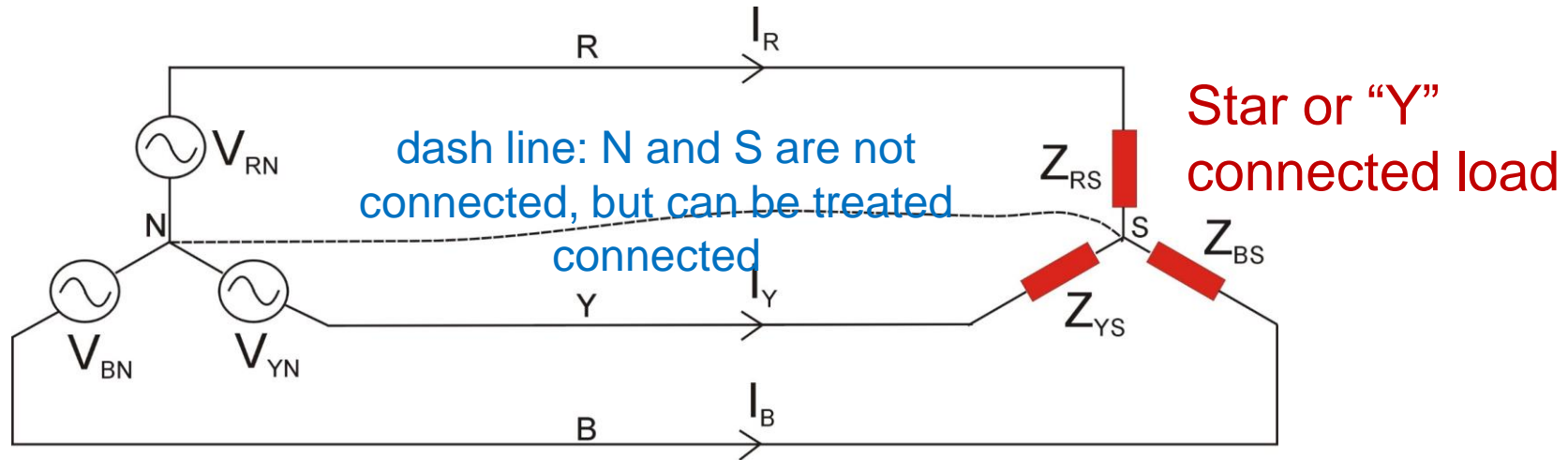

1. **'Balanced'** means that the load Impedances are equal:
 $Z_{RS} = Z_{YS} = Z_{BS}$
2. I_R , I_Y and I_B are termed the **LINE** currents, and **are 120° apart and equal in magnitude**.
3. If the load is balanced, then the load **STAR** point (**S**) is at the same voltage as the Generator Neutral (**N**): $V_{SN} = 0$


$$I_R = \frac{V_{RN}}{Z_{RS}} = I_L \angle -\phi$$

$$I_B = \frac{V_{BN}}{Z_{BS}} = I_L \angle -\phi + 120^\circ$$

$$I_Y = \frac{V_{YN}}{Z_{YS}} = I_L \angle -\phi - 120^\circ$$

BALANCED STAR connected load:

3-PHASE 4-WIRE SYSTEM

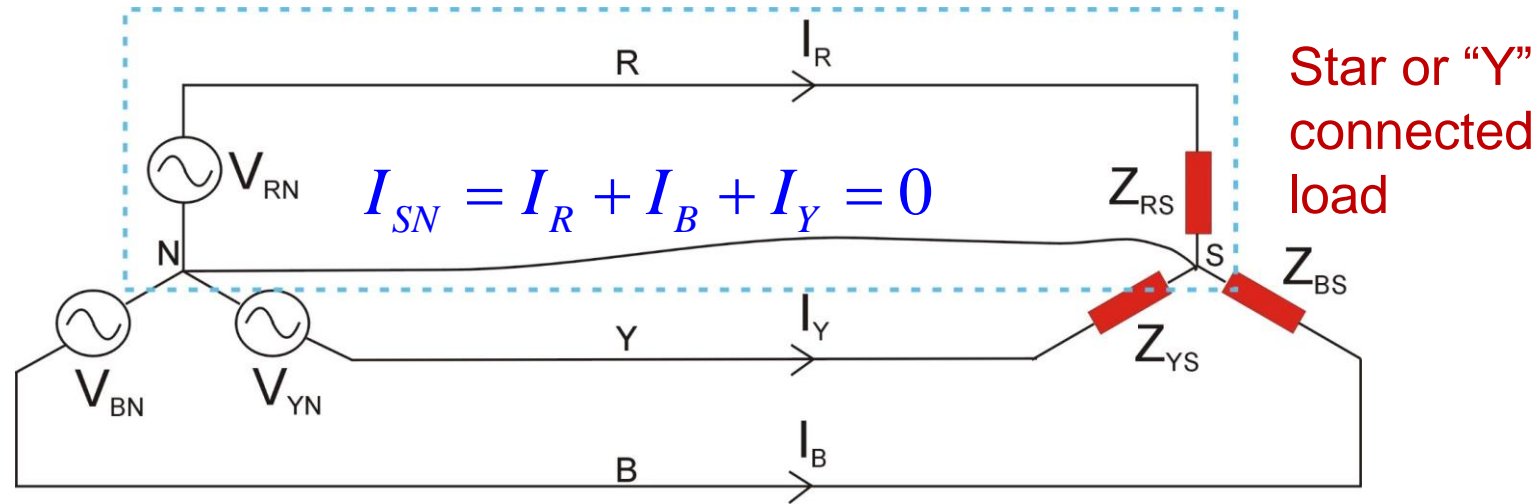

1. The balanced 3-Phase 4-Wire System can be decomposed into three separated Single-Phase Systems:

$$I_R = \frac{V_{RN}}{Z_{RS}} = I_L \angle -\phi$$

$$I_B = \frac{V_{BN}}{Z_{BS}} = I_L \angle -\phi + 120^\circ$$

$$I_Y = \frac{V_{YN}}{Z_{YS}} = I_L \angle -\phi - 120^\circ$$

2. I_R , I_Y and I_B are **120° apart and equal in magnitude**, and


$$I_{SN} = I_R + I_B + I_Y = 0$$

- For Y loads, line current and phase current are the same.


$$\mathbf{I}_a = \frac{\mathbf{V}_{an}}{\mathbf{Z}_{an}}$$

$$\mathbf{I}_b = I \angle (\theta - 120^\circ)$$
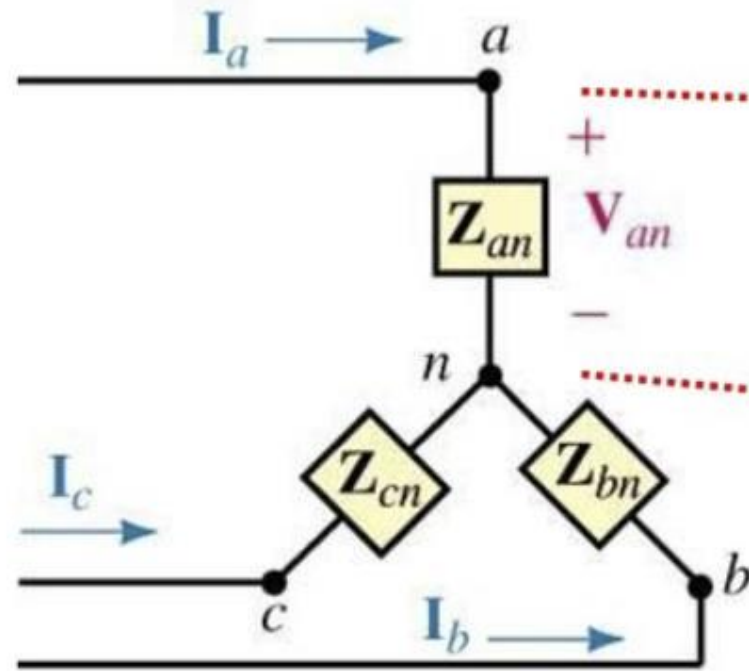
$$\mathbf{I}_c = I \angle (\theta + 120^\circ)$$



Line current

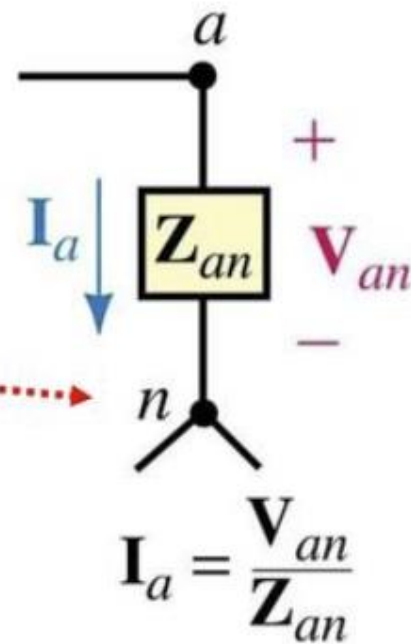

Phase current

BALANCED STAR connected load

Power calculations for each phase :

$$S = |V_{RN}| \cdot |I_R| = V_{ph} \cdot I_L$$


$$P = |V_{RN}| \cdot |I_R| \cdot \cos \phi = V_{ph} \cdot I_L \cdot \cos \phi$$

$$Q = |V_{RN}| \cdot |I_R| \cdot \sin \phi = V_{ph} \cdot I_L \cdot \sin \phi$$

where V_{ph} is the rms magnitude of the phase voltage, and I_L is the rms line current and ϕ is the angle between them

Total Real Power in 3-phase system:


$$P_T = 3 \cdot |V_{ph}| \cdot |I_L| \cdot \cos \phi$$

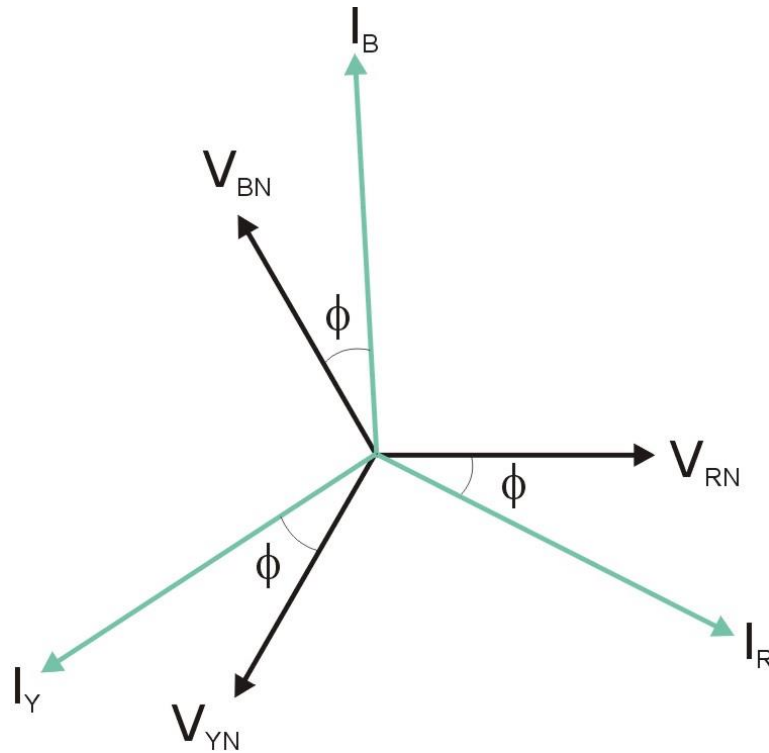

Phasor Diagram



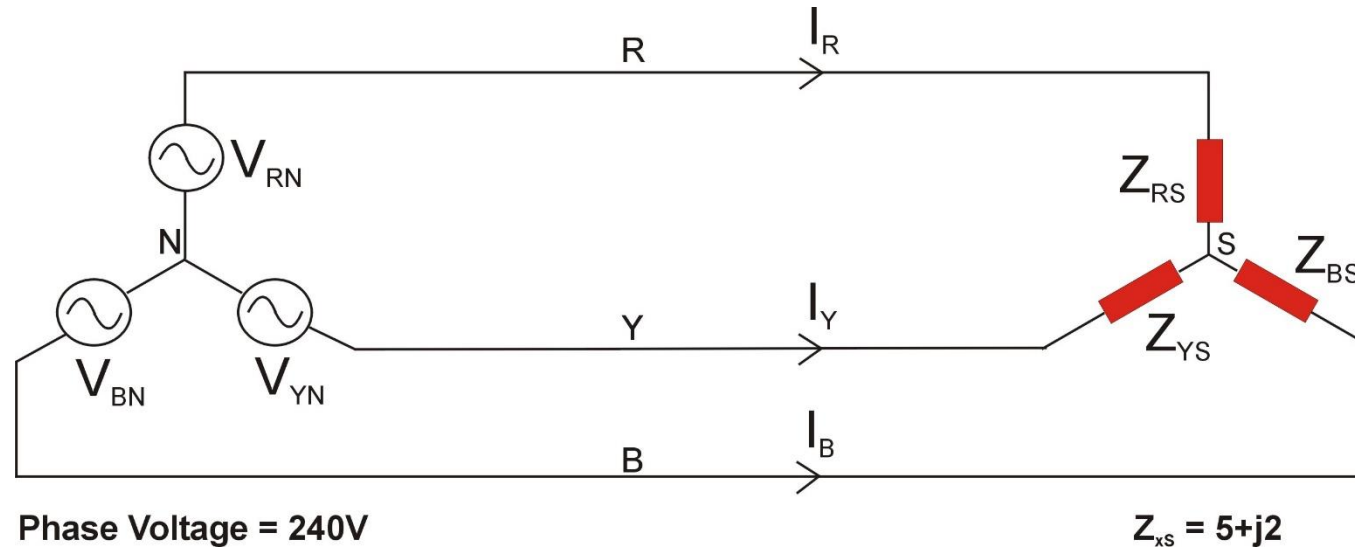AN EXAMPLE OF BALANCED STAR CONNECTED LOAD




For the balanced 3-phase 3-wire system, determine the following:

1. The magnitude of the line voltages
2. The line currents I_R , I_Y and I_B
3. The phasor diagram showing all line currents and phase voltages
4. The TOTAL real power supplied by the 3 phase supply

Solution: 1. $V_L = \sqrt{3}V_{ph} = 240\sqrt{3} = 415.7V$

2. $I_R = V_{RN} / (5 + j2) = 240\angle 0^\circ / 5.39\angle 21.8^\circ = 44.5\angle -21.8^\circ$
 $I_B = 44.5\angle 98.2^\circ$
 $I_R = 44.5\angle -141.8^\circ$

3.

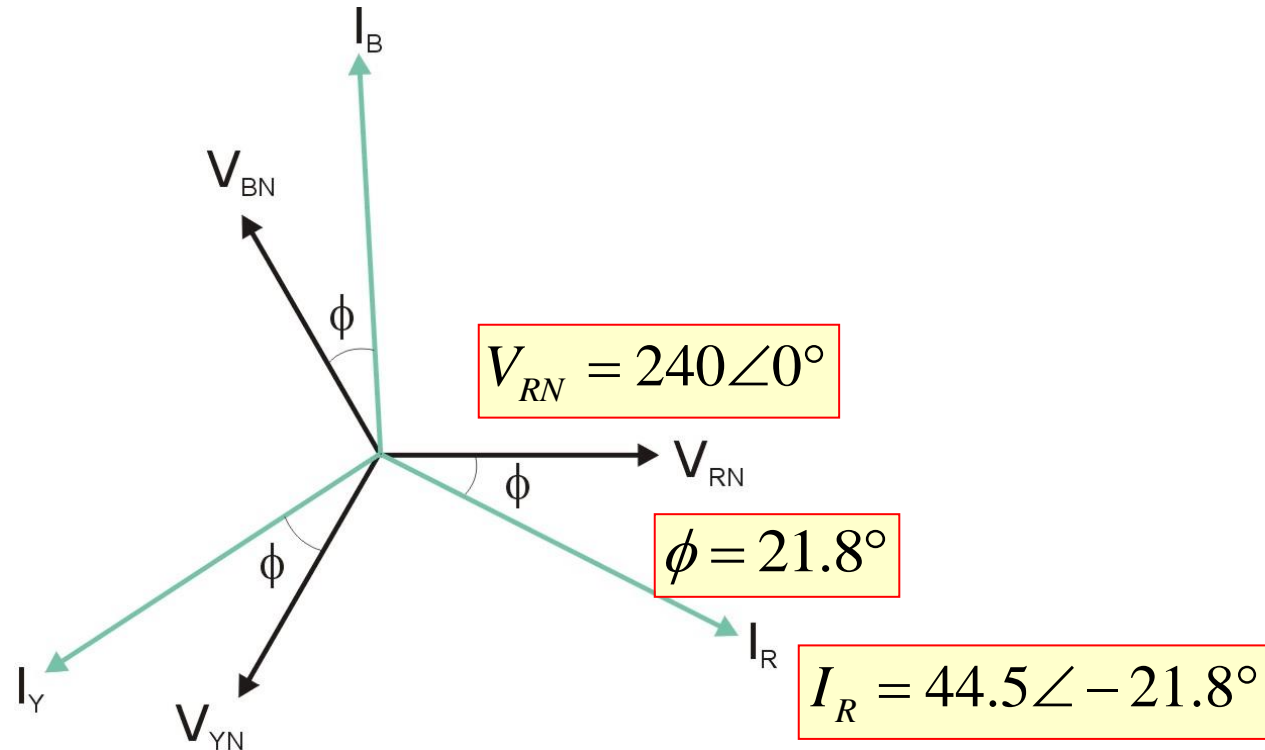


4.

$P_{total} = 3V_{ph}I_{ph} \cos \phi = 3I_R^2 R = 3 \times (44.5)^2 \times 5 = 29703.75W$

AN EXAMPLE OF BALANCED STAR CONNECTED LOAD

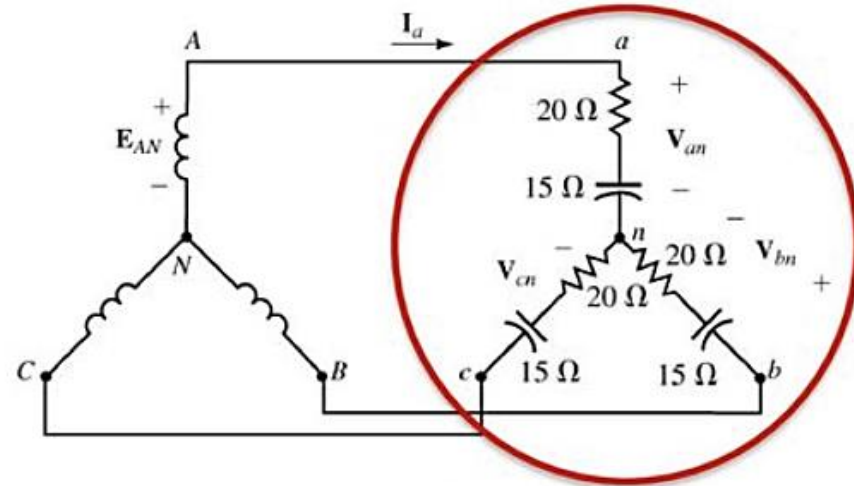For the load depicted below, $E_{AB} = 208\angle 0^\circ$ V . Find the phase voltages and line voltages and currents (remember that for a Y system, the phase and line currents are the same).



Notice the balanced load

AN EXAMPLE OF BALANCED STAR CONNECTED LOAD

For the load depicted below, $\mathbf{E}_{AB} = 208 \angle 0^\circ \text{ V}$. Find the phase voltages and line voltages and currents (remember that for a Y system, the phase and line currents are the same).

Line Voltages:

$$\bar{\mathbf{E}}_{AB} = 208 \angle 0^\circ \text{ V}$$

$$\bar{\mathbf{E}}_{BC} = 208 \angle -120^\circ \text{ V}$$

$$\bar{\mathbf{E}}_{CA} = 208 \angle 120^\circ \text{ V}$$

Phase Voltages:

$$\mathbf{E}_{AN} = \frac{\mathbf{E}_{AB}}{\sqrt{3} \angle 30^\circ} = \frac{208 \angle 0^\circ \text{ V}}{\sqrt{3} \angle 30^\circ} = 120 \angle -30^\circ \text{ V}$$

$$\mathbf{E}_{BN} = \mathbf{E}_{AN} \angle (\theta - 120^\circ) = 120 \angle (-30^\circ - 120^\circ) = 120 \angle -150^\circ \text{ V}$$


$$\mathbf{E}_{CN} = \mathbf{E}_{AN} \angle (\theta + 120^\circ) = 120 \angle (-30^\circ + 120^\circ) = 120 \angle 90^\circ \text{ V}$$

Phase/Line Currents:

$$\mathbf{I}_a = \frac{\mathbf{E}_{an}}{\mathbf{Z}_{an}} = \frac{208 \angle 0^\circ}{20 - j15} = 4.8 \angle 7^\circ \text{ A}$$


$$\mathbf{I}_b = \mathbf{I}_a \angle (\theta - 120^\circ) = 4.8 \angle (7^\circ - 120^\circ) = 4.8 \angle 113^\circ \text{ A}$$
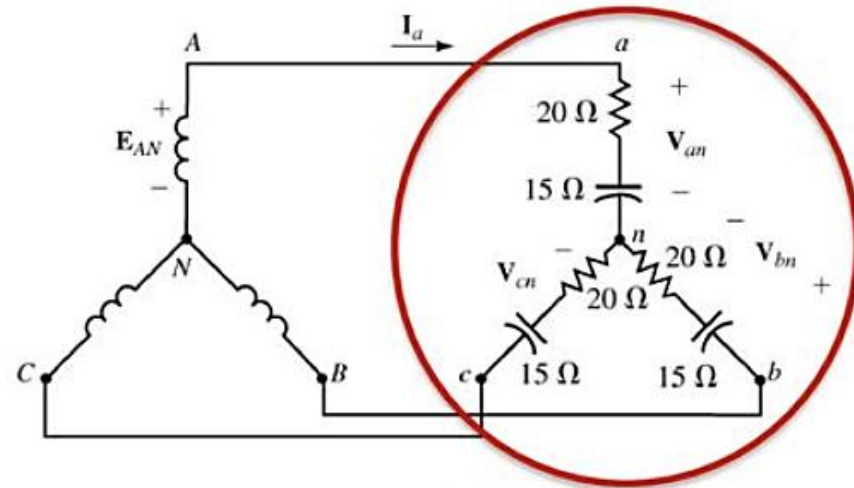
$$\mathbf{I}_c = \mathbf{I}_a \angle (\theta + 120^\circ) = 4.8 \angle (7^\circ + 120^\circ) = 4.8 \angle 127^\circ \text{ A}$$



Notice the balanced load

BALANCED DELTA CONNECTED 3 PHASE LOAD

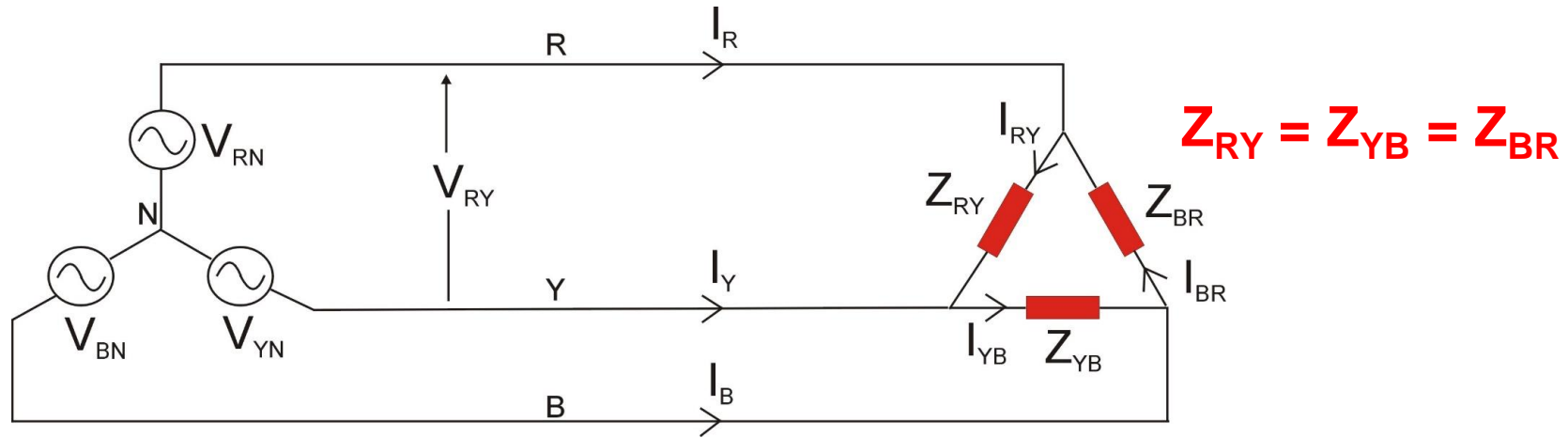

Load phase currents I_{RY} , I_{YB} , I_{BR} and line currents I_R , I_Y , I_B :

$$I_{RY} = \frac{V_{RY}}{Z_{RY}} = I_{ph} \angle -\phi$$

$$I_{YB} = \frac{V_{YB}}{Z_{YB}} = I_{ph} \angle (-\phi - 120^\circ)$$

$$I_{BR} = \frac{V_{BR}}{Z_{BR}} = I_{ph} \angle (-\phi + 120^\circ)$$


$$I_R = I_{RY} - I_{BR} = \sqrt{3} \cdot I_{ph} \angle -\phi - 30^\circ$$

$$I_Y = I_{YB} - I_{RY} = \sqrt{3} \cdot I_{ph} \angle -\phi - 150^\circ$$

$$I_B = I_{BR} - I_{YB} = \sqrt{3} \cdot I_{ph} \angle -\phi + 90^\circ$$

where all the currents are **phasors**

BALANCED DELTA CONNECTED 3 PHASE LOAD

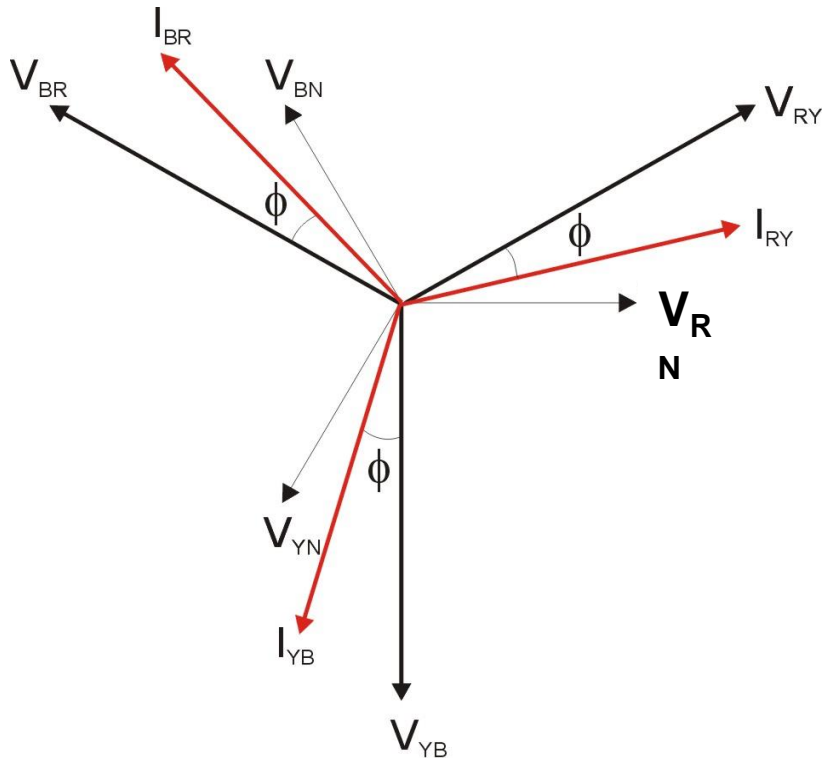

Phasor Diagram

Power calculations for any phase:

$$S = |V_{RY}| \cdot |I_{RY}| = V_L \cdot I_{ph}$$


$$P = |V_{RY}| \cdot |I_{RY}| \cdot \cos \phi = V_L \cdot I_{ph} \cdot \cos \phi$$

$$Q = |V_{RY}| \cdot |I_{RY}| \cdot \sin \phi = V_L \cdot I_{ph} \cdot \sin \phi$$

where V_L is the rms magnitude of the line voltage, and I_{ph} is the rms load phase current and ϕ is the angle between them

BALANCED DELTA CONNECTED 3 PHASE LOAD

Phasor Diagram

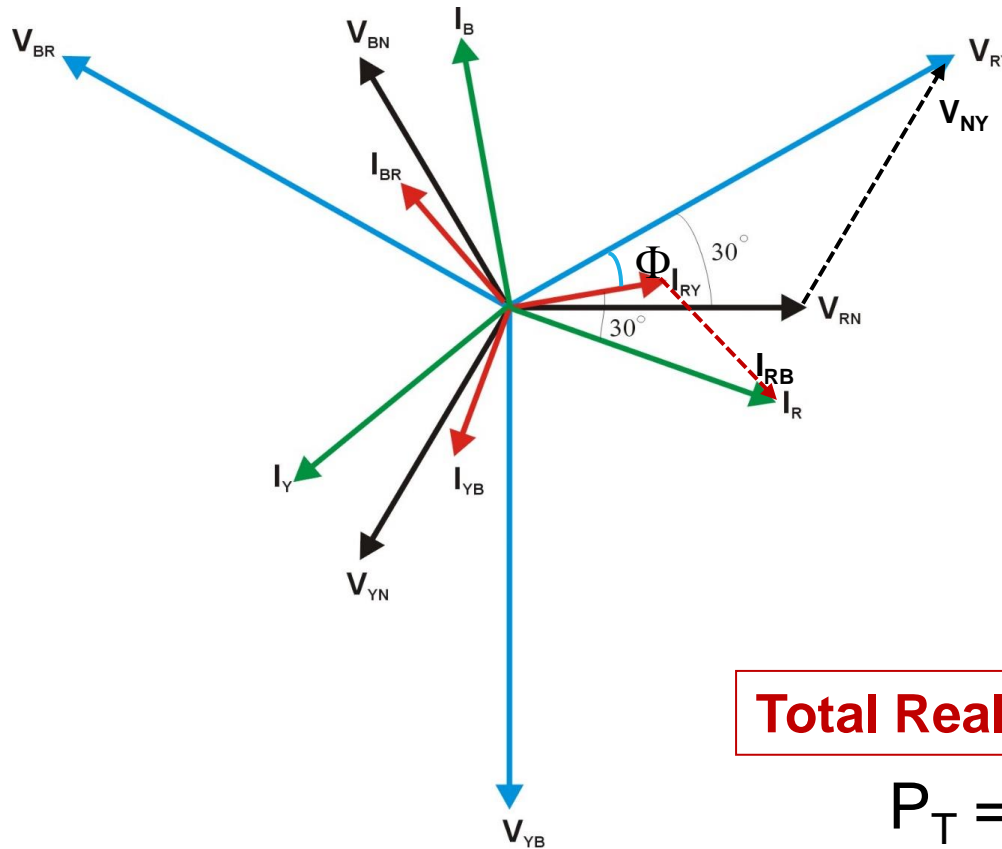

Notes:

1. Line Voltages (eg V_{RY}) are $\sqrt{3}$ x Phase Voltages (eg V_{RN}) and LEAD the phase voltages by 30°
2. Line Currents (eg I_R) are $\sqrt{3}$ x Load Phase Currents (eg I_{RY}) and LAG the phase currents by 30°

Total Real Power in 3-phase system:

$$P_T = 3 \cdot |V_L| \cdot |I_{ph}| \cdot \cos\Phi$$
$$= 3 \cdot |V_{ph}| \cdot |I_L| \cdot \cos\Phi$$



AN EXAMPLE OF BALANCED STAR CONNECTED LOAD

In the balanced 3-phase system of **Fig. Q.2**, determine the RMS phase and line voltages and currents in the resistors, the average power dissipated per phase and the total average power dissipated.

$$v_a(t) = 167.9 \cos(62.8t) \quad (\text{time-domain representation})$$
$$R_a = R_b = R_c = 30\Omega$$


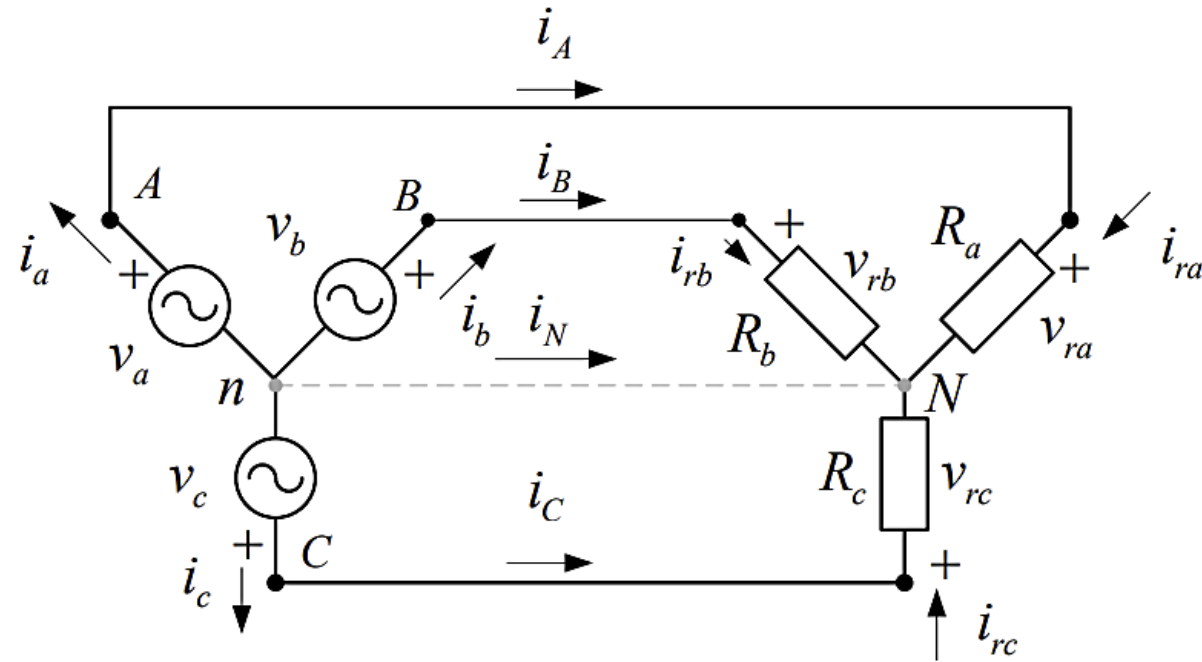


Fig. Q.2. A simple 3-phase, 3- or 4-wire system. (Wye – Wye Circuit).

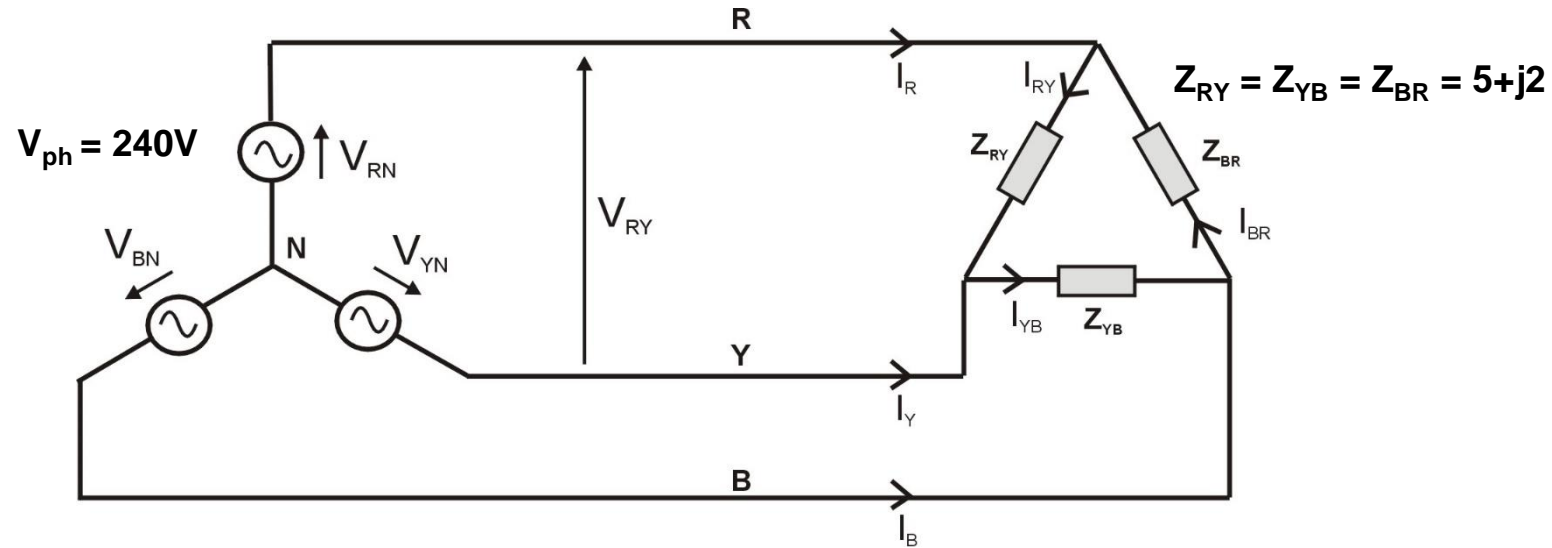AN EXAMPLE OF BALANCED DELTA CONNECTED LOAD



For the balanced 3 phase Delta connected load determine the following:

1. The magnitude of the line voltages
2. The line currents I_R , I_Y and I_B
3. The phasor diagram showing all currents and voltages
4. The TOTAL real power supplied by the 3 phase supply


Solution: 1. $V_L = \sqrt{3}V_{ph} = 240\sqrt{3} = 415.7V$

2. $V_{RY} = \sqrt{3}V_{RN} \angle 30^\circ,$

$$I_{RY} = V_{RY} / Z_{RY} = 77.2 \angle 8.2^\circ, I_R = \sqrt{3}I_{RY} \angle -30^\circ = 133.7 \angle -21.8^\circ$$

$$I_B = 133.7 \angle 98.2^\circ, I_Y = 133.7 \angle -141.8^\circ$$


3.

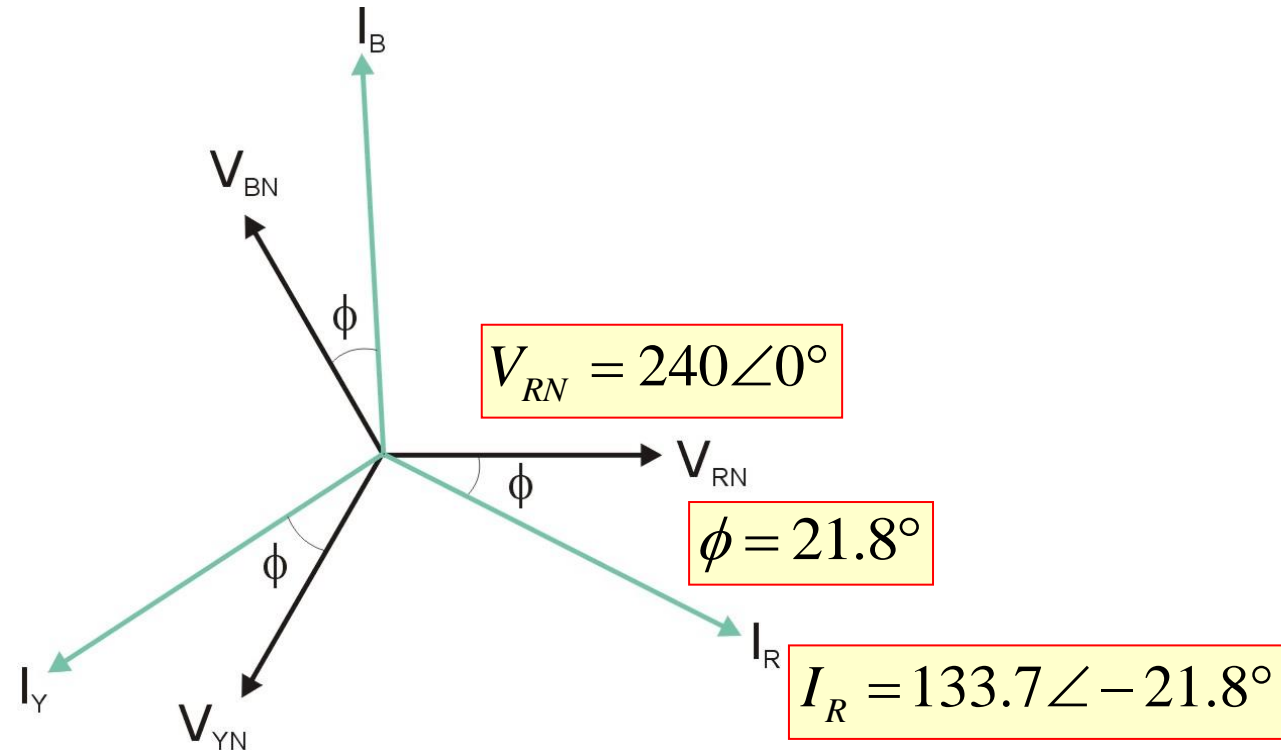

4.

$$P_{total} = 3V_{ph}I_{ph} \cos \phi = 3I_{RY}^2 R = 3 \times (77.2)^2 \times 5 = 89398W$$

POWER MEASUREMENTS IN 3 PHASE SYSTEMS

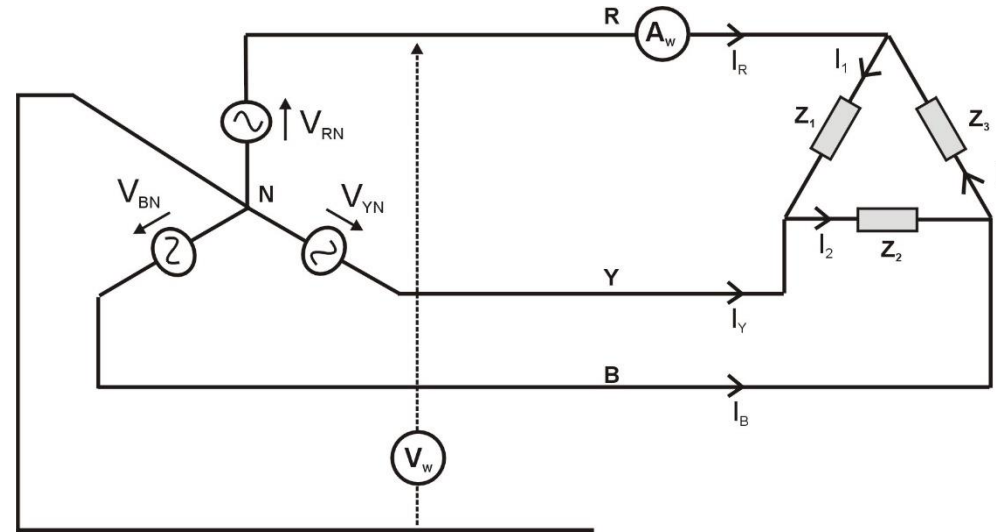


‘Classic’ **Wattmeter** Measures:


● Voltage (V)

● Current (A) → Real Power **P** (W)

● Power Factor

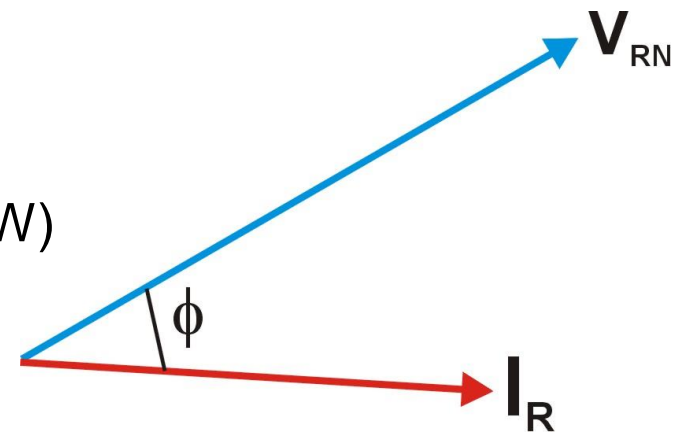

POWER MEASUREMENT: 3 WATTMETER METHOD

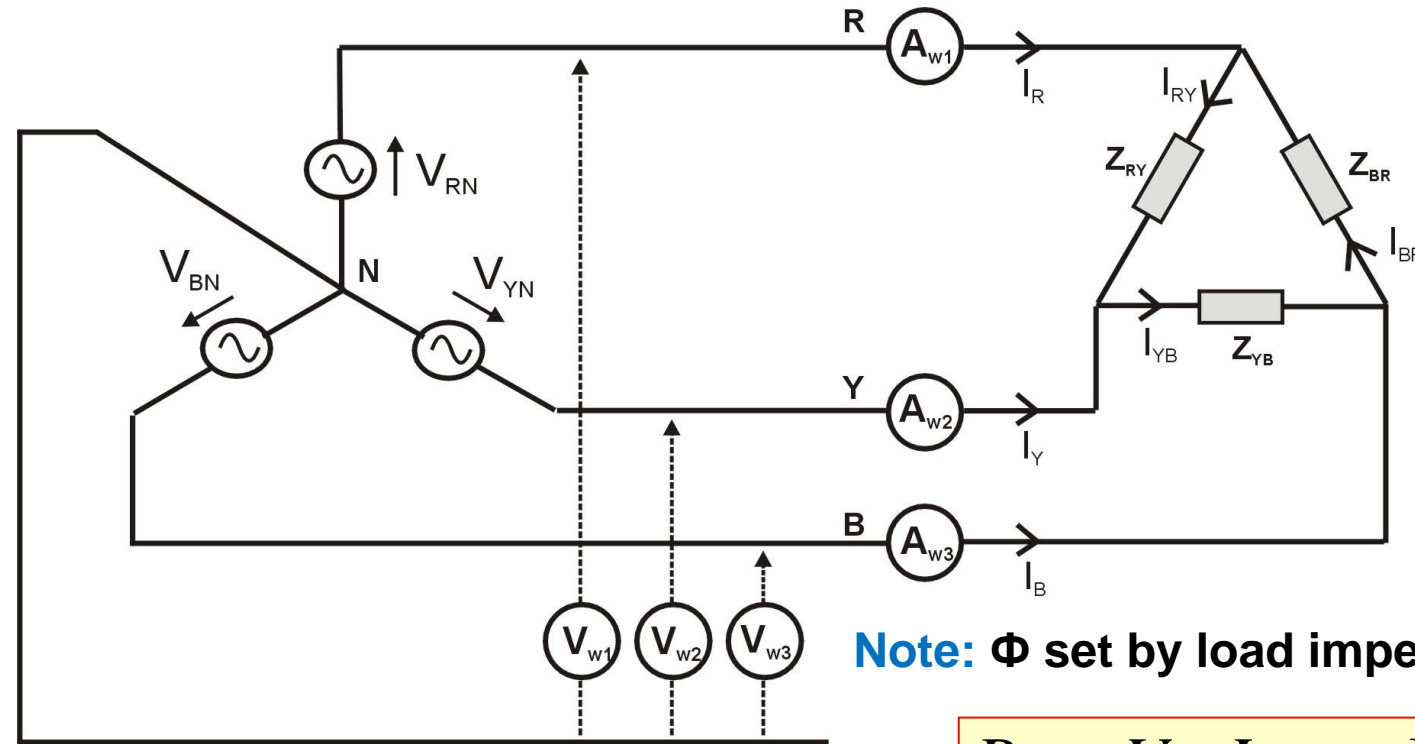


Note: Φ set by load impedance

Wattmeter 1: V_{W1} , A_{W1} , & Φ_{W1}

Wattmeter 2: V_{W2} , A_{W2} , & Φ_{W2}

Wattmeter 3: V_{W3} , A_{W3} & Φ_{W3}

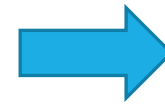


$$P_{W1} = V_{RN} I_R \cos \Phi_1$$

$$P_{W2} = V_{YN} I_Y \cos \Phi_2$$

$$P_{W3} = V_{BN} I_B \cos \Phi_3$$

$$P_{Total} = P_{W1} + P_{W2} + P_{W3}$$

POWER MEASUREMENT: 2 WATTMETER METHOD

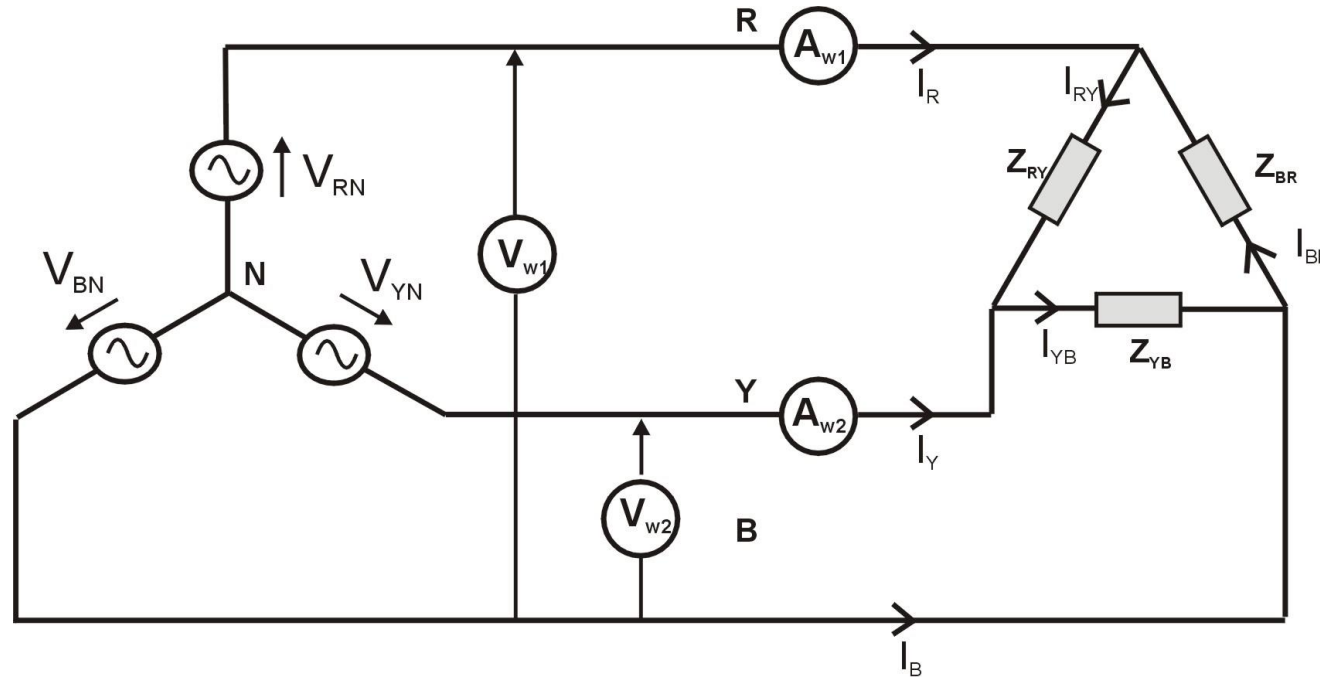

$$P_{W1} = |V_{RB}| \cdot |I_R| \cdot \cos \Phi_{W1} \quad \text{Where } \Phi_{W1} = \text{angle between } V_{RB} \text{ and } I_R$$

$$P_{W2} = |V_{YB}| \cdot |I_Y| \cdot \cos \Phi_{W2} \quad \text{Where } \Phi_{W2} = \text{angle between } V_{YB} \text{ and } I_Y$$

➡
$$P_{Total} = P_{W1} + P_{W2} = |V_{RB}| \cdot |I_R| \cdot \cos \phi_{W1} + |V_{YB}| \cdot |I_Y| \cdot \cos \phi_{W2}$$

AN EXAMPLE OF 2 WATTMETER METHOD


For a balanced DELTA connected load, from Phasor Diagram,

$$\phi + 30^\circ + \phi_{W1} = 60^\circ$$

$$\phi_{W2} = 30^\circ + \phi$$

$$\begin{aligned} P_{Total} &= P_{W1} + P_{W2} \\ &= |V_{RB}| \cdot |I_R| \cdot \cos \phi_{W1} + |V_{YB}| \cdot |I_Y| \cdot \cos \phi_{W2} \\ &= V_L I_L \cos(30^\circ - \phi) + V_L I_L \cos(30^\circ + \phi) \end{aligned}$$
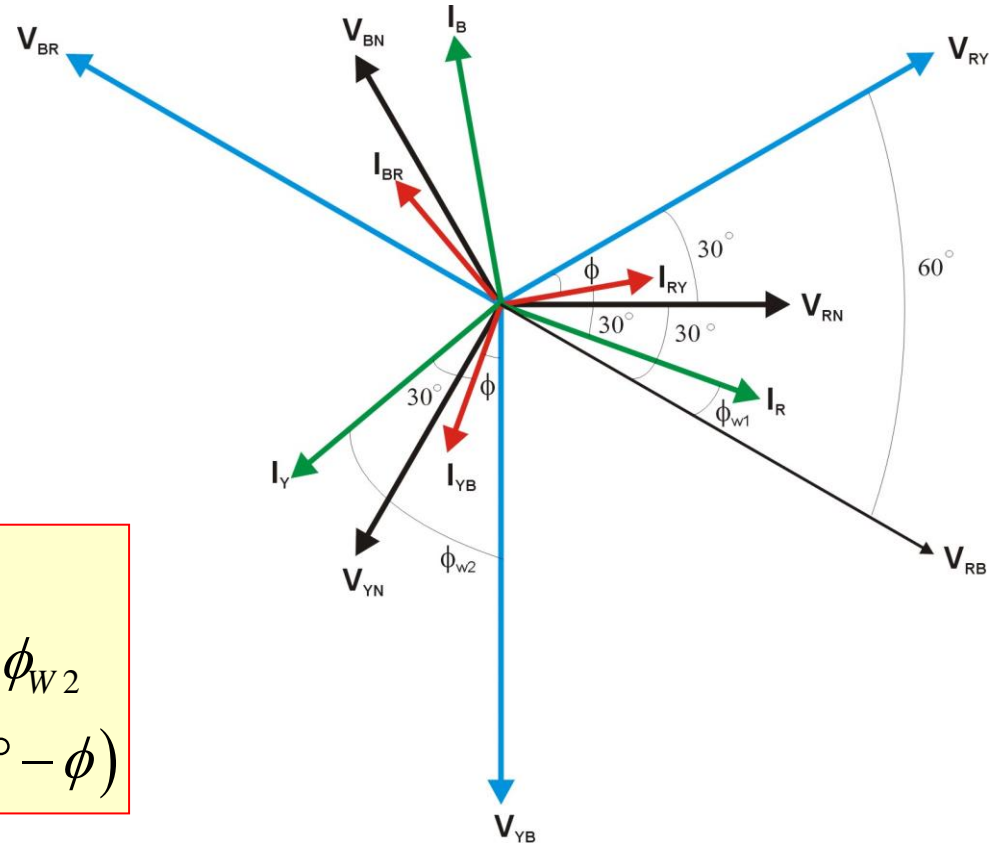
$$\begin{aligned} P_{Total} &= V_L I_L \left(\frac{\sqrt{3}}{2} \cos \phi + \frac{1}{2} \sin \phi \right) + V_L I_L \left(\frac{\sqrt{3}}{2} \cos \phi - \frac{1}{2} \sin \phi \right) \\ &= \sqrt{3} V_L I_L \cos \phi = 3 V_{ph} I_L \cos \phi = 3 V_L I_{ph} \cos \phi \end{aligned}$$



Modern Digital Sampling Power Meters/Analysers




Manufacturers:

Voltech

Fluke

Yokagawa

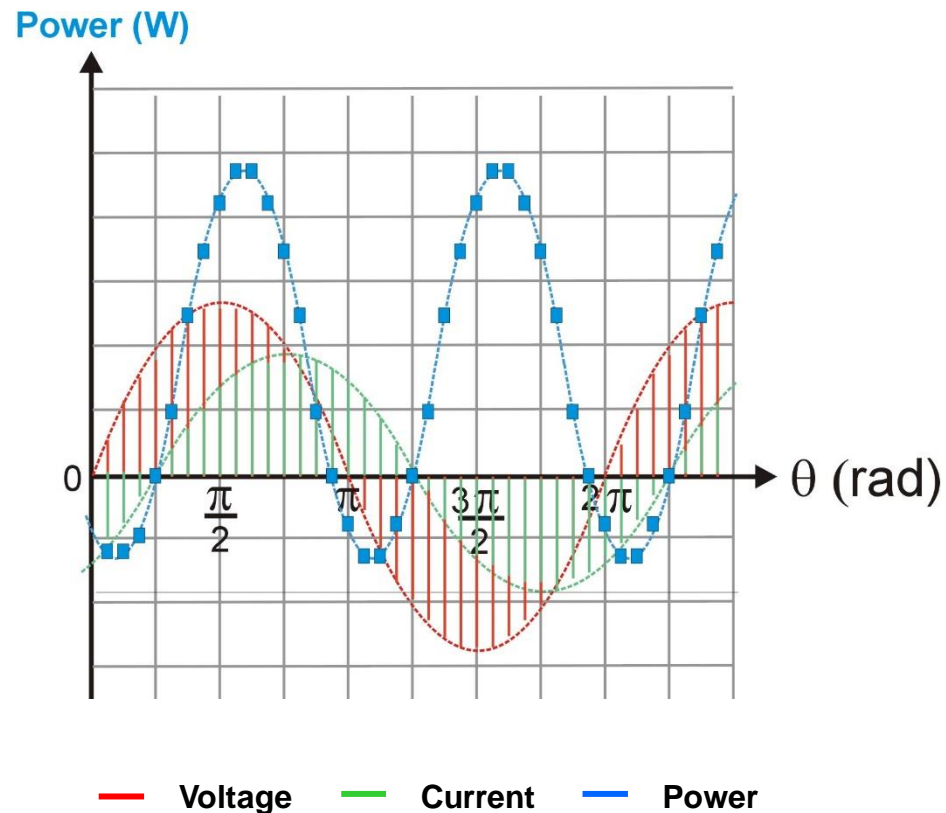

$$Power(W) = \frac{1}{N} \sum_0^N v.i$$

where N is the number of samples in a period



#03 Three-Phase AC Power Systems (1)