




University
of Glasgow

Electronic System Design 3

Lecture 10.2: Amplifier noise performance and source matching


Dr Duncan Bremner

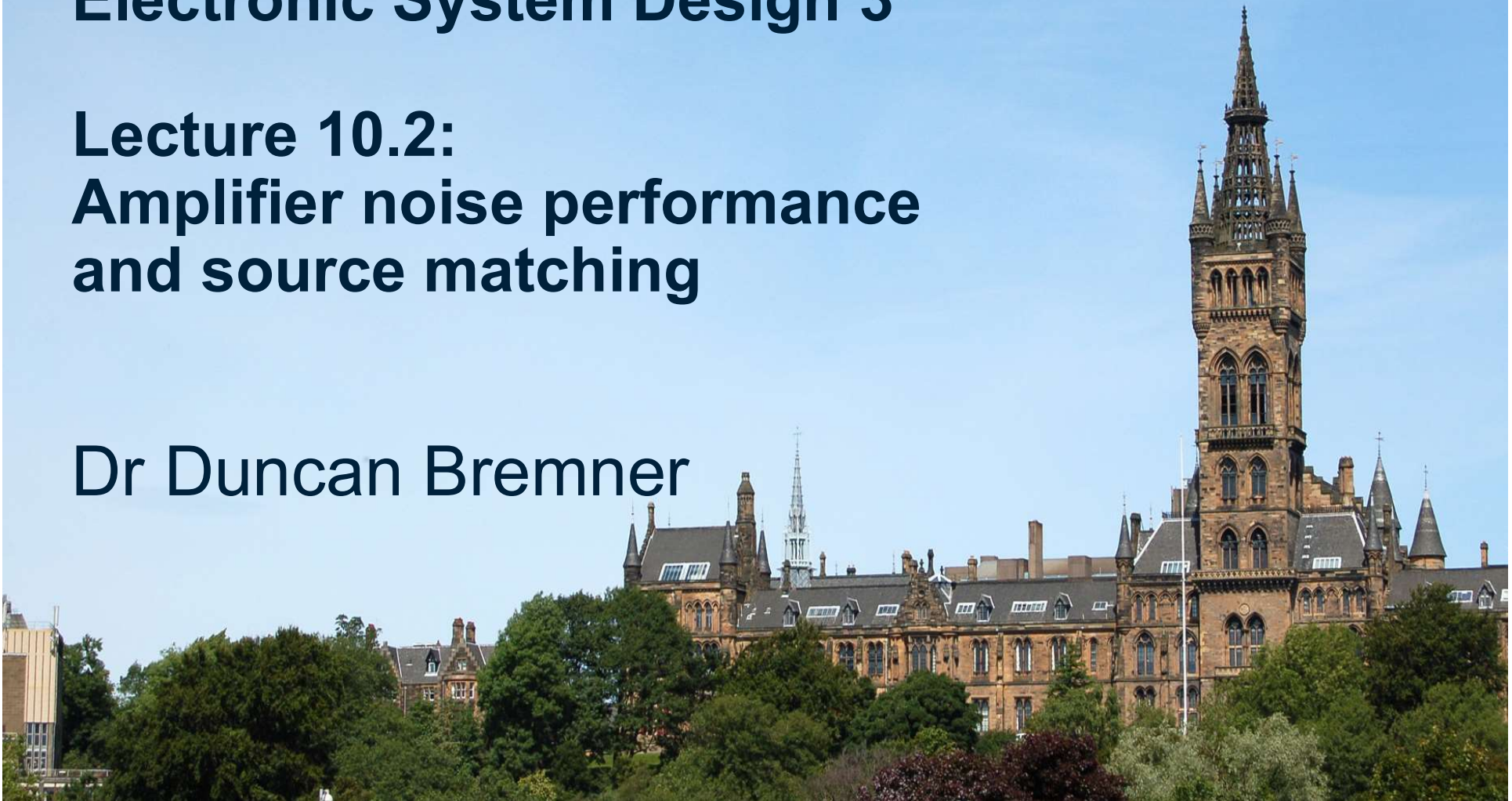




...more real Amplifiers

VOLTAGE NOISE vs SOURCE RESISTANCE

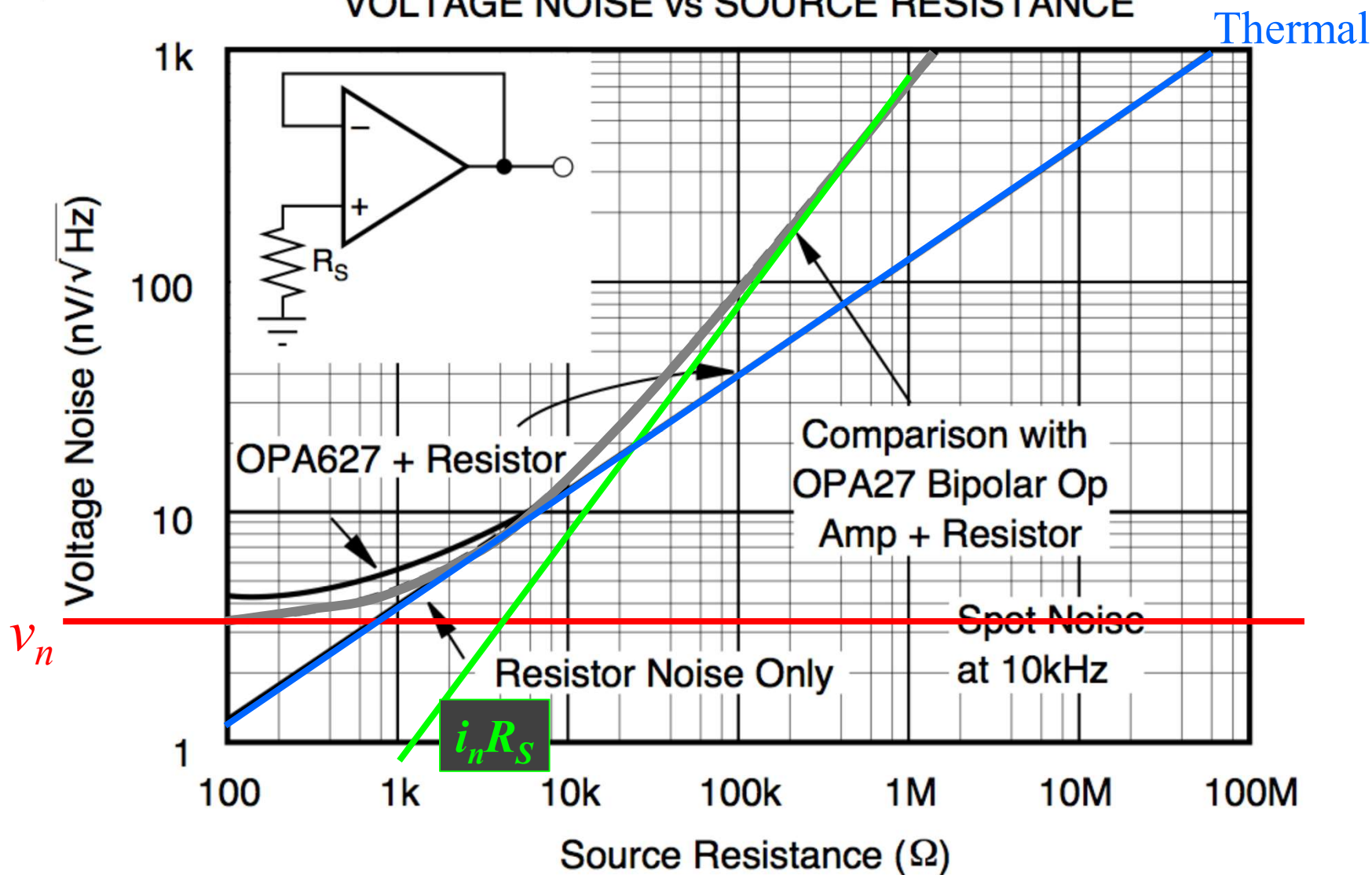

OPA277 Noise Performance

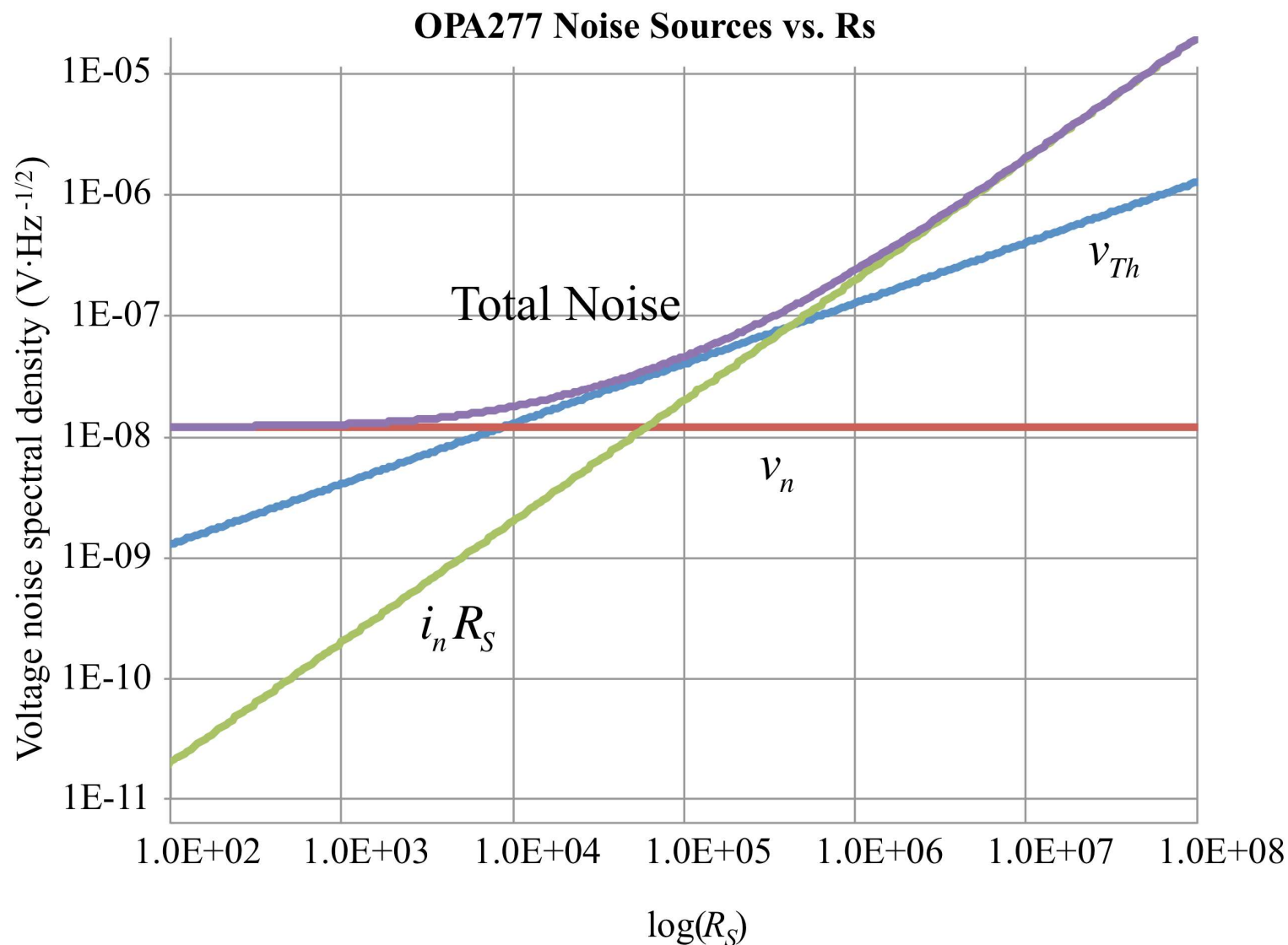

Noise Figure

All amplifiers add noise to the thermal noise of the source

$$\sqrt{4k_B TR_S} < \sqrt{4k_B TR_S + i_n^2 R_S^2 + v_n^2} = v_{ni}$$

The “goodness” of the amplifier is how **little** it makes things worse.

Define $NF \equiv \frac{v_{ni}}{\sqrt{4k_B TR_S}}$ Usually expressed in dB

$$NF = 20 \log_{10} \left(\frac{v_{ni}}{\sqrt{4k_B TR_S}} \right) dB \quad \text{Always } > 0$$

Noise figure

The noise figure depends on the amplifier **and** the source resistance


There is **no** “best” opamp, it depends on what it is being used for.

Four excellent opamps:


Opamp	v_n (nV·Hz ^{-1/2})	i_n (fA·Hz ^{-1/2})	R_{OPT}
AD8597	1.07	2400	446Ω
ADA4530	14	0.07	200MΩ
OPA827	4	2.2	1.82MΩ
OPA277	12	200	60kΩ

Source Resistor matching

Noise Figure (dB) vs. R_s vs. Opamp

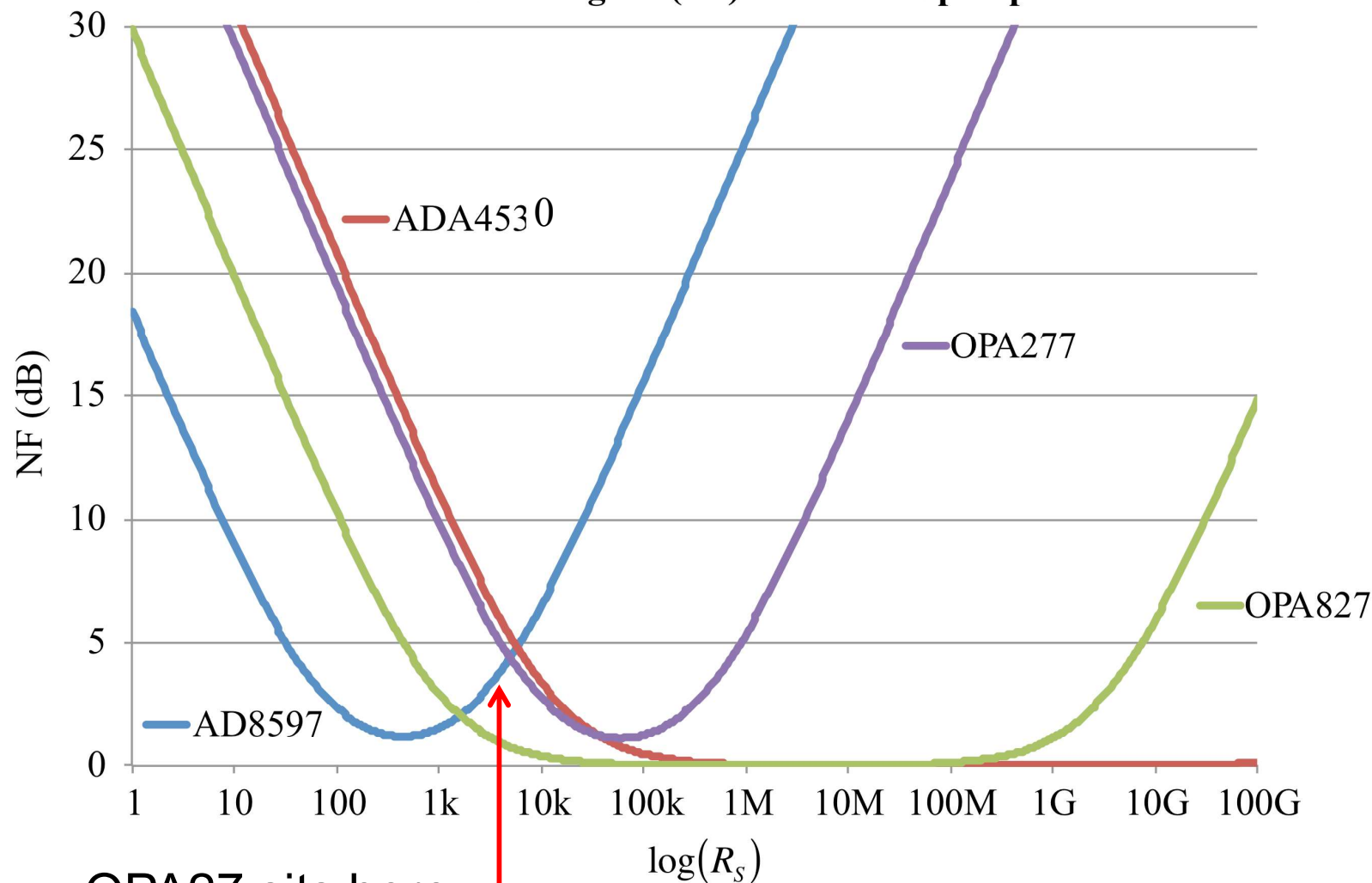

OPA27 sits here

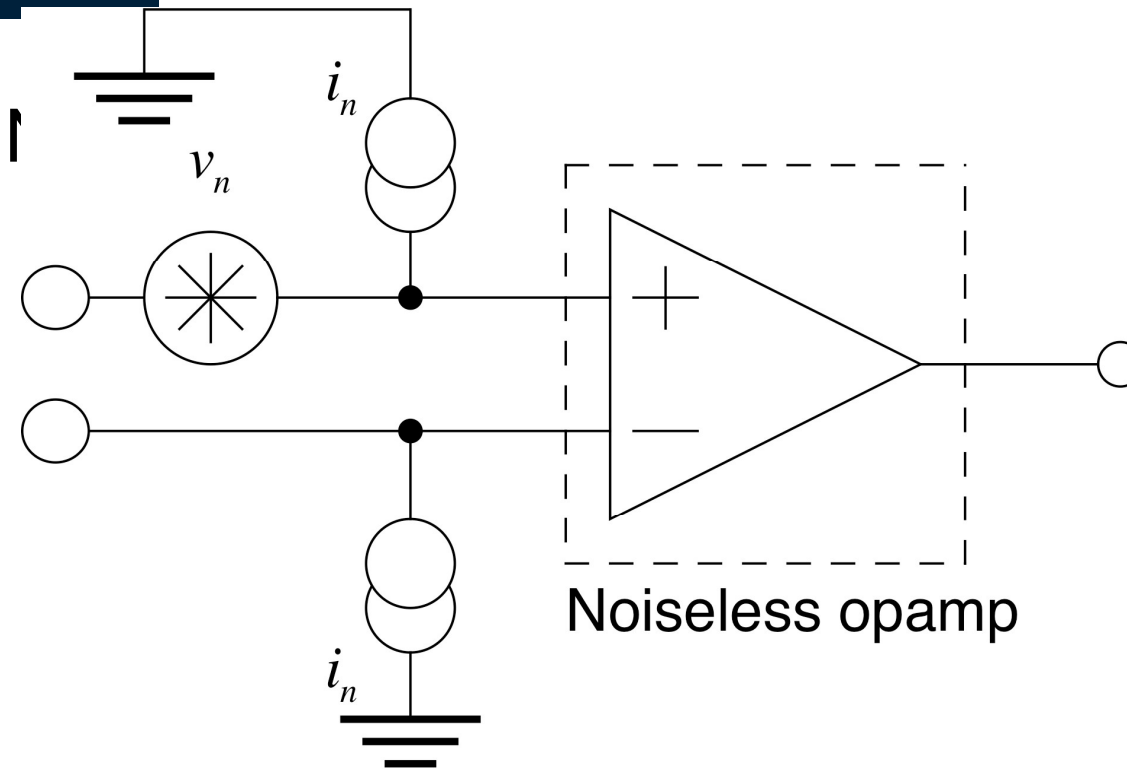

Note that the two i_n sources are uncorrelated: **Add as squares**

Note that the sources go in the same place as bias current and offset voltage



Shot Noise


Due to electrons crossing a potential barrier

- Charge is quantized
- Emission is **uncorrelated**

Photodiode


Base current

Diode current

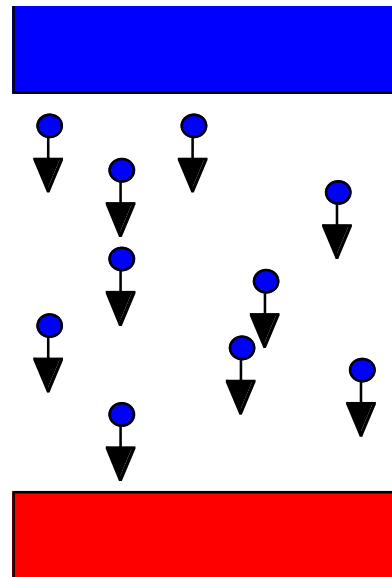

Uncorrelated

Shot Noise

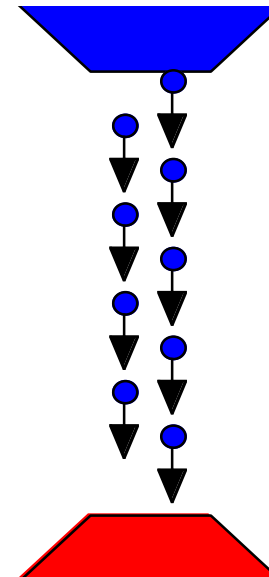

Metal film
resistor

Correlated

No Shot Noise



Shot Noise (2)

$$i_{sh} = \sqrt{2qI_{DC}B}$$

q = electron charge

I_{DC} = DC current flow

B = Bandwidth (Hz)

Shot noise **only occurs** when current is flowing

Shot noise **increases** with current

$$\text{Signal : Noise ratio} = \frac{I_{DC}}{i_{sh}} = \sqrt{\frac{I_{DC}}{2qB}} \text{ improves with } I_{DC}$$



University
of Glasgow

Thank you
谢谢

INSPIRING
PEOPLE