

Tutorial 5 for CAD

Sample Questions and Exercises

2020-21

Exercise 1

- Given a sinusoidal signal

$$v = 5\cos(2\pi 500t + 120^\circ)\text{V}$$

- a. find the frequency in hertz.
- b. find the period in seconds.
- c. find the frequency in radians/s.
- d. plot the instantaneous frequency as a function of time.

Exercise 2

- Represent $v(t) = 100\cos(2\pi 60t + 120^\circ)$ V by its phasor and plot the phasor.

Exercise 3

- Convert the following complex numbers in polar coordinates to Cartesian coordinates (rectangular coordinates)

a. $\mathbf{I} = 5\angle 30^\circ \text{ A}$


b. $\mathbf{I} = 6\angle 120^\circ \text{ A}$

c. $\mathbf{I} = 10\angle -120^\circ \text{ A}$

d. $\mathbf{I} = 20\angle -60^\circ \text{ A}$

Exercise 4


- For the circuit shown below

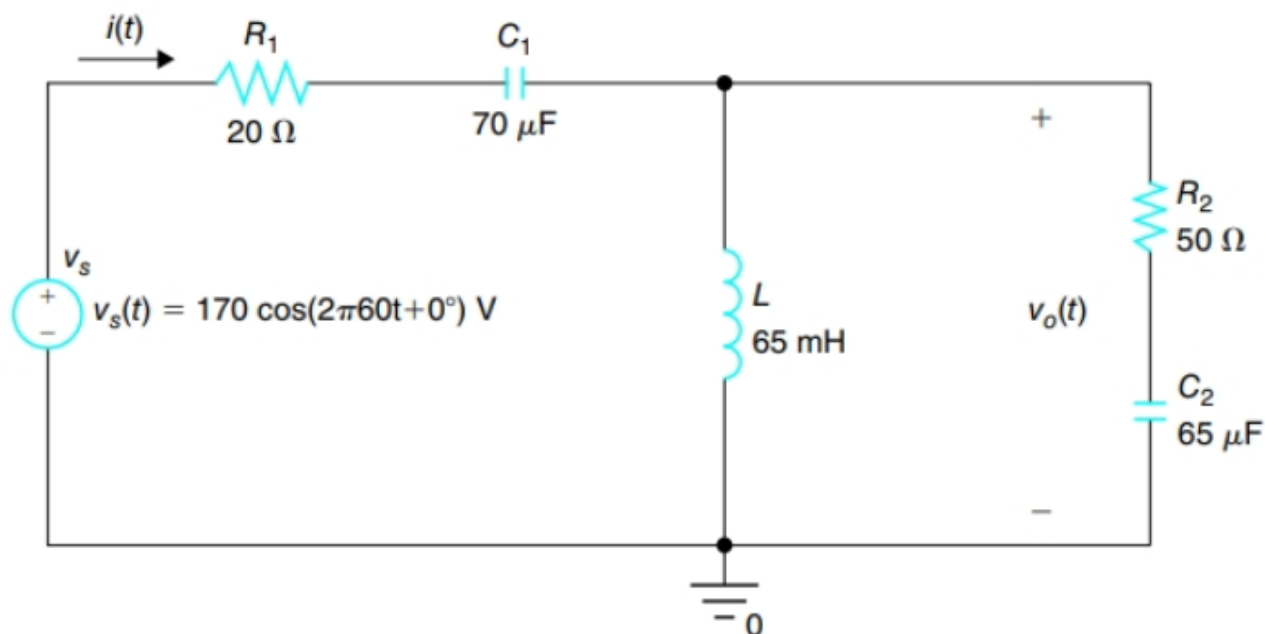

- draw the phasor-transformed circuit.
- find the phasors for $i(t)$ and $v_o(t)$.
- find the time domain waveforms $i(t)$ and $v_o(t)$.

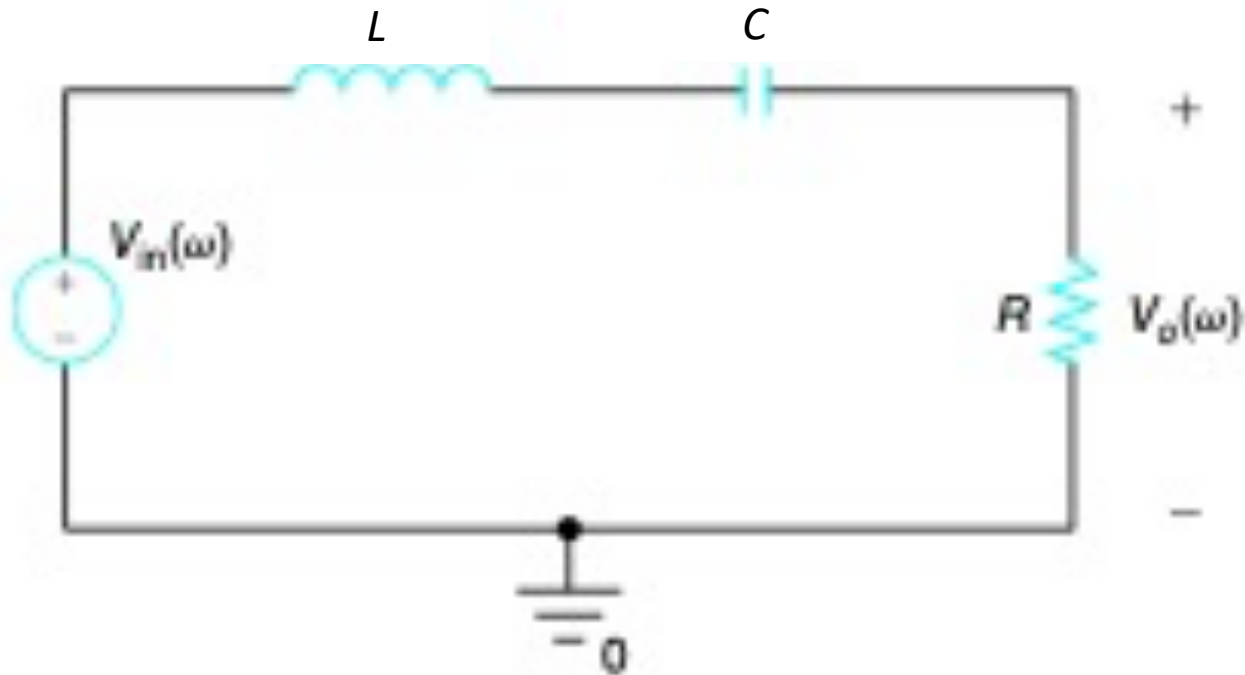Exercise 5

- Design a BPF of the type show in figure below:



(Questions are in the next page)


Exercise 5

Taking a lower cutoff frequency of 20.1 kHz, an upper cutoff frequency of 20.3 kHz and $R=20\text{ k}\Omega$, calculate:

- a. 3dB Bandwidth ($\omega_{3\text{dB}}$)
- b. Resonant frequency (ω_o)
- c. Value of inductor (L)
- d. Value of capacitor (C)
- e. Quality factor (Q)

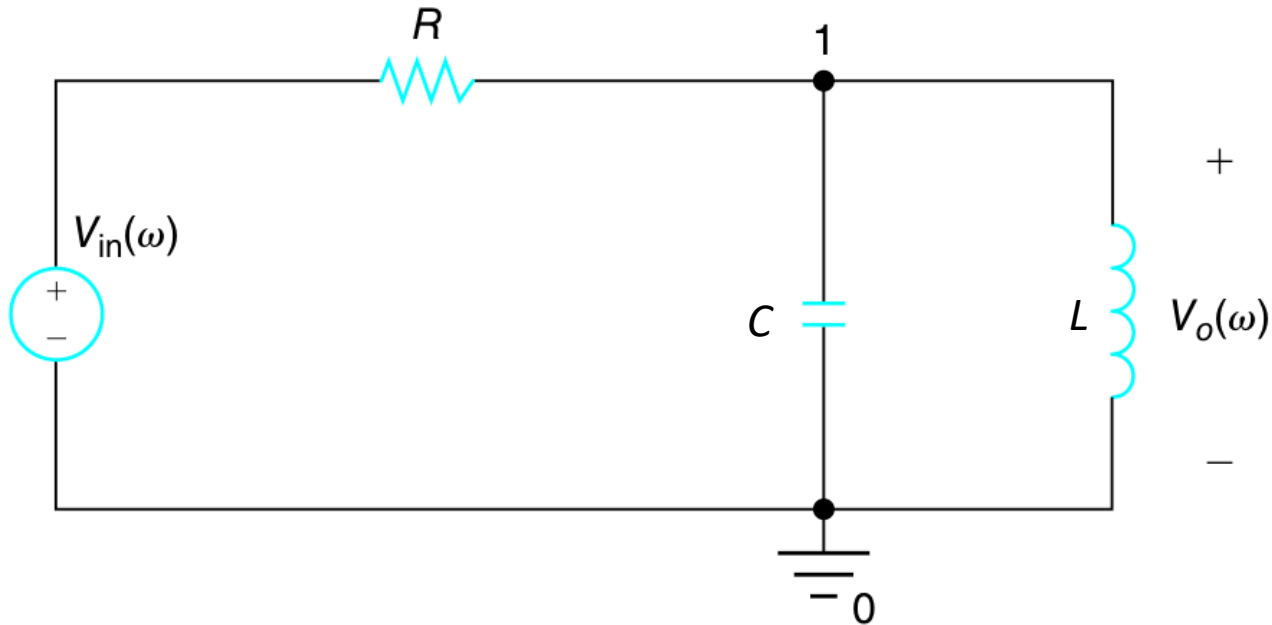Exercise 6

- Let $R = 5\text{k}\Omega$, $L=20\text{mH}$, and $C=0.5\mu\text{F}$ for the circuit below:



(Questions are in the next page)

Exercise 6

Find:

- a. The transfer function (H_{ω})
- b. Resonant frequency (ω_o)
- c. Lower cut-off frequency (ω_1)
- d. Upper cut-off frequency (ω_2)
- e. 3dB bandwidth (ω_{3dB})
- f. Quality factor (Q)
- g. Plot the magnitude and phase response on a linear scale
- h. Determine the type of the filter.