


# Tutorial 6 for CAD

## Sample Questions and Exercises

2019 Fall

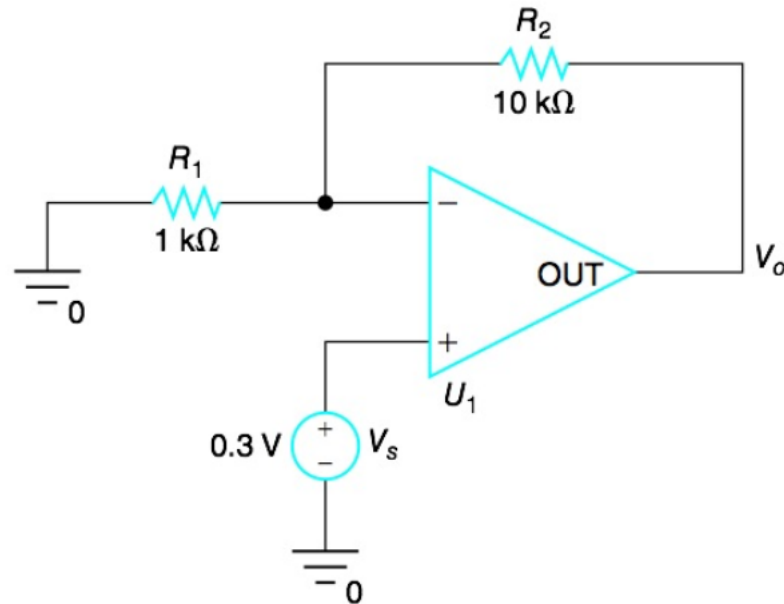
# 1 Ideal OP AMP

- Find  $V_o$  in the circuit shown below



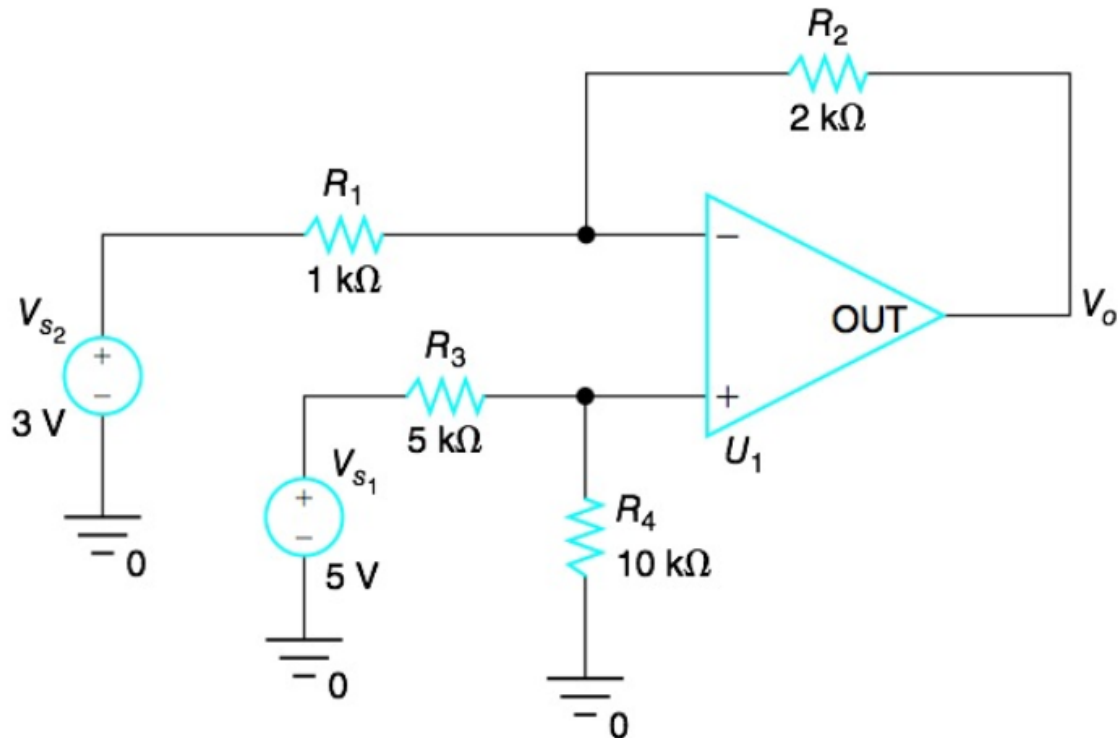
## 2 Sum and Difference

- Find  $V_o$  in the circuit shown below



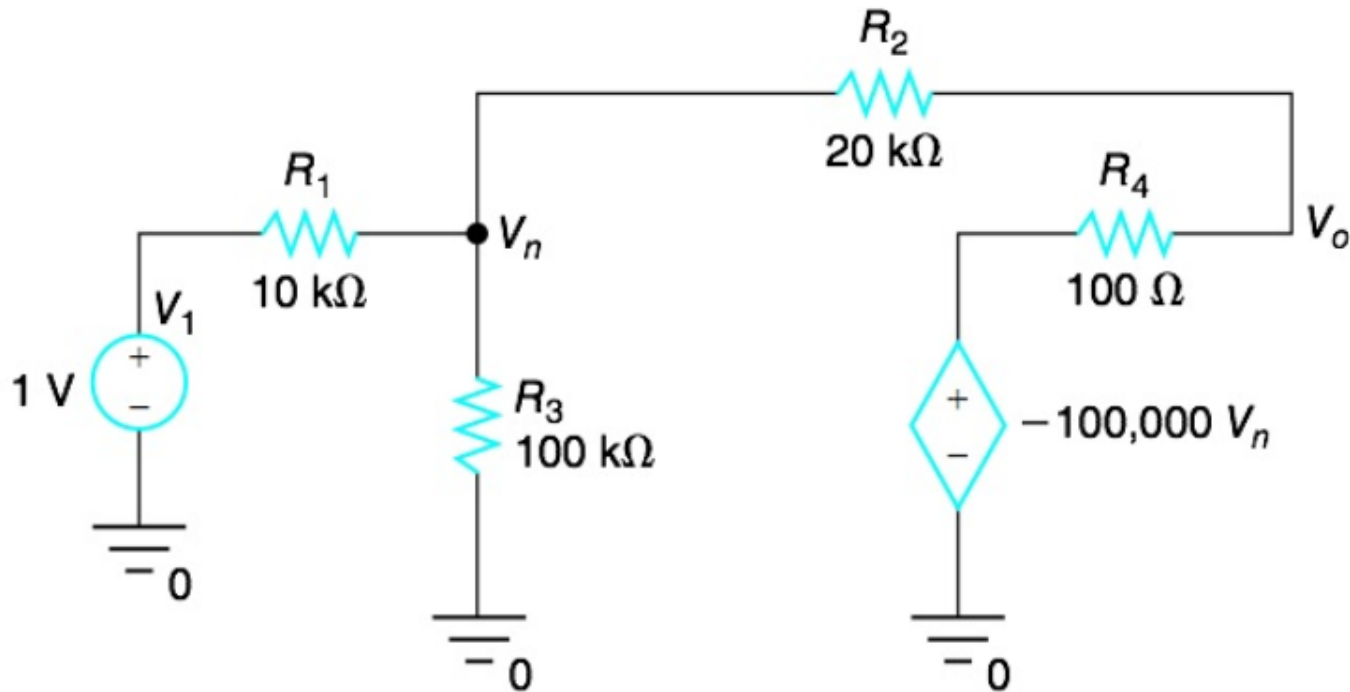
# 3 Inverting Configuration

- Find  $V_o$  in the circuit shown below



# 4 Noninverting Configuration

- In the circuit below

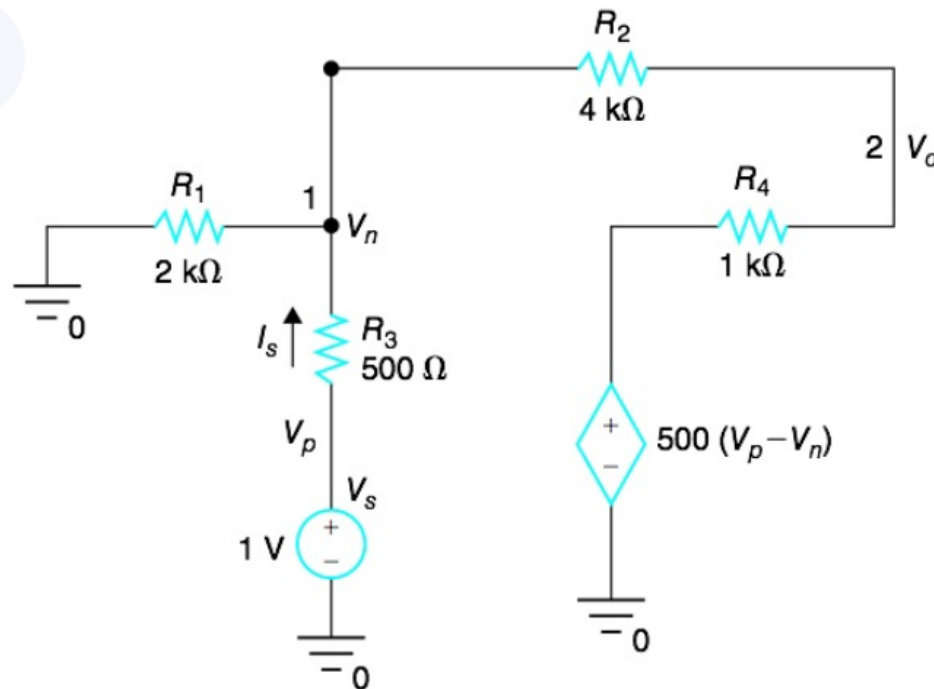

(Questions are in the next page)

# 4 Noninverting Configuration

- a. write a node equation at node 1 by summing the currents away from node 1.
- b. write a node equation at node 2 by summing the currents away from node 2. ( $V_p = V_s = 1 \text{ V}$ )
- c. solve the two node equations to find numerical values of  $V_n$  and  $V_o$ .
- d. find the value of  $I_s$  through  $R_3$ . Find the input resistance  $R_{in} = V_s/I_s$ .