



University
of Glasgow

UESTC 3003: Electronic System Design

Static Errors


Lecture 2.5: Input Offset Currents

Dr Duncan Bremner

WORLD
CHANGING
GLASGOW



Offset Current

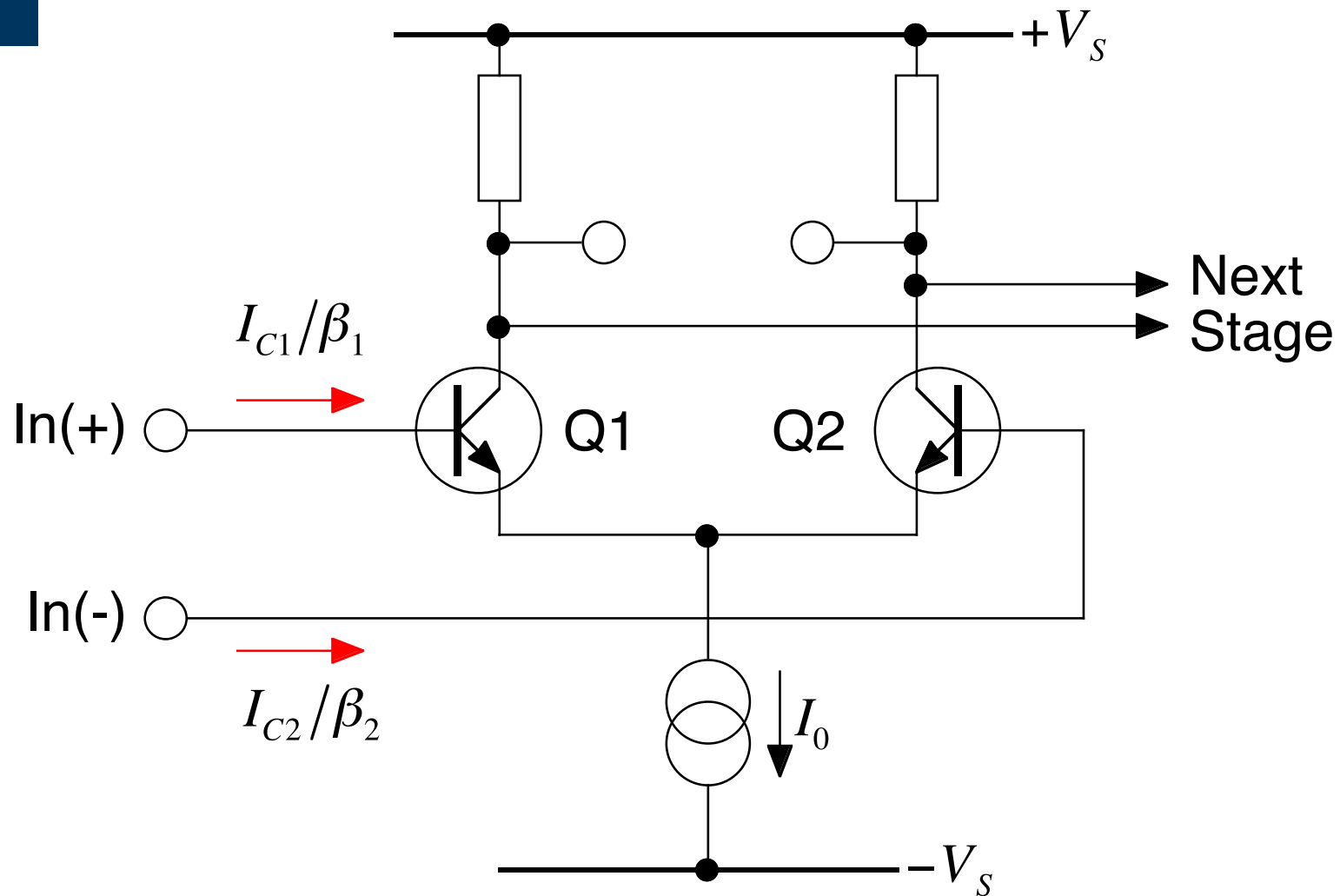

Transistors are closely matched, but... β is up to $\approx 5\%$ out

The difference between the bias currents is the *Offset Current*:

Offset Current (2)

$$I_{OS} = |I_B(+)-I_B(-)| \quad \text{(Ignore sign)}$$

Note that matching DC resistance compensates for I_B not I_{OS}

Matched resistor trick is only good to about 5% of the total error

Many modern opamps correct for bias current

Exceptions are

- Cheap opamps
- Fast opamps (esp. current feedback)
- Some specialised opamps (e.g. audio)

In the worst case the currents flowing into the inputs are equal and opposite: $I_{OS} \leq 2I_B$

If bias current has been corrected only the error is left

=> Balancing resistors makes things **worse**

READ THE DATA SHEET CAREFULLY (it is not always easy to see)!

Data Sheet

OP27

FEATURES

Low noise: 80 nV p-p (0.1 Hz to 10 Hz), 3 nV/ $\sqrt{\text{Hz}}$
Low drift: 0.2 $\mu\text{V}/^\circ\text{C}$
High speed: 2.8 V/ μs slew rate, 8 MHz gain bandwidth
Low V_{OS} : 10 μV
CMRR: 126 dB at VCM of ± 11 V
High open-loop gain: 1.8 million
Available in die form

GENERAL DESCRIPTION

The OP27 precision operational amplifier combines the low offset and drift of the OP07 with both high speed and low noise. Offsets down to 25 μV and maximum drift of 0.6 $\mu\text{V}/^\circ\text{C}$ make the OP27 ideal for precision instrumentation applications. Low noise, $e_n = 3.5$ nV/ $\sqrt{\text{Hz}}$, at 10 Hz, a low 1/f noise corner frequency of 2.7 Hz, and high gain (1.8 million), allow accurate high-gain amplification of low-level signals. A gain bandwidth product of 8 MHz and a 2.8 V/ μs slew rate provide excellent dynamic accuracy in high speed, data-acquisition systems.

A low input bias current of ± 10 nA is achieved by use of a bias current cancellation circuit. Over the military temperature range, this circuit typically holds I_B and I_{OS} to ± 20 nA and 15 nA, respectively.

The output stage has good load driving capability. A guaranteed swing of ± 10 V into 600 Ω and low output distortion make the OP27 an excellent choice for professional audio applications.

(Continued on Page 3)

PIN CONF

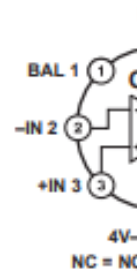


Figure 1. 8-Le

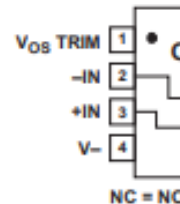


Figure 2. 8-Lead CERDIP -
8-Lead PDIP (P-Suffix)

FUNCTIONAL BLOC


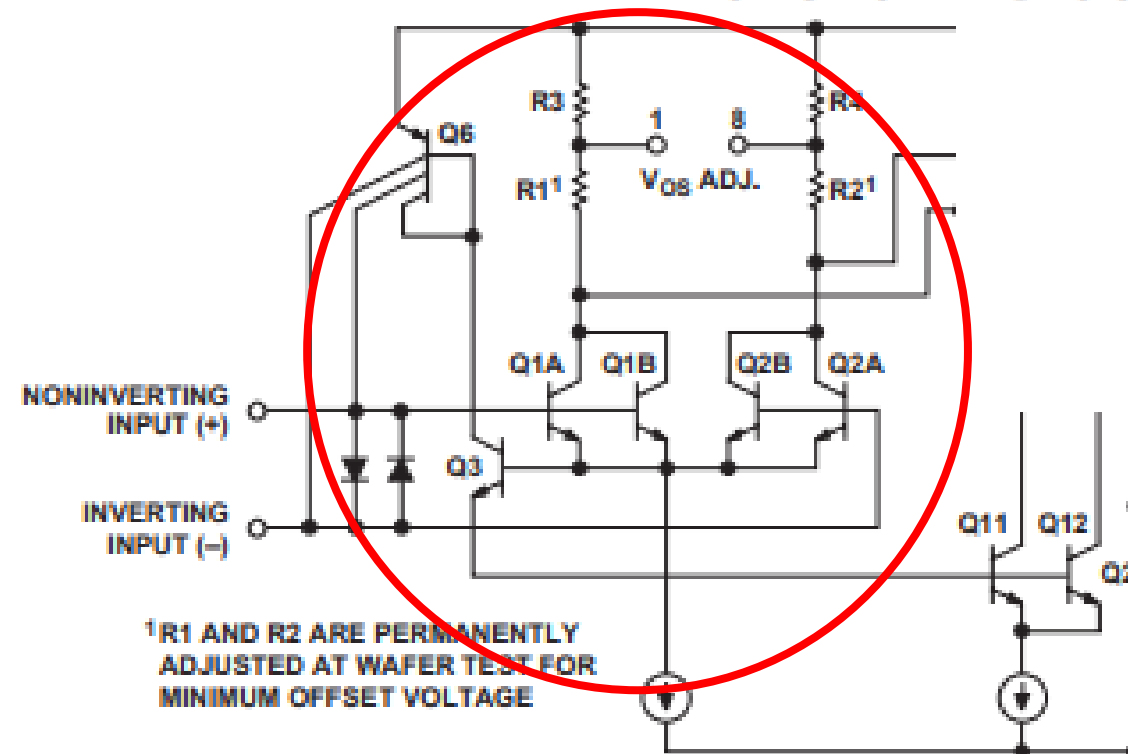
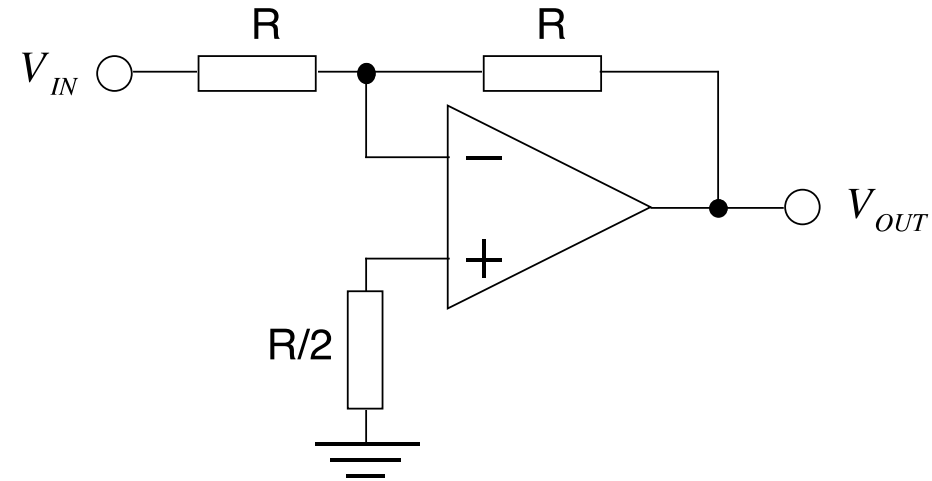


Figure 3

... and learn to read schematic diagrams
See reference MT-38 for how it works...

Offset Current (3)

Example: Inverting amplifier, gain of -1

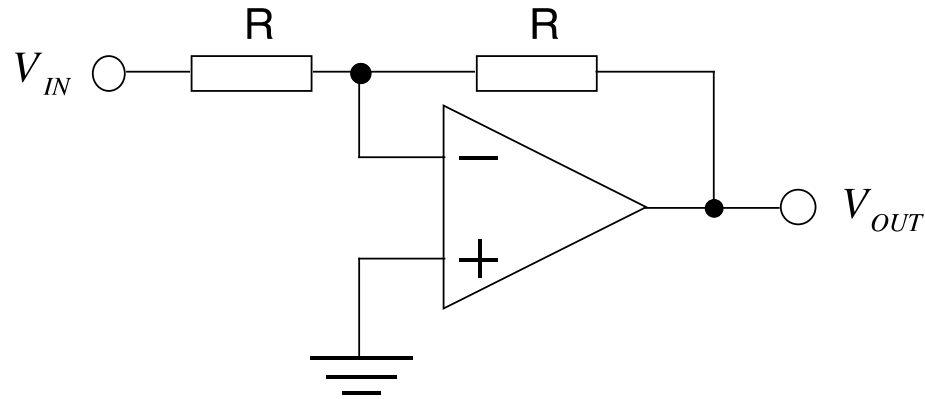

Error if no compensation =
 $R \times I_B(-)$

Error if compensated =


$$R \times (I_B(-) - I_B(+)) = R \times I_{OS}$$

$$\text{If } I_B(-) = -I_B(+) \text{ error} = 2R \times I_B(-)$$

Potentially **worse** than uncompensated

Offset Current (4)

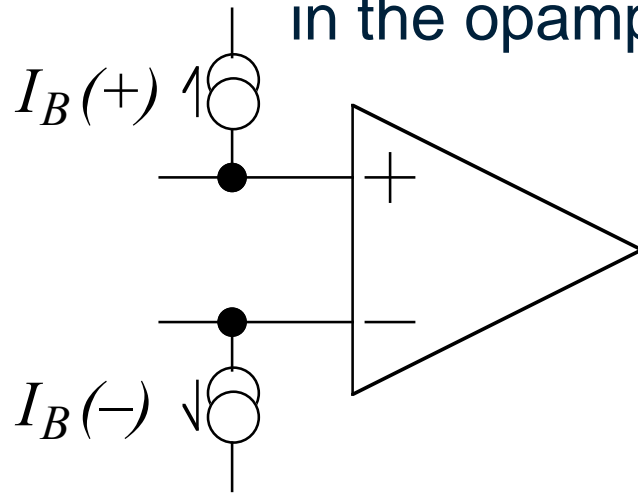
The model for current errors in the opamp is now:-



This is how the currents are defined in data sheets

From now on, use this model only

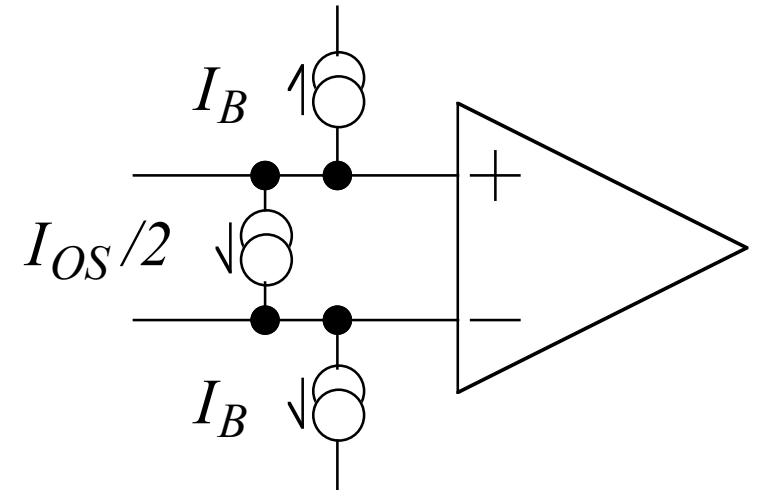
But we express $I_B(-)$ and $I_B(+)$ in terms of their average and difference:






Offset Current (5)

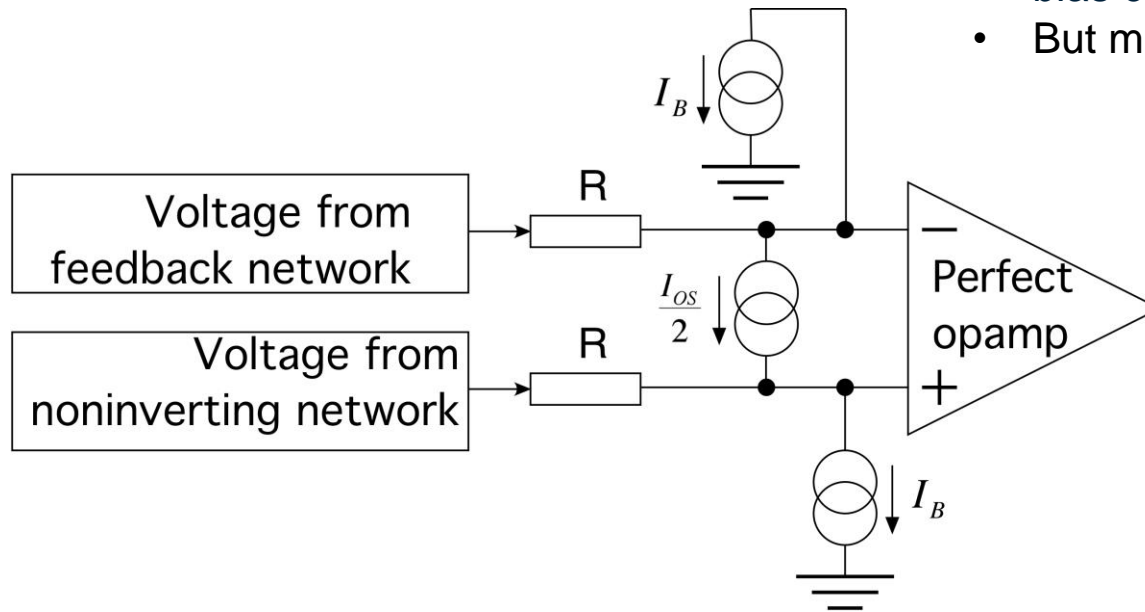- Equal source impedances compensate for bias current *in general*
- But make offset current worse *in general*



is equivalent to

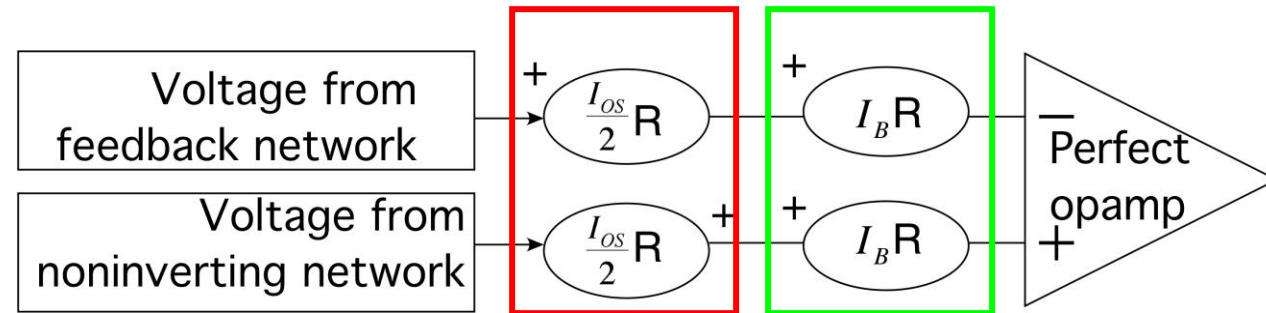

Cancels

Adds

Don't try to combine bias and offset current to work out specific values of current: these are only limiting specifications:

Example: NE5532, typical spec at 25°C $I_B = 200nA$; $I_{OS} = 10nA$

maximum spec at 25°C $I_B = 800nA$; $I_{OS} = 150nA$

Possible values:

$$I_B(+)=800nA; \quad I_B(-)=780nA \quad I_B(+)= -780nA; \quad I_B(-)= -700nA$$

$$I_B(+)=0nA; \quad I_B(-)= -150nA \quad I_B(+)= -800nA; \quad I_B(-)= -800nA$$

Impossible values:

$$I_B(+)=800nA; I_B(-)=820nA$$

$$I_B(+)= -75nA; \quad I_B(-)= 76nA$$

$$I_B = 810nA!$$

$$I_{OS} = 151nA!$$

If impedances are (very) unbalanced, use bias current spec.
If impedances are balanced, use offset current spec.

Practical consideration:

FET input opamps have very low bias current

But bias current is often **exponential** with temperature:

$$T = 20^{\circ}\text{C}, \quad I_B = 50\text{ pA}$$

$$T = 30^{\circ}\text{C}, \quad I_B = 100\text{ pA}$$

$$T = 40^{\circ}\text{C}, \quad I_B = 200\text{ pA}$$

$$T = 80^{\circ}\text{C}, \quad I_B = 3.2\text{ nA!}$$

Bipolar opamp's bias much more stable with temperature


Important point if designing for rugged environment

Automotive

Military / Aerospace

But not for normal domestic / lab conditions!

Example

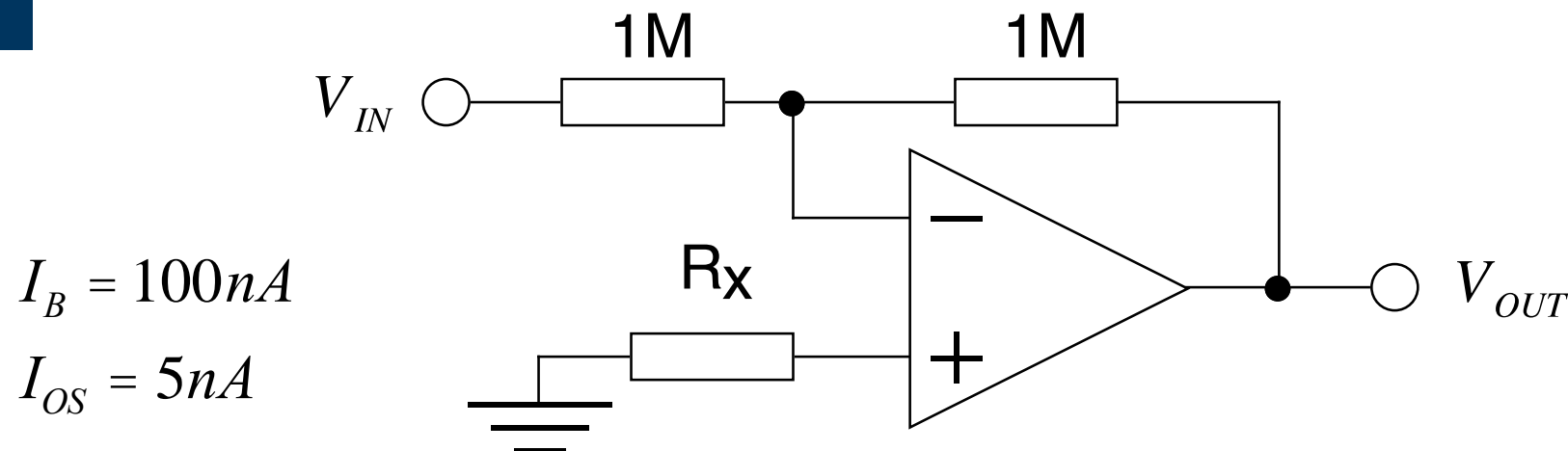

If R_X is 0, what is the error?


$$Error = R \times I_B (-) = R \times I_B = 100mV$$

If R_X is 500k, what is the error?

$$Error = R \times I_{OS} = 5mV$$

Question: What happens if all resistors are reduced e.g. $\times 0.1$?
 What is the limit on scaling resistors? **Hint: It's Free!**

Example: Integrator

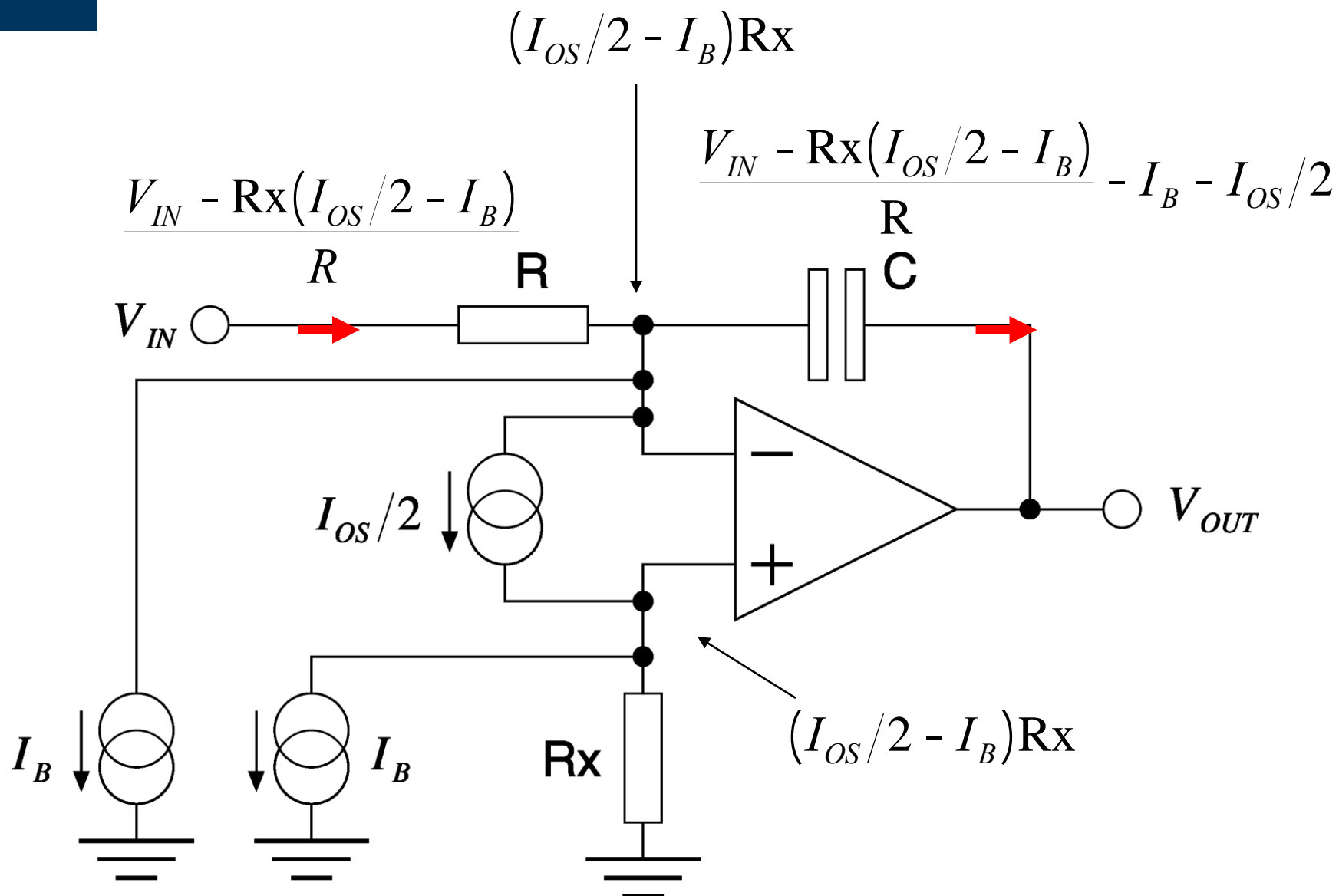



Neglecting constant terms
(including constant of integration)

Example (2)

$$V_{OUT} = \frac{-1}{C} \int i dt = \frac{-1}{C} \int \frac{V_{IN} - R_X(I_{OS}/2 - I_B) - I_B - I_{OS}/2}{R} dt$$

$$= - \int \frac{V_{IN}}{RC} - \frac{(R_X(I_{OS}/2 - I_B) + R I_B + R I_{OS}/2)}{RC} dt$$

$$\therefore \text{Error (RTI)} = - \left([R_X(I_{OS}/2 - I_B) + R I_B + R I_{OS}/2] \right)$$

$$= - \left((R_X + R) \cdot \frac{I_{OS}}{2} + (R_X - R) \cdot I_B \right)$$

If unmatched resistances,
R_x=0, just consider bias current

$$\text{Error (RTI)} = -R I_B$$


If matched resistances, Error (RTI) =

$$R_X=R, \text{ just consider offset current} \quad -R(I_{OS}/2 - I_B) - R I_B - R I_{OS}/2 = -R I_{OS}$$

$$I_B = 100nA$$

$$I_{OS} = 5nA$$

Example (3)

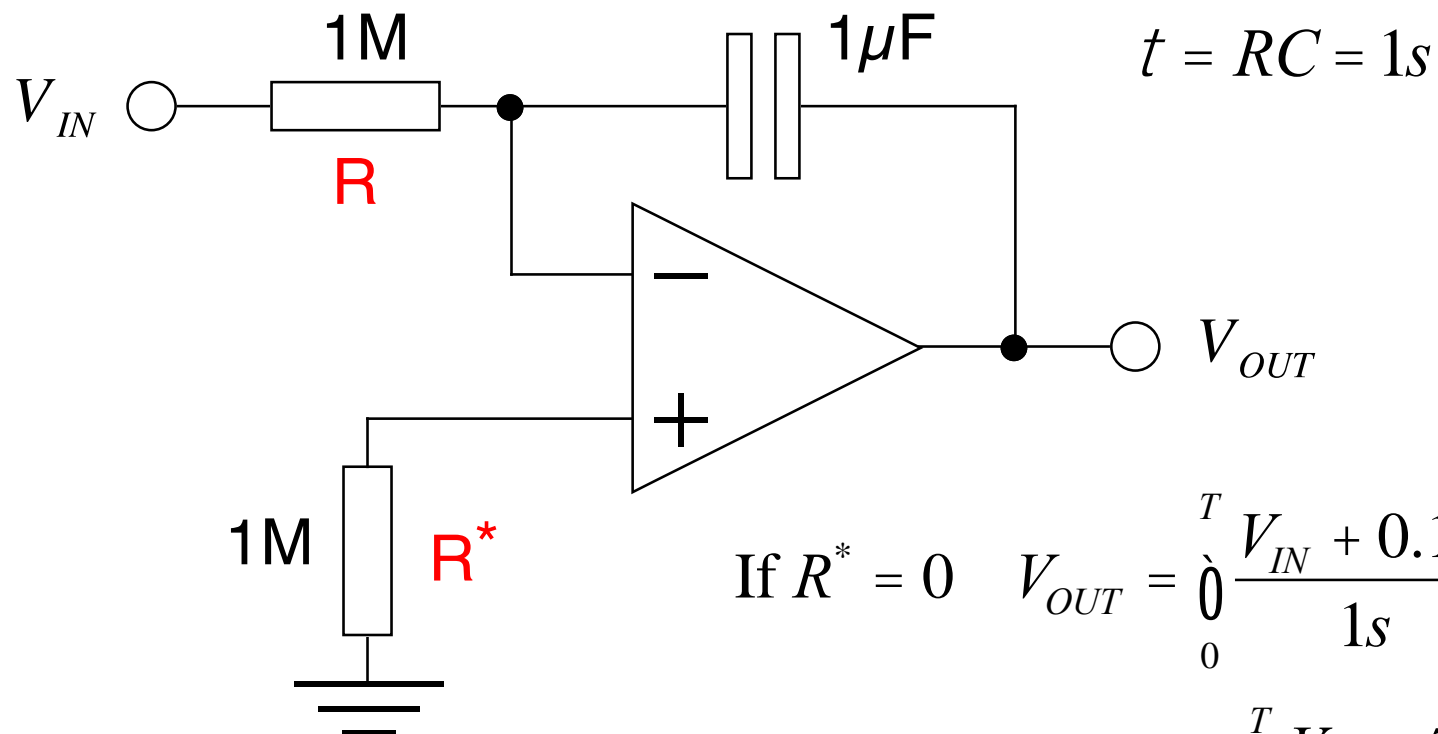

$$\text{If } R^* = 0 \quad V_{OUT} = \int_0^T \frac{V_{IN} + 0.1V}{1s} dt$$

$$\text{If } R^* = 1M \quad V_{OUT} = \int_0^T \frac{V_{IN} + 5mV}{1s} dt$$

Note that the current error corresponds to a change to the **input voltage**. If $R^*=1M$ then the error is “5mV Referred to input”, RTI



University
of Glasgow

Thank you
谢谢

INSPIRING
PEOPLE

#UofGWorldChangers



@UofGlasgow