


Tutorial 4 for CAD

Sample Questions and Exercises

2019 Fall

1 Natural Response of RC Circuit

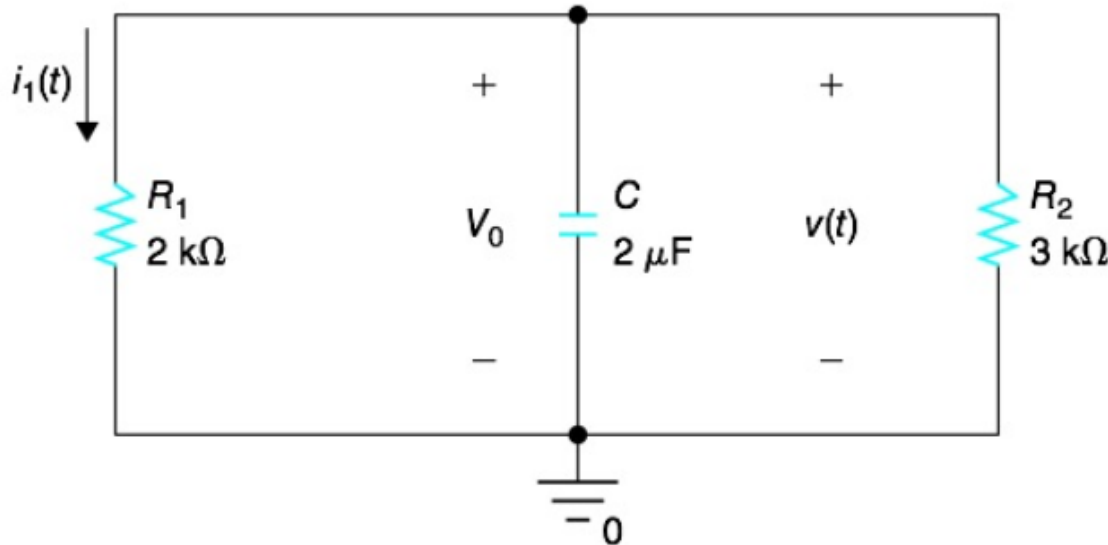
- The initial voltage across the capacitor at $t=0$ in the circuit shown below is $V_0 = 3\text{V}$



- Find voltage $v(t)$, $t \geq 0$, across capacitor C .
- Find current $i_1(t)$, $t \geq 0$, through resistor R_1 .


2 Step Response of RC Circuit

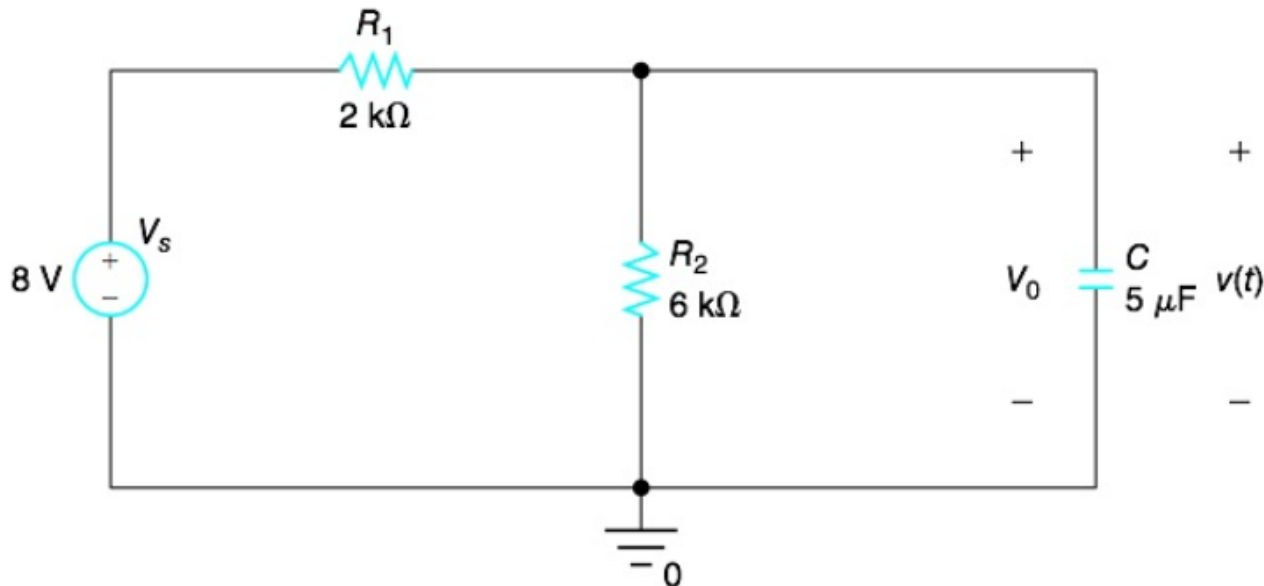- The initial voltage across the capacitor at $t = 0$ in the circuit shown below is 1V. Voltage V_s is applied at $t=0$; that is, $V_s = 8 u(t)$ V. Find voltage $v(t)$, $t \geq 0$, across the capacitor.



3 Natural Response of RL Circuit

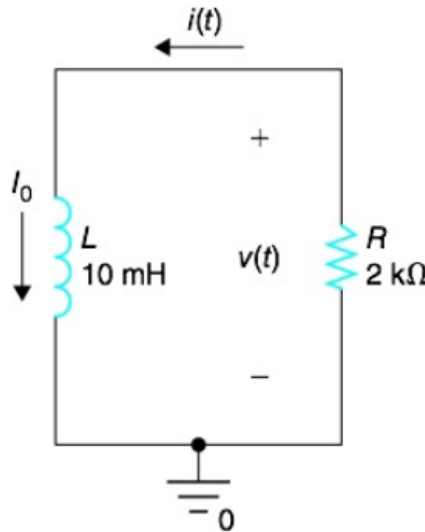
- The initial current through the inductor at $t=0$ in the circuit shown below is 5 mA.



- Find the current $i(t)$, $t \geq 0$, through the inductor and plot $i(t)$.
- Find voltage $v(t)$, $t \geq 0$, across the inductor and plot $v(t)$.

4 Step Response of RL Circuit

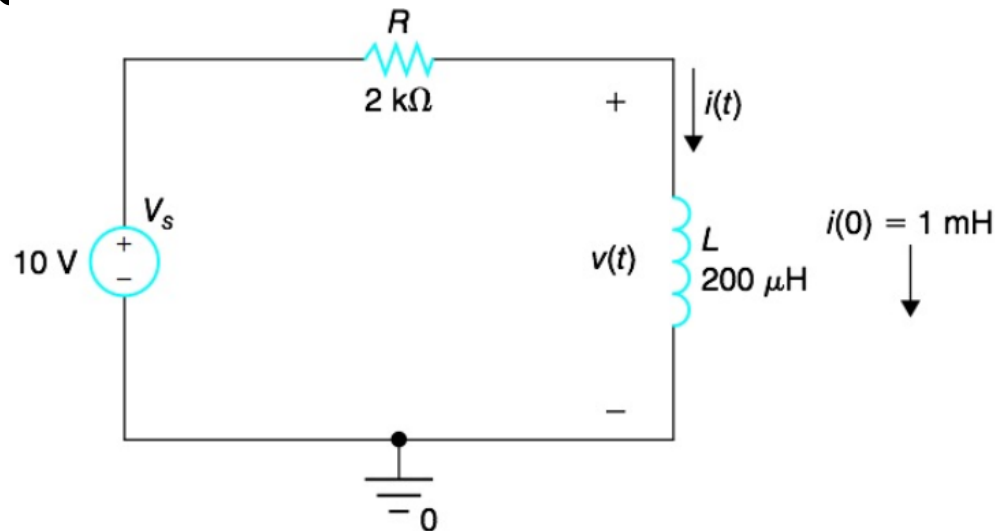
- The initial current through the inductor at $t=0$ in the circuit shown below is 1mA. The voltage V_s is applied at $t=0$: that is. $V_s=10u(s)$ V.



- Find current $i(t)$, $t \geq 0$, through the inductor and plot $i(t)$.
- Find voltage $v(t)$, $t \geq 0$, across the inductor and plot $v(t)$.

5 Step Response of a Series RLC Circuit

- In the circuit shown below

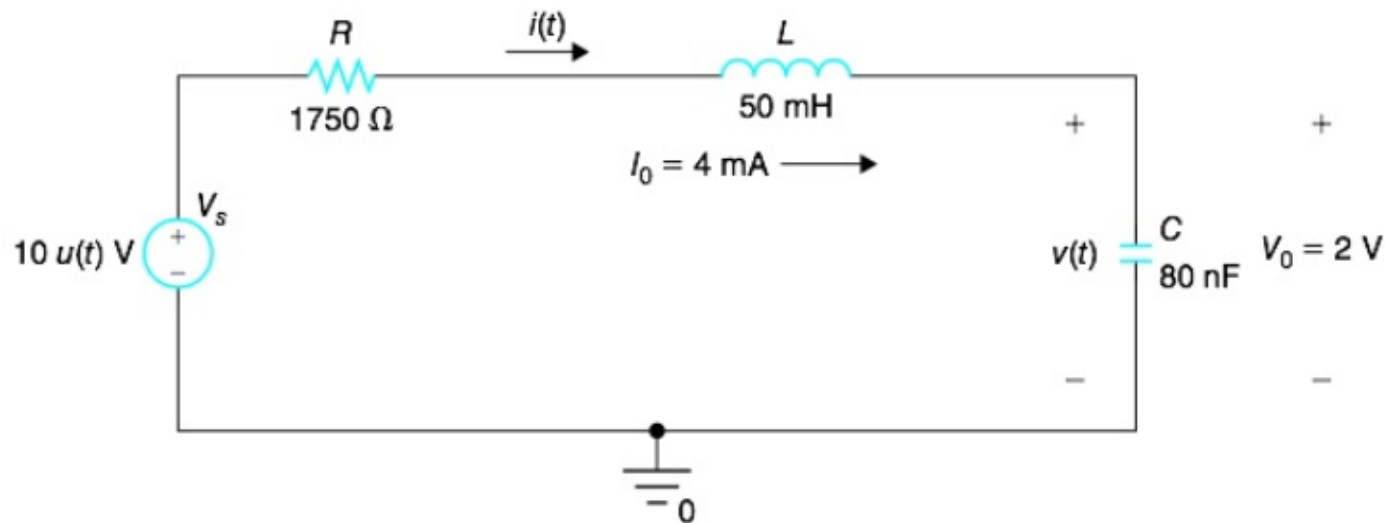

(Questions are in next page)

5 Step Response of a Series RLC Circuit

- a. find α .
- b. find ω_0 .
- c. write a differential equation in $v(t)$.
- d. find the characteristic equation.
- e. find the roots of the characteristic equation.
- f. find the final value of voltage $v(t)$ across the capacitor.
- g. find voltage $v(t)$ across the capacitor for $t \geq 0$ and plot $v(t)$.
- h. find current $i(t)$ for $t \geq 0$ and plot $i(t)$.