
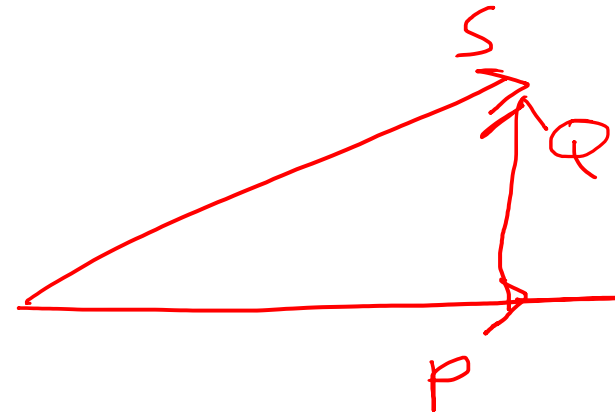


Transformers Example

26th October 2021

Q1

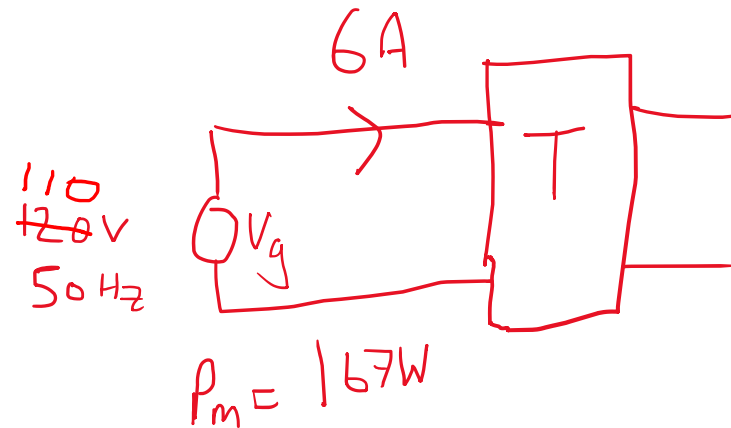


Apparent power supplied to core:

$$S_m = V_g I_o = \underline{110 \times 6} = \underline{660 \text{ VA}}$$

$$\text{Iron Losses} = P_m = \underline{167 \text{ W}}$$

$$\therefore \text{Reactive power absorbed by core} = \underline{Q_m} = \sqrt{S_m^2 - P_m^2} = \sqrt{660^2 - 167^2} = \underline{638.5 \text{ VAR}}$$

VAR

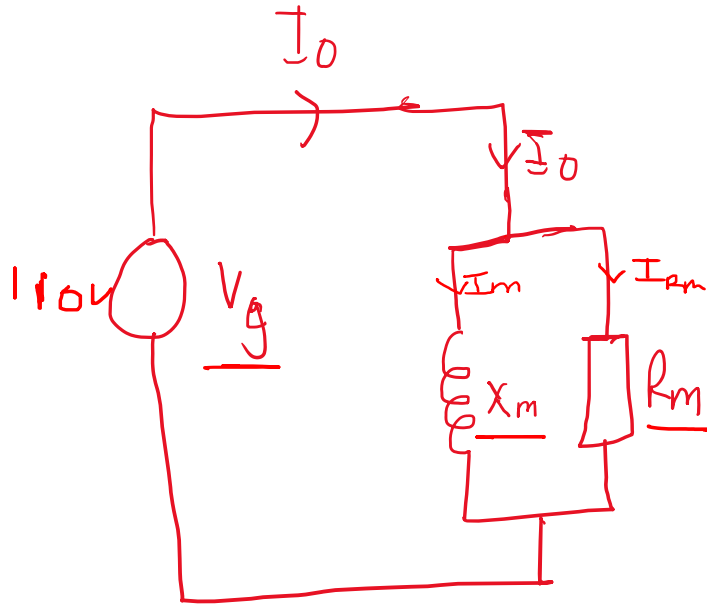

For part (b) and (c) we need to find X_m and R_m

$$R_m = \frac{V_g^2}{P_m} = \frac{110^2}{167} = \underline{72.5\Omega}$$

$$(c) \quad X_m = \frac{V_g^2}{Q_m} = \frac{110^2}{638.5} = \underline{18.95\Omega}$$

$$(b) \quad \underline{Z_m} = R_m // X_m = \frac{72.5 \times j18.95}{72.5 + j18.95} = \frac{1373.9 \angle 90^\circ}{74.94 \angle 14.65^\circ} = \underline{18.3 \angle 75.35^\circ \Omega}$$


Magnetizing Current:

$$I_m = \frac{V_g}{jX_m} = \frac{110}{18.95 \angle 90^\circ} = 5.8A$$


$$\underline{5.8 \angle -90^\circ A}$$

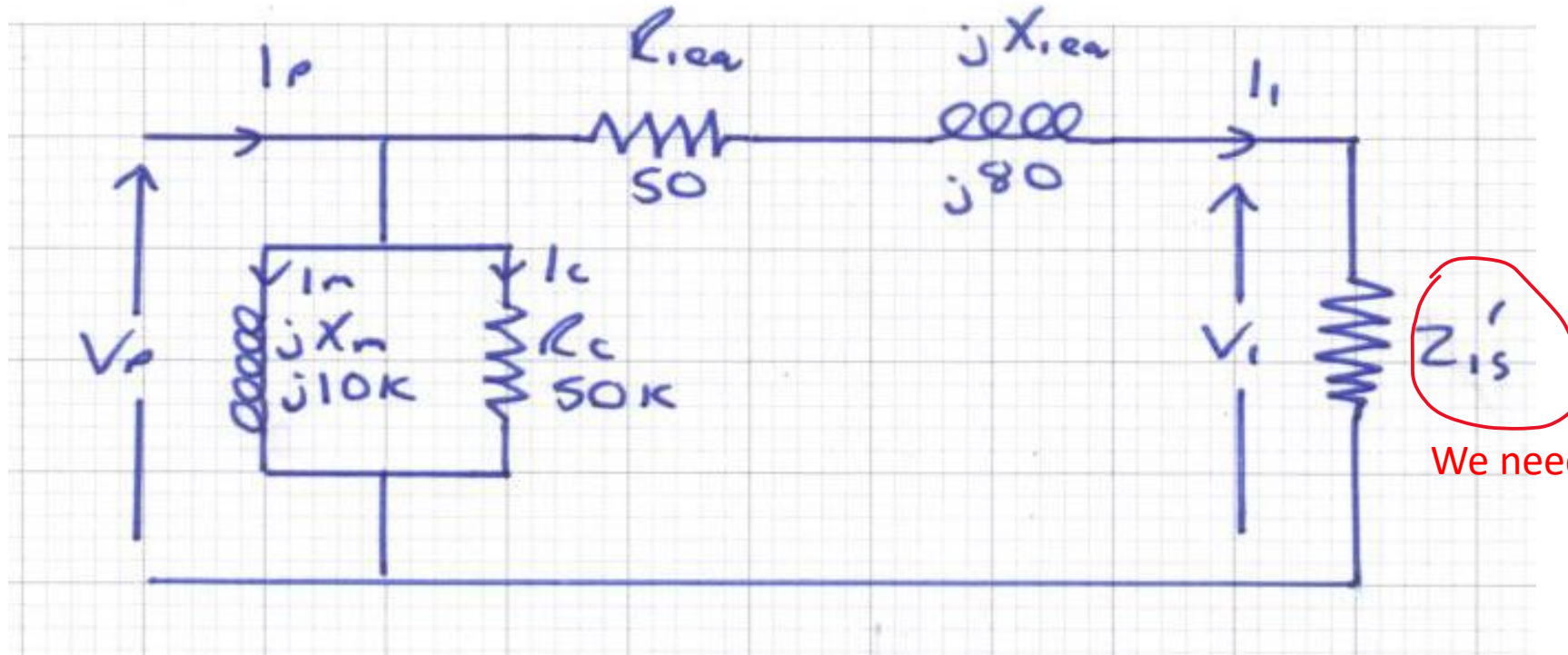Q2

Remember: Draw diagrams when solving problems. It makes it easier to see what you are doing (and easier to give better marks !)




We need to find this

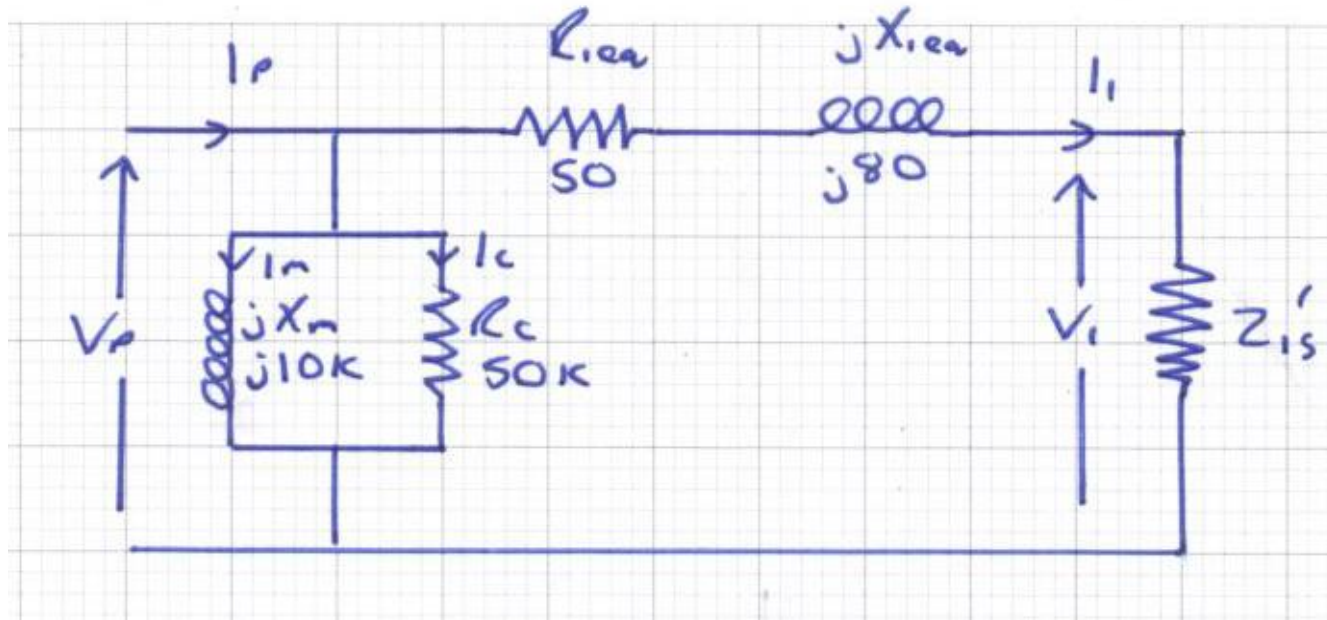

A resistive load of 1.6Ω is connected across the secondary terminals of a 10kV/400V transformer.

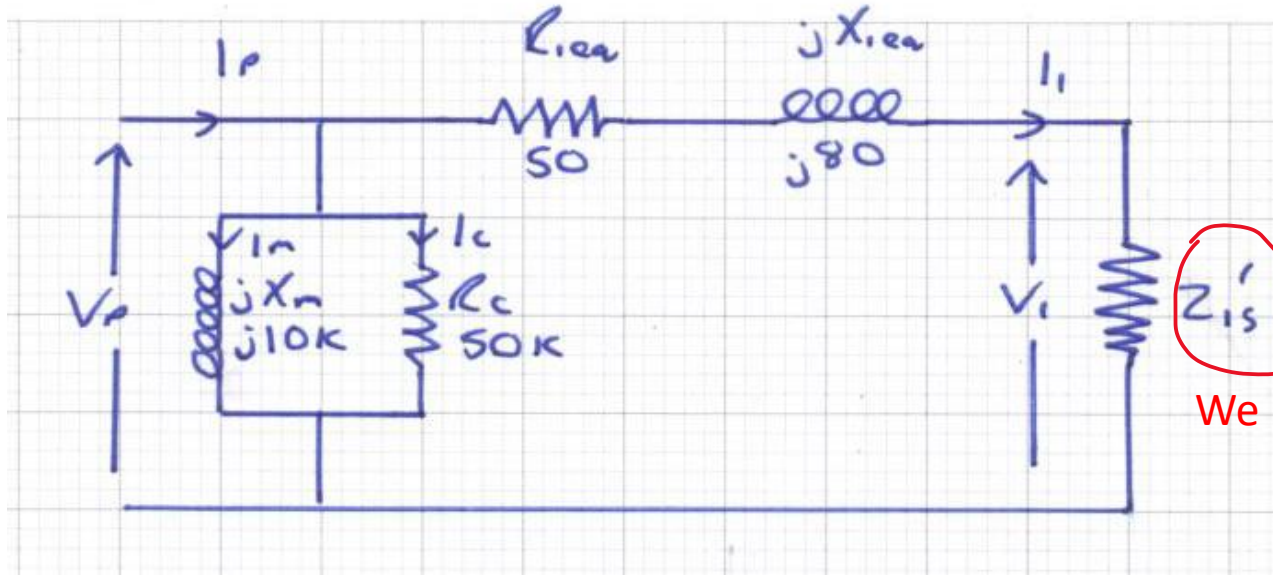
$$\text{Turns Ratio} = \frac{V_P}{V_{Soc}} = \frac{10000}{400} = 25$$



We need to find this

$$Z'_{1s} = (\text{Turns Ratio})^2 \times Z_s = 25^2 \times 1.6 = 1000 \, \Omega$$

The output current (I_s)

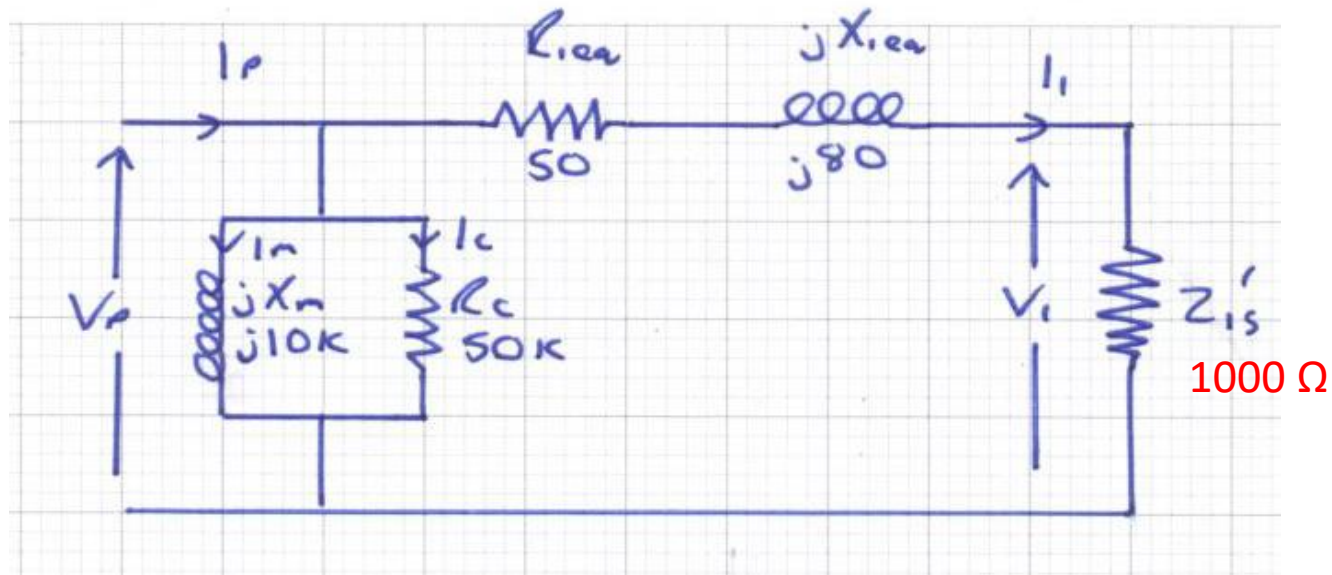


$$V_p = I_1 (R_{1eq} + jX_{1eq} + Z'_{1s})$$

$$\therefore I_1 = \frac{V_p}{R_{1eq} + jX_{1eq} + Z'_{1s}} = \frac{10000}{1050 + j80} = \frac{10000 \angle 0^\circ}{1053 \angle 4.35^\circ} = 9.5 \angle -4.35^\circ \text{ A}$$

$$I_s = \left(\frac{n_p}{n_s} \right) I_1 = 25 \times 9.5 \angle -4.35^\circ = 237.5 \angle -4.35^\circ \text{ A}$$


The output voltage under load (V_s)

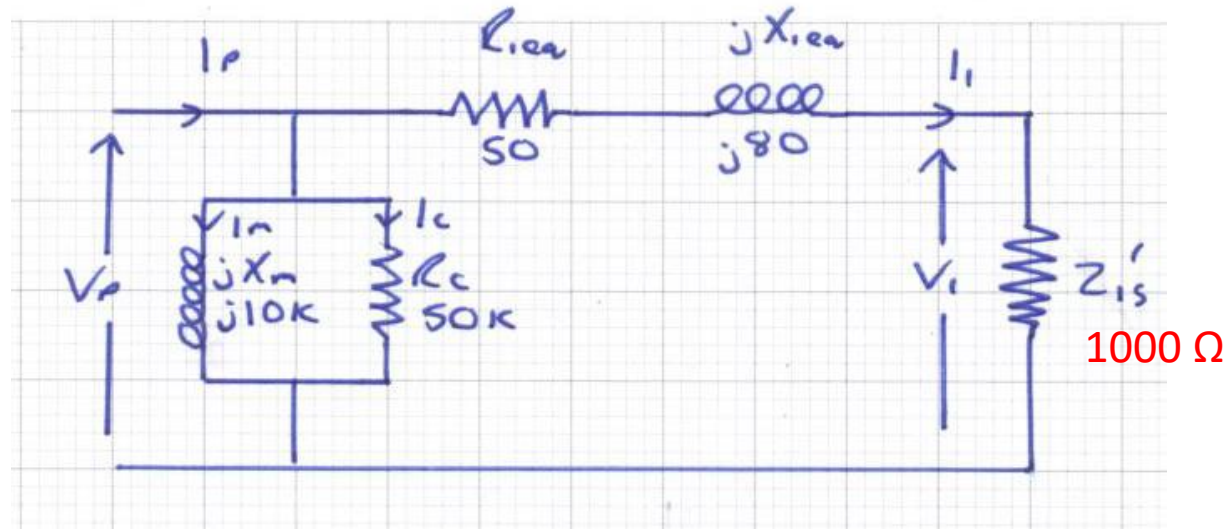

$$V_1 = I_1 Z'_{1s} = 9.5 \angle -4.35^\circ \times 1000 \angle 0^\circ = 9500 \angle -4.35^\circ \text{ V}$$

$$V_s = \left(\frac{n_s}{n_p} \right) V_1 = \frac{1}{25} \times 9500 \angle -4.35^\circ = 380 \angle -4.35^\circ \text{ V}$$


The iron and copper loss

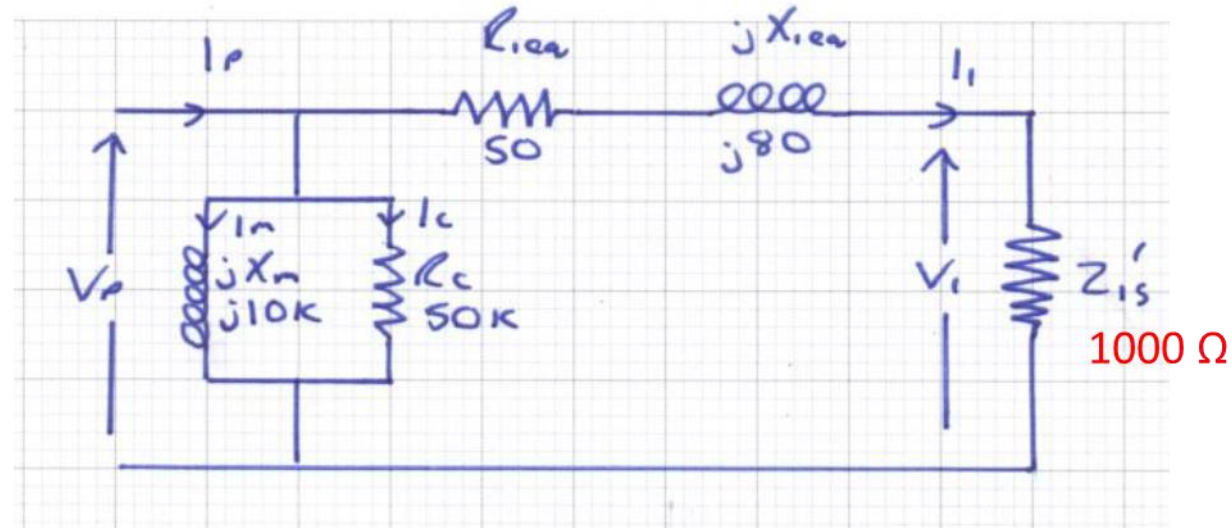

$$\text{Iron Loss } P_{iron} = \frac{V_p^2}{R_c} = \frac{10000^2}{50000} = 2 \text{ kW}$$


$$\text{Copper Loss } P_{Cu} = I_1^2 R_{1eq} = 9.5^2 \times 50 = 4.51 \text{ kW}$$

The magnetising current (I_m)

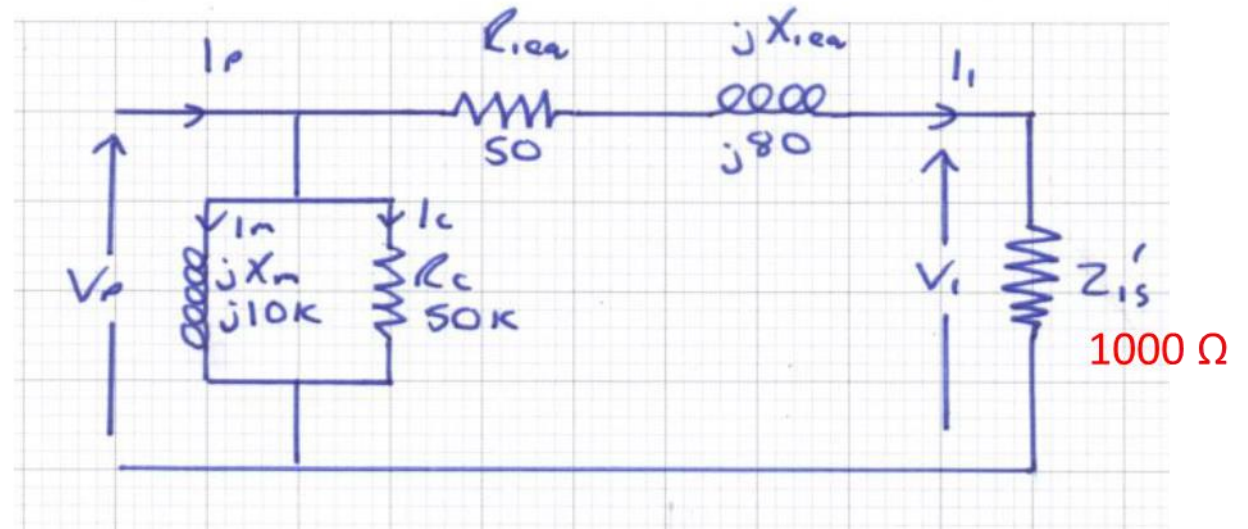

$$\text{Magnetizing Current } I_m = \frac{V_p}{jX_n} = \frac{10000 \angle 0^\circ}{10000 \angle 90^\circ} = 1 \angle -90^\circ \text{ A}$$

The Input Current (I_p)

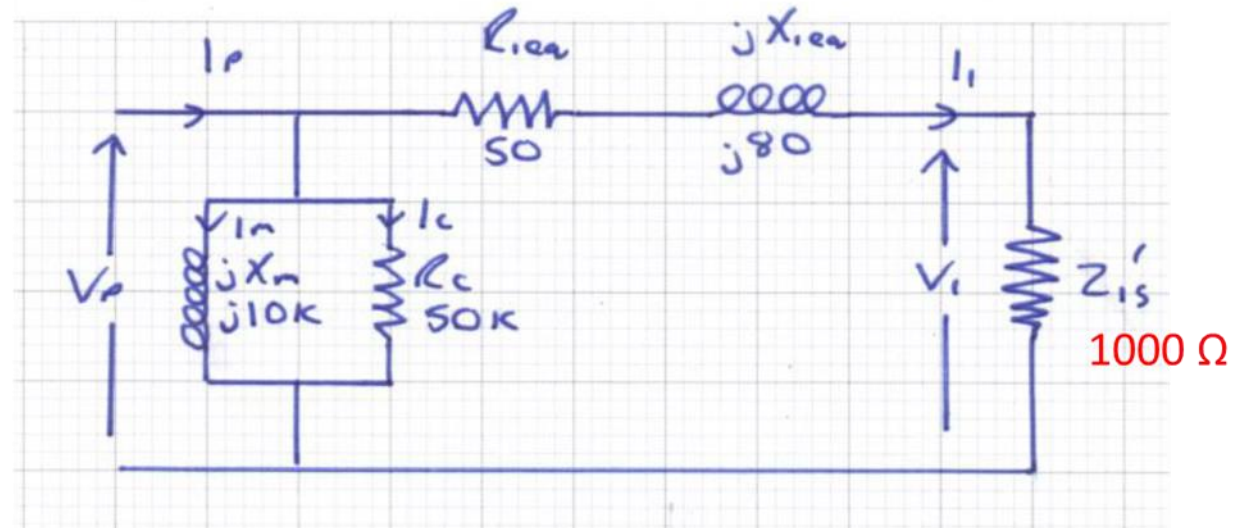

$$I_p = I_1 + I_m + I_c$$


$$I_1 = 9.5 \angle -4.35^\circ = 9.47 - j0.75 \text{ A}$$

$$I_m = 1 \angle -90^\circ = 0 - j1 \text{ A}$$


$$I_c = \frac{V_p}{R_c} = \frac{10000 \angle 0^\circ}{50000 \angle 0^\circ} = 0.2 \angle 0^\circ = 0.2 + j0 \text{ A}$$

$$\therefore I_p = 9.47 - j0.75 - j1 + 0.2 = 9.67 - j1.75 = 9.83 \angle -10.3^\circ \text{ A}$$

Q3

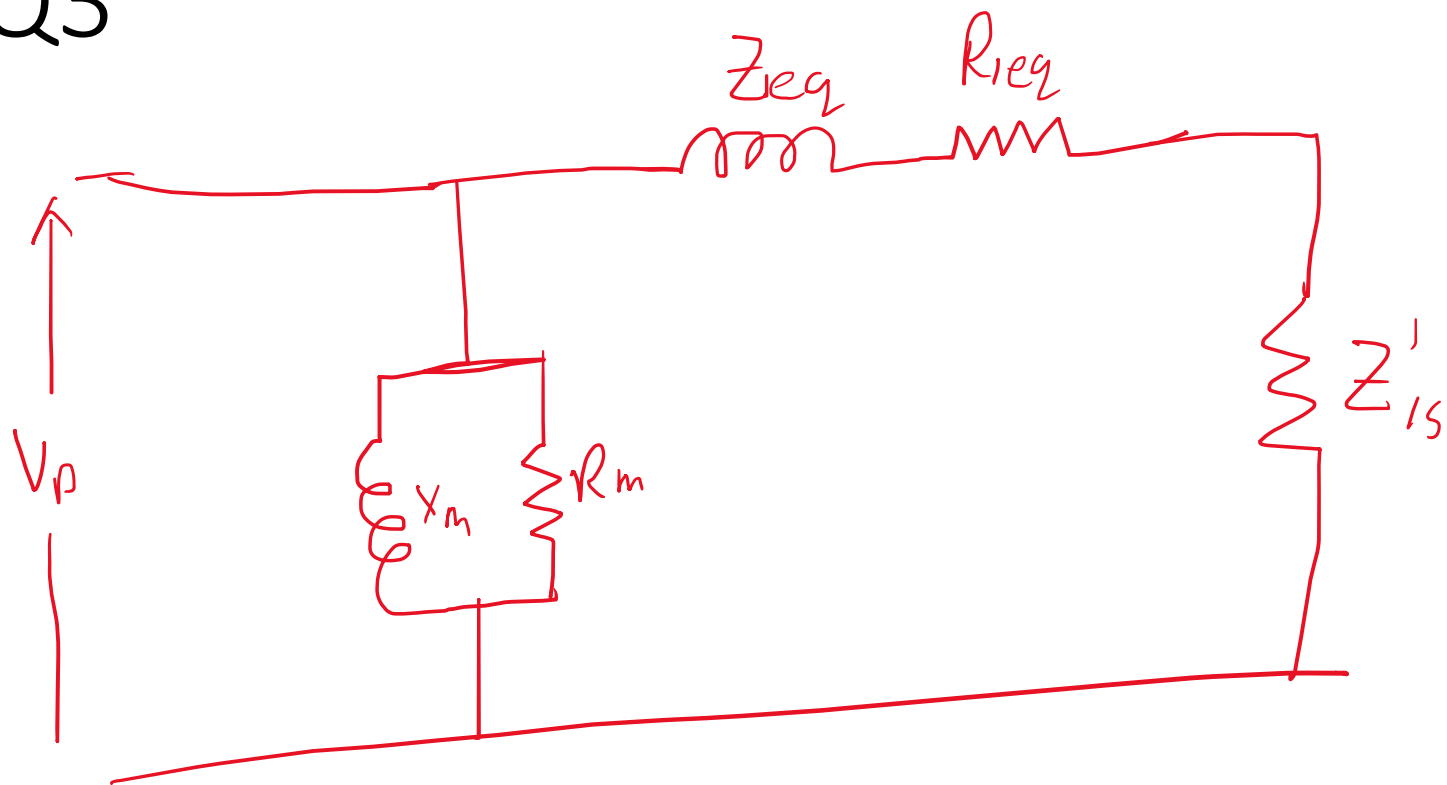

Open Circuit Test

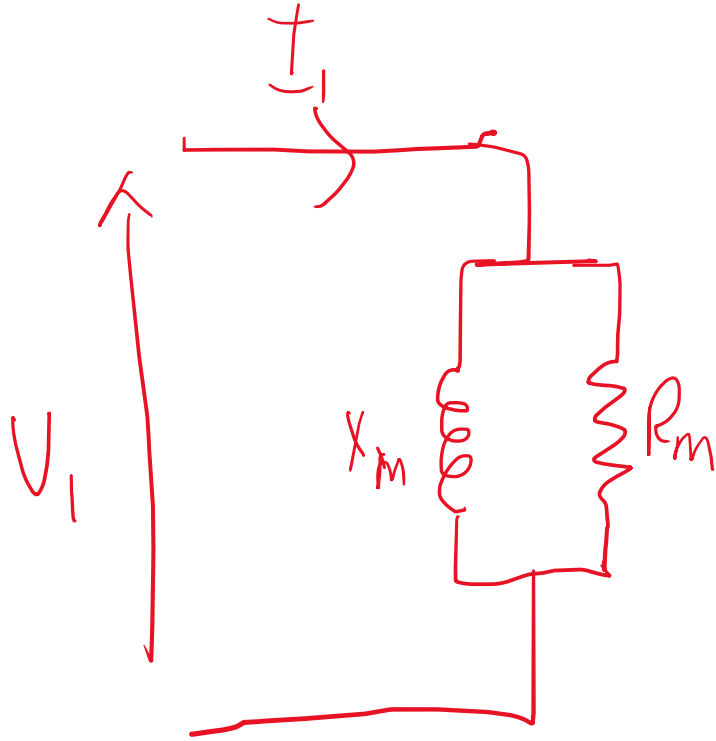

$$\text{Turns Ratio} = \frac{230}{110} = 2.1$$

$$R_m = \frac{V_1^2}{P_{in}} = \frac{230^2}{30} = 1763.3\Omega$$

$$S_p = V_1 I_1 = 230 \times 2 = 460 \text{ VA}$$

$$Q_p = \sqrt{S_p^2 - P_{in}^2} = 459 \text{ VA}_r$$

$$X_m = \frac{V_1^2}{Q_p} = \frac{230^2}{459} = 115.3\Omega$$

Short Circuit Test



$$R_{1eq} = \frac{P_{in}}{I_1^2} = \frac{200}{22^2} = 0.413 \, \Omega$$

$$S_{sc} = V_1 I_1 = 40 \times 22 = 880 \, \text{VA}$$

$$Q_{sc} = \sqrt{S^2 - P^2} = \sqrt{880^2 - 200^2} = 857 \, \text{VAr}$$

$$X_{1eq} = \frac{Q_{sc}}{I_1^2} = \frac{857}{22^2} = 1.77 \, \Omega$$