

Electronic System Design

Lecture 3-4: OpAmp Imperfections Static Errors


Dr Duncan Bremner




Mismatches in the input stage of an opamp will lead to an error in measuring the input *voltage* difference:

Modelling the opamp as an input stage followed by a high gain differential amplifier (an opamp!)

Voltage follower:

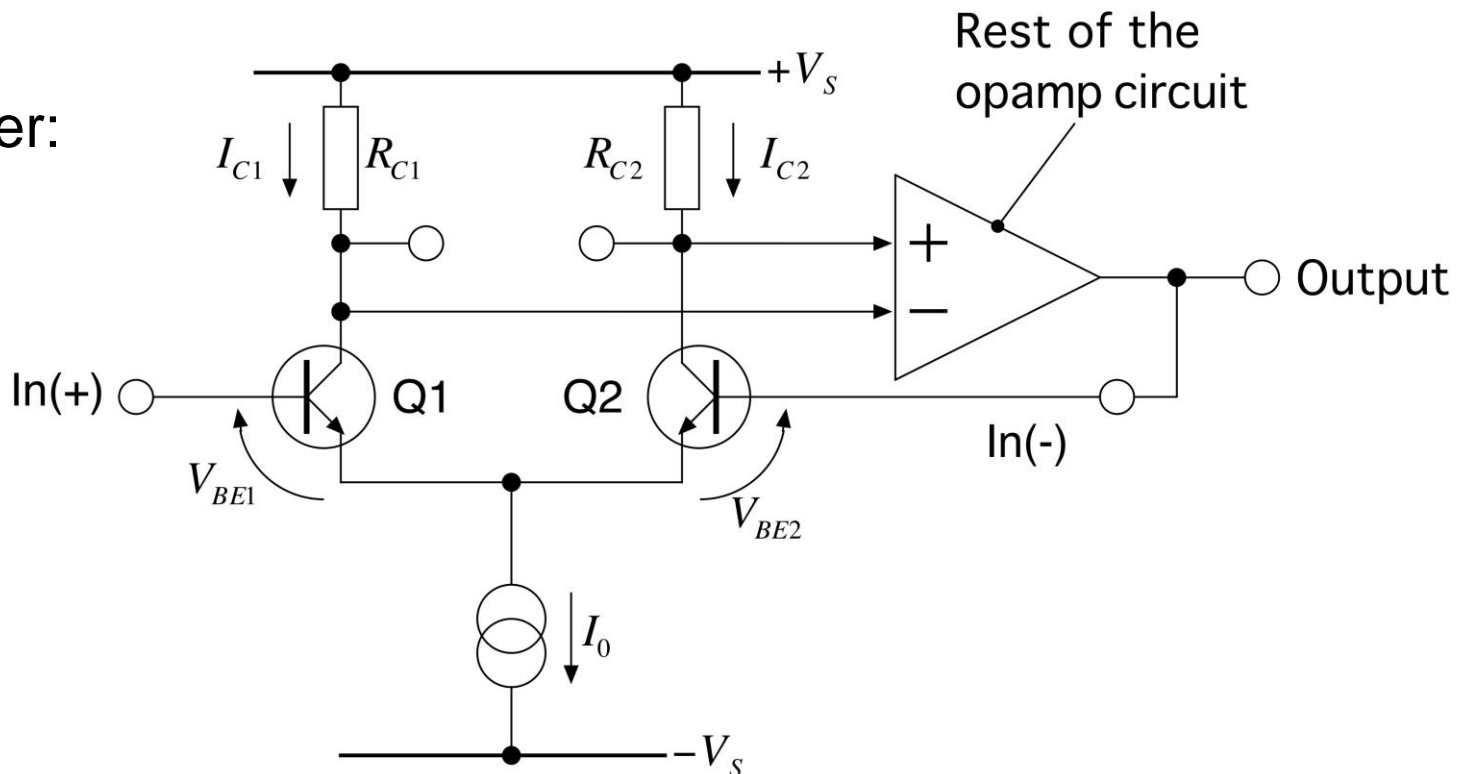

Imperfect Opamps (2)

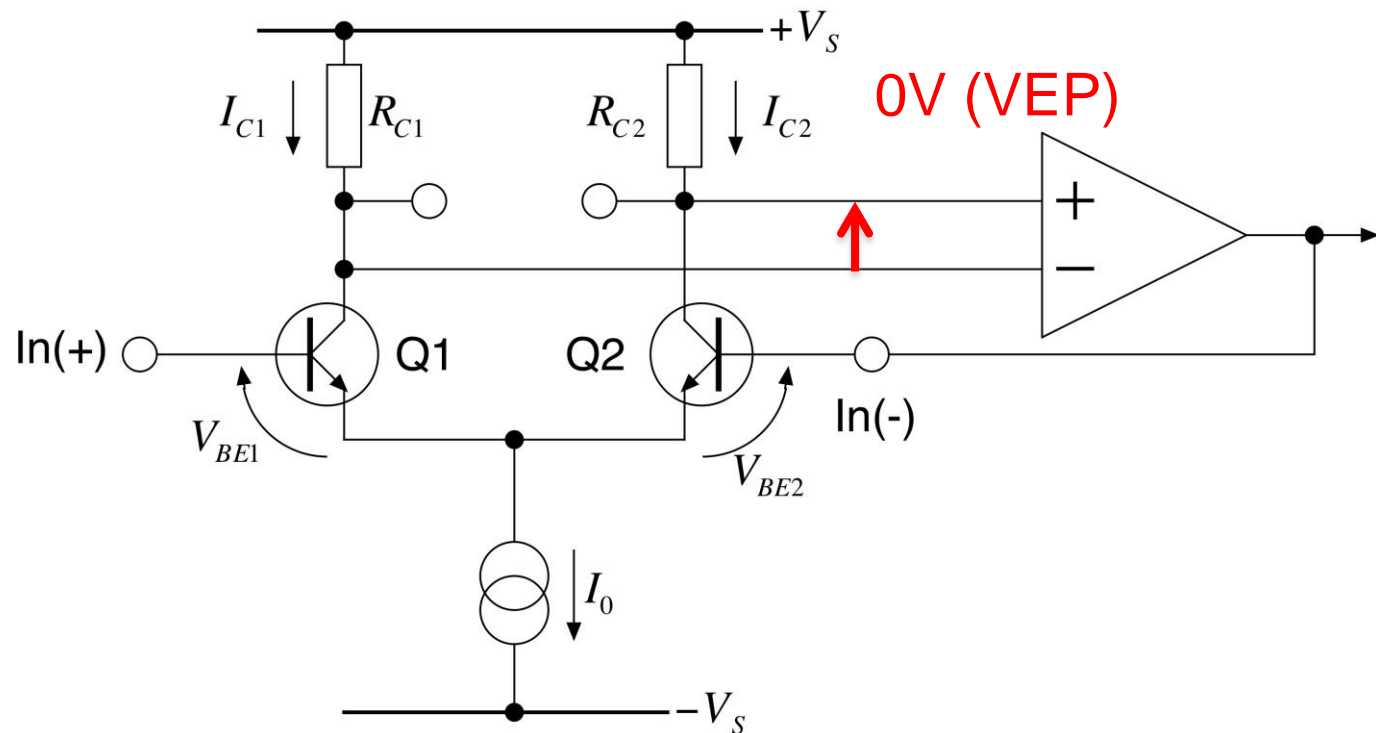


Virtual earth principle makes the two collector voltages equal

If $R_{C1} = R_{C2}$ then it follows that $I_{C1} = I_{C2}$



Imperfect Opamps (2)

 For identical transistors $I_{C1} = I_{C2}$ for $\ln(+)=\ln(-)$



The two transistors are different: $I_{S1} \neq I_{S2}$

$$I_{C1} = I_{S1} \cdot e^{qV_{BE1}/k_B T} \quad \text{Where} \quad \frac{k_B T}{q} \gg 25mV$$
$$I_{C2} = I_{S2} \cdot e^{qV_{BE2}/k_B T}$$

If we require that $I_{C1} = I_{C2}$ then we must have $I_{S1} \cdot e^{V_{BE1}/25mV} = I_{S2} \cdot e^{V_{BE2}/25mV}$


In other words $V_{BE1} \neq V_{BE2}$

To multiply by a constant factor of $\frac{I_{S1}}{I_{S2}}$ we need to add a voltage into the exponential:

$$I_{S1} \cdot e^{V_{BE1} + \frac{\delta}{2} / 25mV} = I_{S2} \cdot e^{V_{BE2} - \frac{\delta}{2} / 25mV}$$

Then the feedback loop balances when there is a small difference δ between inputs

Imperfect Opamps (2)

 

Since the scale of the curve is V_T and the transistor matching is good we expect the value of δ to be less than V_T : 25mV

Looking at 110 bipolar opamps from RS:

29 Have offset voltage $< 0.1\text{mV}$

26 Have offset voltage $< 0.2\text{mV}$


6 Have offset voltage $< 1\text{mV}$

14 Have offset voltage $< 5\text{mV}$

29 Have offset voltage $< 25\text{mV}$


Only 6 have offset voltage $> 25\text{mV}$

Offset Voltage (2)

 

Feedback makes $V_{IN(-)}$ equal to $V_{IN(+)} +$ an **Offset Voltage**

Equivalent circuit

 


Offset voltage (3)


Note that V_{OS} can be in series with either input

Choose whichever makes analysis easier

 Theoretically need to change sign of source but.....



OP181/OP281/OP481—Typical

 

OP181 Spec:

$V_{OS} = 1.5 \text{ mV Max}$

6-sigma specification

$\sigma = 250 \mu V$


Offset results from inequivalence of input transistors:

Statistical, average is 0: **Can have either sign.**

Can be in series with either input unchanged, as the sign is undefined.




How to fix it Old days: “Offset Nulling”

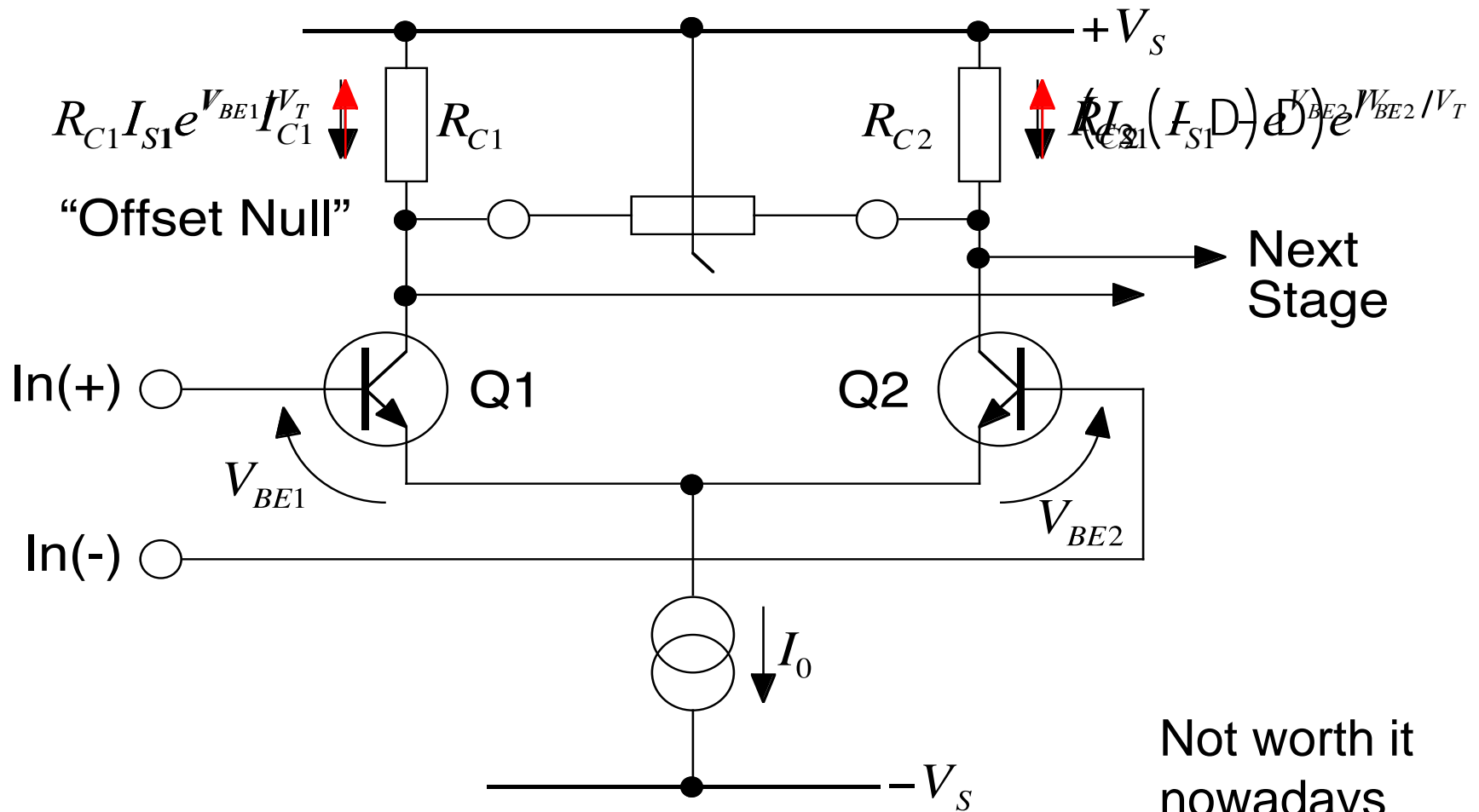

Offset Voltage (6)

Better methods:

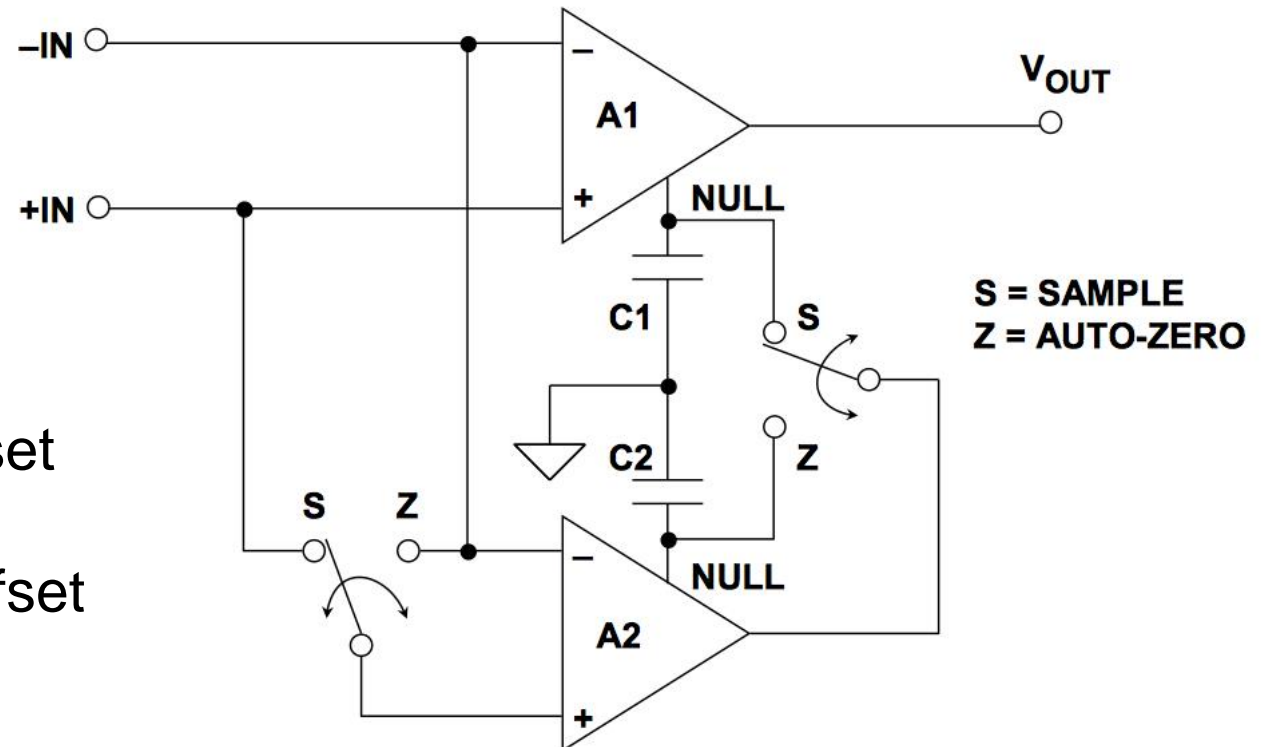- Buy a better conventional opamp
- In a digitizing system measure offset and subtract in software
- **Chopper stabilization:**



Z: A2 measures and corrects its own offset voltage

S: A2 corrects A1 offset voltage

Chopper Stabilization:

Lowest V_{OS} (TLC2652 $1\mu V$ max!)

Low I_B (CMOS amplifier)

Zero $1/f$ noise (will become clear later)

Compatible with single supply operation / low power

Full bandwidth linear amplification

Enormous DC gain ($A1 + A2$ gains!)

BUT


Switching noise at $\approx 10\text{kHz}$

Multiple chopper amplifiers: Switching noise can beat at low frequencies (needs to be synchronized)

Saturation of $A1$ leads to a big voltage difference which $A2$ tries to correct: Insanely slow recovery from saturation / power-up

Use for special occasions only!


Example 1 Inverting Amplifier

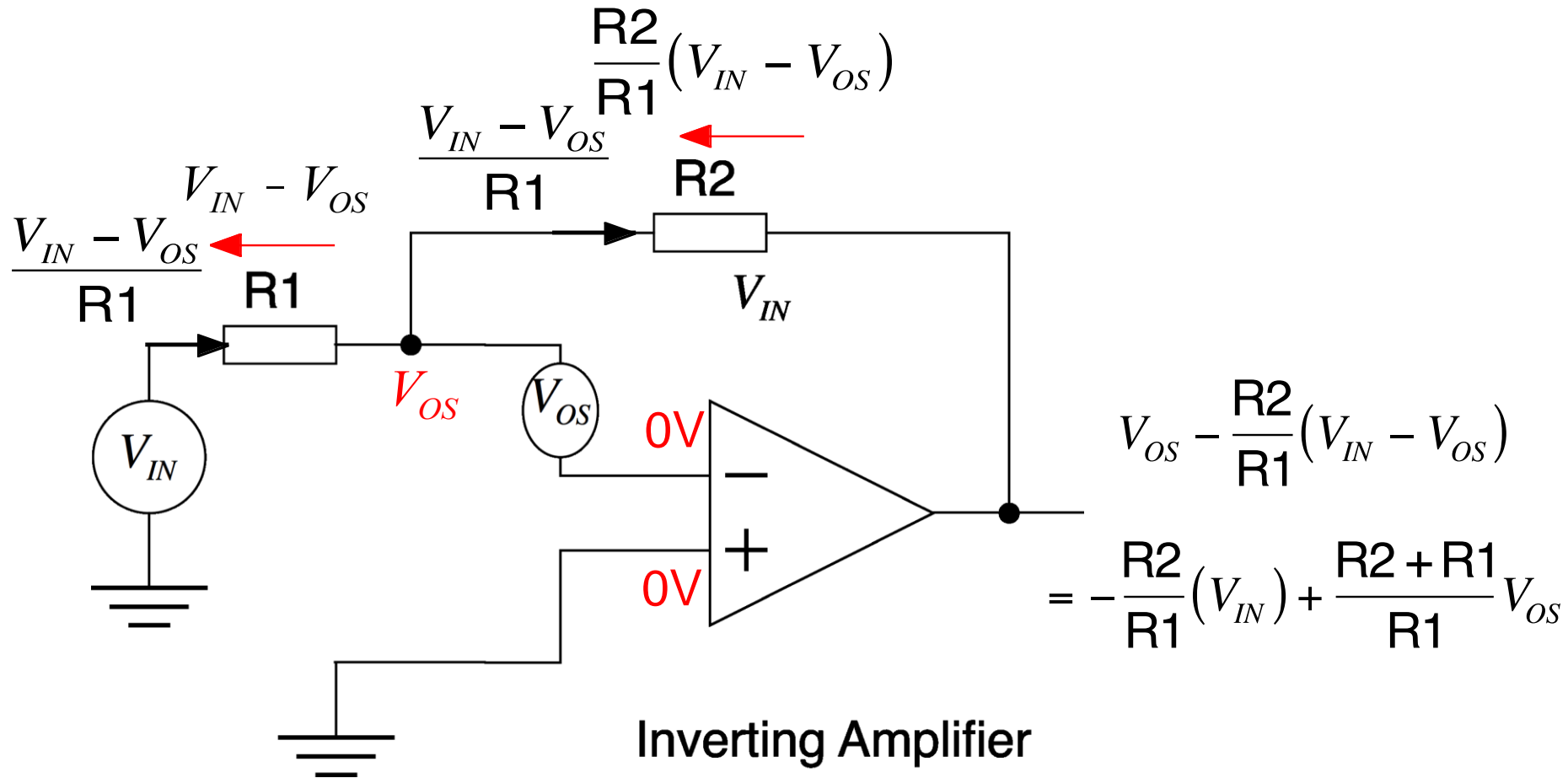

Noninverting gain for V_{OS} error

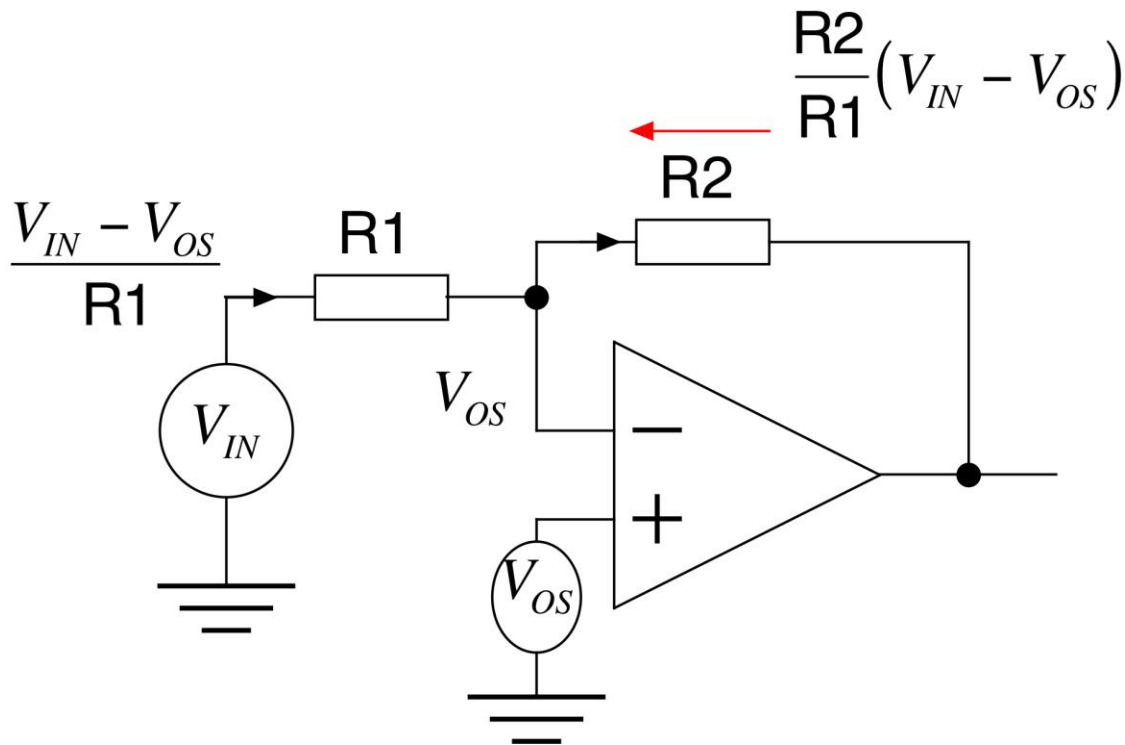Example 1 (again)

V_{OS} is a source representing a lack of symmetry: It can be placed in Series with **either** input




$$V_{OS} - \frac{R2}{R1}(V_{IN} - V_{OS})$$


$$= -\frac{R2}{R1}V_{IN} + \frac{R2+R1}{R1}V_{OS}$$

1: Sign doesn't matter 2: Simpler calculation 3: Noninverting gain!



Example 2 Noninverting Amplifier

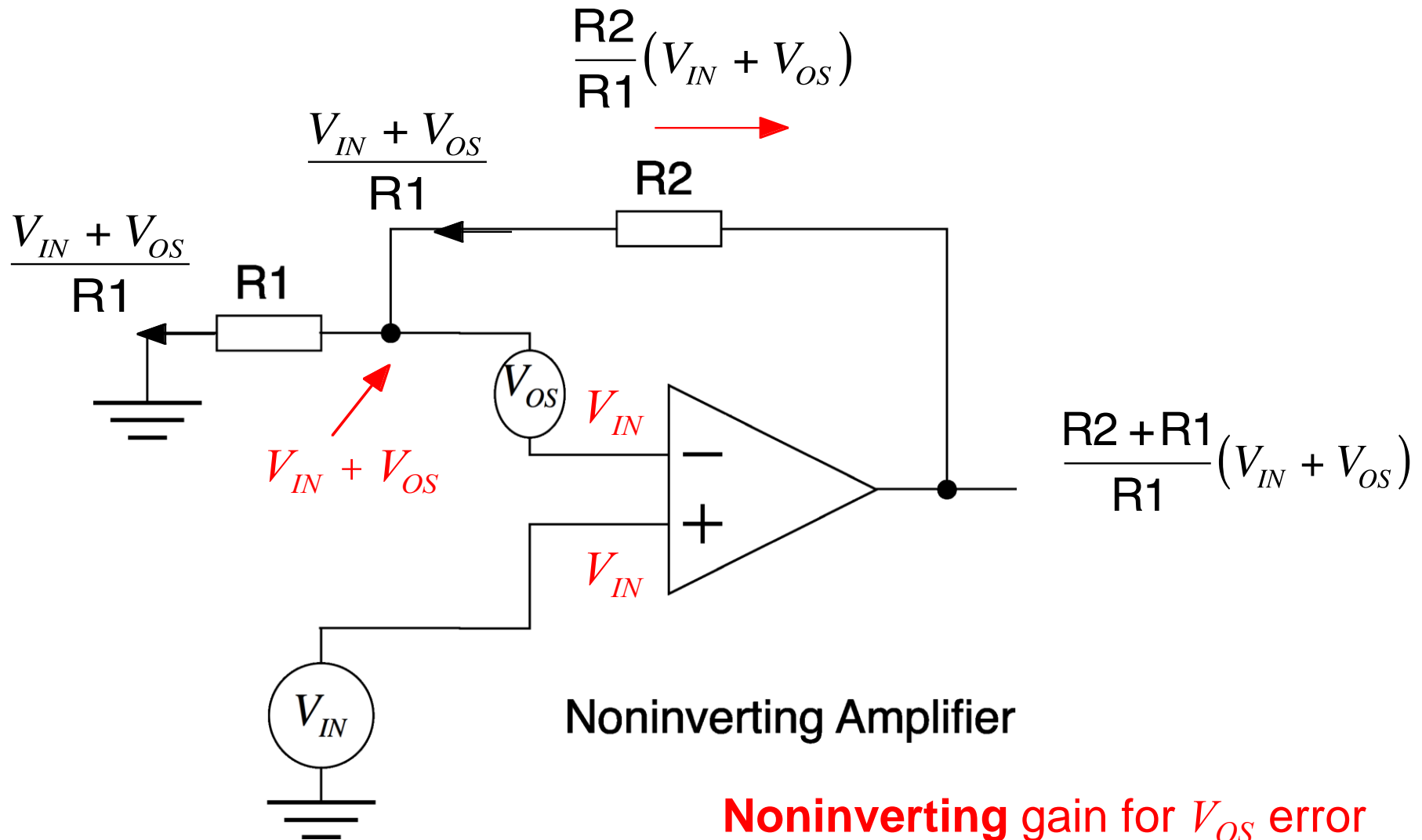


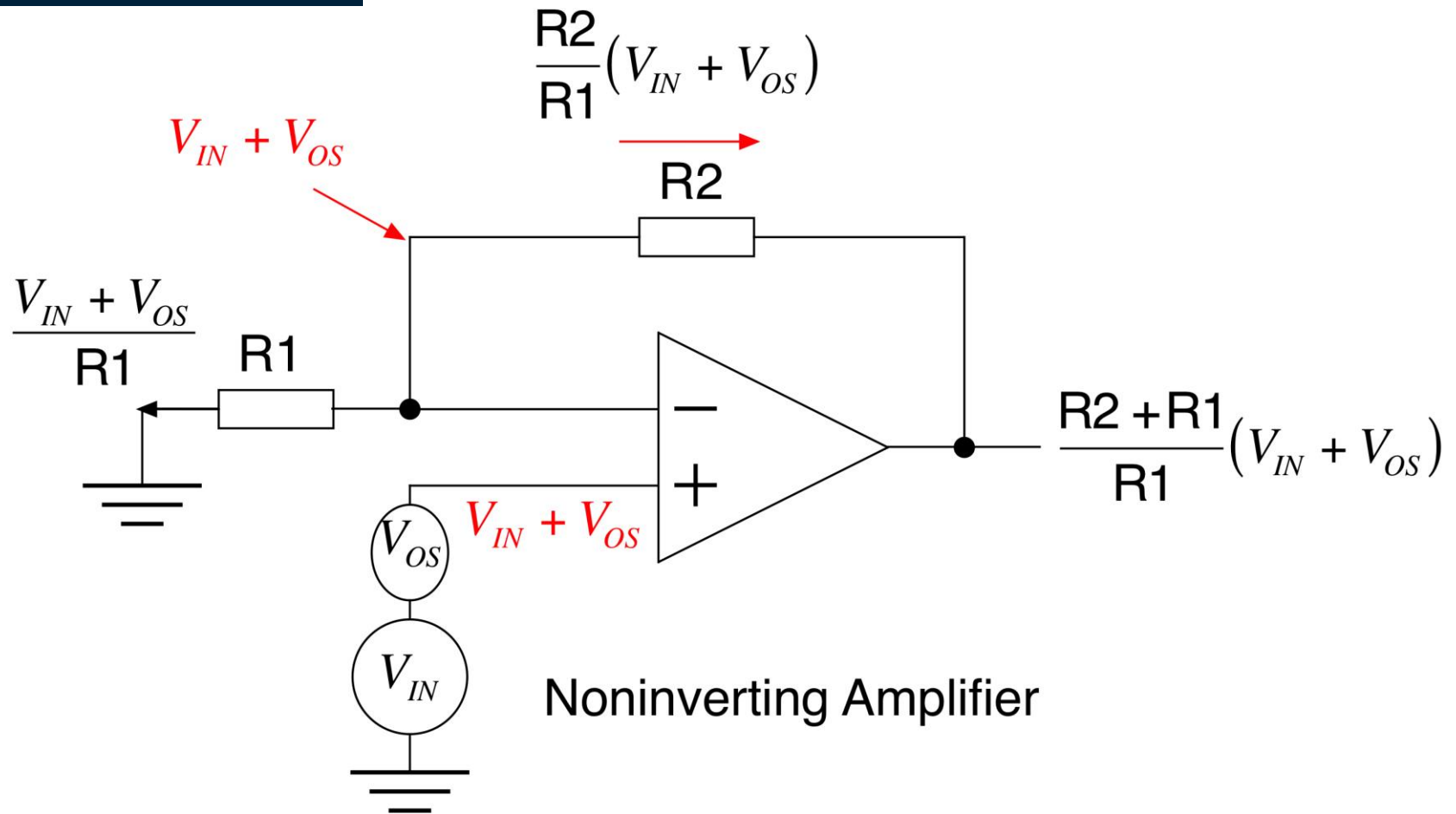

Same result by a more obvious method

Design example

Thermocouple Amplifier

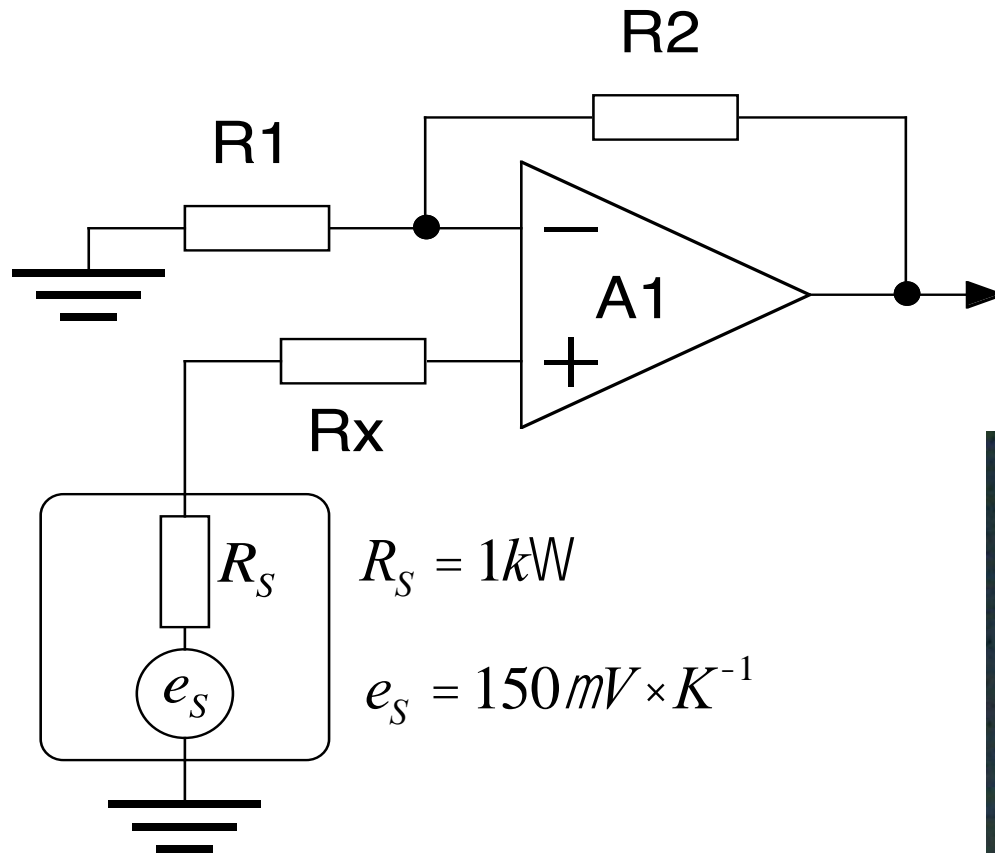


Specification:

$$O/P = 10mV K^{-1}$$

Better than 1K accuracy

At 20K difference

 


Picture Courtesy Erik Johansson

Design Example (2)

$$150\mu V \cdot K^{-1} \rightarrow 10mV \cdot K^{-1} \quad \therefore \text{Gain} = 67$$

Naïve Design:

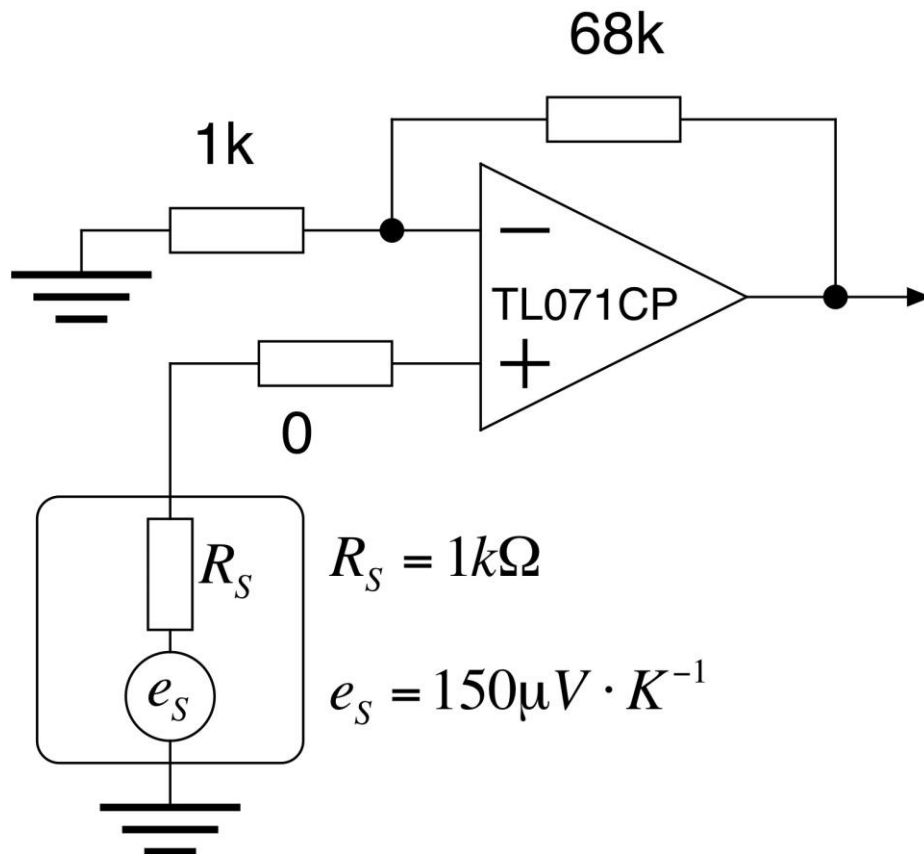

(1% resistors)

Errors to consider

Offset voltage
Bias Current
Offset Current
Gain Error

electrical characteristics, $V_{CC\pm} = \pm 15\text{ V}$ (unless otherwise noted)

PARAMETER		TEST CONDITIONS†		T _A ‡	TL071C TL072C TL074C			TL071AC TL072AC TL074AC			TL071BC TL072BC TL074BC			TL071I TL072I TL074I			UNIT
					MIN	TYP	MAX	MIN	TYP	MAX	MIN	TYP	MAX	MIN	TYP	MAX	
V _{IO}	Input offset voltage	V _O = 0,	R _S = 50 Ω	25°C	3 10			3 6			2 3			3 6			mV
				Full range	13			7.5			5			8			
αV _{IO}	Temperature coefficient of input offset voltage	V _O = 0,	R _S = 50 Ω	Full range	18			18			18			18			μV/°C
I _{IO}	Input offset current	V _O = 0		25°C	5 100			5 100			5 100			5 100			pA
				Full range	10			2			2			2			nA
I _{IB}	Input bias current§	V _O = 0		25°C	65 200			65 200			65 200			65 200			pA
				Full range	7			7			7			20			nA
V _{ICR}	Common-mode input voltage range				±11	-12 to 15		±11	-12 to 15		±11	-12 to 15		±11	-12 to 15		V
V _{OM}	Maximum peak output voltage swing	R _L = 10 kΩ			±13.5			±12 ±13.5			±12 ±13.5			±12 ±13.5			V
		R _L ≥ 10 kΩ			Full range			±12			±12			±12			
		R _L ≥ 2 kΩ			Full range			±10			±10			±10			
A _{VD}	Large-signal differential voltage amplification	V _O = ±10 V, R _L = 8 kΩ		25°C	50 200			50 200			50 200			50 200			V/V

PARAMETER		TEST CONDITION [†]		T _A [‡]	TL071C TL072C TL074C			MIN
					TYP	MAX		
V _{IO}	Input offset voltage	V _O = 0,	R _S = 50 Ω	25°C	3	10		
				Full range		13		
αV _{IO}	Temperature coefficient of input offset voltage	V _O = 0,	R _S = 50 Ω	Full range	18			
I _{IO}	Input offset current	V _O = 0		25°C	5	100		
				Full range		10		
I _{IB}	Input bias current [§]	V _O = 0		25°C	65	200		
				Full range		7		

† All characteristics are measured under open-loop conditions.

‡ Full range is $T_A = 0^\circ\text{C}$ to 70°C for TL07_C, TL07_A.

§ Input bias currents of a FET-input operational amplifier that maintain the junction temperature as close to the ambient temperature as possible.

Design example (3)

Offset Voltage error (Noninverting)

$$V_{OUT} = \frac{R2 + R1}{R1} (V_{IN} + V_{OS})$$


$$V_{OUT} = 69(V_{IN} + V_{OS}) = 69(V_{IN} + 10mV) = 69(V_{IN}) + 690mV$$

Error due to input offset voltage = 69K

Design Example (4)

Bias and offset current error: Assume all other sources zero
(Superposition)



Source impedance = $R1 // R2$

 


Design Example (5)

Currents flowing into inputs are equivalent to voltages in series with the inputs:


Is equivalent to

  

Is equivalent to

 


Note sign!

 


Design example (6)

 
So the current errors appear as input voltage errors



Error due to input current is equivalent to a voltage offset of

$$v_{ierr} = \left[\left(\frac{I_{os}}{2} - I_b \right) (R_X + 1k\Omega) \right] - \left[- \left(\frac{I_{os}}{2} + I_b \right) (R1 // R2) \right] \quad \text{(Note sign)}$$


Design Example (7)

 

Source resistance $R_S = 1k\Omega$ is approximately the same as $1k\Omega // 69k\Omega$, so no matching resistor; **$R_x = 0$**

$$v_{ierr} = \left(\frac{I_{os}}{2} - I_b \right) (R_X + 1k\Omega) + \left(\frac{I_{os}}{2} + I_b \right) (R1 // R2)$$

Error RTO due to current error is

$$\begin{aligned} v_{iout} &= 69 \cdot \left(\left(\frac{I_{os}}{2} - I_b \right) (1k\Omega) + \left(\frac{I_{os}}{2} + I_b \right) (0.986k\Omega) \right) \\ &= 69 \cdot \left(\frac{I_{os} \cdot 1.986k\Omega}{2} - I_b (1 - 0.986k\Omega) \right) \end{aligned}$$

Note that **we don't know** the sign of offset current, or the offset voltage, so we just **take the total magnitude** of the error:

$$v_{iout} = 69 \cdot (I_{OS} \cdot 0.993k\Omega + I_b \cdot 0.014k\Omega)$$

$$I_B = 200pA \quad \therefore \text{error at O/P} = 2.8nV \cdot 69 = 194nV$$

Error due to input bias current = 19.4μK

Offset current error:

$$I_{OS} = 100pA. \text{ error at O/P} = 99nV \cdot 69 = 6.8\mu V \equiv 0.7mK$$

Corrected

Design Example (9)

Summary:

Offset voltage error = 69K

Worst error! Kill! Kill! kill!

Bias Current error = 19.4 μ K

Negligible

Offset Current error = 0.7mK

Negligible

Gain Error (systematic) = 0.68K

Need to do a **bit** better

Gain error (random) = 0.4K

Maybe OK, maybe not...

Overall error should be no more than 1K

To be continued....

From naïve design, V_{OS} is most difficult problem, then gain.

Specification:

O/P = 10mV K^{-1}

Better than 1K accuracy

At 20K difference

Need some way to distribute
Errors rationally

Define a **budget** for the errors

- V_{OS} is worst: Big Budget
- Gain is almost OK. \Rightarrow Moderate budget
- Current errors are negligible. \Rightarrow Tiny Budget.

(OK to use background information:) (Prices are indicative)


- 5% Resistor £0.008
- 1% Resistor £0.017
- 0.5% Resistor £0.154
- 0.1% Resistor £0.60
- 0.01% Resistor £10.20

The Budget:

- V_{OS} 0.5K Implies $V_{OS} \leq 0.5K * 150\mu V/K = 75\mu V$
- Gain 0.35K **Implies** 0.5% resistors
- I_B, I_{OS} 0.1K Implies $I_{OS} * 0.993k\Omega \leq 0.1K * 150\mu V/K = 15\mu V$
 $\Rightarrow I_{OS} \leq 15nA$

Note— The budget is something you **choose**: There is no perfect answer. If necessary you can redistribute later on.

 Log price vs. log tolerance for a resistor



Cost of a resistor is proportional to $1 / \text{tolerance}$

Hunt the Opamp!

Note: Choose one you can actually **get**: Farnell, RS...

Some technologies are intrinsically bad: ignore
(e.g. current feedback)

Ignore things which may be a problem and don't help with the
present problem (e.g. fast amps)

Start with cheap components

Limit to available power supply ($\pm 15V$ in this case)

Eliminate on main spec first $V_{OS} \leq 75\mu V$



Design Example (13) Error budgets (4)

Use design tools; e.g. TI, Analog, Linear or distributors: Digi-Key;

Product Index > Integrated Circuits (ICs) > Linear - Amplifiers - Instrumentation, OP Amps, Buffer Amps

not on price

Product Index > Integrated Circuits (ICs) > Linear - Amplifiers - Instrumentation, OP Amps, Buffer Amps

To get the most from Digi-Key's part search:

Only select from one box at a time, click the "Apply Filters" button, and repeat.

To select multiple values within a box, hold down 'Ctrl' while selecting values within the box.

Series	Manufacturer	Amplifier Type	Number of Circuits	Output Type	Slew Rate	Gain Bandwidth Product	-3db Bandwidth	Current - Input Bias	Voltage - Input Offset	Current Supply
*	Advanced Linear Devices Inc	-	-	Buffered	0.0027 V/μs	-	*	*	50μV	*
-	ams	Audio	1	CMOS	0.003 V/μs	1kHz	-	-	60μV	-
Apex Precision Power®	Analog Devices Inc	Auto-Zero	2	CMOS, Rail-to-Rail	0.004 V/μs	1.5kHz	250Hz	0.002pA	65μV	0.33μA
APEX™ 20K	Apex Microtechnology	Buffer	3	Differential	0.0041 V/μs	2kHz	500Hz	0.003pA	70μV	0.35μA
Beyond-the-Rails™	Avago Technologies US Inc.	Chopper (Zero-Drift)	4	Differential, Rail-to-Rail	0.0042 V/μs	2.5kHz	1kHz	0.005pA	74μV	0.4μA
BI-FET II™	CEL	Current Feedback	5	Open Drain	0.0045 V/μs	2.7kHz	1.5kHz	0.01pA	75μV	0.45μA
BI-FET™	Cirrus Logic Inc	Current Sense	6	Phase Reversal Free, Rail to Rail	0.005 V/μs	3kHz	2.5kHz	0.02pA	80μV	0.475μA
C-Load™	Diodes Inc	Differential	8	Push-Pull	0.006 V/μs	3.5kHz	3.1kHz	0.03pA	85μV	0.6μA
CLAMPIN™	Diodes Inc	General Purpose	10	Push-Pull, Rail-to-Rail	0.0077 V/μs	4kHz	5kHz	0.04pA	90μV	680nA
Difet®	Fairchild Optoelectronics Group	Instrumentation	12	Rail-to-Rail	0.01 V/μs	5kHz	7.5kHz	0.05pA	95μV	0.7μA

☐ In stock
☐ Lead free
☐ RoHS Compliant

Reset Apply Filters

Click RoHS icon next to part number for RoHS Compliant Substitutes.

To see real-time pricing, click either the Digi-Key part number or unit price link.

Page 1/1,239 (1 2 3 4 5 6 7 8 9 10 ... Last Next)

All prices are in British pound

Image	Digi-Key Part Number	Manufacturer Part Number	Description	Series	Manufacturer	Amplifier Type	Number of Circuits	Output Type	Slew Rate	Gain Bandwidth Product	-3db Bandwidth	Current - Input Bias	Voltage - Input Offset	Current - Output / Channel	Voltage - Supply, Single/Dual (±)	Operating Temperature	Mounting Type	Package / Case	Supplier Device Package	Packaging	Quantity Available	Minimum Quantity	Unit Price
	296-17440-2-ND	RC4558IDR	IC OPAMP GP 3MHZ DUAL 8SOIC	-	Texas Instruments	General Purpose	2	-	1.7 V/μs	3MHz	-	150nA	500μV	2.5mA	10 V ~ 30 V, ±5 V ~ 15 V	-40°C ~ 85°C	Surface Mount	8-SOIC (0.154", 3.90mm Width)	8-SOIC	Tape & Reel (TR) Alternate Packaging	7,500 - Immediate 167,500 - Factory Stock	2,500	0.0620
	296-17440-1-ND	RC4558IDR	IC OPAMP GP 3MHZ DUAL 8SOIC	-	Texas Instruments	General Purpose	2	-	1.7 V/μs	3MHz	-	150nA	500μV	2.5mA	10 V ~ 30 V, ±5 V ~ 15 V	-40°C ~ 85°C	Surface Mount	8-SOIC (0.154", 3.90mm Width)	8-SOIC	Cut Tape (CT) Alternate Packaging	7,829 - Immediate 167,500 - Factory Stock	1	0.3400
	296-17440-6-ND	RC4558IDR	IC OPAMP GP 3MHZ DUAL 8SOIC	-	Texas Instruments	General Purpose	2	-	1.7 V/μs	3MHz	-	150nA	500μV	2.5mA	10 V ~ 30 V, ±5 V ~ 15 V	-40°C ~ 85°C	Surface Mount	8-SOIC (0.154", 3.90mm Width)	8-SOIC	Digi-Reel® Alternate Packaging	7,829 - Immediate	1	Calcul

OP-07 seems to meet offset voltage spec, and is very cheap.

What about the offset current spec?

Budget: $I_{OS} \leq 15\text{nA}$

Download the data sheet and check I_{OS} **and** V_{OS}

$V_{OS} = 60\mu\text{V}$ typical, $150\mu\text{V}$ max

$V_{OS} \text{ spec} \leq 75\mu\text{V}$

$I_{OS} = 0.8\text{nA}$ (typical) 6nA max

$I_{OS} \text{ spec} \leq 15\text{nA}$

So the OP-07 actually **doesn't** work.


Repeat for other opamps sorted in order of price

Opamp	Price	Vos μ V (typ)	Vos μ V (max)	Ib pA(typ)	Ib pA(max)	Ios pA(typ)	Ios pA(max)	Comments
OP07C	0.36	60	150	1800	7000	800	6000	"Classic"
LT1013CP	0.778	60	300	15000	30000	200	1500	dual
TLC277CP	0.88	200	500	0.6	40	0.1	7	CMOS dual
TLE2022IP	1.15	150	500	35000	70000	500	6000	dual
OP177GP	1.47	20	60	500	2800	300	2800	Standard
OPA277PA	1.53	20	50	500	2800	500	2800	Improved 177
TLE2021CP	1.57	120	600	25000	70000	200	3000	
TLE2141CP	1.61	225	1400	800000	2000000	8000	100000	
OP37GPZ	2.15	30	100	15000	80000	12000	75000	Min gain 5 OP
TLC2201CP	2.19	100	500	1		0.5		CMOS
OP97FPZ	2.2	30	75	30	150	30	150	
LT1006CN8	2.52	30	80	10000	25000	150	900	
OP27GPZ	2.86	30	100	15000	80000	12000	75000	"Low noise"
LT1097CN8	2.91	10	50	40	250	40	250	
MAX492CPA	3.12	200	500	25000	60000	500	6000	Low power sin
MAX437CPA	3.18	5	15	10000	35000	7000	30000	"Low noise"
LT1057CN8	3.22	200	800	7	75	4	50	JFET
LT1050CN8	3.65	0.5	5	10	75	20	125	Chopper
OP213FPZ	3.84		150	240000	600000		50000	
TLC2652CP	4.32	0.6	3	4		2		Chopper \pm 5V

OP177 is the cheapest that works:

$V_{OS}=60\mu\text{V}$ max, $I_{OS}=2.8\text{nA}$ max £1.47 each

Final design, 0.5% resistors

 

Costs:

•Naïve:

Amp: £0.60

Rs: £0.066

Total £0.67

•Designed:

Amp: £1.47

Rs: £0.50

Total £1.97

Cost x 3, accuracy x 70



University
of Glasgow

Thank you
谢谢

INSPIRING
PEOPLE