



University  
of Glasgow

# Electronic System Design 3

## Lecture 5.2: Figure of Merit


### Worked Examples

Dr Duncan Bremner




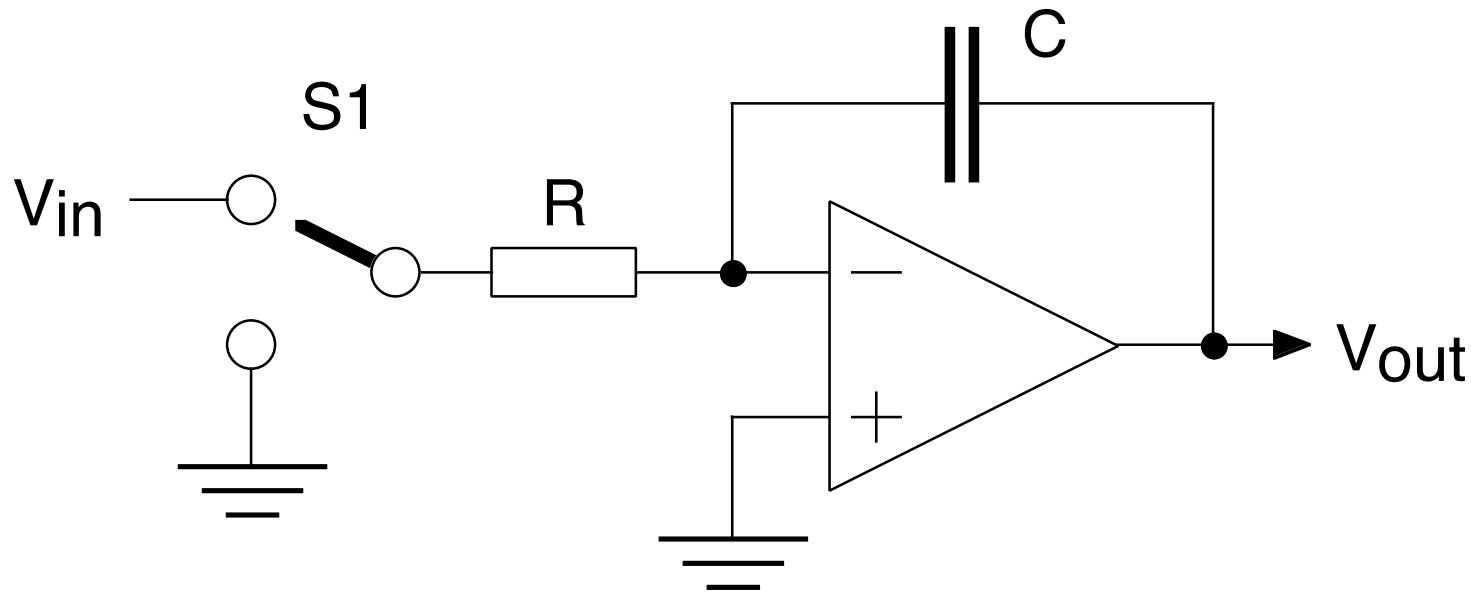
## Integrate-and-Hold circuit:- Revisited



If S1 connects to  $V_{in}$  circuit is an integrator  $V_{out} = -\int \frac{V_{in}}{RC} dt$

If S1 connects to 0V circuit is a memory  $V_{out} = \text{constant}$

How can we use analysis to improve performance?



## Figure of merit (1)

To improve performance we need a better opamp...

Performance depends significantly on  $I_B$  and  $V_{OS}$ .

$$\left| \frac{dV_{out}}{dt} \right| = \frac{1}{\tau} (I_B R + V_{OS})$$

**Make this bit good!**

Given a choice of two opamps best opamp has smaller  $(I_B R + V_{OS})$

You don't care if the problem is a big  $I_B$  or a big  $V_{OS}$  or a combination

$$I_B R + V_{OS} = F \text{ (Figure of merit)} = I_B \cdot 2M + V_{OS}$$

$$\text{TL071CP: } F = 200\text{pA} \cdot 2\text{M}\Omega + 10\text{mV} = 10.4\text{mV}$$

Note that  $F$  is a function of the external circuit: Different circuits have different Figures of Merit. There is no “Best” opamp




## Figure of Merit (2)

Having downloaded data on many opamps use a spreadsheet to calculate  $F$ . Using the same data set as before:

Opamp	Price	Vos $\mu\text{V}$ (max)	Ib pA(max)	$F(\mu\text{V})$
OP07C	0.36	150	7000	1.42E+04
LT1013CP	0.778	300	30000	6.03E+04
TLC277CP	0.88	500	40	5.80E+02
TLE2022IP	1.15	500	70000	1.41E+05
OP177GP	1.47	60	2800	5.66E+03
OPA277PA	1.53	50	2800	5.65E+03
TLE2021CP	1.57	600	70000	1.41E+05
TLE2141CP	1.61	1400	2000000	4.00E+06
OP37GPZ	2.15	100	80000	1.60E+05
OP97FPZ	2.2	75	150	3.75E+02
LT1006CN8	2.52	80	25000	5.01E+04
OP27GPZ	2.86	100	80000	1.60E+05
LT1097CN8	2.91	50	250	5.50E+02
MAX492CPA	3.12	500	60000	1.21E+05
MAX437CPA	3.18	15	35000	7.00E+04
LT1057CN8	3.22	800	75	9.50E+02
LT1050CN8	3.65	5	75	1.55E+02
OP213FPZ	3.84	150	600000	1.20E+06



## Figure of Merit (3)

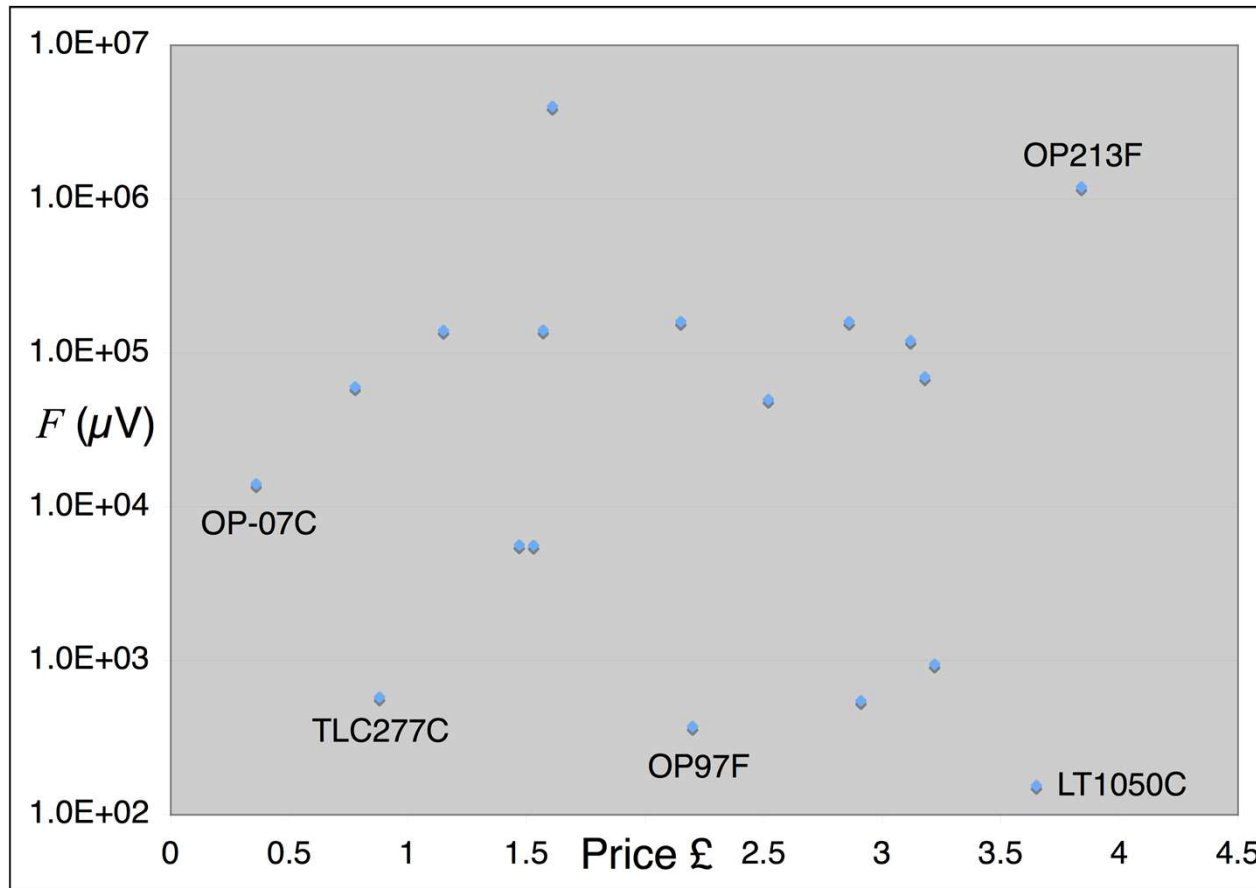


TLC277 is 4x worse Than the best and is 88p (dual). Best is LT1050C, 4x more expensive.

OP213 is even more expensive and second worst.

Choose cheapest which meets spec.



Figure of Merit (4)

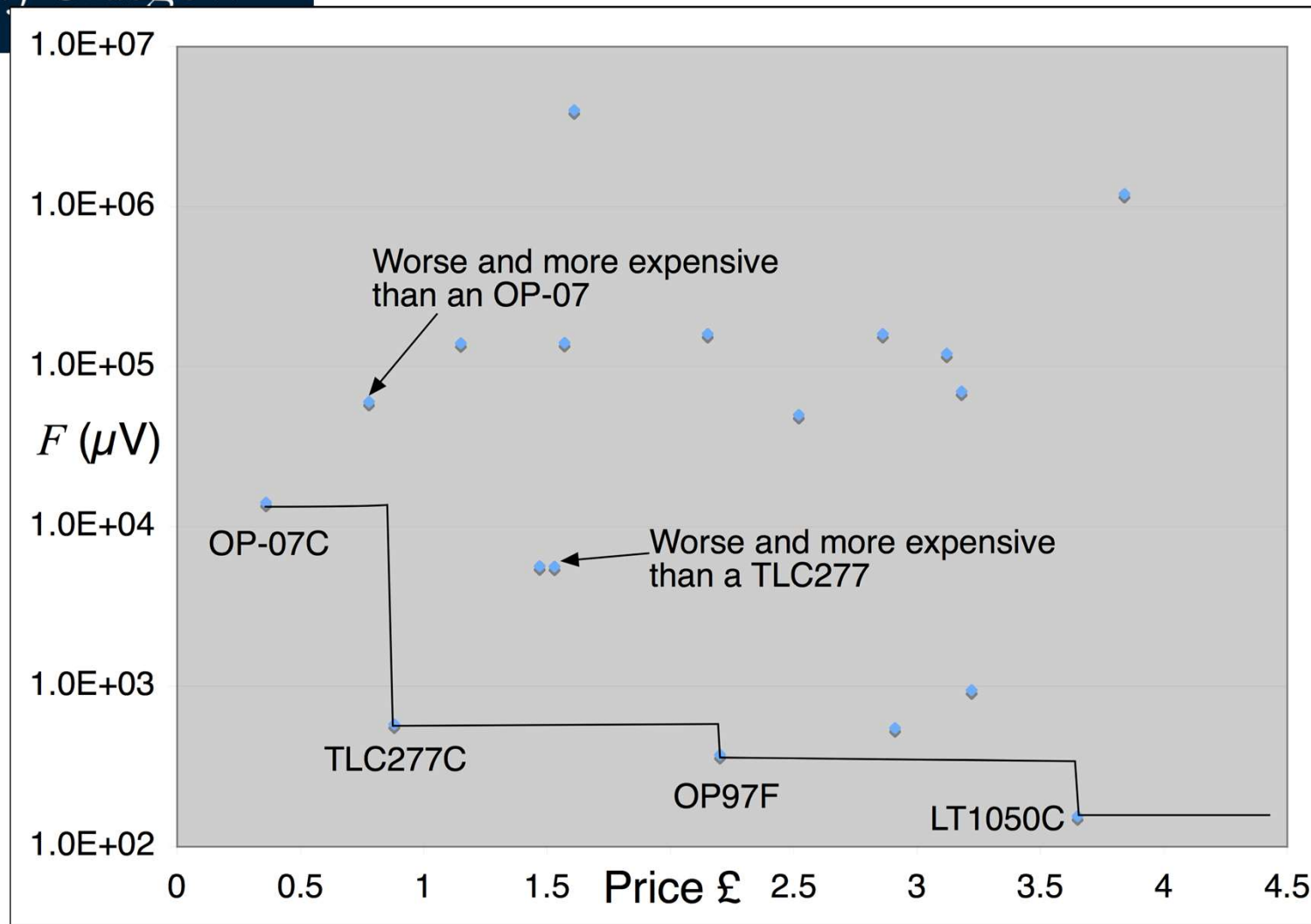

**Only** good choices are OP07, then TLC277, then OP97, then LT1050. **All others are more expensive than a better opamp.**



University  
of Glasgow

## Figure of Merit(5)

### Things to take away

- “Best” opamp depends on what it is used for
- Second worst design **is 8 000x** worse than the best for the same price
- Good cheap design is only 4x worse than most expensive


**Money does not buy success!**

- Expensive design may have other problems (chopper)
- Hunting for components is a pain (=> acquire **favourites**)

Proper system design is always worth it.



## Figure of Merit Example 2

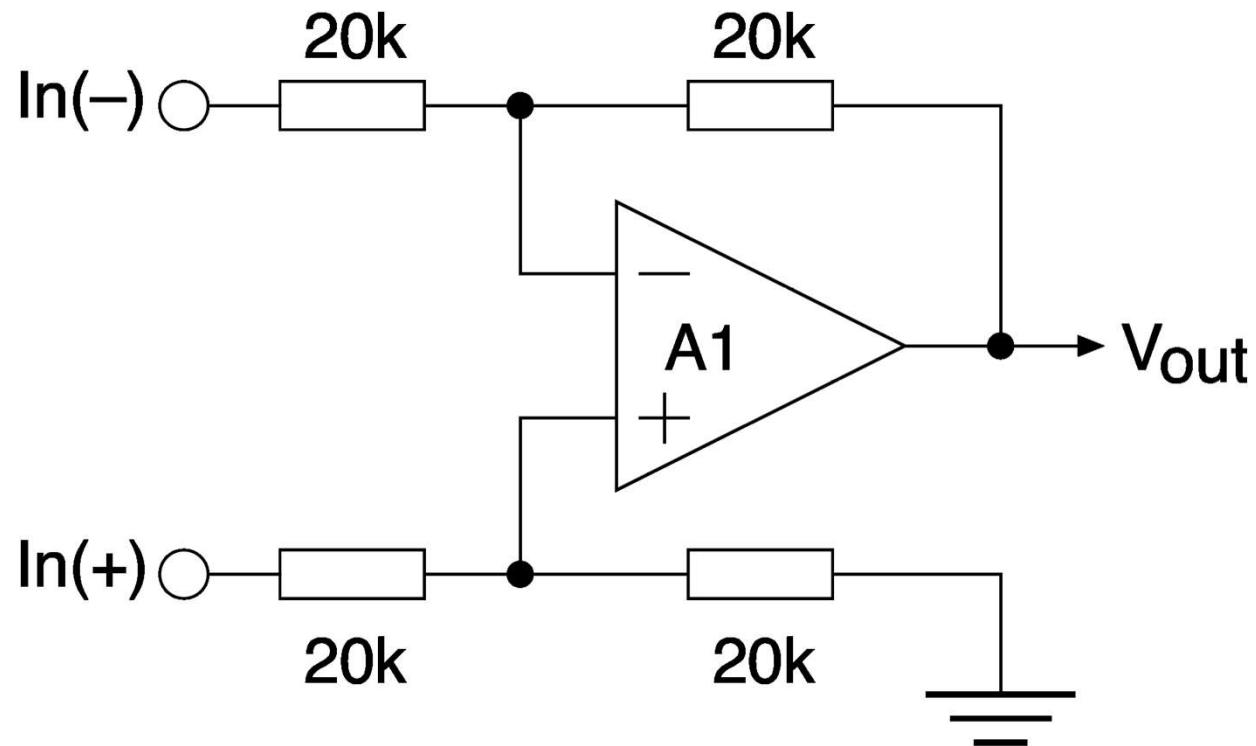

Differential amplifier


Note: Impedances are already matched: Ignore  $I_B$ , just  $I_{OS}$




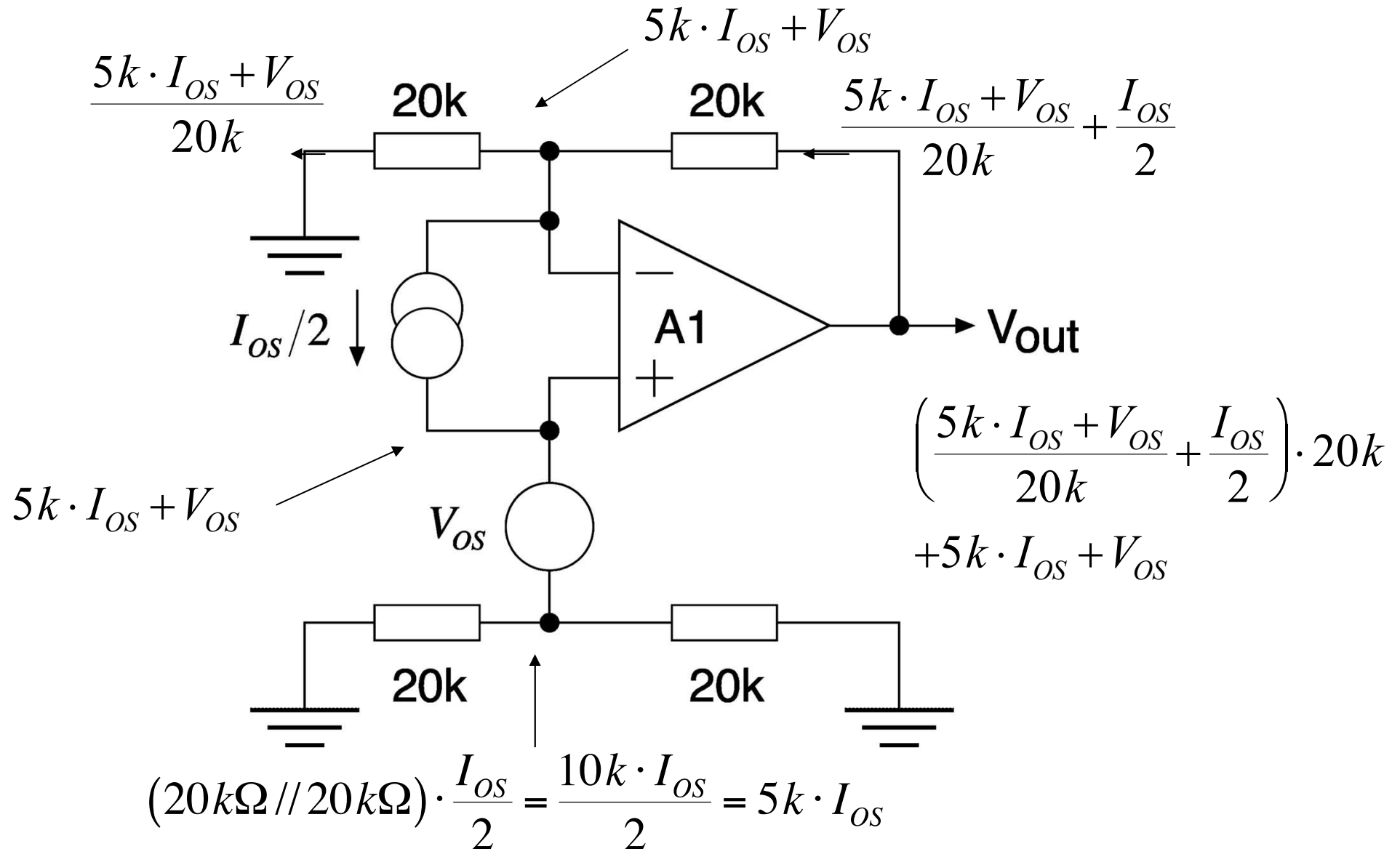
## Figure of Merit Example 2 (2)

Calculate error RTO: (Set inputs to zero: Superposition!)





## Figure of Merit Example 2 (3)

$$\begin{aligned}\text{Error(RTO)} &= \left( \frac{5k \cdot I_{os} + V_{os}}{20k} + \frac{I_{os}}{2} \right) \cdot 20k + 5k \cdot I_{os} + V_{os} \\ &= 2V_{os} + 20k \cdot I_{os}\end{aligned}$$

Let this be the figure of merit:

$$F = 2V_{os} + 20k \cdot I_{os}$$



## Figure of Merit Example 2 (4)


Using the same set of opamps:

Opamp	Price	Vos $\mu\text{V}$ (max)	Ios pA(max)	F ( $\mu\text{V}$ )
OP07C	0.36	150	6000	420
LT1013CP	0.778	300	1500	630
TLC277CP	0.88	500	7	1000.14
TLE2022IP	1.15	500	6000	1120
OP177GP	1.47	60	2800	176
OPA277PA	1.53	50	2800	156
TLE2021CP	1.57	600	3000	1260
TLE2141CP	1.61	1400	100000	4800
OP37GPZ	2.15	100	75000	1700
TLC2201CP	2.19	500	<1>	1000.02
OP97FPZ	2.2	75	150	153
LT1006CN8	2.52	80	900	178
OP27GPZ	2.86	100	75000	1700
LT1097CN8	2.91	50	250	105
MAX492CPA	3.12	500	6000	1120
MAX437CPA	3.18	15	30000	630
LT1057CN8	3.22	800	50	1601
LT1050CN8	3.65	5	125	12.5
OP213FPZ	3.84	150	50000	1300



## Figure of Merit Example 2 (5)

Graphing:

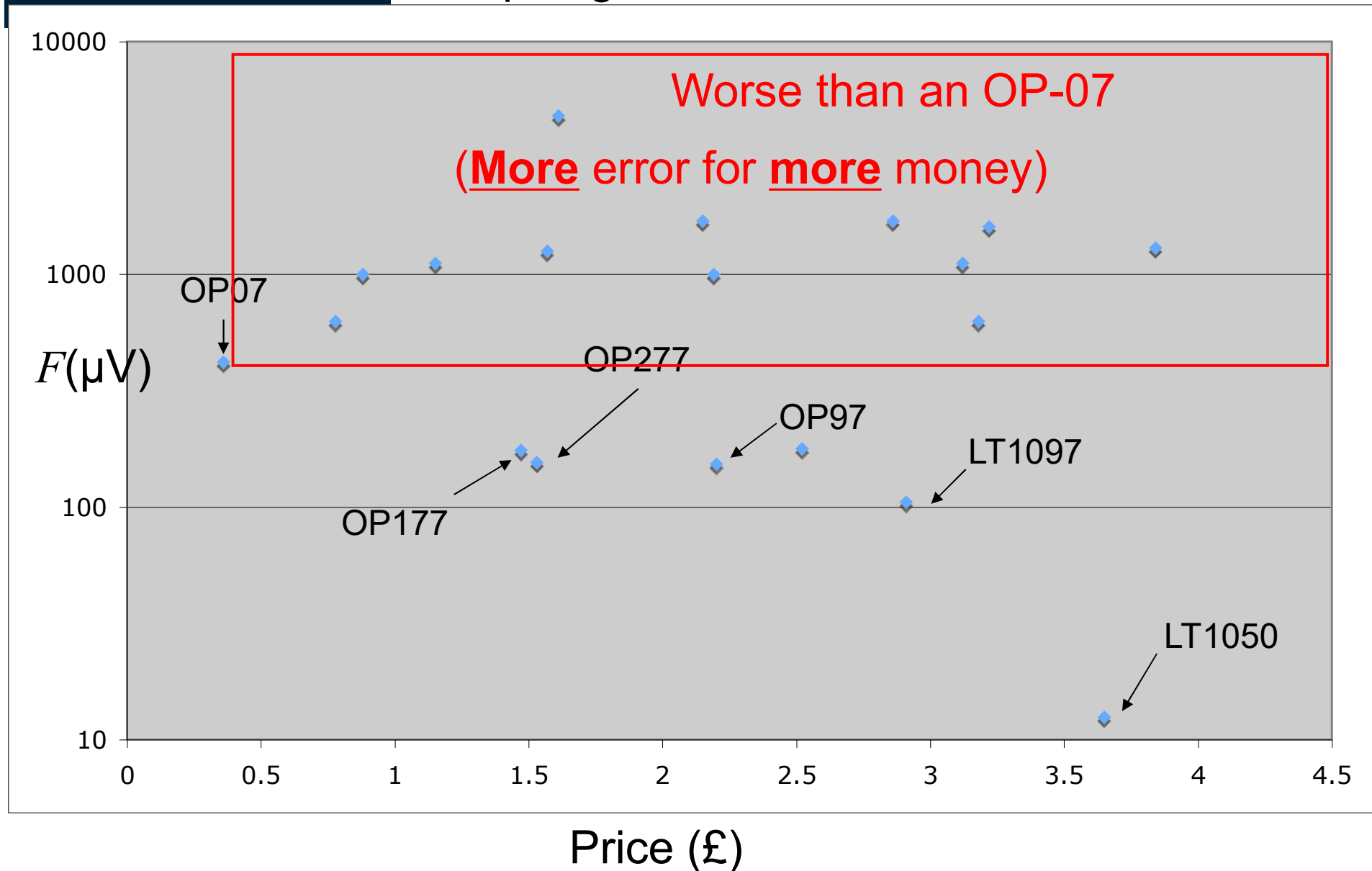



Final choice: Read the datasheet for other specifications which may be important, especially changes with time, temperature, power supply etc. Also any “*Unusual*” normal specifications (LMC660)

## LMC660

### CMOS Quad Operational Amplifier

#### General Description

The LMC660 CMOS Quad operational amplifier is ideal for operation from a single supply. It operates from +5V to +15.5V and features rail-to-rail output swing in addition to an input common-mode range that includes ground. Performance limitations that have plagued CMOS amplifiers in the

- Low input offset voltage: 3 mV
- Low offset voltage drift: 1.3  $\mu\text{V}/^\circ\text{C}$
- Ultra low input bias current: 2 fA
- Input common-mode range includes  $V^-$
- Operating range from +5V to +15.5V supply
- $I_{\text{sc}} = 375 \mu\text{A}/\text{amplifier}$ ; independent of  $V^+$


Parameter	Conditions	Typ (Note 4)	LMC660AI	LMC660C	Units
			Limit (Note 4)	Limit (Note 4)	
Output Swing	$V^+ = 5\text{V}$ $R_L = 2 \text{ k}\Omega$ to $V^+/2$	4.87	4.82	4.78	V
		0.10	0.15	0.19	V
			0.17	0.21	max
Input Common-Mode Voltage Range	$V^+ = 5\text{V} \text{ \& } 15\text{V}$ For $\text{CMRR} \geq 50 \text{ dB}$	-0.4	-0.1	-0.1	V
		$V^+ - 1.9$	0	0	max
			$V^+ - 2.3$ $V^+ - 2.5$	$V^+ - 2.3$ $V^+ - 2.4$	V min

Incompatible with its own  
output!




## Single supply opamp LM8261:

Symbol	Parameter	Condition	Typ <sup>(2)</sup>	Limit <sup>(3)</sup>	Units
$V_{OS}$	Input Offset Voltage	$V_{CM} = 0.5V$ & $V_{CM} = 2.2V$	$\pm 0.7$	$\pm 5$ $\pm 7$	mV max
TC $V_{OS}$	Input Offset Average Drift	$V_{CM} = 0.5V$ & $V_{CM} = 2.2V$ <sup>(4)</sup>	$\pm 2$	—	$\mu V/C$
$I_B$	Input Bias Current	$V_{CM} = 0.5V$ <sup>(5)</sup>	-1.20	-2.00 -2.70	$\mu A$ max
		$V_{CM} = 2.2V$ <sup>(5)</sup>	+0.49	+1.00 +1.60	

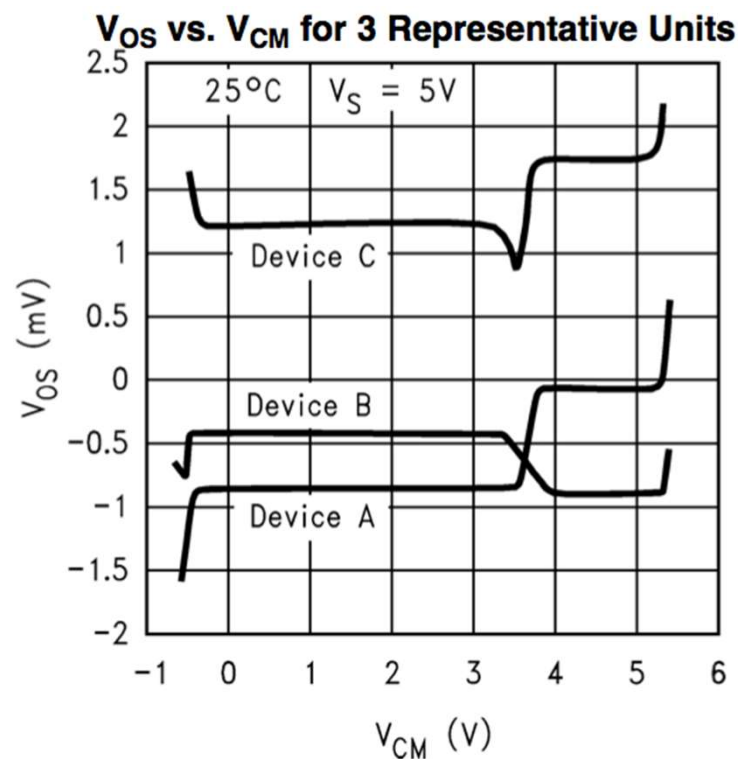

Parameter varies  
A lot with  $V_{CM}$ !  
e.g.  $dI_B/dV_{CM}$

$$= R_{IN}$$

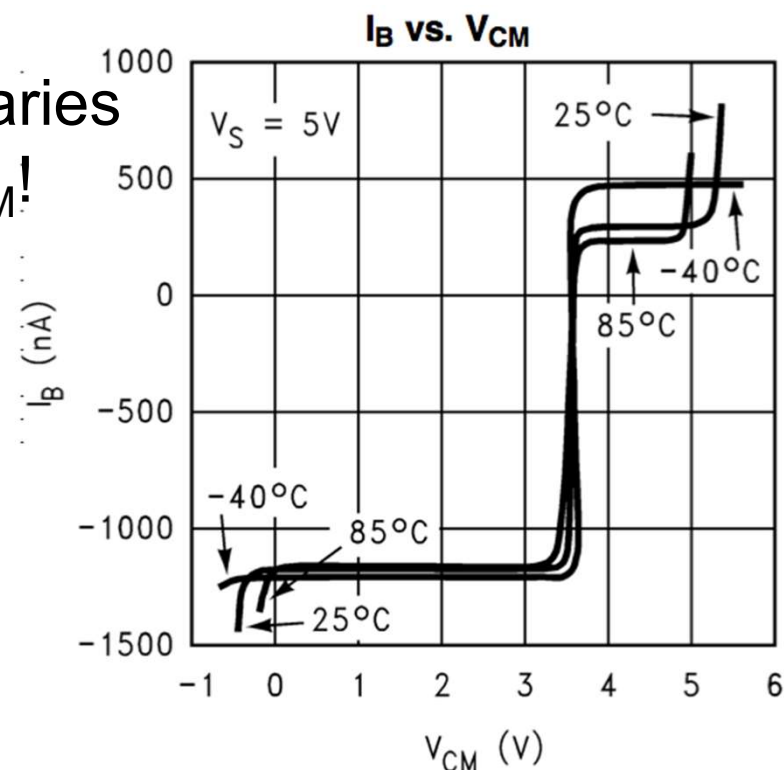

### 7.1.1 A) Input Stage

**$V_{OS}$  vs.  $V_{CM}$  for 3 Representative Units**

25°C  $V_S = 5V$

Device C

Device B


Device A

$V_{OS}$  (mV)

$V_{CM}$  (V)

These devices

These devices  
operate here...

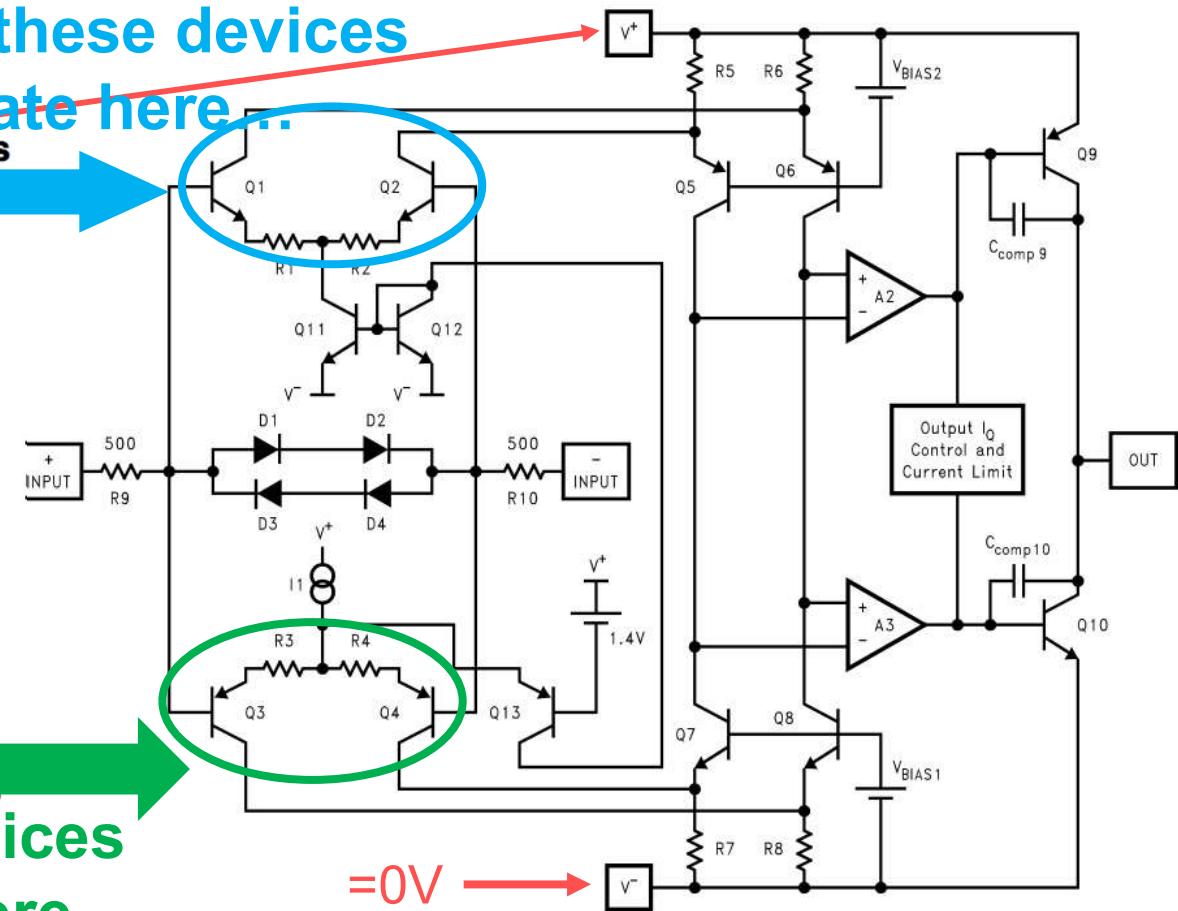

**Figure 49. Simplified Schematic Diagram**

**Read the datasheet to find out the full story!!!**





University  
of Glasgow

Thank you  
谢谢

INSPIRING  
PEOPLE