

Three-Phase AC (2)

Balanced Delta Connected Load

Loads may also be connected in a delta configuration. Let's consider a balanced delta connected load as depicted in Figure 1. The Load phase currents are I_{RY} , I_{YB} , I_{BR} and the line currents are I_R , I_Y , I_B .

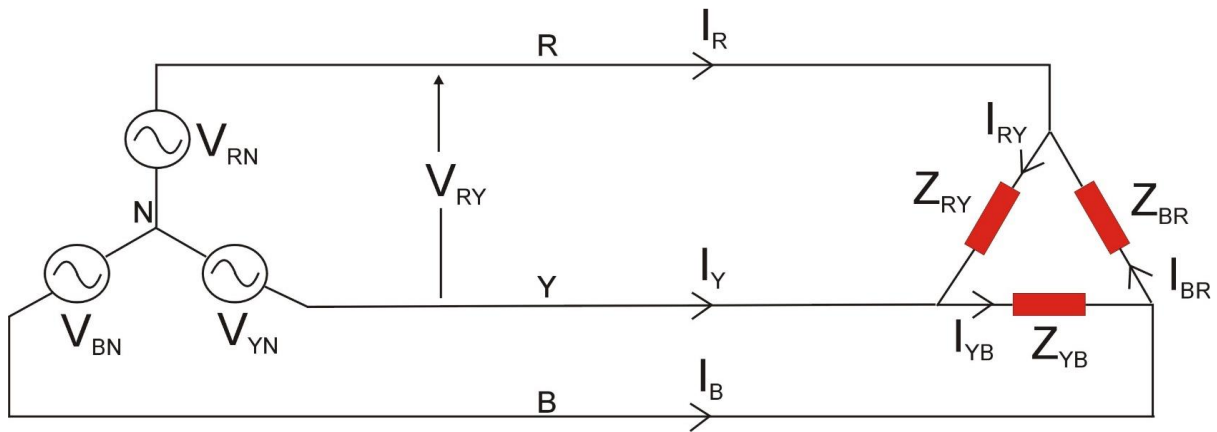


Figure 1. A Balanced Delta (Δ) connected load where $Z_{RY}=Z_{YB}=Z_{BR}$.

We can now write expressions for the phase currents:

$$I_{RY} = \frac{V_{RY}}{Z_{RY}} = I_{PH} \angle -\phi \quad (1)$$

$$I_{YB} = \frac{V_{YB}}{Z_{YB}} = I_{PH} \angle (-\phi - 120^\circ) \quad (2)$$

$$I_{BR} = \frac{V_{BR}}{Z_{BR}} = I_{PH} \angle (-\phi + 120^\circ) \quad (3)$$

We can now find expressions for the line currents:

$$I_R = I_{RY} - I_{BR} = \sqrt{3} I_{ph} \angle -\phi - 30^\circ \quad (4)$$

$$I_Y = I_{YB} - I_{RY} = \sqrt{3} I_{ph} \angle -\phi - 150^\circ \quad (5)$$

$$I_B = I_{BR} - I_{YB} = \sqrt{3} I_{ph} \angle -\phi + 90^\circ \quad (6)$$

A phasor diagram is shown in Figure 2:

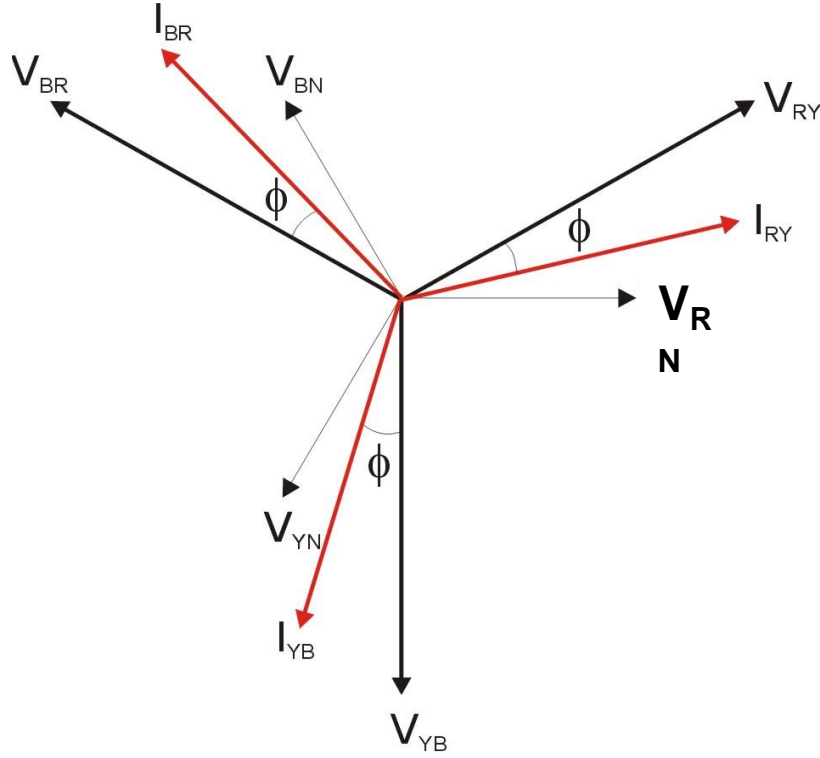


Figure 2. Phasor Diagram for Balanced Delta Load

For any single phase we can calculate the apparent power (S), real power (P) and reactive power (Q):

$$S = |V_{RY}| |I_{RY}| = V_L I_L \quad (7)$$

$$P = S \cdot \cos \phi \quad (8)$$

$$Q = S \cdot \sin \phi \quad (9)$$

where V_L is the rms magnitude of the line voltage, I_{ph} is the rms load phase current and ϕ is the angle between them.

The total real power in the 3-phase system is three times the single-phase real power:

$$P_T = 3V_L I_{ph} \cos \phi = 3V_{ph} I_L \cos \phi \quad (10)$$