

# What we have studied so far

## With Prof Lianping Hou

- Electric Circuits
- Power Switches
- Uncontrolled and Controllable Switches
- Heatsinks


## Since Week-8

- Snubber Circuits
- Switched Mode Power Supplies (DC converters)
- DC-AC converters (Inverters)
- PWM Inverters

## To do

- Applications and Systems
- Revision of Numerical Questions

## Course Structure

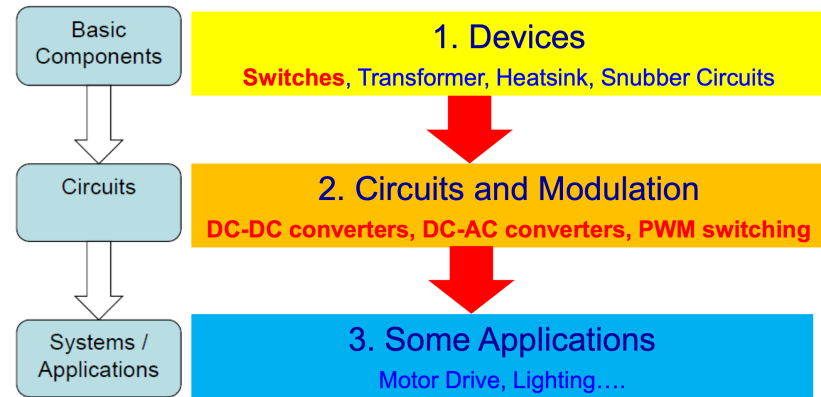

## Today's Lecture

- Applications and Systems
- Numerical Problems



University  
of Glasgow

# Power Electronics

## Applications and Systems

Dr Shuja Ansari  
Shuja.Ansari@glasgow.ac.uk

Reading material in Chapters 12,13,14,16,17  
and 18 in the textbook

# Applications - High level

- Application we have covered so far
  - Power Supplies
  - Inverters
- Other Applications
  - Motor drive applications (Chapters 12,13 and 14)
  - Electric Vehicles
  - Residential applications
  - Industrial applications
  - Electric Utility applications

# Motor drive applications

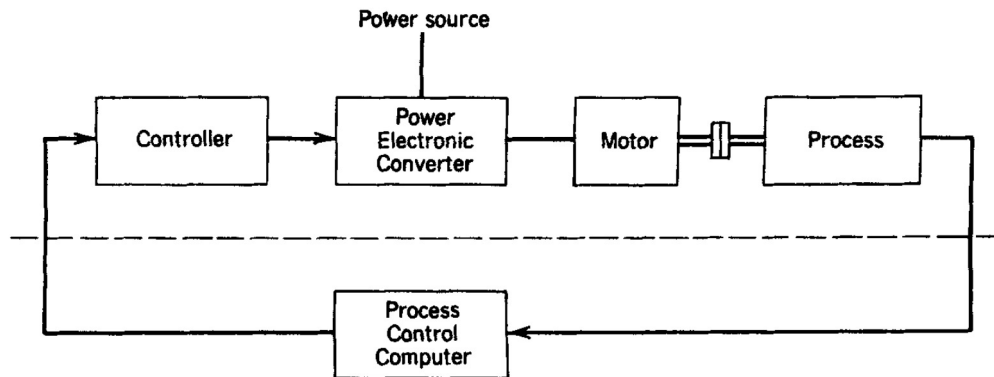


Figure 12-1 Control of motor drives.



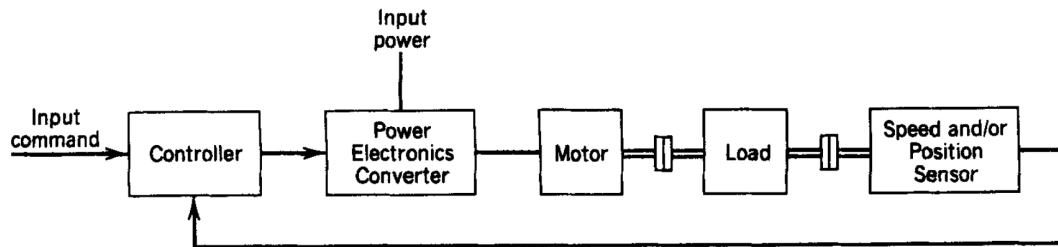
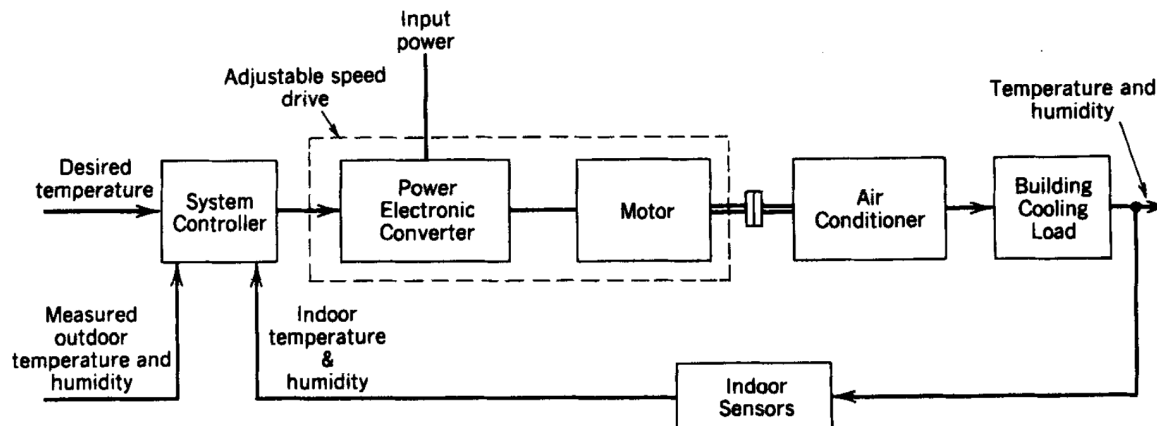


Figure 12-2 Servo drives.

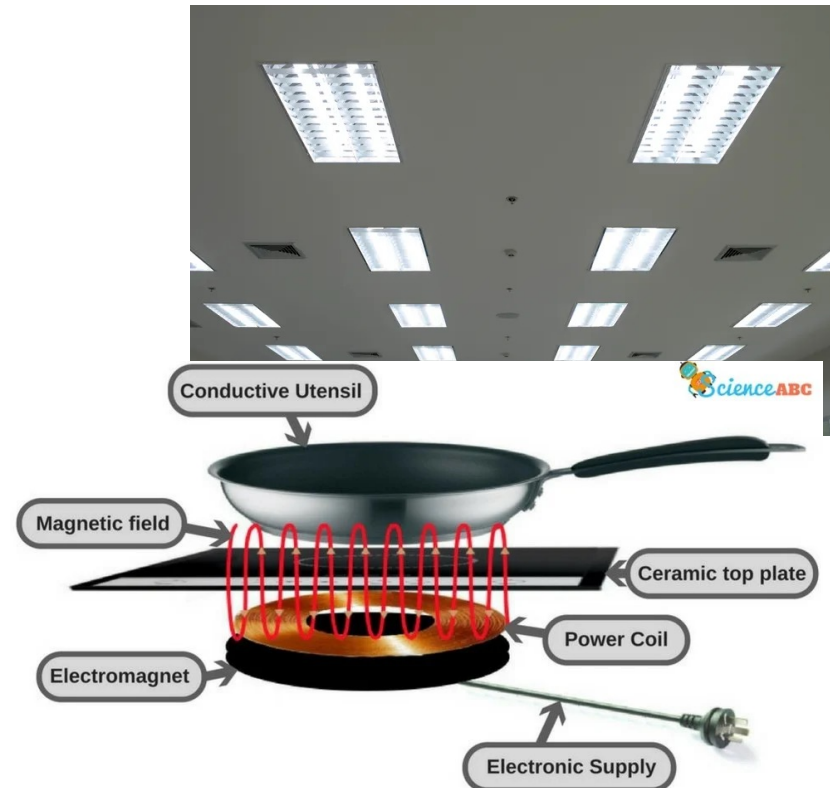
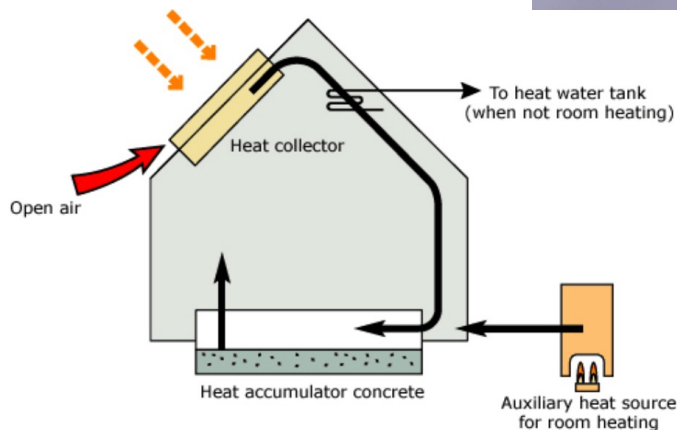
# Residential Applications

- Space Heating and Air Conditioning
- High Frequency Fluorescent Lighting
- Induction Cooking




# Industrial Applications


- Induction heating
- Electric welding
- Controllers



# Electric Vehicle

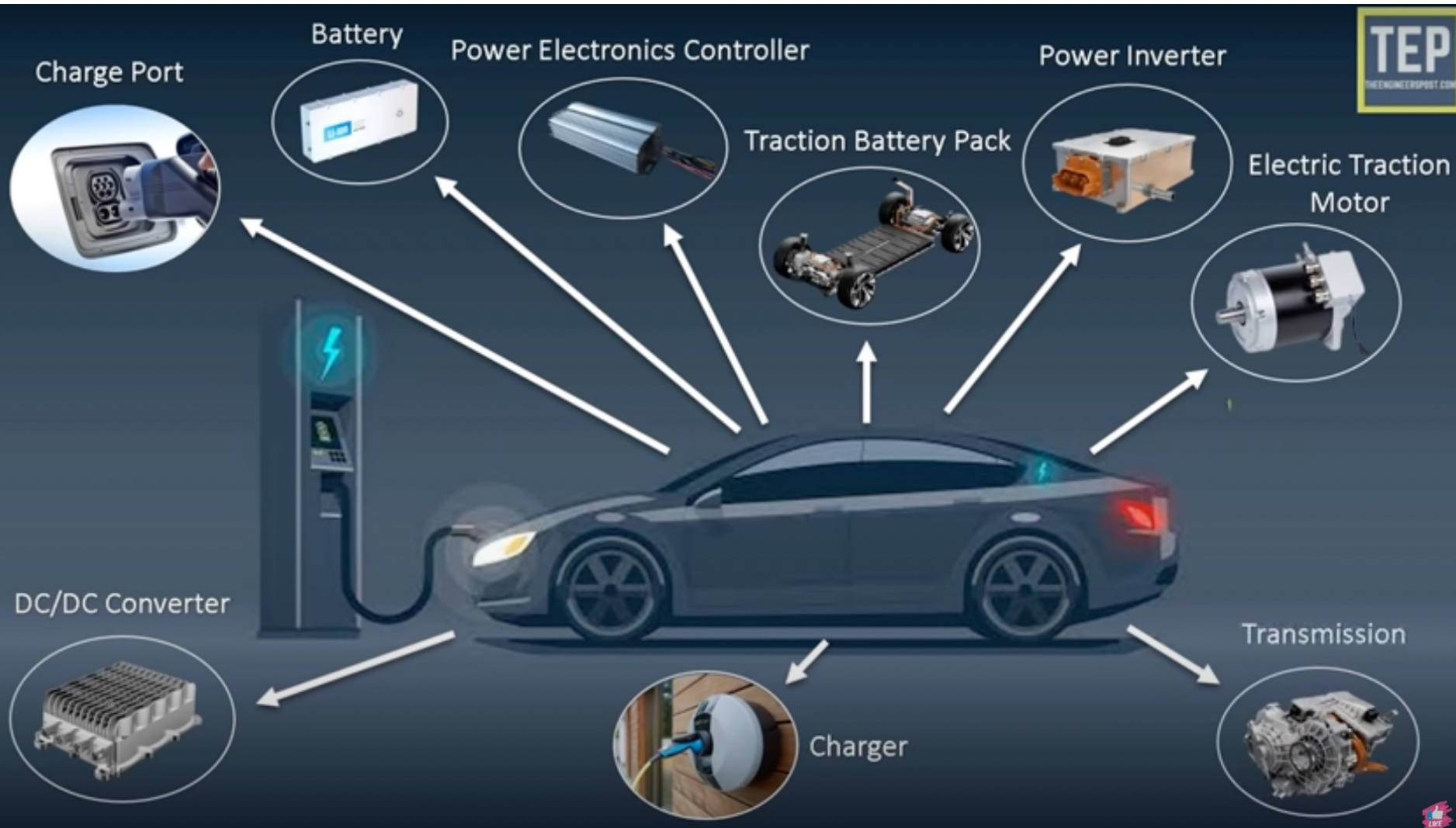



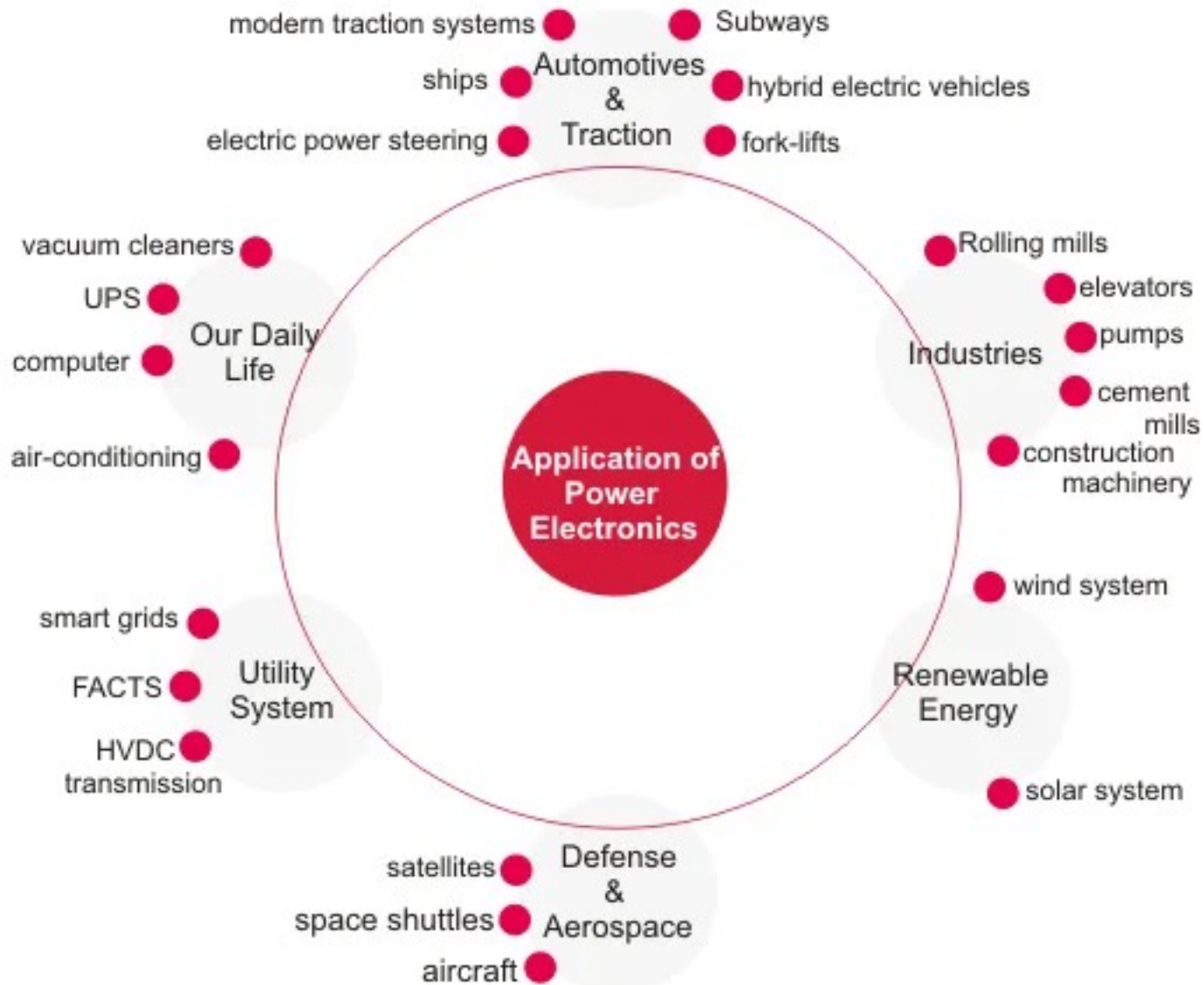




# Additional links for self study

- Electric Vehicle – parts and functions
  - <https://www.youtube.com/watch?v=tJfERzrG-D8>
- Applications
  - <https://www.youtube.com/watch?v=6KHJ5JA4BbY>
- <https://www.electrical4u.com/application-of-power-electronics/>

**27-1** Consider the step-down converter circuit shown in Fig. 24-3 without the turn-on snubber. The dc input voltage  $V_d$  is 500 V, the load current  $I_o = 500$  A, and the switching frequency is 1 kHz. The free-wheeling diode has a reverse-recovery time  $t_{rr} = 10 \mu\text{s}$ . The GTO has a current fall time  $t_{fi} = 1 \mu\text{s}$ , a maximum reapplied voltage rate  $dv/dt = 50 \text{ V}/\mu\text{s}$ , and a maximum controllable anode current  $I_{AM} = 1000$  A.

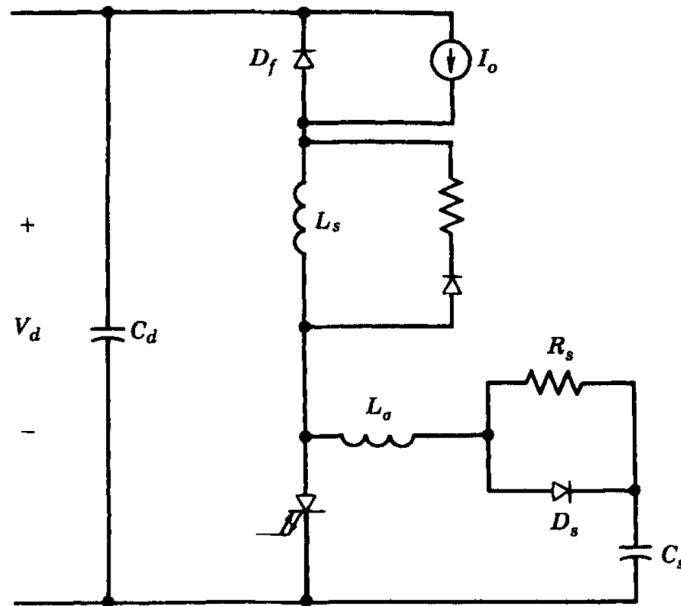- (a) Find the appropriate values for resistance  $R_s$  and capacitance  $C_s$  for the turn-off snubber circuit.  
 (b) Estimate the power dissipated in the snubber resistance.



27.1

$$V_d = 500 \text{ V}$$

$$I_o = 500 \text{ A}$$

$$f_s = 1 \text{ kHz}$$

$$t_{rr} = 10 \mu\text{s}$$

$$t_{fi} = 1 \mu\text{s}$$


$$a) R_s = ?, C_s = ? ; \text{ turn-off snubber}$$

$$\frac{dv}{dt} = \frac{I_o}{C_s} \Rightarrow C_s = I_o \left( \frac{dv}{dt} \right)^{-1}$$

$$C_s = (500) \left( \frac{1}{50 \times 10^6} \right) = \frac{500}{5} \times 10^{-7}$$

$$C_s = 100 \times 10^{-7} = 10 \times 10^{-6} = 10 \mu\text{F}$$

$$I_{C_{smax}} = I_{AM} - I_o - I_{rr}$$

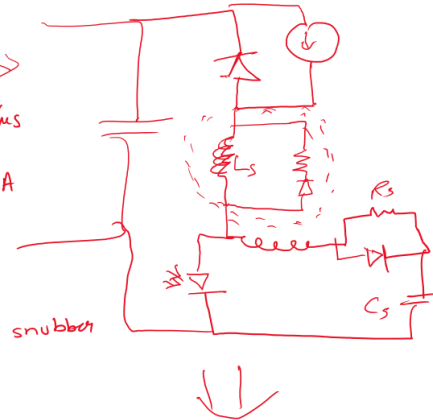

**Figure 24-3** Step-down converter circuit using a GTO as the switching device with turn-on and turn-off snubbers.

Assuming

$$I_{rr} = 0.2 I_o$$

$$I_{C_{smax}} = 1000 - 500 - (0.2)(500)$$

$$I_{C_{smax}} = 400 \text{ A}$$

$$R_s = \frac{V}{I_{C_{smax}}} = \frac{500}{400} = 1.3 \Omega$$

$$\begin{aligned} \text{b) Power dissipated} &= f C V^2 \\ &= (1 \times 10^3) (10^{-5}) (500)^2 \\ &= 10^{-2} (250000) \\ &= 2.5 \text{ kW} \end{aligned}$$

**27-2** The GTO in the circuit of Problem 27-1 is to be protected by a turn-on snubber circuit such as is shown in Fig. 24-3. The maximum rate of rise of the anode current,  $di_A/dt$ , is  $300 \text{ A}/\mu\text{s}$ . Find appropriate values for the inductance and resistance.

27.2

$$\frac{di_A}{dt} = 300 \text{ A}/\mu\text{s}$$

$$L_s = ? \quad R_s = ?$$

$$V = L \frac{di_A}{dt} \Rightarrow 500 = L(300 \times 10^6)$$

$$L = \frac{500}{300} \times 10^{-6} = 1.7 \times 10^{-6} = 1.7 \mu\text{H}$$


$$\text{Voltage across GTO at turn-off} = V_d + I_o R_s$$

$$I_o R_s = 0.2 V_d$$

$$R_s = \frac{(0.2)(500)}{500} = 0.2 \Omega$$

**27-4** Consider the flyback converter circuit shown in Fig. 27-6. The input voltage is 100 V as is the dc output voltage. The transformer has a 1:1 turns ratio and a leakage inductance of 10  $\mu\text{H}$ . The transistor, which can be considered as an ideal switch, is driven by a square wave with a 50% duty cycle. The snubber resistance is zero. The diode has a reverse-recovery time  $t_{rr}$  of 0.3  $\mu\text{s}$ .

- Draw an equivalent circuit suitable for snubber design calculations.
- Find the value of snubber capacitance  $C_s$  that will limit the peak overvoltage to 2.5 times the dc output voltage.

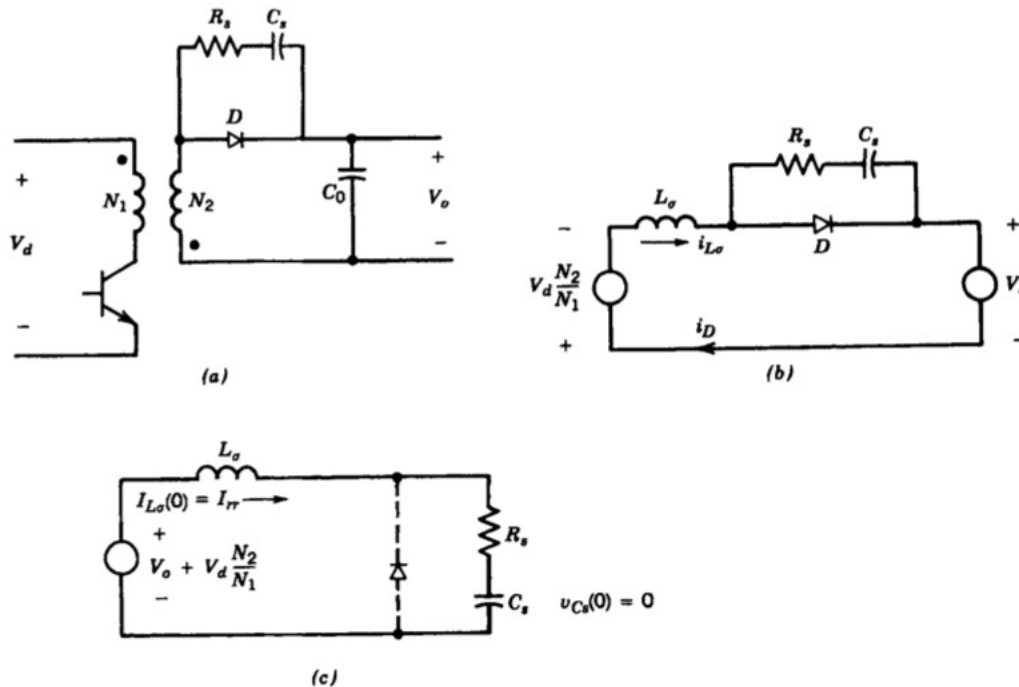

**Figure 27-6** (a) Flyback converter circuit operating in an incomplete demagnetization mode. (b) Equivalent circuit on the secondary side and (c) the simplified equivalent circuit after the snap-off of the diode current.  $L_\sigma$  is the transformer leakage inductance.

27-4

$V_d = 100\text{V}$ ,  $V_o = 100\text{V}$ ,  $V_{in} = 200\text{V}$   
 $L = 10\mu\text{H}$   
 $t_{rr} = 0.3\mu\text{s}$

a)

$$V = L \frac{di}{dt} = (100) + (100) = 200\text{V}$$

$$\frac{di}{dt} = \frac{200}{10 \times 10^{-6}} = 20 \times 10^8 \text{ A/s}$$

$$\frac{di}{dt} = \frac{I_L}{t_{rr}} \Rightarrow I_L = (20 \times 10^8)(0.3 \times 10^{-6})$$

$$I_L = 6\text{A}$$

b)  $C_s = ?$

$$V_{Cs, \max} = 2.5 \times 200 = 500 \text{ V}$$

$$V = IR \\ \Rightarrow R = \frac{V}{I}$$

$$R_s = \sqrt{\frac{L}{C_{\text{switch}}}} \Rightarrow R_s^2 = \frac{L}{C_{\text{switch}}}$$

$$C_{\text{switch}} = \frac{L}{R_s^2} = L \frac{I^2}{V^2} = \frac{(10 \times 10^{-6})(6)^2}{(200)^2}$$

$$C_{\text{switch}} = 9 \text{ nF}$$

$$V_{Cs, \max} = V_{in} \left( 1 + \sqrt{1 + \frac{C_{\text{switch}}}{C_s}} \right)$$

$$V_{Cs, \max} = 200 \left( 1 + \sqrt{1 + \frac{C_{\text{switch}}}{C_s}} \right) = 500 \text{ V}$$

$$1 + \sqrt{1 + \frac{C_{\text{switch}}}{C_s}} = \frac{500}{200}$$

$$\sqrt{1 + \frac{C_{\text{switch}}}{C_s}} = \frac{5}{2} - 1$$

$$1 + \frac{C_{\text{switch}}}{C_s} = (1.5)^2 \Rightarrow \frac{C_{\text{switch}}}{C_s} = 2.25 - 1$$

$$\frac{C_{\text{switch}}}{C_s} = 1.25$$

$$C_s = \frac{9}{1.25} = 7.2 \text{ nF}$$

**27-5** Repeat Problem 27-4 with a resistance  $R_s$  included in the snubber circuit. Find both the value of snubber capacitance and optimum value of snubber resistance.

27.5

$$R_{\text{snubber}} = \sqrt{\frac{L}{C_{\text{snub}}}} = \sqrt{\frac{10 \times 10^{-6}}{9 \times 10^{-9}}}$$

$$R_s = 33.3 \, \Omega$$

**27-6** Estimate the power dissipated in the snubber resistance found in Problem 27-4 if the square-wave switching frequency is 20 kHz.

27.6

$$P = f C V^2$$

$$P = (20 \times 10^3) (7.2 \times 10^{-9}) (200)^2$$

$$P = 5.76 \text{ W}$$



**7-1** In a step-down converter, consider all components to be ideal. Let  $v_o \approx V_o$  be held constant at 5 V by controlling the switch duty ratio  $D$ . Calculate the minimum inductance  $L$  required to keep the converter operation in a continuous-conduction mode under all conditions if  $V_d$  is 10–40 V,  $P_o \geq 5$  W, and  $f_s = 50$  kHz.

7-1



$$V_o = V_o = 5V$$

$$L = ?$$

$$10 < V_d < 40V$$

$$P_o \geq 5W$$

$$f_s = 50kHz$$

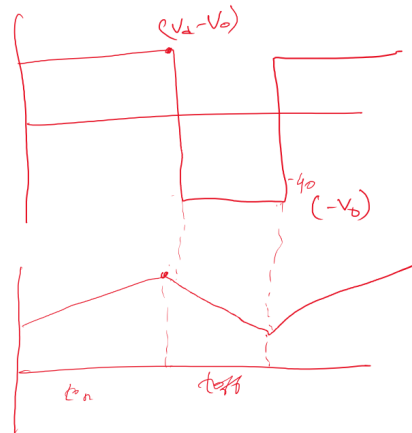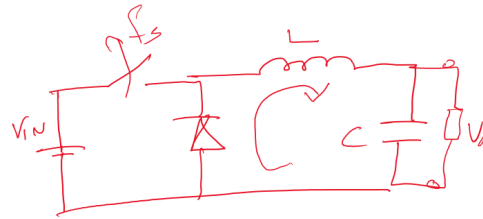

$$\bar{I}_o = \frac{DT_s}{2L} (V_d - V_o)$$

$$P_o = \bar{I}_o V_o$$

$$\bar{I}_o = \frac{P_o}{V_o} = 1A$$

$$L = \frac{DT_s}{2\bar{I}_o} (V_d - V_o) \Rightarrow L = \frac{0.125}{2(50 \times 10^3)(1)} (40 - 5)$$

$$D = \frac{5}{40} = 0.125 \quad \Rightarrow \quad L = 4.375 \times 10^{-5} = 43.75 \mu F$$

**7-2** Consider all components to be ideal. Assume  $V_o = 5\text{ V}$ ,  $f_s = 20\text{ kHz}$ ,  $L = 1\text{ mH}$ , and  $C = 470\text{ }\mu\text{F}$ . Calculate  $\Delta V_o$  (peak-peak) if  $V_d = 12.6\text{ V}$ , and  $I_o = 200\text{ mA}$ .

7-2

$$V_o = 5\text{ V}$$

$$f_s = 20\text{ kHz}$$

$$L = 1\text{ mH}$$

$$C = 470\text{ }\mu\text{F}$$

$$V_d = 12.6\text{ V}$$

$$I_o = 200\text{ mA}$$

$$\Delta V_o = ?$$



$$\Delta V_o = \frac{\Delta Q}{C} = \frac{1}{C} \cdot \frac{1}{2} \cdot \frac{\Delta i_L}{2} \cdot \frac{T_s}{2}$$

$$\Delta i_L = \frac{V_o}{L} (1-D) T_s \quad \uparrow$$

$$\Delta V_o = \frac{1}{8} \frac{T_s^2 (1-D)}{LC}$$

$$D = \frac{V_o}{V_d} = \frac{5\text{ V}}{12.6\text{ V}} = 0.397$$

$$\Delta V_o = \frac{1}{8} \cdot \frac{(1-0.397)}{(470 \times 10^{-6})(1 \times 10^{-3})} (20000)^2$$

$$\Delta V_o = 2.01\text{ mV}$$

**7-7** In a step-up converter, consider all components to be ideal. Let  $V_d$  be 8–16 V,  $V_o = 24$  V (regulated),  $f_s = 20$  kHz, and  $C = 470 \mu\text{F}$ . Calculate  $L_{\min}$  that will keep the converter operating in a continuous-conduction mode if  $P_o \geq 5$  W.

7-7 Step-up (boost)

$$8 \leq V_d \leq 16$$

$$V_o = 24 \text{ V}$$



$$f_s = 20 \text{ kHz}$$

$$C = 470 \mu\text{F}$$

$$P_o \geq 5 \text{ W}$$

$$L_{\min} = ?$$
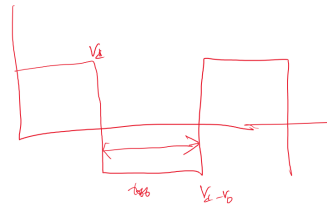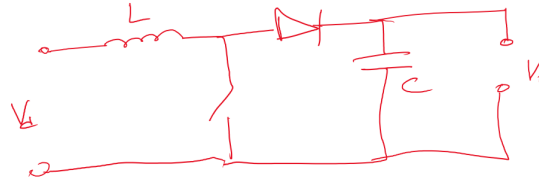
$$I_o = \frac{P}{V} = \frac{5}{24} = 0.2083 \text{ A}$$



$$\text{for } V_d = 8 \text{ V} \Rightarrow \phi = 1 - \frac{8}{24} = 1 - \frac{1}{3} = \frac{2}{3}$$

$$L = \frac{T_s V_o}{2 I_o} \phi (1 - \phi)^2 \Rightarrow \frac{24}{2(20000)(0.2083)} \cdot \frac{2}{3} \left(1 - \frac{2}{3}\right)^2$$

$$L = 0.213 \text{ mH}$$

$$V = L \frac{di}{dt}$$

$$L = V \frac{\Delta t}{\Delta i}$$

$$\left\{ \begin{array}{l} I_o = \frac{T_s V_o}{2L} D(1-D)^2 \\ \frac{T_s}{t_{off}} = \frac{1}{1-D} \end{array} \right.$$

$$\frac{T_s}{t_{off}} = \frac{1}{1-D}$$

$$1-D = \frac{t_{off}}{T_s}$$

$$D = 1 - \frac{t_{off}}{T_s}$$

$$\phi = 1 - \frac{V_d}{V_o}$$

$$\text{for } V_d = 16 \text{ V} \Rightarrow \phi = 1 - \frac{16}{24} = \frac{24-16}{24} = \frac{1}{3}$$

$$L = \frac{24}{2(20000)(0.2083)} \cdot \frac{1}{3} \left(1 - \frac{1}{3}\right)^2$$

$$L = 0.477 \text{ mH}$$

**7-8** In a step-up converter,  $V_d = 12 \text{ V}$ ,  $V_o = 24 \text{ V}$ ,  $I_o = 0.5 \text{ A}$ ,  $L = 150 \mu\text{H}$ ,  $C = 470 \mu\text{F}$ , and  $f_s = 20 \text{ kHz}$ . Calculate  $\Delta V_o$  (peak-peak).

7-8

$$V_d = 12 \text{ V}$$

$$V_o = 24 \text{ V}$$

$$I_o = 0.5 \text{ A}$$

$$L = 150 \mu\text{H}$$

$$C = 470 \mu\text{F}$$

$$f_s = 20 \text{ kHz}$$

$$\Delta V_o = ?$$

$$I_{avg} = \frac{I_{max} - I_o}{2}$$

$$I_{max} = \frac{V_d}{L} \phi T_s$$

$$I_o = \frac{T_s V_o}{2L} \phi (1 - \phi)^2$$

$$\phi = 1 - \frac{V_d}{V_o} = 1 - \frac{12}{24} = 0.5$$

$$I_o = \frac{1}{2(20000)(150 \times 10^{-6})} \cdot 0.5(1 - 0.5)^2$$

$$I_o = 0.5 \text{ A}$$

$$\frac{\Delta Q}{C} = \Delta V_o = \frac{V_o}{R} \cdot \frac{\phi T_s}{C} = \boxed{\frac{I_{avg} \phi T_s}{C}}$$

$$I_{max} = \frac{12}{(150 \times 10^{-6})} \cdot 0.5 \cdot \frac{1}{20,000} = 2 \text{ A}$$

$$I_{avg} = \frac{2 - 0.5}{2} = 0.75 \text{ A}$$

$$\Delta V = \frac{(0.75)(0.5)}{(20,000)(470 \times 10^{-6})} = 37 \text{ mV}$$

**7-12** In a buck-boost converter, consider all components to be ideal. Let  $V_d$  be 8–40 V,  $V_o = 15$  V (regulated),  $f_s = 20$  kHz, and  $C = 470$   $\mu$ F. Calculate  $L_{\min}$  that will keep the converter operating in a continuous-conduction mode if  $P_o \geq 2$  W.

7-12 Buck-boost

$$8 \leq V_d \leq 40$$

$$V_o = 15 \text{ V}$$

$$f_s = 20 \text{ kHz}$$

$$C = 470 \mu\text{F}$$

$$I_o = \frac{2}{15} = 0.133 \text{ A}$$

$$V_o = \frac{\phi V_d}{1 - \phi}$$

$$P_o \geq 2 \text{ W}$$

$$L_{\min} = ?$$

$$1 - \phi$$

$$\frac{1 - \phi}{\phi} = \frac{V_d}{V_o}$$

$$\frac{1}{\phi} - 1 = \frac{V_d}{V_o}$$

$$\frac{1}{\phi} = \frac{V_d}{V_o} + 1 = \frac{V_d + V_o}{V_o} \Rightarrow \phi = \frac{V_o}{V_d + V_o}$$

$$\text{at } V_d = 8 \text{ V}$$

$$\phi = \frac{15}{8 + 15} = \frac{15}{23} = 0.65$$

$$\text{at } V_d = 40 \text{ V}$$

$$\phi = \frac{15}{55} = 0.273$$

smallest  $\phi$  results in largest  $L_{\min}$ .

7-47

$$I_o = \frac{T_s V_o}{2L} (1 - \phi)^2$$

$$L = \frac{T_s V_o}{2 I_o} (1 - \phi)^2 = \frac{15}{2(20000)(0.133)} (1 - 0.273)^2$$

$$L = 1.49 \text{ mH}$$