


# Common mode Rejection Ratio (CMRR)

What is it and why does it matter?

25<sup>th</sup> October 2021
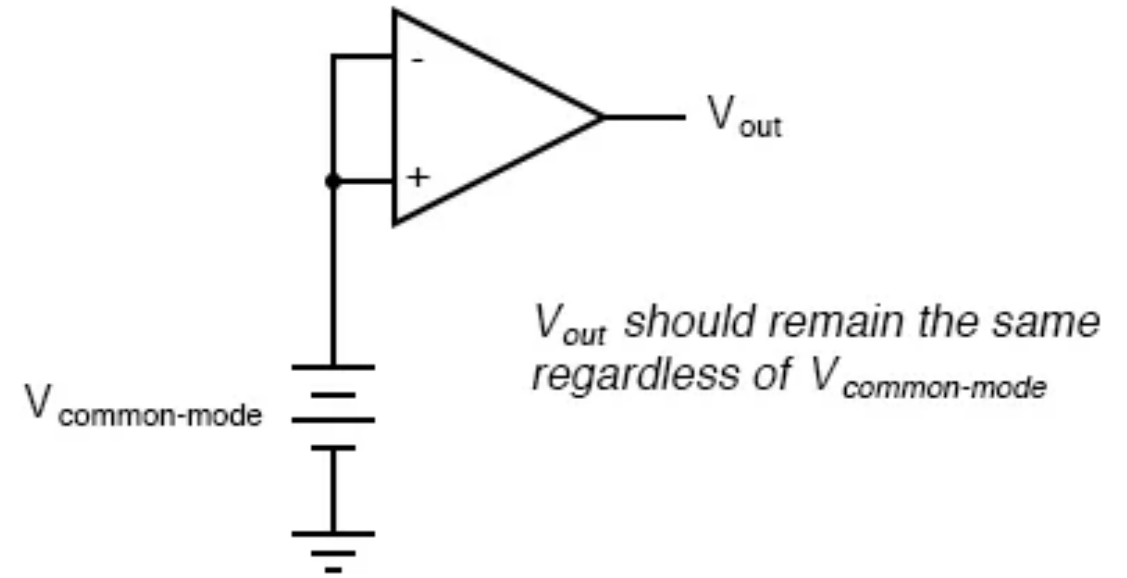
# Common Mode Voltage

- An ideal differential amplifier only amplifies the voltage difference between its two inputs.
- If the two inputs of a differential amplifier were to be shorted together there should be no change in output voltage.
- Voltage that is common between either of the inputs and ground, as “ $V_{\text{common-mode}}$ ” is in this case, is called *common-mode voltage*.



# Common Mode Gain


- The operational amplifier, being a differential amplifier with high differential gain, would ideally have zero common-mode gain.
- In reality this is not easily attained.
  - Thus, common-mode voltages will invariably have some effect on the op-amp's output voltage.

# Common Mode Rejection Ratio

- The op amp common-mode rejection ratio (CMRR) is the ratio of the common-mode gain to differential-mode gain.
  - For example, if a differential input change of  $Y$  volts produces a change of 1 V at the output, and a common-mode change of  $X$  volts produces a similar change of 1 V, then the CMRR is  $X/Y$ .
- When the common-mode rejection ratio is expressed in dB, it should strictly be referred to as common-mode rejection (CMR) but:
  - there is very little consistency in this throughout the semiconductor industry with regards to the use of dB or ratio values for CMR or CMRR.
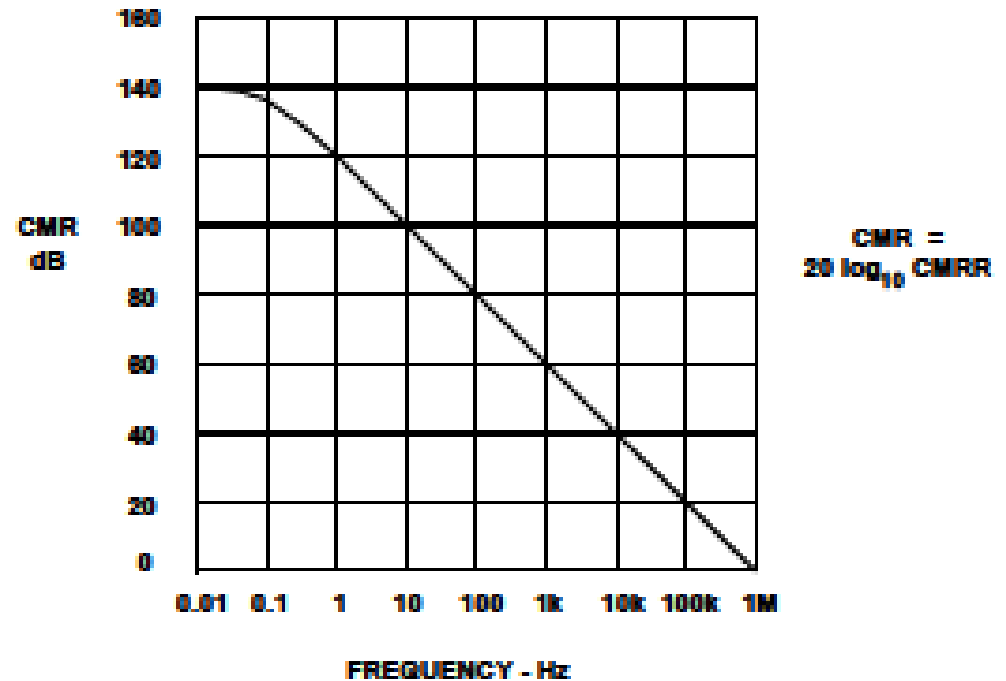
# Typical Values of CMR (or CMRR)


- Typical low frequency CMR values can be between 70 dB and 120 dB, but at higher frequencies CMR deteriorates.



CMRR for the OP177
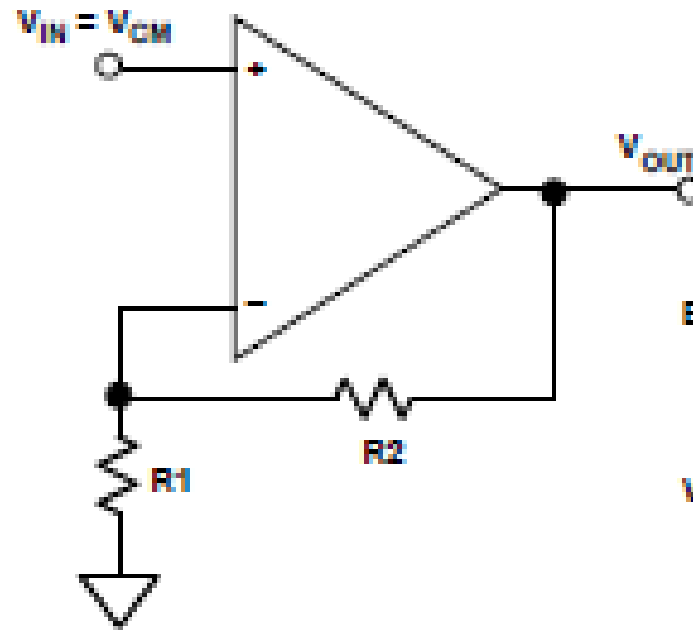
# Non-inverting Mode

- CMRR produces a corresponding output offset voltage error in op amps configured in the noninverting mode.



$$\text{ERROR (RTI)} = \frac{V_{CM}}{\text{CMRR}} = \frac{V_{IN}}{\text{CMRR}}$$

$$V_{OUT} = \left[ 1 + \frac{R2}{R1} \right] \left[ V_{IN} + \frac{V_{IN}}{\text{CMRR}} \right]$$

$$\text{ERROR (RTO)} = \left[ 1 + \frac{R2}{R1} \right] \left[ \frac{V_{IN}}{\text{CMRR}} \right]$$

Calculating Offset Error Due to Common-Mode Rejection Ratio (CMRR)

# Inverting Mode

- Because the common mode rejection ratio in a typical op-amp is very high, common-mode gain is usually not a great concern in circuits where the op-amp is being used with negative feedback.
- If the common-mode input voltage of an amplifier circuit were to suddenly change, thus producing a corresponding change in the output due to common-mode gain, that change in output would be quickly corrected as negative feedback and differential gain (being *much* greater than common-mode gain) worked to bring the system back to equilibrium.