




University  
of Glasgow

# Electronic System Design 3

## Lecture 7.1: Instrumentation Amps and Common Mode Rejection

Dr Duncan Bremner

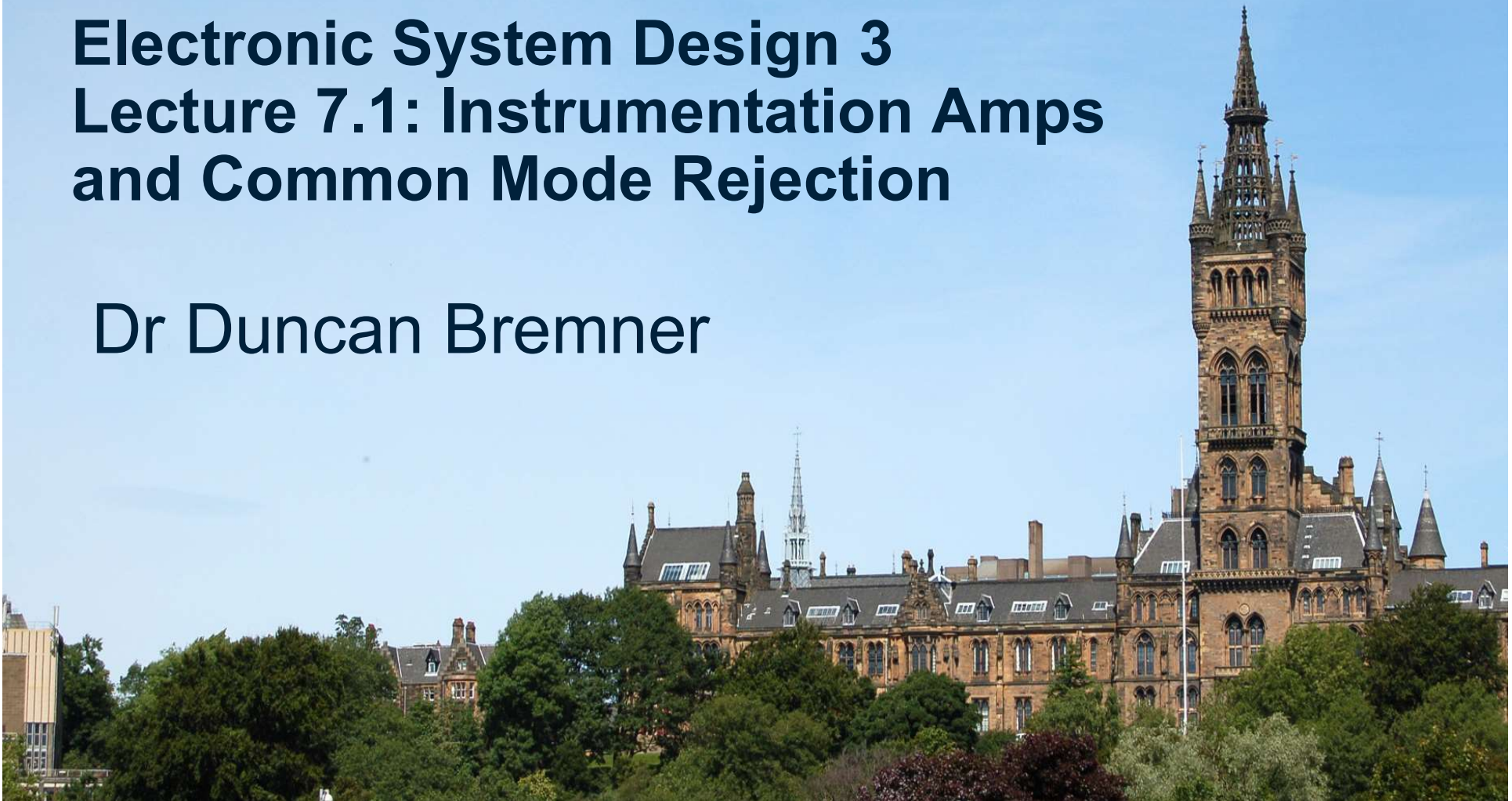



University  
of Glasgow

...From previous lecture

## Common-Mode Rejection

Problem with previous circuit is that ground is a signal level...

And a sewer for random stray currents


Use **PLAN B**

Measure the **difference** between the two leads and let them vary with respect to "Ground" however they like


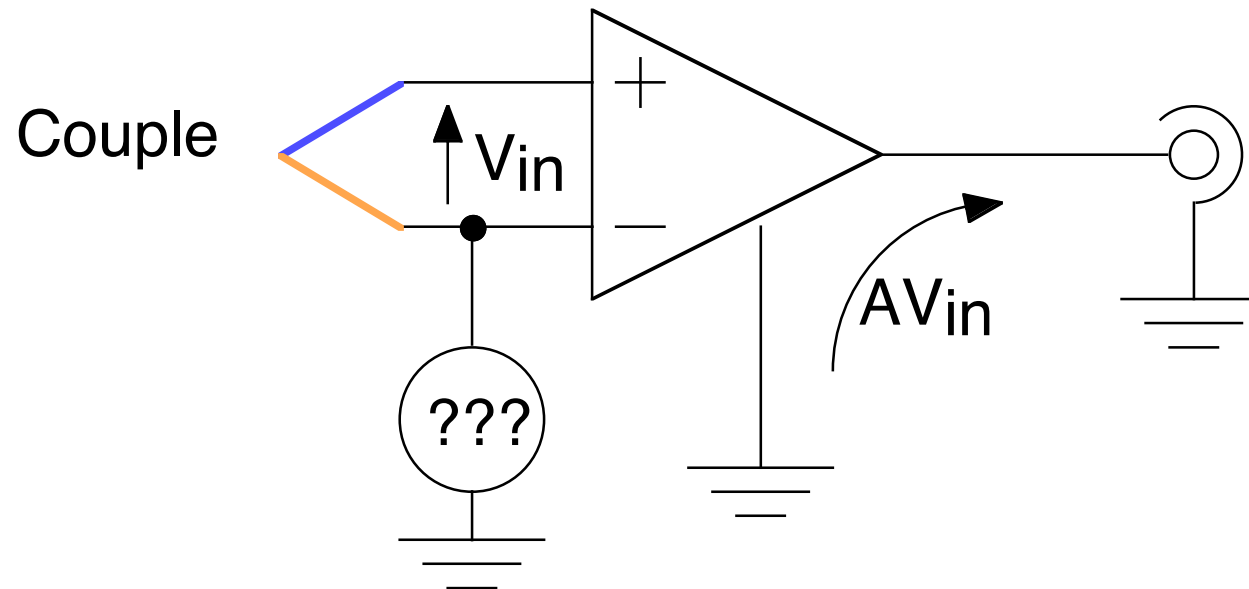
## Common-Mode Rejection (2)


Component “X” = **Instrumentation Amplifier**



- Component X
- Has a big gain (O/P is big, so no more problems)
  - Doesn't care what ground potential “???” Is  
= **Common-mode rejection**
  - Produces an output voltage with respect to an explicit third (output ground) input



# Perfect Instrumentation Amplifier

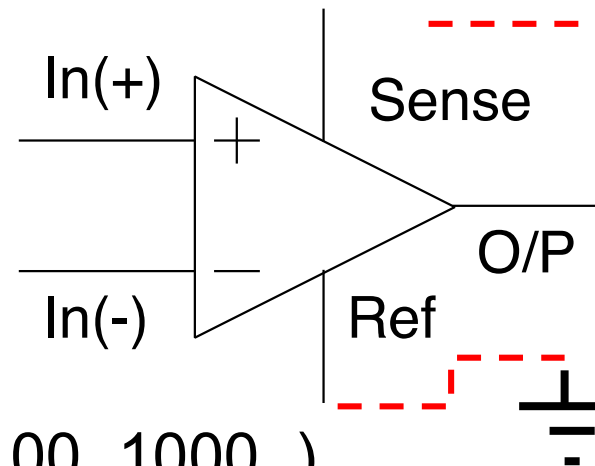

- Gain is finite (e.g. 100, 1000..)
- Gain is pure differential (Function of  $\text{In}(+) - \text{In}(-)$  only)
- Gain is ideally ZERO for pure common-mode signals
- "Sense" is feedback connection.
- 'Ref' is usually Ground

If "Sense" connected to "O/P"

$$(\text{O/P} - \text{Ref}) = A_V (\text{In}(+) - \text{In}(-)) + A_{CM} \left( \frac{\text{In}(+) + \text{In}(-)}{2} \right)$$


**Only if 'Perfect' Inst Amp;  $A_{CM} = 0$**

(Where  $A_V$  is the differential voltage gain and  $A_{CM}$  is the common-mode voltage gain)



## Instrumentation Amplifier (2)

### Application

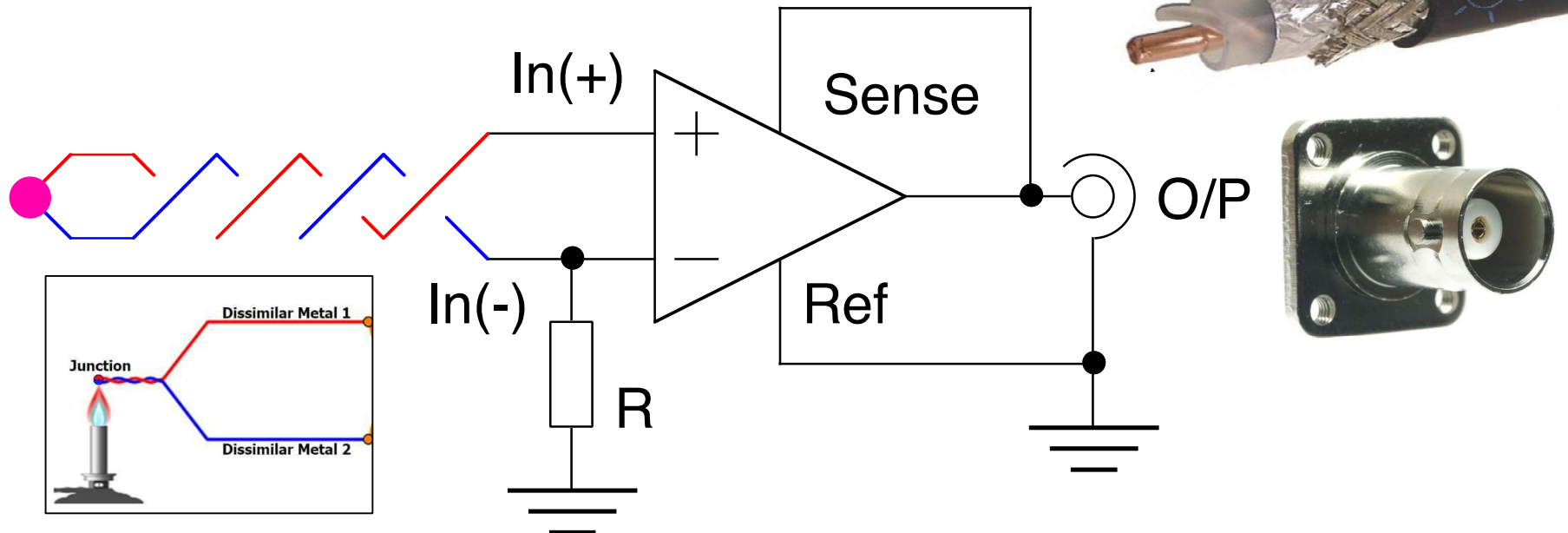

Instrumentation amp (INA) is connected to thermocouple by a twisted pair, to avoid magnetic pickup.

Ref is connected to the ground of the O/P connector

=> Voltage **between** inner & outer of coaxial cable is O/P


R is a large resistor to bleed away bias current (see later)

Circuit is immune to voltage present on "ground"




## Instrumentation Amplifier (3)

Improved:

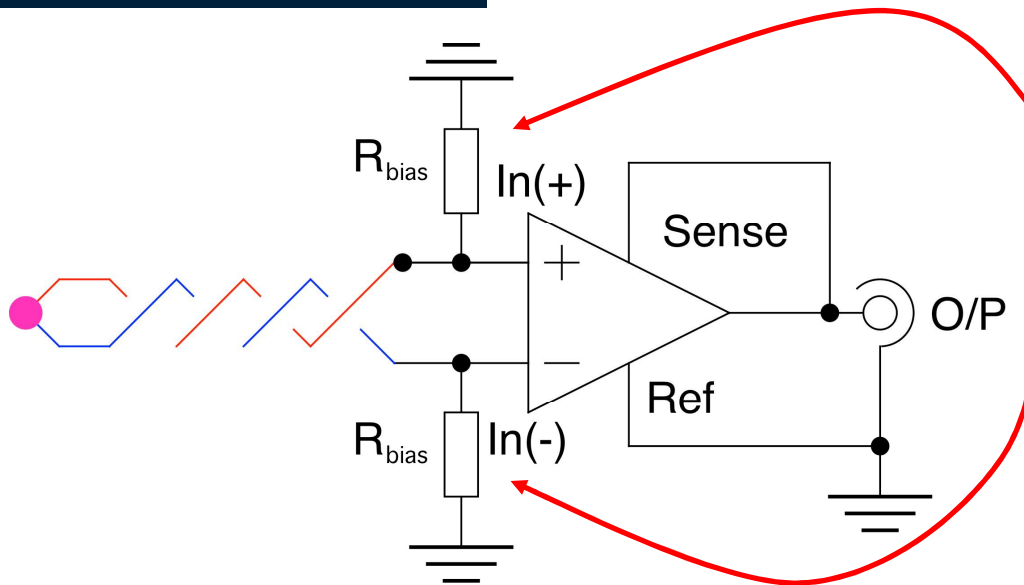

Since the name of the game is rejecting the average voltage; symmetry is always a good idea.

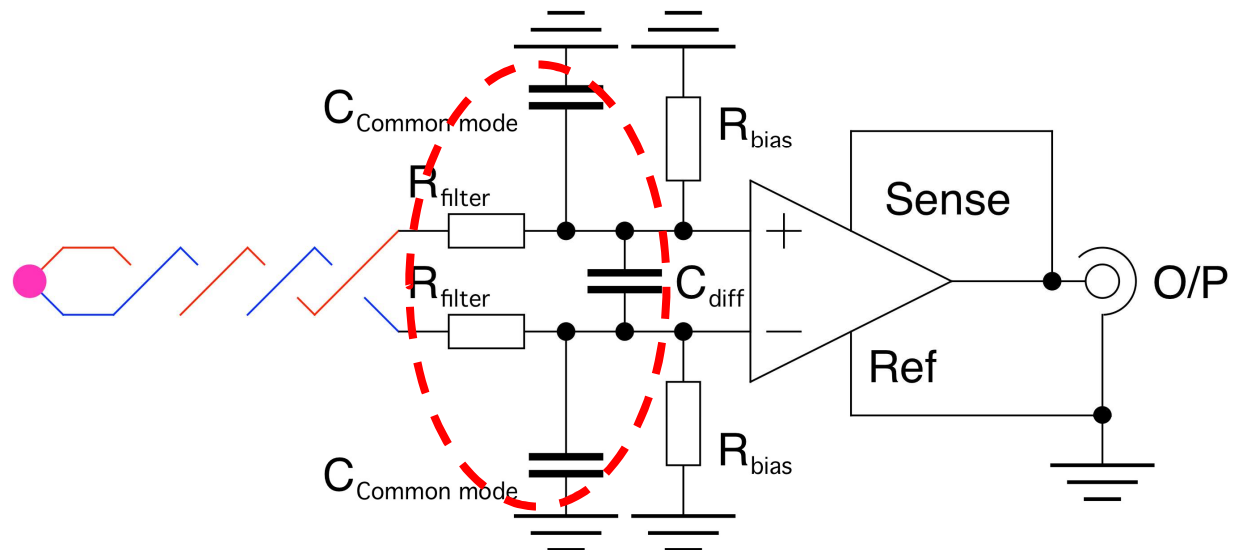Adding a low pass filter (symmetrical) to eliminate radiofrequency interference is a good practical move





## THAT 1510 Microphone Preamp

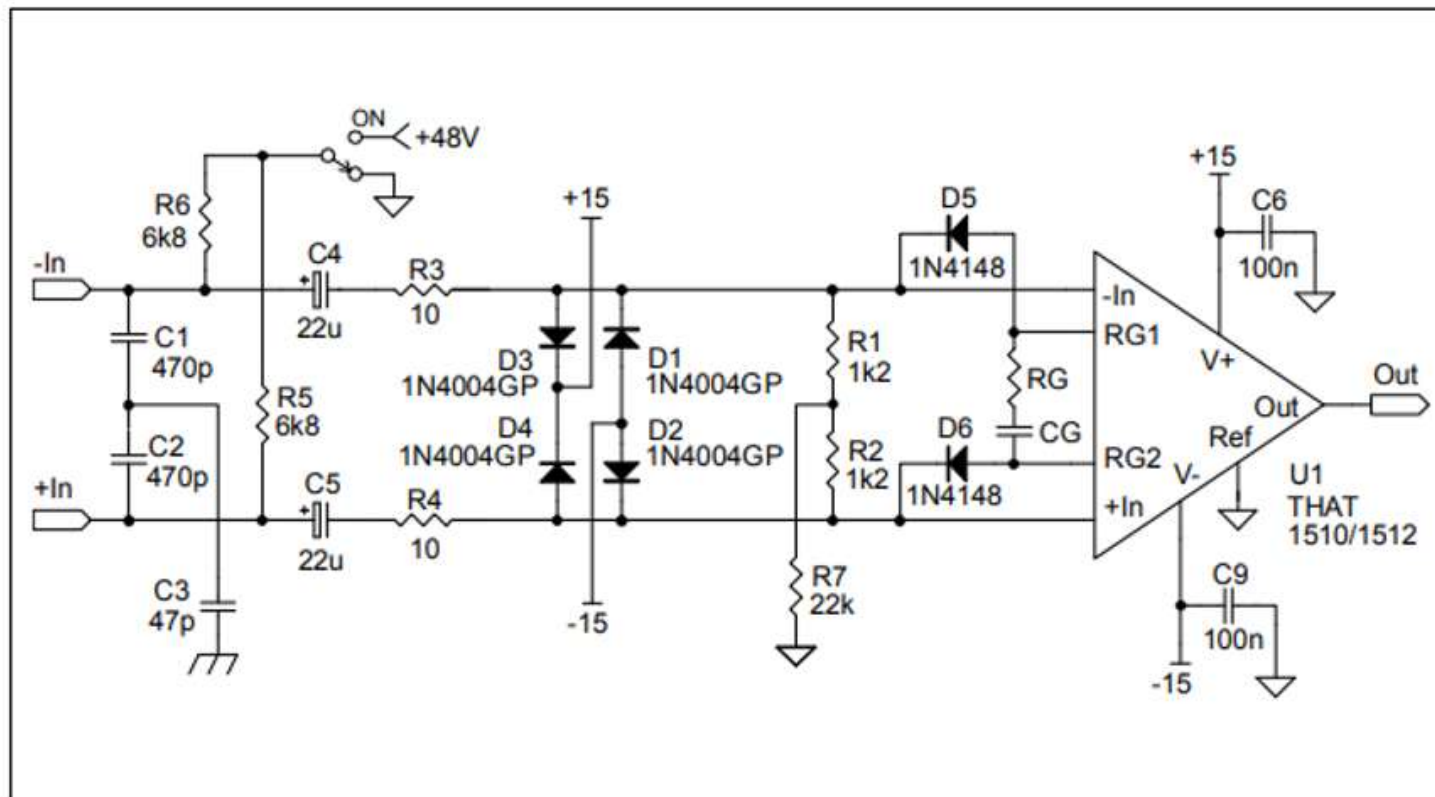


Figure 5. Recommended 1510 / 1512 Circuit with Phantom Power







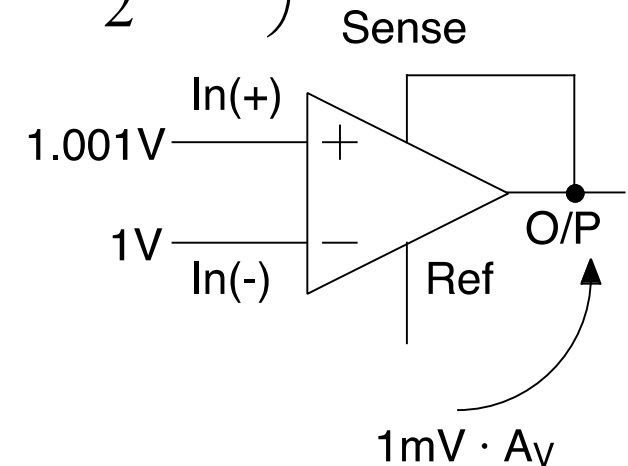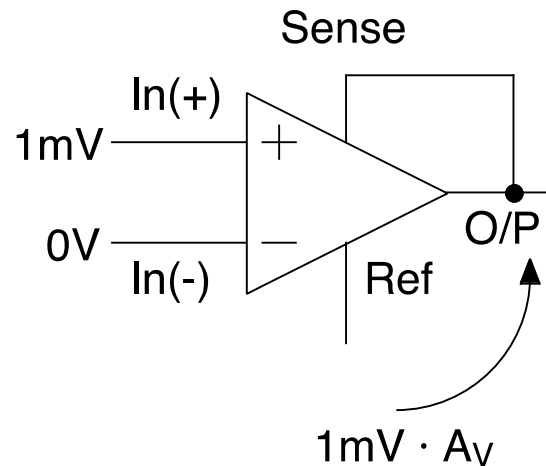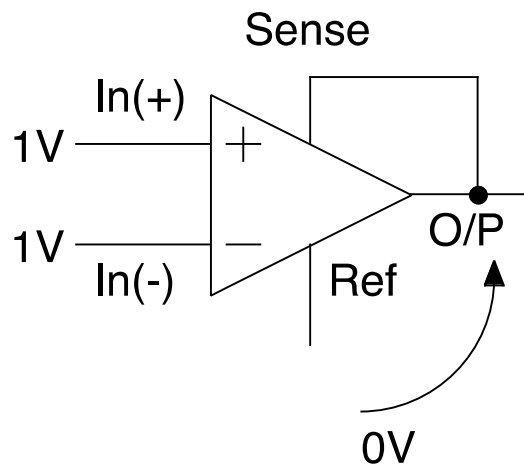
## Common-Mode Rejection Ratio (CMRR)

**Perfect** instrumentation amplifier  
has a “common-mode” gain = 0

$$(O/P - Ref) = A_V (In(+) - In(-)) = A_V (In(+) - In(-)) + 0 \left( \frac{In(+) + In(-)}{2} \right)$$




In practice no instrumentation amp is perfect: A change in the average (common-mode) voltage will give a change in output

$$(O/P - Ref) = A_V (In(+) - In(-)) + A_{CM} \frac{(In(+) + In(-))}{2}$$

Normally  $A_V \gg A_{CM}$ ;  $\frac{A_V}{A_{CM}} = CMRR$



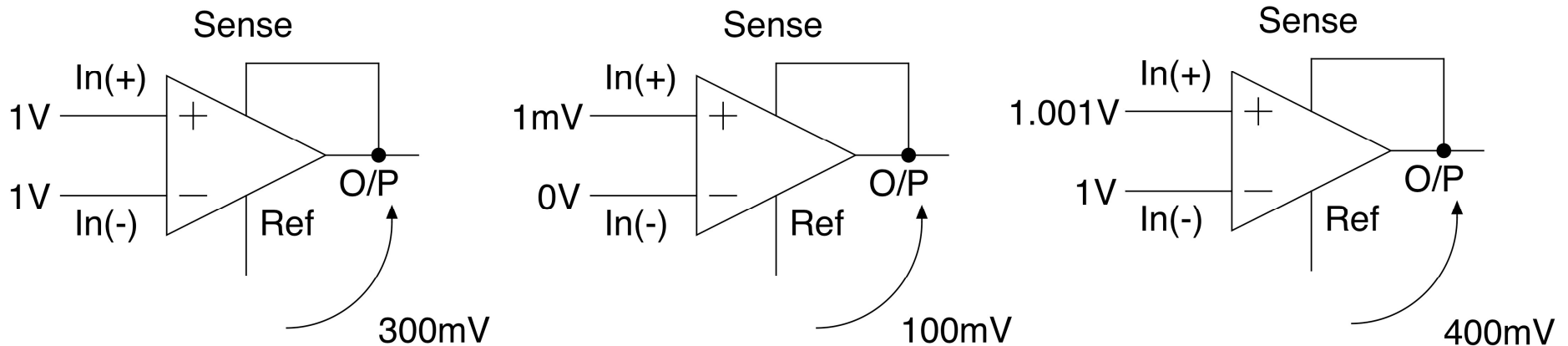Thus if  $A_v = 100$  and  $A_{CM} = 0.30$  (so  $CMRR = 333 = 50.4\text{dB}$ ):



So an input of 333mV on both inputs gives **Exactly** the same output as 1mV difference between both inputs: With a CMRR of 333 the minimum voltage difference you can detect is 1mV for a common - mode voltage of 300mV.

If the common mode voltage is 1V the minimum detectable differential voltage is 3mV.

**Important:** minimum detectable signal is assumed when the 'error' signal is the same as the 'real or wanted' signal.



University  
of Glasgow

Thank you  
谢谢

INSPIRING  
PEOPLE