




University  
of Glasgow

# Electronic System Design 3

## Lecture 10.1: Amplifier Noise analysis

Dr Duncan Bremner

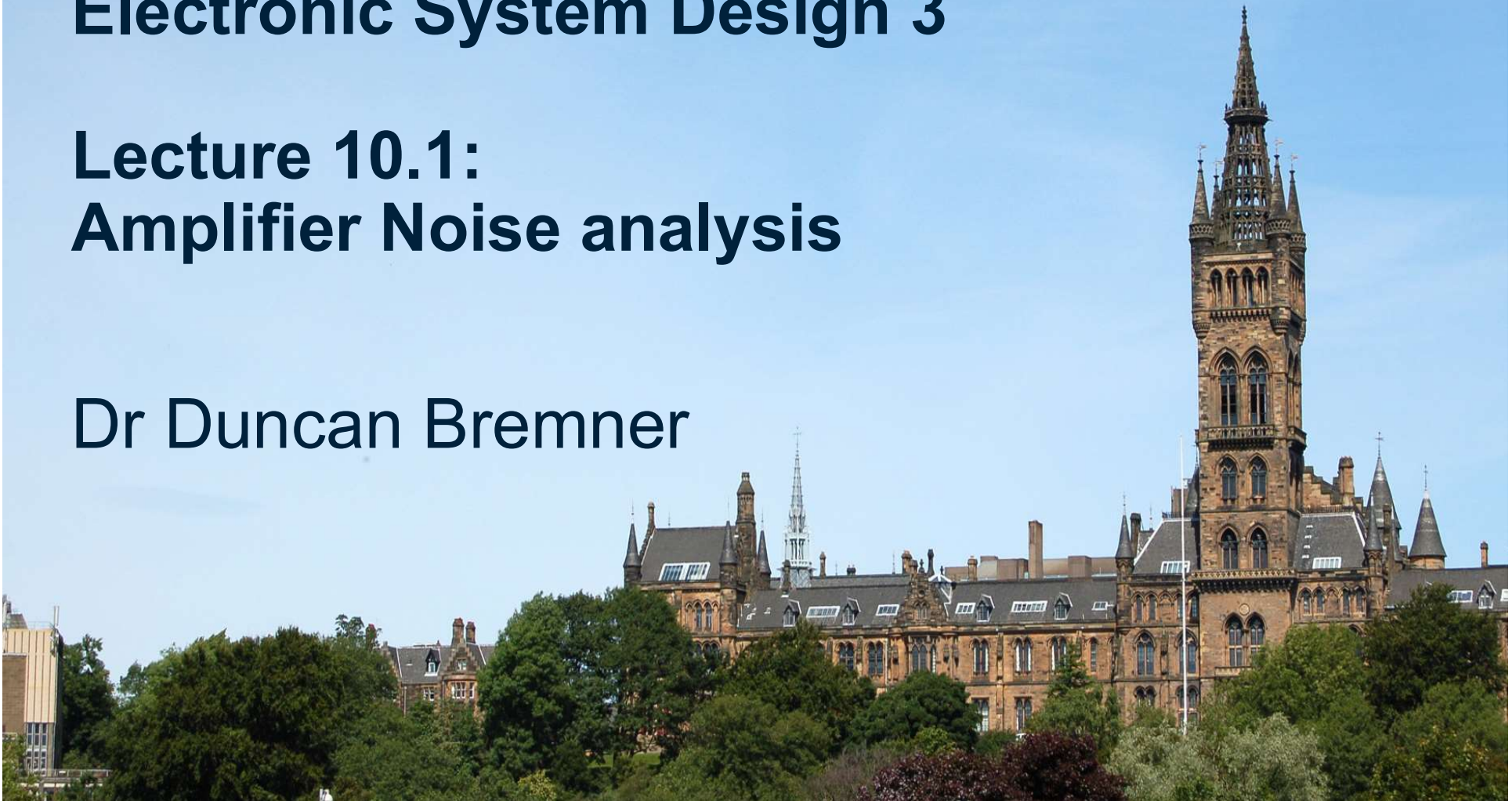

# Amplifier Noise

**All** resistors have the same thermal noise

Amplifiers have different noise levels

Noise depends on **details** of amplifier design


- Shot noise of input bias current
- Use of bias current cancellation
- Size of input transistor (flicker noise)
- Type of input transistor
  - Bipolar (low  $e_n$ )
  - MOS (low  $i_n$ )
  - JFET (lowish  $e_n, i_n$ )
- Input stage quiescent current / Resistor values

Input current noise and Input voltage noise. (Can't fix both!)


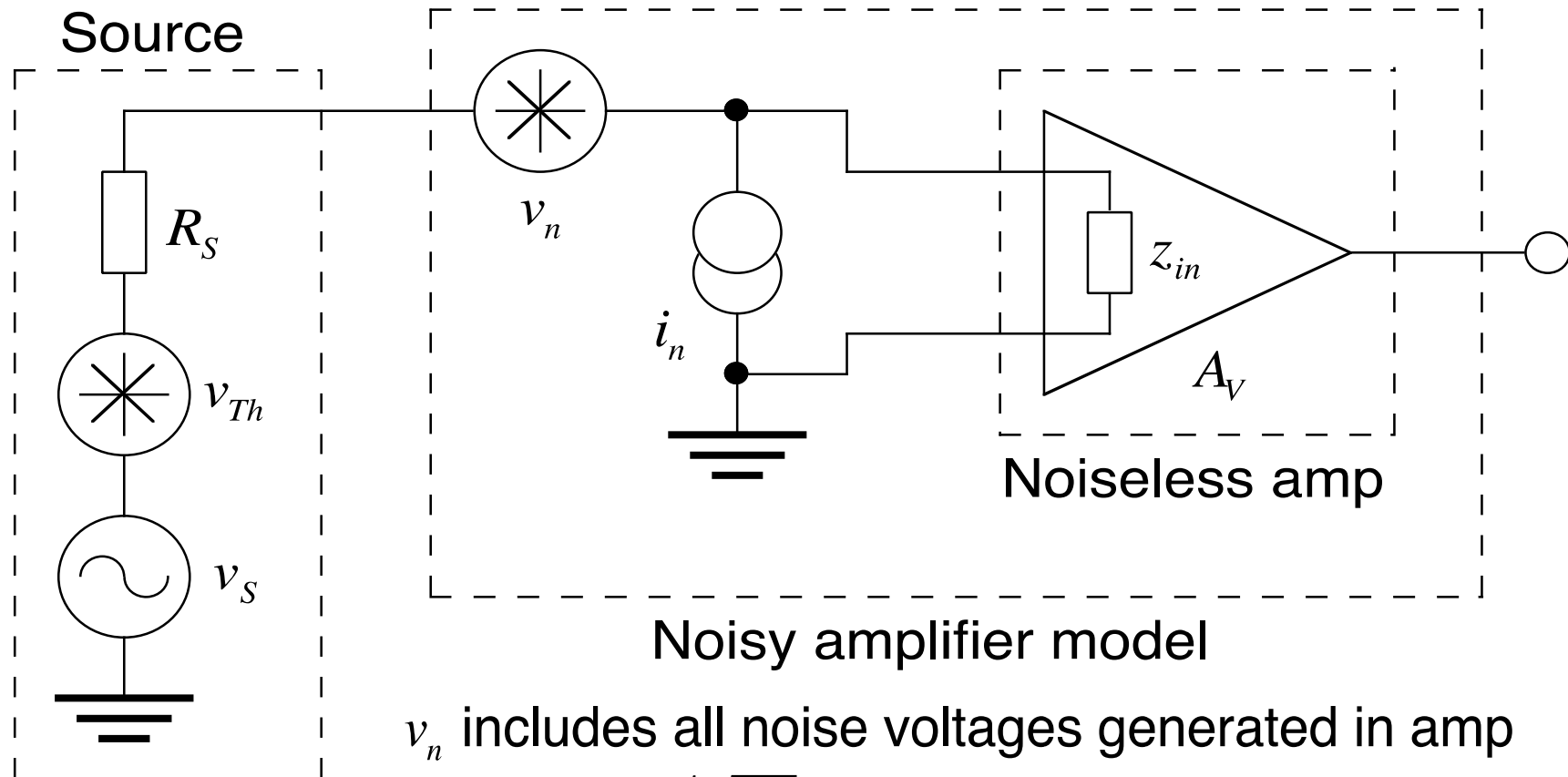
# Voltage Amplifier Noise Model

Need to compare amplifiers: Use a simplified model



Noisy amplifier model

$v_n$  includes all noise voltages generated in amp  
Units are  $V/\sqrt{\text{Hz}}$  (voltage noise spectral density)

$v_n$  is a function of frequency  
 $i_n$  is the same for noise current,  $A/\sqrt{\text{Hz}}$



## Amplifier Noise Model (2)

Equivalent input noise:

- Combine **all** noise sources into a single source at input  
(Add squares)
- Calculate output noise due to noise source
- Divide by system gain from source to O/P

System gain  $K = A_V \frac{z_{in}}{R_S + z_{in}}$  (Just like 1st year)

$$\text{From } v_{Th} : V_{OUT(Th)}^2 = |A_V|^2 \left| \frac{z_{in}}{R_S + z_{in}} \right|^2 v_{Th}^2$$

$$\text{From } v_n : V_{OUT(n)}^2 = |A_V|^2 \left| \frac{z_{in}}{R_S + z_{in}} \right|^2 v_n^2$$

$$\text{From } i_n : V_{OUT(i_n)}^2 = |A_V|^2 |z_{in} \parallel R_S|^2 i_n^2$$



## Amplifier Noise Model (3)

$$V_{OUT}^2(Total) = |A_V|^2 \left| \frac{Z_{in}}{R_S + Z_{in}} \right|^2 \left( v_{Th}^2 + v_n^2 \right) + |A_V|^2 |Z_{in} // R_S|^2 i_n^2$$

Divide by system gain


$$\frac{V_{OUT}^2(Total)}{K^2} = v_{Th}^2 + v_n^2 + \frac{|A_V|^2 \frac{|Z_{in}|^2 |R_S|^2}{|Z_{in} + R_S|^2}}{|A_V|^2 \frac{|Z_{in}|^2}{|Z_{in} + R_S|^2}} i_n^2 = v_{ni}^2$$

$$\Rightarrow v_{ni}^2 = v_{Th}^2 + v_n^2 + i_n^2 |R_S|^2$$

Interesting observation: Independent of  $Z_{in}$



## Amplifier Noise Model (4)

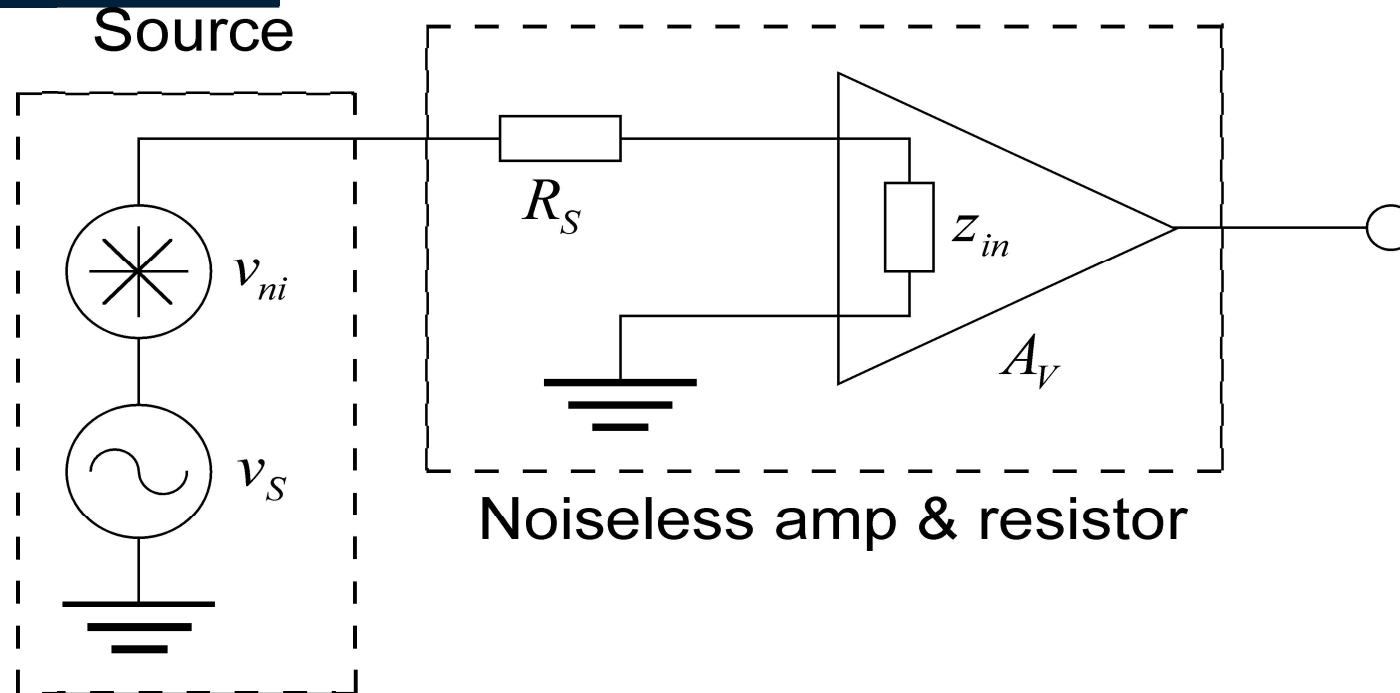


All noise sources replaced by single noise generator

- Independent of amplifier gain
- Independent of amplifier input resistance

Makes comparison of amplifiers easier

# Graphical Noise Calculations

Effect of source resistance on noise

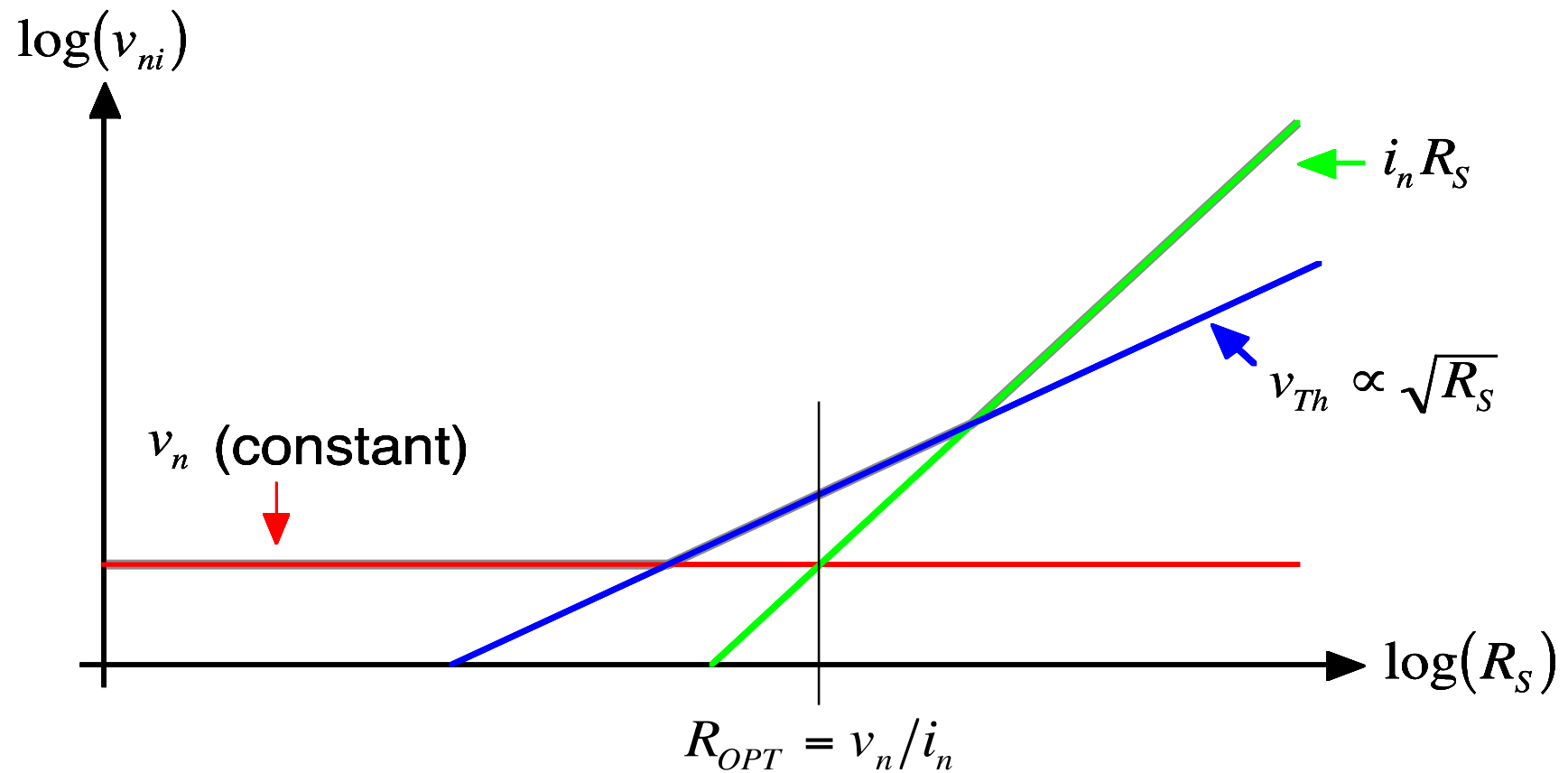


At  $R_s = R_{OPT}$  amplifier adds minimum noise to (irreducible) thermal noise



# Let's look at a real amplifier...

VOLTAGE NOISE vs SOURCE RESISTANCE

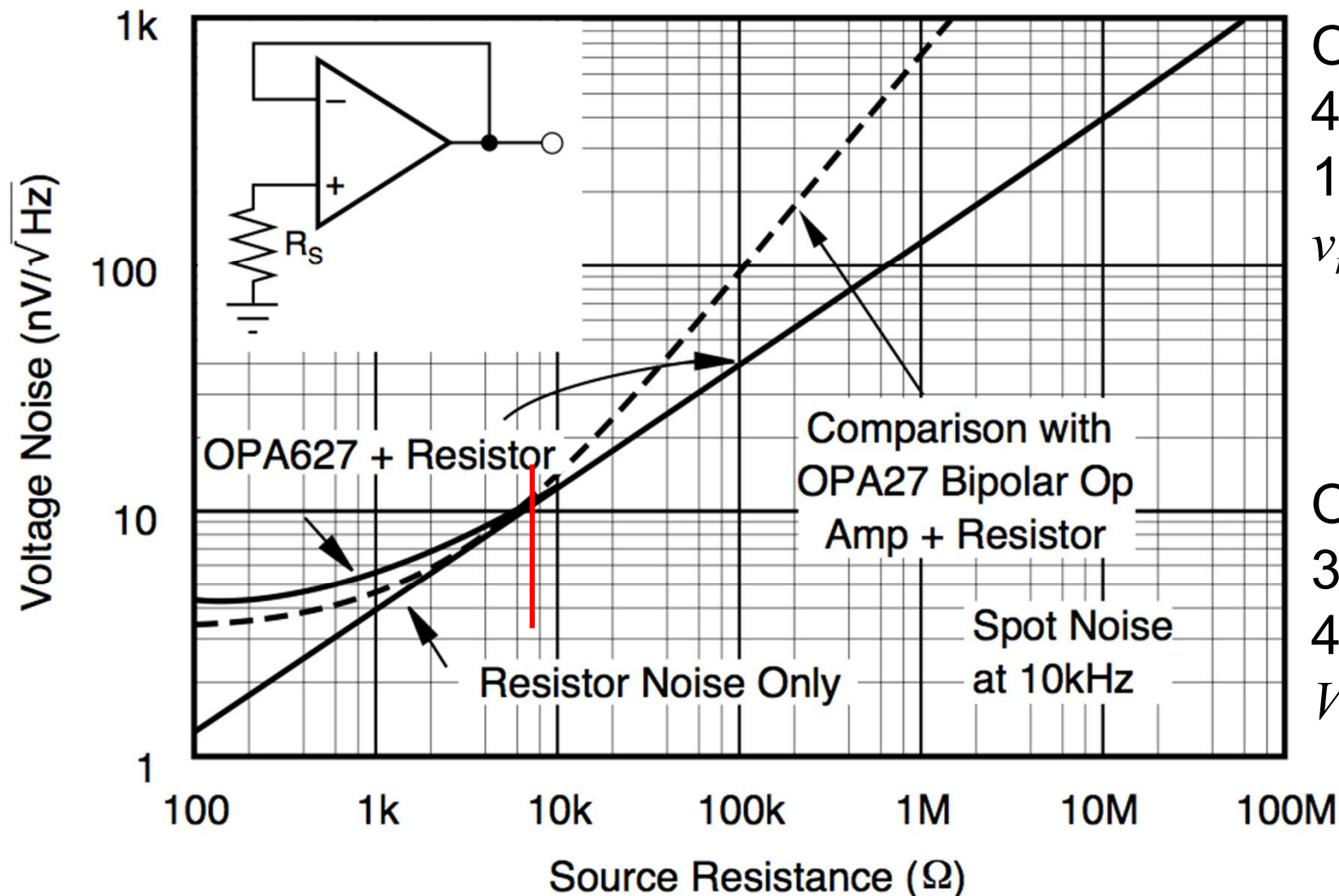

OPA627:  
 $4.5\text{nV Hz}^{-1/2}$   
 $1.6\text{fA Hz}^{-1/2}$   
 $v_n/i_n = 2.8\text{M}\Omega$

OPA27:  
 $3\text{nV Hz}^{-1/2}$   
 $400\text{fA Hz}^{-1/2}$   
 $V_n/i_n = 7.5\text{k}\Omega$





University  
of Glasgow

Thank you  
谢谢

INSPIRING  
PEOPLE