


# Tutorial 3 for CAD

## Sample Questions and Exercises

2020-21

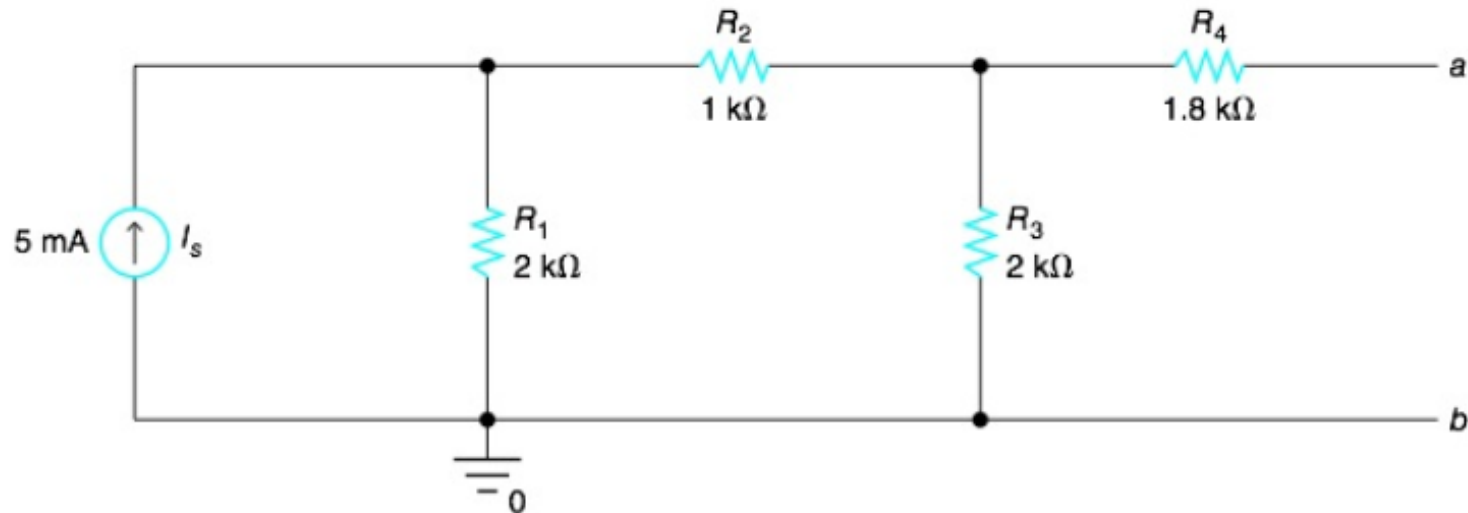
# 1 Thevenin Equivalent Circuit

- Find the Thevenin equivalent circuit between a and b for the circuit shown below



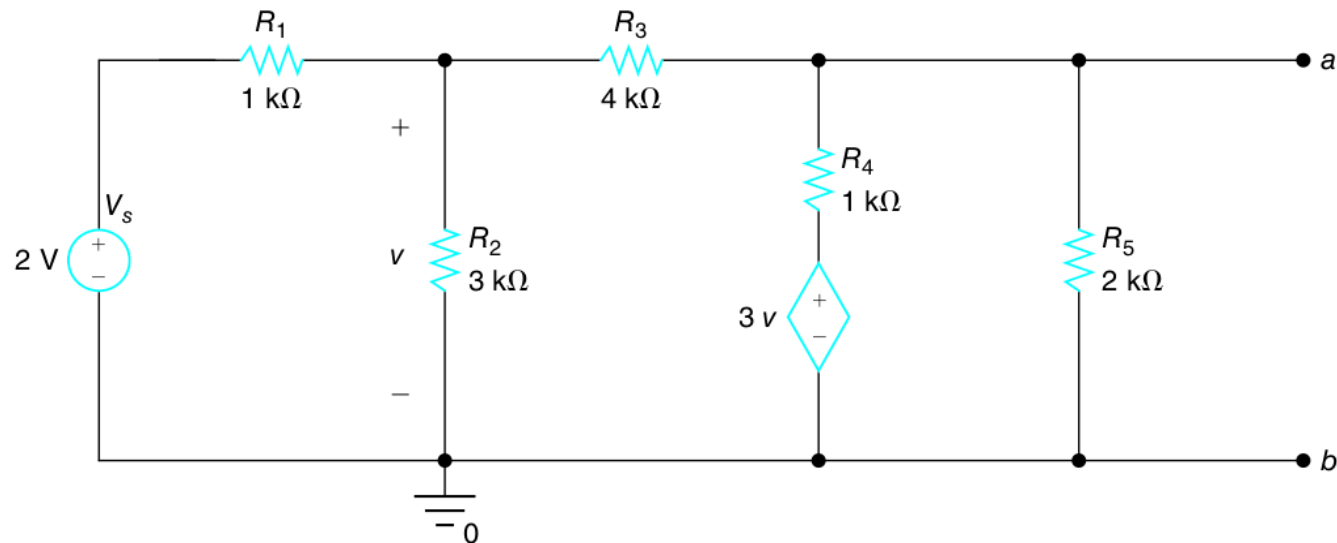
## 2 Thevenin Equivalent Circuit

- Find the Thevenin equivalent circuit between a and b for the circuit shown below



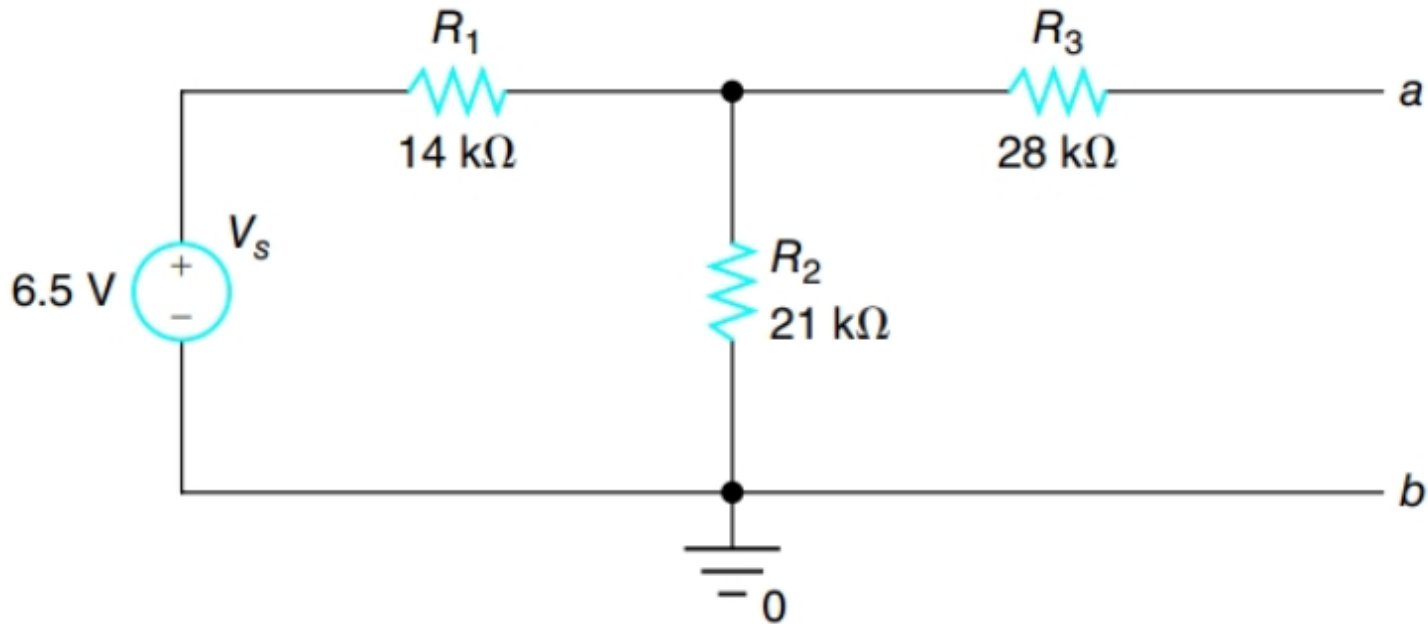
### 3 Norton Equivalent Circuit

- Find the Norton equivalent circuit between a and b for the circuit shown below



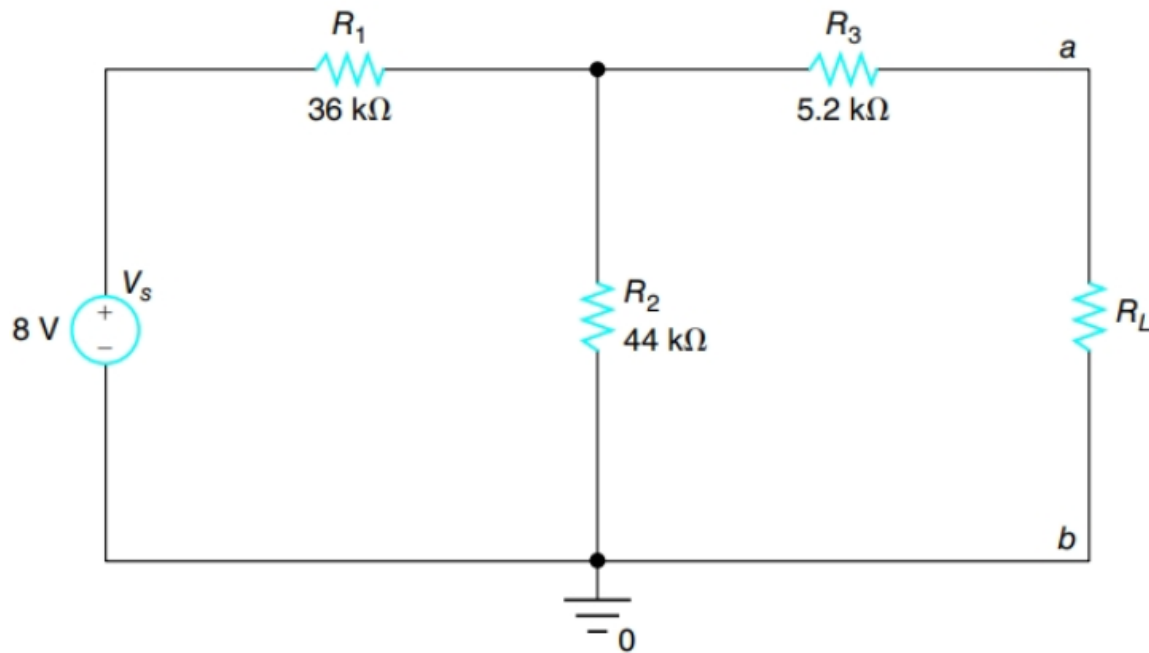
# 4 Maximum Power Transfer

- Find the load resistance value  $R_L$  for maximum power transfer, and find the maximum power transferred to the load for the circuit shown below


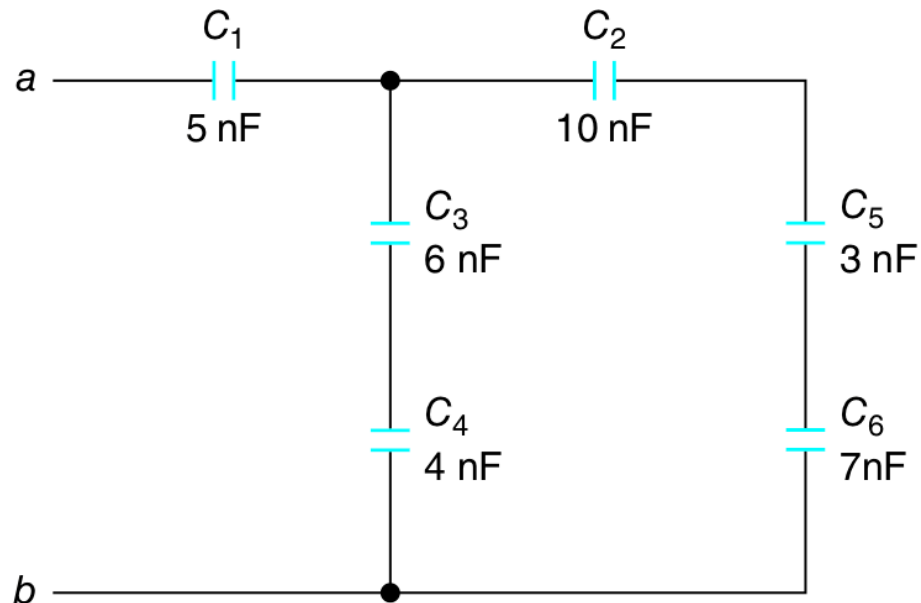
# 5 Capacitors


- Find the equivalent capacitance between  $a$  and  $b$  for the circuit shown in Figure below:


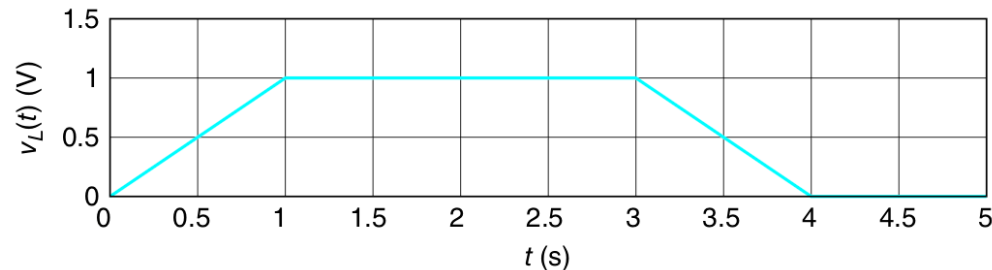
# 6 Inductors

- The voltage across an inductor with inductance of 510 mH is given by as  $v_L(t)$  and shown in the figure below:

$$v_L(t) = \begin{cases} t, & 0 \leq t < 1 \\ 1, & 1 \leq t < 3 \\ -t + 4, & 3 \leq t < 4 \\ 0, & \text{otherwise} \end{cases} \text{ V}$$



- Find and plot the current through the inductor  $i_L(t)$ .
- Find and plot the instantaneous power  $p(t)$  on the inductor.
- Find and plot the instantaneous energy  $w(t)$  stored on the inductor.