



Circuit Analysis and Design

Academic year 2019/2020 – Semester 1 – Presentation 4

Masood Ur-Rehman, Qammer H. Abbasi, Guodong Zhao

[masood.urrehman](mailto:masood.urrehman@glasgow.ac.uk), [qammer.abbasi](mailto:qammer.abbasi@glasgow.ac.uk), [guodong.zhao](mailto:guodong.zhao@glasgow.ac.uk)@glasgow.ac.uk

“A good student never steal or cheat”

- 2

Equivalent Resistance of Parallel Connection of Two Resistors

- Two resistors R_1 and R_2 are connected in parallel as shown in Figure 2.34(a).
- I_1 = current through R_1 , I_2 = current through R_2 , V = voltage across R_1 and R_2
- KCL:

$$I = I_1 + I_2 = \frac{V}{R_1} + \frac{V}{R_2} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V \Rightarrow V = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} I = R_{eq} I$$

- The equivalent resistance

$$R_{eq} = R_1 \parallel R_2 = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$

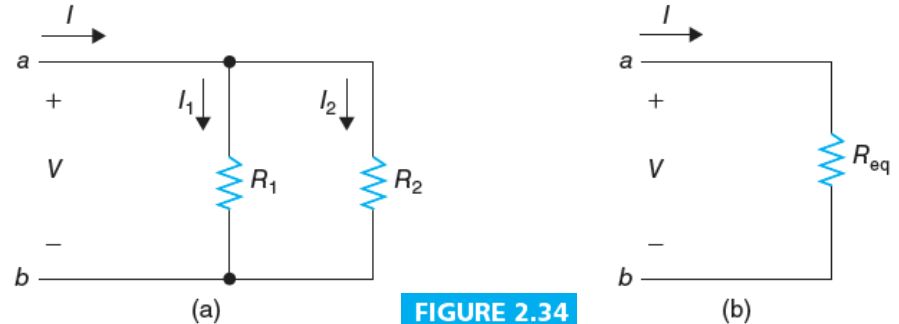


FIGURE 2.34

- The circuit shown in Figure 2.34(a) can be replaced by the equivalent circuit shown in Figure 2.34(b).

Properties of $R_{eq} = R_1 \parallel R_2$

$$R_{eq} = R_1 \parallel R_2 = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$

- $R_{eq} < R_1, R_{eq} < R_2$

The equivalent resistance is smaller than the smaller of the two.

- $R_1 \parallel 0 = 0, R_1 \parallel \infty = R_1.$
- If $R_1 \ll R_2, R_1 \parallel R_2 \approx R_1.$
- If $R_1 = R_2 = R, R_1 \parallel R_2 = R \parallel R = R/2.$

Equivalent Resistance of Parallel Connection of n Resistors

- n resistors R_1, R_2, \dots, R_n are connected in parallel as shown in Figure 2.35(a).
- I_1 = current through R_1 , I_2 = current through R_2 , ..., I_n = current through R_n
- V = voltage across R_1, R_2, \dots, R_n , equivalent circuit in Figure 2.35(b).
- KCL

$$I = I_1 + I_2 + \dots + I_n = \frac{V}{R_1} + \frac{V}{R_2} + \dots + \frac{V}{R_n} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \right) V$$

$$V = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}} I = R_{eq} I$$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$

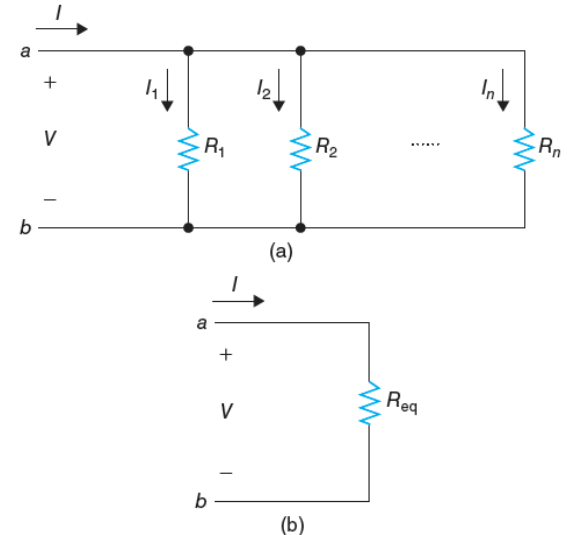


FIGURE 2.35

Circuit with Parallel Connection of Resistors

- Find I_1 , V_1 , V_2 , I_2 , I_3 , V_3 , I_4 , I_5 , and I_6 in the circuit shown in Figure 2.36.

$$R_a = R_2 \parallel R_3 = \frac{R_2 \times R_3}{R_2 + R_3} = \frac{21k\Omega \times 28k\Omega}{21k\Omega + 28k\Omega} = \frac{588}{49} k\Omega = 12k\Omega$$

$$R_b = R_4 \parallel R_5 \parallel R_6 = \frac{1}{\frac{1}{33} + \frac{1}{40} + \frac{1}{88}} k\Omega = \frac{1}{0.06667} k\Omega = 15k\Omega$$

- The circuit reduces to the one in Figure 2.37. The current I_1 is

$$I_1 = \frac{V_s}{R_1 + R_a + R_b} = \frac{15V}{30k\Omega} = 0.5mA$$

- $V_1 = R_1 I_1 = 1.5V$, $V_2 = R_a I_1 = 6V$,
 $V_3 = R_b I_1 = 7.5V$, $I_2 = V_2 / R_2 = 0.2857mA$
 $I_3 = V_2 / R_3 = 0.2143mA$, $I_4 = V_3 / R_4 = 0.2273mA$,
 $I_5 = V_3 / R_5 = 0.1875mA$, $I_6 = V_3 / R_6 = 0.08523mA$

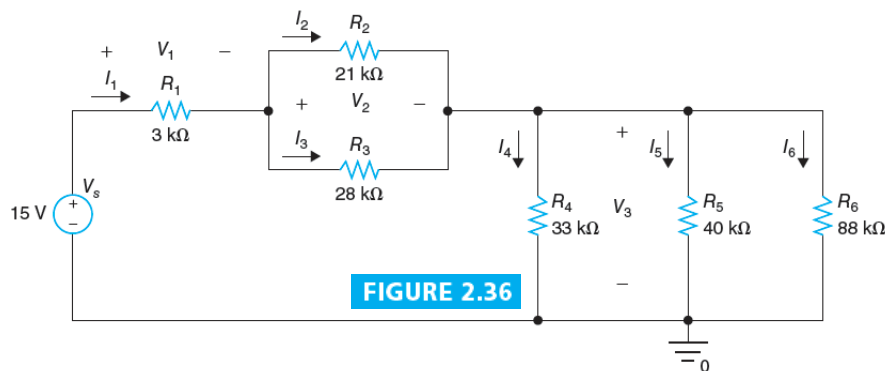


FIGURE 2.36

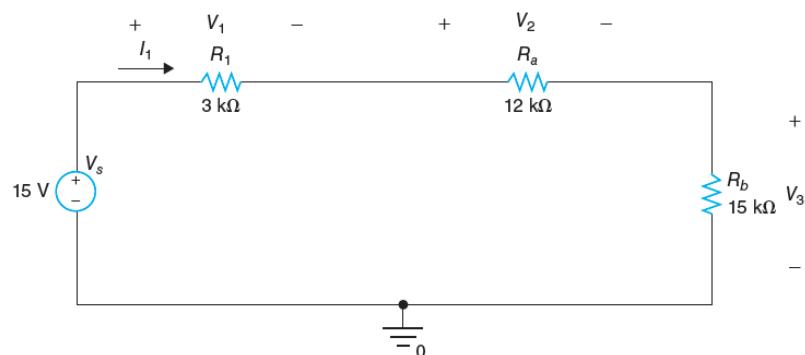


FIGURE 2.37

EXAMPLE 2.11

- Find the equivalent resistance between terminals a and b for the circuit shown in Figure 2.38.

$$R_6 = R_4 \parallel R_5 = \frac{50 \times 75}{50 + 75} \text{ k}\Omega = 30 \text{ k}\Omega$$

- $R_7 = R_3 + R_6 = 60 \text{ k}\Omega$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_7}} = \frac{1}{\frac{1}{45} + \frac{1}{90} + \frac{1}{60}} \text{ k}\Omega = 20 \text{ k}\Omega$$

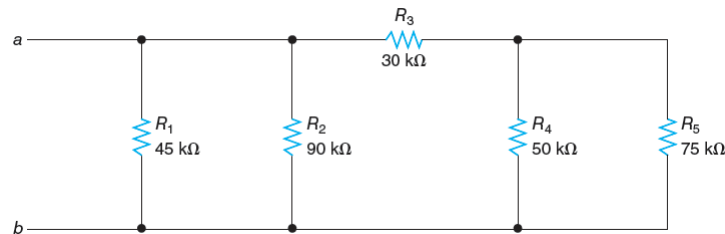


FIGURE 2.38

EXAMPLE 2.12

- Find the equivalent resistance seen from the voltage source. Also find I , I_1 , I_2 , V_1 , V_2 , V_3 , and power absorbed by resistors and power released by the voltage source.
- $R_a = R_3 \parallel R_4 = R_3 \times R_4 / (R_3 + R_4) = 100/25 \text{ k}\Omega = 4 \text{ k}\Omega$, $R_{eq} = R_1 + R_2 + R_a = 9 \text{ k}\Omega$
- $I = V_s / R_{eq} = 9/9000 \text{ A} = 1 \text{ mA}$
- $V_1 = R_1 I = 2 \text{ V}$, $V_2 = R_2 I = 3 \text{ V}$, $V_3 = R_a I = 4 \text{ V}$
- $I_1 = V_3 / R_3 = 0.8 \text{ mA}$, $I_2 = V_3 / R_4 = 0.2 \text{ mA}$
- $P_{R1} = I V_1 = 2 \text{ mW}$, $P_{R2} = I V_2 = 3 \text{ mW}$, $P_{R3} = I_1 V_3 = 3.2 \text{ mW}$, $P_{R4} = I_2 V_3 = 0.8 \text{ mW}$
- $P_{V_s} = -I V_s = -9 \text{ mW}$
- Power absorbed by resistors = 9 mW
- Power released by voltage source = 9 mW

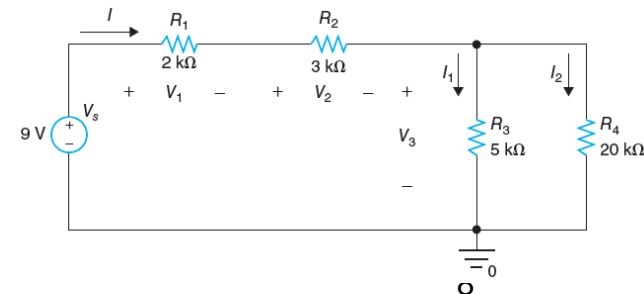


FIGURE 2.40

EXAMPLE 2.13

- Find R_{eq} seen from the voltage source in the circuit shown in Fig.2.43. Also find $I_1, I_2, I_3, I_4, I_5, V_1, V_2, V_3$, and power absorbed by resistors and power released by the voltage source.
- $R_a = R_4 \parallel R_5 = R_4 \times R_5 / (R_4 + R_5) = 24/10 \text{ k}\Omega = 2.4 \text{ k}\Omega$, $R_b = R_3 + R_a = 4 \text{ k}\Omega$
- $R_c = R_2 \parallel R_b = R_2 \times R_b / (R_2 + R_b) = 64/20 \text{ k}\Omega = 3.2 \text{ k}\Omega$, $R_{eq} = R_1 + R_c = 5 \text{ k}\Omega$
- $I_1 = V_s / R_{eq} = 10/5000 \text{ A} = 2 \text{ mA}$, $V_1 = V_s - R_1 I_1 = 6.4 \text{ V}$, $I_2 = V_1 / R_2 = 6.4/16000 \text{ A} = 0.4 \text{ mA}$
- $I_3 = I_1 - I_2 = 1.6 \text{ mA}$, $V_2 = V_1 - R_3 I_3 = 3.84 \text{ V}$, $I_4 = V_2 / R_4 = 3.84/4000 \text{ A} = 0.96 \text{ mA}$, $V_{R5} = V_3$
- $I_5 = V_2 / R_5 = 3.84/6000 \text{ A} = 0.64 \text{ mA}$, $V_{R1} = R_1 I_1 = 3.6 \text{ V}$, $V_{R3} = R_3 I_3 = 2.56 \text{ V}$, $V_{R2} = V_1$, $V_{R4} = V_3$
- $P_{R1} = I_1 V_{R1} = 7.2 \text{ mW}$, $P_{R3} = I_3 V_{R3} = 4.096 \text{ mW}$, $P_{R2} = I_2 V_{R2} = 2.56 \text{ mW}$
- $P_{R4} = I_4 V_{R4} = 3.6864 \text{ mW}$
- $P_{R5} = I_5 V_{R5} = 2.4576 \text{ mW}$
- $P_{Vs} = -I_1 V_s = -20 \text{ mW}$, Power released = 20 mW
- Power absorbed by five resistors = 20 mW

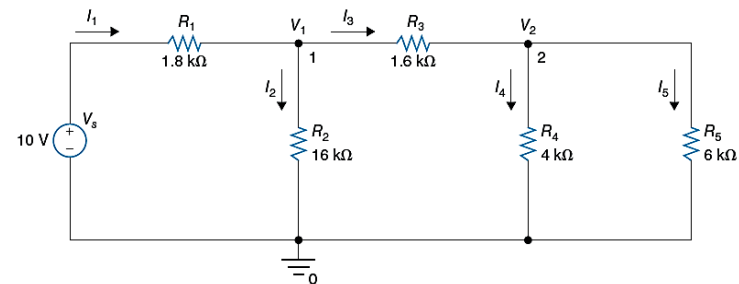


FIGURE 2.43

EXAMPLE 2.14

- Find the equivalent resistance seen from the current source. Also find I_a , I_1 , I_2 , I_3 , I_4 , I_5 , I_6 , I_7 , V_1 , V_2 , V_3 for the circuit shown in Figure 2.46.
- $R_8 = R_1 \parallel R_2 = R_1 \times R_2 / (R_1 + R_2) = 1200/80 \text{ k}\Omega = 15 \text{ k}\Omega$, $R_9 = R_3 + R_8 = 20 \text{ k}\Omega$
- $R_a = R_4 \parallel R_9 = R_4 \times R_9 / (R_4 + R_9) = 600/50 \text{ k}\Omega = 12 \text{ k}\Omega$
- $R_{10} = R_6 \parallel R_7 = R_6 \times R_7 / (R_6 + R_7) = 960/64 \text{ k}\Omega = 15 \text{ k}\Omega$, $R_b = R_5 + R_{10} = 36 \text{ k}\Omega$
- $R_{eq} = R_a \parallel R_b = R_a \times R_b / (R_a + R_b) = 432/48 \text{ k}\Omega = 9 \text{ k}\Omega$
- $V_1 = R_{eq} I_s = 9000 \times 0.002 = 18 \text{ V}$, $I_a = V_1 / R_a = 18/12000 \text{ A} = 1.5 \text{ mA}$, $I_5 = I_s - I_a = 0.5 \text{ mA}$
- $I_4 = V_1 / R_4 = 18/30000 \text{ A} = 0.6 \text{ mA}$, $I_3 = I_a - I_4 = 0.9 \text{ mA}$, $V_2 = V_1 - R_3 I_3 = 13.5 \text{ V}$
- $I_1 = V_2 / R_1 = 0.675 \text{ mA}$
- $I_2 = V_2 / R_2 = 0.225 \text{ mA}$
- $V_3 = V_1 - R_5 I_5 = 7.5 \text{ V}$
- $I_6 = V_3 / R_6 = 0.3125 \text{ mA}$
- $I_7 = V_3 / R_7 = 0.1875 \text{ mA}$

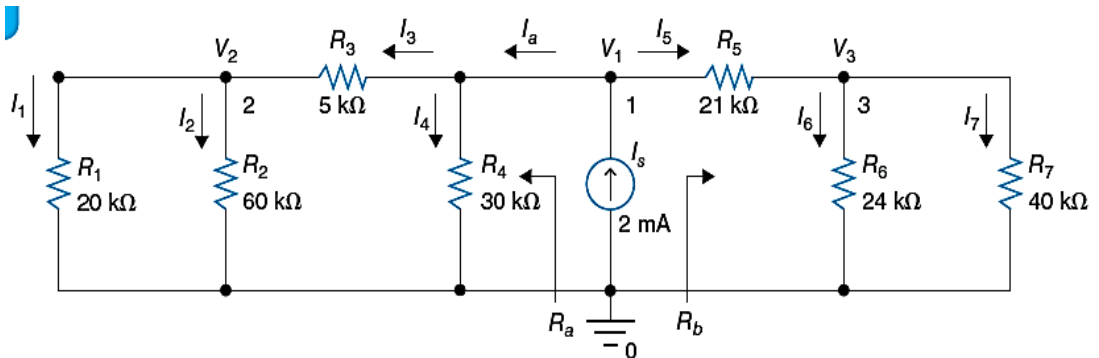


FIGURE 2.46

Voltage Divider Rule for Two Resistors

- A voltage source is connected to a series connection of resistors R_1 and R_2 as shown in Figure 2.49.
- The current through the resistors is given by $I = \frac{V_s}{R_1 + R_2}$


- The voltage across R_1 is given by

$$V_1 = I \times R_1 = \frac{V_s}{R_1 + R_2} \times R_1 = V_s \times \frac{R_1}{R_1 + R_2}$$

- The voltage across R_2 is given by

$$V_2 = I \times R_2 = \frac{V_s}{R_1 + R_2} \times R_2 = V_s \times \frac{R_2}{R_1 + R_2}$$

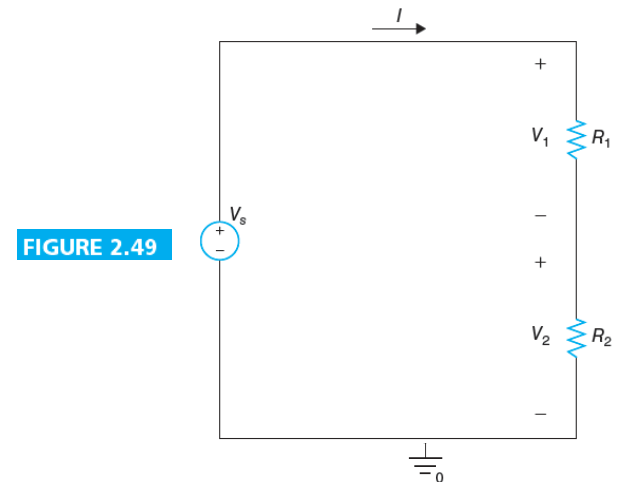- The voltage from the voltage source is divided between R_1 and R_2 in proportion to the resistance values.



Voltage Divider Rule for n Resistors

- A voltage source is connected to a series connection of n resistors R_1, R_2, \dots, R_n .
- The current through the resistors is given by

$$I = \frac{V_s}{R_1 + R_2 + \dots + R_n} \qquad I = \frac{V_s}{R_1 + R_2 + \dots + R_n}$$

- The voltage across R_i is given by

$$V_i = I \times R_i = \frac{V_s}{R_1 + R_2 + \dots + R_n} \times R_i = V_s \times \frac{R_i}{R_1 + R_2 + \dots + R_n}$$

- The voltage from the voltage source is divided among n resistors in proportion to the resistance values.



Circuit Analysis Using Voltage Divider Rule

- We are interested in finding V_1 , V_2 , and V_3 .
- $R_a = R_1 \parallel R_2 = R_1 \times R_2 / (R_1 + R_2) = 6/5 \text{ k}\Omega = 1.2 \text{ k}\Omega$
- $R_b = R_3 \parallel R_4 = R_3 \times R_4 / (R_3 + R_4) = 12/8 \text{ k}\Omega = 1.5 \text{ k}\Omega$
- $R_c = R_5 \parallel R_6 = R_5 \times R_6 / (R_5 + R_6) = 23.805/10.35 \text{ k}\Omega = 2.3 \text{ k}\Omega$

$$V_1 = V_s \times \frac{R_a}{R_a + R_b + R_c} = 10 \times \frac{1.2}{1.2 + 1.5 + 2.3} \text{ V} = 10 \times \frac{1.2}{5} \text{ V} = 2.4 \text{ V}$$

$$V_2 = V_s \times \frac{R_b}{R_a + R_b + R_c} = 10 \times \frac{1.5}{1.2 + 1.5 + 2.3} \text{ V} = 10 \times \frac{1.5}{5} \text{ V} = 3 \text{ V}$$

$$V_3 = V_s \times \frac{R_c}{R_a + R_b + R_c} = 10 \times \frac{2.3}{1.2 + 1.5 + 2.3} \text{ V} = 10 \times \frac{2.3}{5} \text{ V} = 4.6 \text{ V}$$

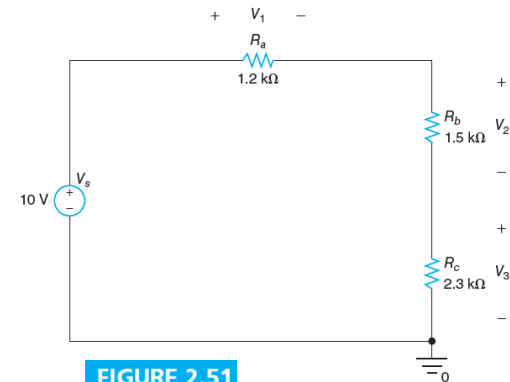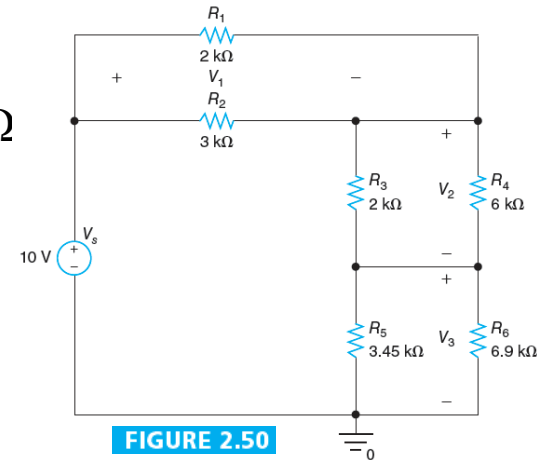


EXAMPLE 2.15

- Find V_1 , V_2 , and V_3 in the circuit shown in Figure 2.52.
- $R_a = R_2 \parallel R_3 = R_2 \times R_3 / (R_2 + R_3) = 24/10 \text{ k}\Omega = 2.4 \text{ k}\Omega$

$$V_1 = V_s \times \frac{R_1}{R_1 + R_a + R_4} = 14 \times \frac{1.2}{1.2 + 2.4 + 3.4} \text{ V} = 14 \times \frac{1.2}{7} \text{ V} = 2.4 \text{ V}$$

$$V_2 = V_s \times \frac{R_a}{R_1 + R_a + R_4} = 14 \times \frac{2.4}{1.2 + 2.4 + 3.4} \text{ V} = 14 \times \frac{2.4}{7} \text{ V} = 4.8 \text{ V}$$

$$V_3 = V_s \times \frac{R_4}{R_1 + R_a + R_4} = 14 \times \frac{3.4}{1.2 + 2.4 + 3.4} \text{ V} = 14 \times \frac{3.4}{7} \text{ V} = 6.8 \text{ V}$$

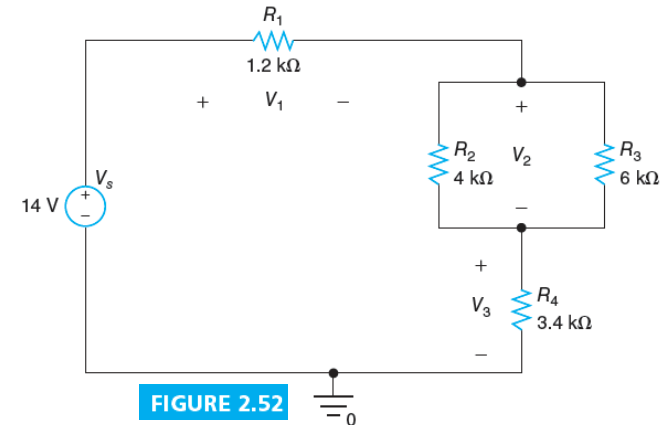

EXAMPLE 2.16

- Find V_1 , V_2 , and V_3 in the circuit shown in Figure 2.54.
- $R_a = R_1 \parallel (R_2 + R_3) = 28 \times 52 / (28 + 52) \text{ k}\Omega = 18.2 \text{ k}\Omega$
- $R_b = R_4 \parallel (R_5 + R_6) = 38 \times 57 / (38 + 57) \text{ k}\Omega = 22.8 \text{ k}\Omega$

$$V_1 = V_s \times \frac{R_b}{R_a + R_b} = 20.5 \times \frac{22.8}{18.2 + 22.8} \text{ V} = 20.5 \times \frac{22.8}{41} \text{ V} = 11.4 \text{ V}$$

$$V_2 = V_1 + (V_s - V_1) \times \frac{R_3}{R_2 + R_3} = 11.4 \text{ V} + 9.1 \times \frac{32}{20 + 32} \text{ V} = 11.4 \text{ V} + 5.6 \text{ V} = 17 \text{ V}$$

$$V_3 = V_1 \times \frac{R_6}{R_5 + R_6} = 11.4 \times \frac{30}{27 + 30} \text{ V} = 6 \text{ V}$$

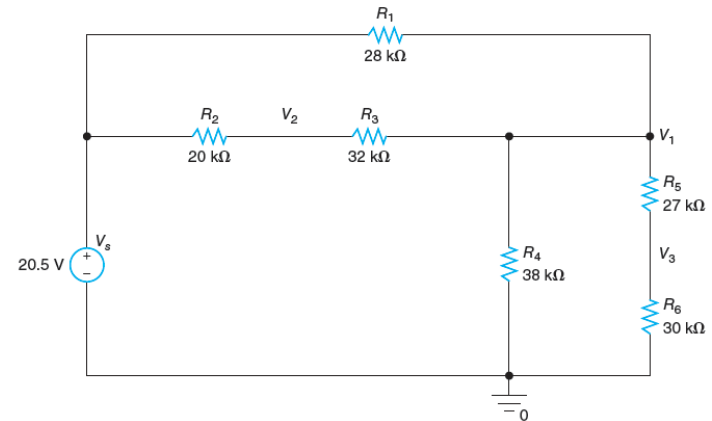


FIGURE 2.54

Current Divider Rule for Two Resistors in Parallel

- Two resistors are connected in parallel to a current source (Fig.2.58).

The equivalent resistance of R_1 and R_2 is given by

$$R = R_1 \parallel R_2 = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

The voltage across R_1 and R_2 is given by

$$V = I_s R = I_s \times \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$


- The current through R_1 and R_2 are given respectively by

$$I_1 = \frac{V}{R_1} = I_s \times \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2}} = I_s \times \frac{G_1}{G_1 + G_2} = I_s \times \frac{R_2}{R_1 + R_2}, \quad I_2 = \frac{V}{R_2} = I_s \times \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}} = I_s \times \frac{G_2}{G_1 + G_2} = I_s \times \frac{R_1}{R_1 + R_2}$$

- The current I_s from the current source is divided between R_1 and R_2 in proportion to the conductance (inverse of resistance) value. More current flows through smaller resistance.

FIGURE 2.58

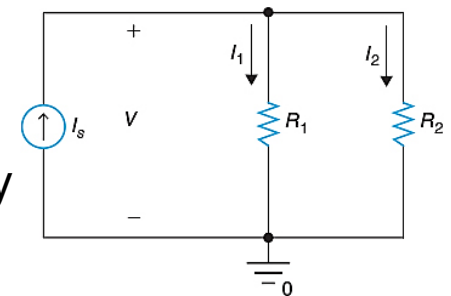A circuit with two resistors in parallel.



Current Divider Rule for n Resistors in Parallel

- n resistors are connected in parallel to a current source with current I_s .
- The equivalent resistance is given by

$$R = R_1 \parallel R_2 \parallel \dots \parallel R_n = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$

- The voltage across the resistors is given by $V = I_s R = I_s \times \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$
- The current through the i th resistor R_i is

$$I_i = \frac{V}{R_i} = I_s \times \frac{\frac{1}{R_i}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}} = I_s \times \frac{G_i}{G_1 + G_2 + \dots + G_n}$$

- The current I_s from the current source is divided between resistors in proportion to the conductance (inverse of resistance) values.

Circuit Analysis Using Current Divider Rule

- Find I_1 , I_2 , I_3 in the circuit shown in Figure 2.59.
- $R_a = R_3 + (R_1 \parallel R_2) = 0.8 \text{ k}\Omega + 1.2 \text{ k}\Omega = 2 \text{ k}\Omega$
- $R_b = R_7 + (R_5 \parallel R_6) = 2.6 \text{ k}\Omega + 2.4 \text{ k}\Omega = 5 \text{ k}\Omega$

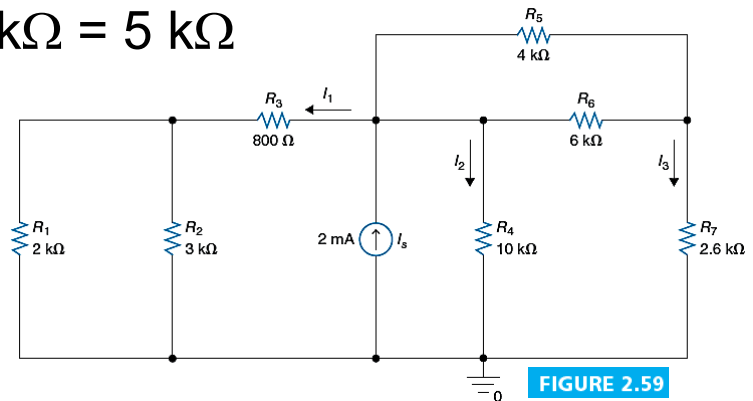


FIGURE 2.59

$$I_1 = I_s \times \frac{\frac{1}{R_a}}{\frac{1}{R_a} + \frac{1}{R_4} + \frac{1}{R_b}} = 2 \times \frac{\frac{1}{2}}{\frac{1}{2} + \frac{1}{10} + \frac{1}{5}} \text{ mA} = 2 \times \frac{5}{8} \text{ mA} = 1.25 \text{ mA}$$

$$I_2 = I_s \times \frac{\frac{1}{R_4}}{\frac{1}{R_a} + \frac{1}{R_4} + \frac{1}{R_b}} = 2 \times \frac{\frac{1}{10}}{\frac{1}{2} + \frac{1}{10} + \frac{1}{5}} \text{ mA} = 2 \times \frac{1}{8} \text{ mA} = 0.25 \text{ mA}$$

$$I_3 = I_s \times \frac{\frac{1}{R_b}}{\frac{1}{R_a} + \frac{1}{R_4} + \frac{1}{R_b}} = 2 \times \frac{\frac{1}{5}}{\frac{1}{2} + \frac{1}{10} + \frac{1}{5}} \text{ mA} = 2 \times \frac{2}{8} \text{ mA} = 0.5 \text{ mA}$$

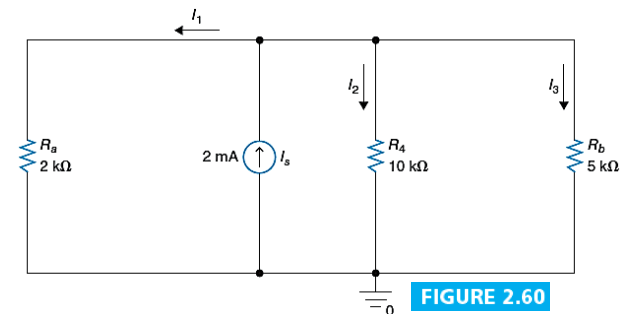


FIGURE 2.60

EXAMPLE 2.17


- In the circuit shown in Fig.2.61, use the current divider rule to find the currents I_1 , I_2 , I_3 , I_4 , I_5 .

$$I_1 = I_s \times \frac{R_2}{R_1 + R_2} = 22 \times \frac{7}{4 + 7} \text{ mA} = 22 \times \frac{7}{11} \text{ mA} = 14 \text{ mA} \quad I_2 = I_s \times \frac{R_1}{R_1 + R_2} = 22 \times \frac{4}{4 + 7} \text{ mA} = 22 \times \frac{4}{11} \text{ mA} = 8 \text{ mA}$$

$$I_3 = I_s \times \frac{\frac{1}{R_3}}{\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}} = 22 \times \frac{\frac{1}{2}}{\frac{1}{2} + \frac{1}{4} + \frac{1}{6}} \text{ mA} = 22 \times \frac{6}{11} \text{ mA} = 12 \text{ mA}$$

$$I_4 = I_s \times \frac{\frac{1}{R_4}}{\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}} = 22 \times \frac{\frac{1}{4}}{\frac{1}{2} + \frac{1}{4} + \frac{1}{6}} \text{ mA} = 22 \times \frac{3}{11} \text{ mA} = 6 \text{ mA}$$

$$I_5 = I_s \times \frac{\frac{1}{R_5}}{\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}} = 22 \times \frac{\frac{1}{6}}{\frac{1}{2} + \frac{1}{4} + \frac{1}{6}} \text{ mA} = 22 \times \frac{2}{11} \text{ mA} = 4 \text{ mA}$$

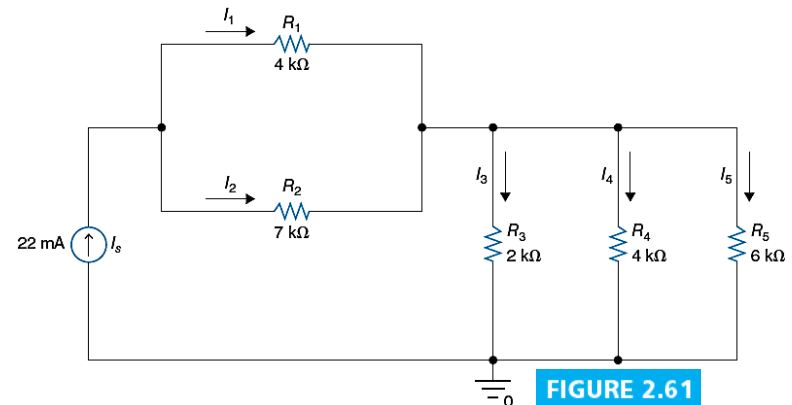


EXAMPLE 2.18

- Find $I_1, I_2, I_3, I_4, I_5, I_6, I_7, I_8, I_9$ in the circuit shown in Figure 2.63.
- $R_a = R_2 + (R_3 \parallel R_4) = 3 \text{ k}\Omega$
- $R_b = (R_5 \parallel R_6) + (R_7 \parallel R_8) = 3 \text{ k}\Omega + 2 \text{ k}\Omega = 5 \text{ k}\Omega$
- Application of current divider rule on R_1, R_a, R_b , we obtain

$$I_1 = I_s \times \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_a} + \frac{1}{R_b}} = 10 \times \frac{\frac{1}{7.5}}{\frac{1}{7.5} + \frac{1}{3} + \frac{1}{5}} \text{ mA} = 10 \times \frac{2}{10} \text{ mA} = 2 \text{ mA}$$

$$I_2 = I_s \times \frac{\frac{1}{R_a}}{\frac{1}{R_1} + \frac{1}{R_a} + \frac{1}{R_b}} = 10 \times \frac{\frac{1}{3}}{\frac{1}{7.5} + \frac{1}{3} + \frac{1}{5}} \text{ mA} = 10 \times \frac{5}{10} \text{ mA} = 5 \text{ mA}$$

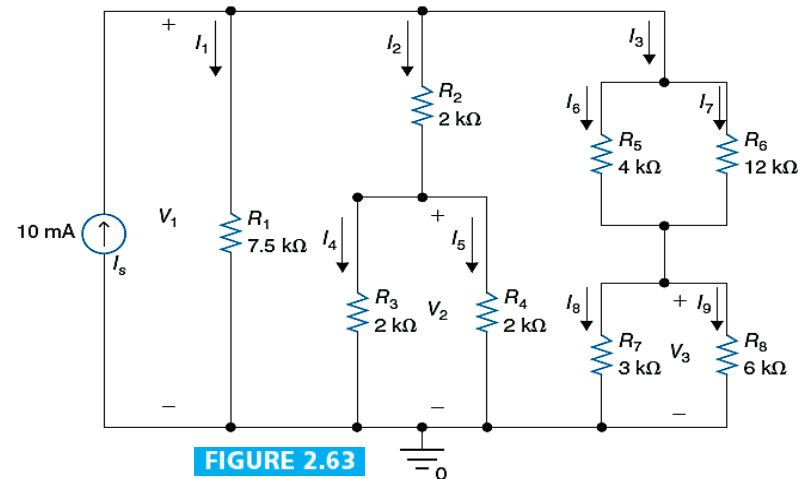


EXAMPLE 2.18 (Continued)

$$I_3 = I_s \times \frac{\frac{1}{R_b}}{\frac{1}{R_1} + \frac{1}{R_a} + \frac{1}{R_b}} = 10 \times \frac{\frac{1}{5}}{\frac{1}{7.5} + \frac{1}{3} + \frac{1}{5}} \text{ mA} = 10 \times \frac{3}{10} \text{ mA} = 3 \text{ mA}$$

$$I_4 = I_2 \times \frac{R_4}{R_3 + R_4} = 2.5 \text{ mA} = I_5$$

$$I_6 = I_3 \times \frac{R_6}{R_5 + R_6} = 2.25 \text{ mA}, I_7 = 0.75 \text{ mA}$$
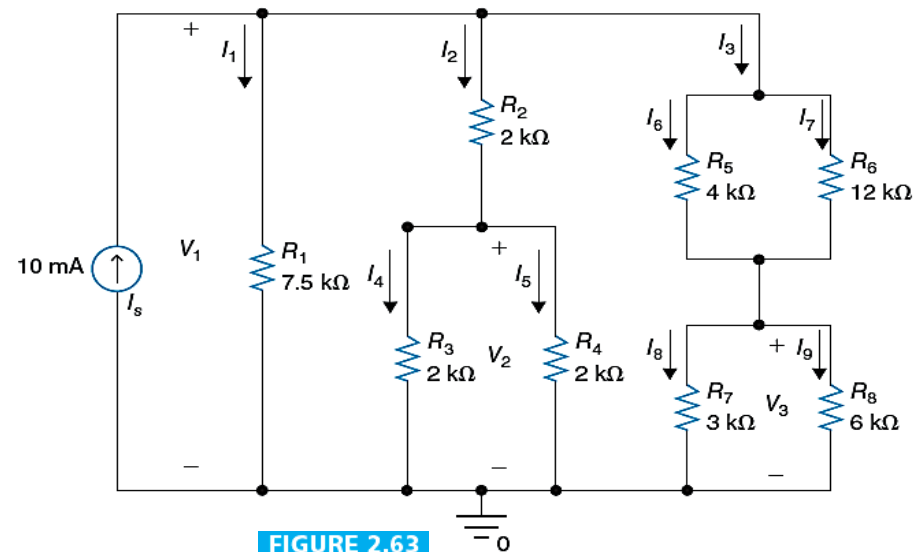
$$I_8 = I_3 \times \frac{R_8}{R_7 + R_8} = 2 \text{ mA}, I_9 = 1 \text{ mA}$$



Summary of key concepts weeks 2-3

- **Resistance** (definition and physical meaning)

$$R = \frac{\ell}{\sigma A} = \frac{\ell \rho}{A}$$

- **Ohm's law**

$$V = RI, \quad I = \frac{V}{R}, \quad R = \frac{V}{I}$$

- **KCL**

The sum of currents entering a node equals the sum of currents leaving the same node.

The sum of currents leaving a node is zero.

The sum of currents entering a node is zero.

Summary (Continued)

- **KVL**

The sum of voltage drops around a loop or mesh is equal to zero.

- **Equivalent resistance of series** connection of n resistors

$$R_{eq} = R_1 + R_2 + \dots + R_n$$

- **Equivalent resistance of parallel** connection of two resistors

$$R_{eq} = R_1 \parallel R_2 = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$

Summary (Continued)

- Equivalent resistance of parallel connection of n resistors

$$R_{eq} = R_1 \parallel R_2 \parallel \dots \parallel R_n = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$

- **Voltage divider** rule (two resistors are connected in series to a voltage source)

$$V_1 = V_s \times \frac{R_1}{R_1 + R_2}, \quad V_2 = V_s \times \frac{R_2}{R_1 + R_2}$$

- **Voltage divider rule** (n resistors are connected in series to a voltage source)

$$V_i = V_s \times \frac{R_i}{R_1 + R_2 + \dots + R_n}$$

Summary (Continued)

- **Current divider** rule (two resistors are connected in parallel to a current source)

$$I_1 = I_s \times \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2}} = I_s \times \frac{R_2}{R_1 + R_2}, \quad I_2 = I_s \times \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}} = I_s \times \frac{R_1}{R_1 + R_2}$$

- **Current divider** rule (n resistors are connected in parallel to a current source)

$$I_i = I_s \times \frac{\frac{1}{R_i}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$

Summary (Continued)

- What will we study in next lecture.