


Tutorial 2 for CAD

Sample Questions and Exercises

2020-21


1 Equivalent Resistance

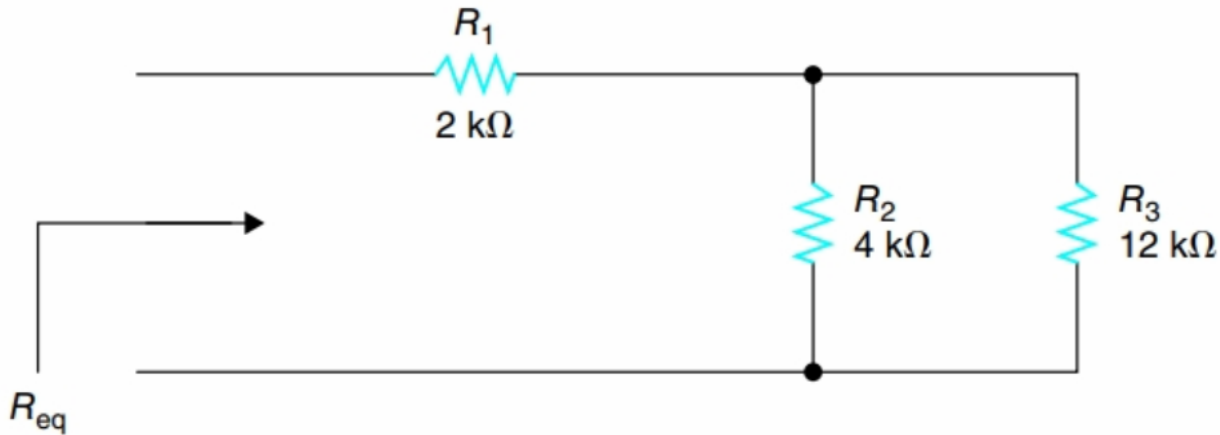- Find the equivalent resistance R_{eq} of the circuit shown below




2 Voltage Divider Rule

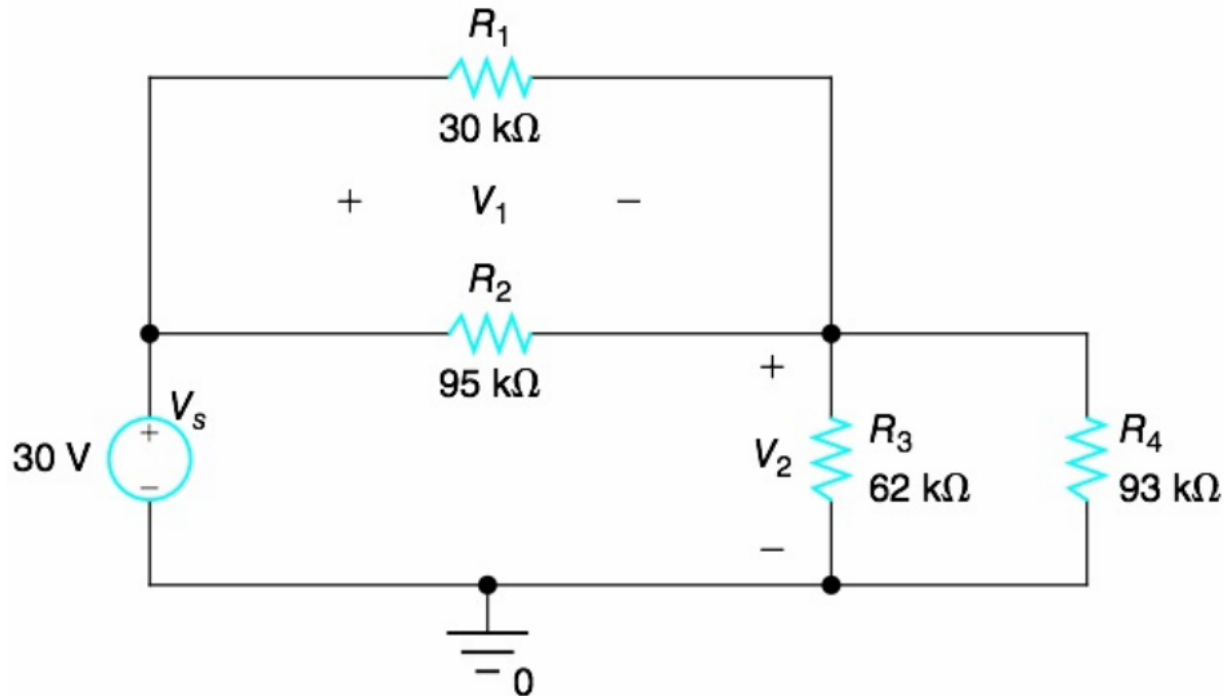- Use the voltage divider rule to find voltage V_1 and V_2 in the circuit shown in the following figure




3 Current Divider Rule

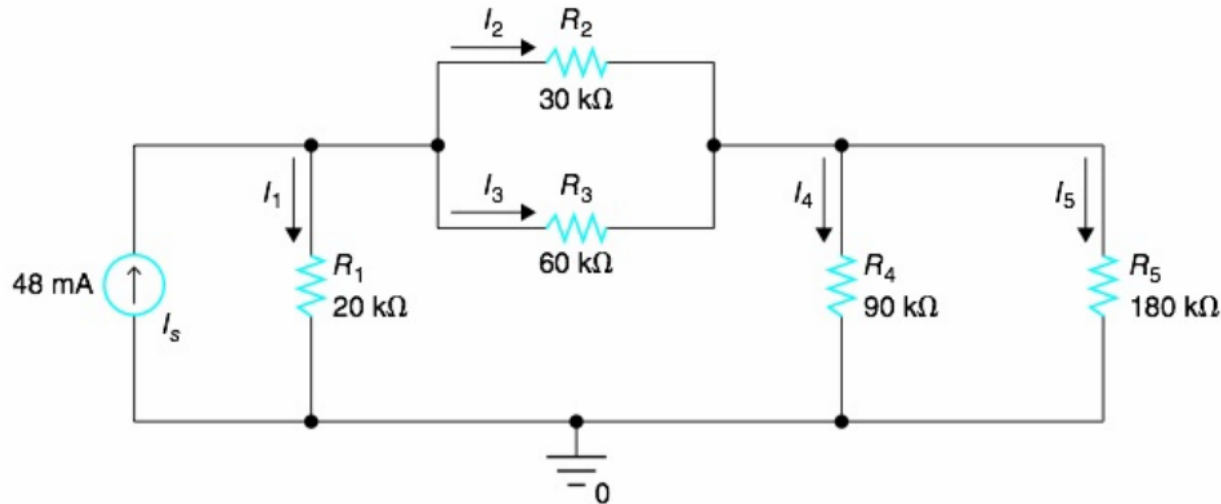- Use the current divider rule to find I_1 , I_2 , I_3 , I_4 , and I_5 in the circuit shown below




4 Node Analysis

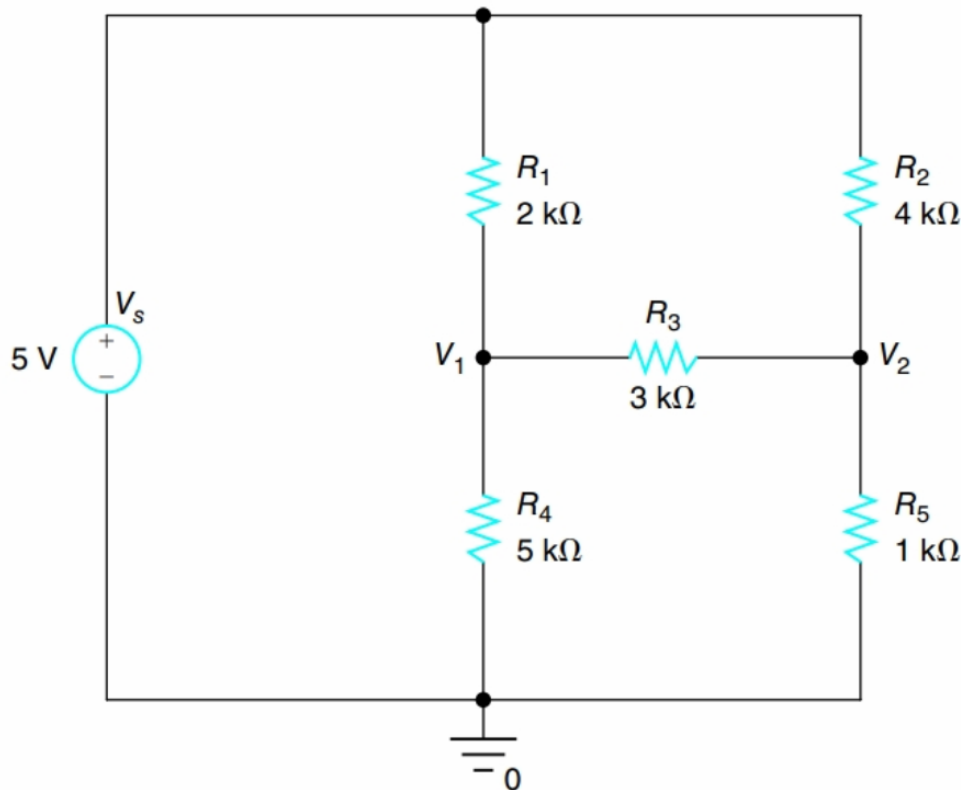- Find the voltage V_1 and V_2 in the circuit shown below




5 Supernode

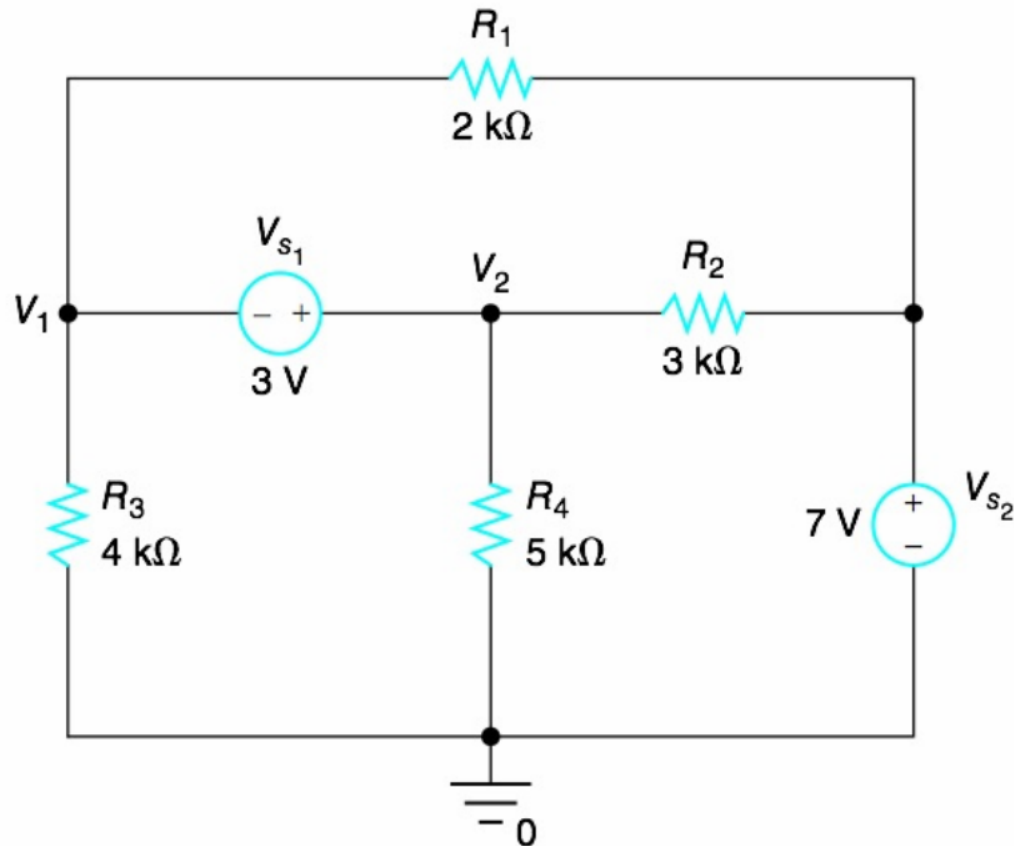- Find the voltage V_1 and V_2 in the circuit shown below




6 Mesh Analysis

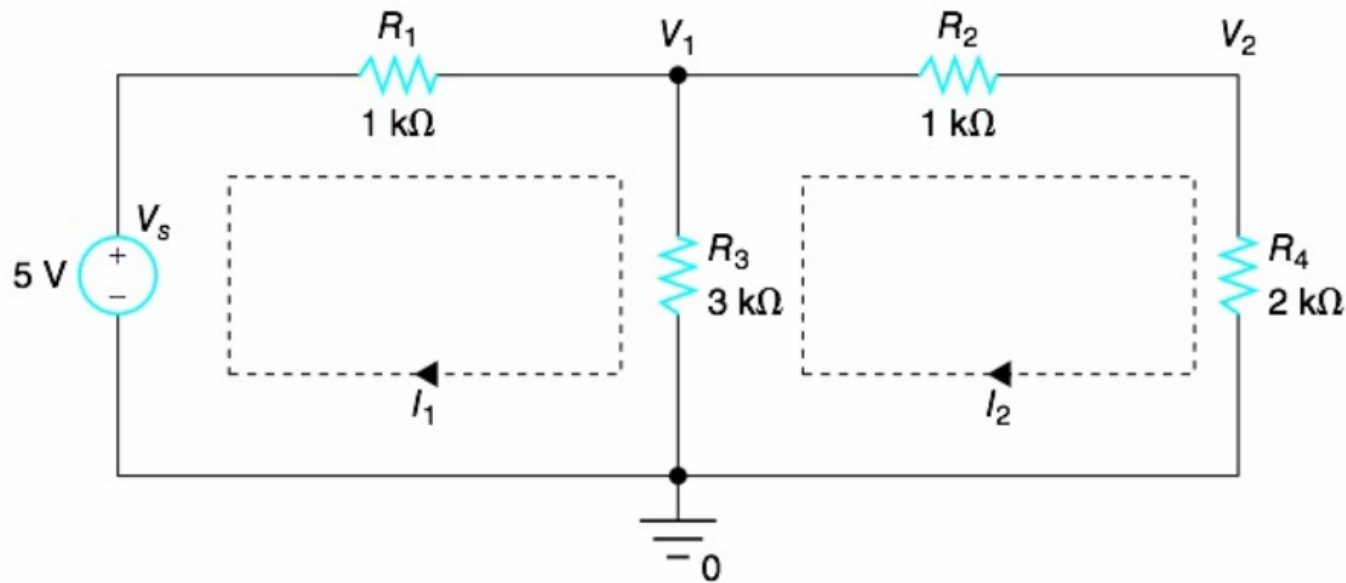- Find mesh currents I_1 and I_2 and node voltage V_1 and V_2 in the circuit shown below



7 Superposition Principle

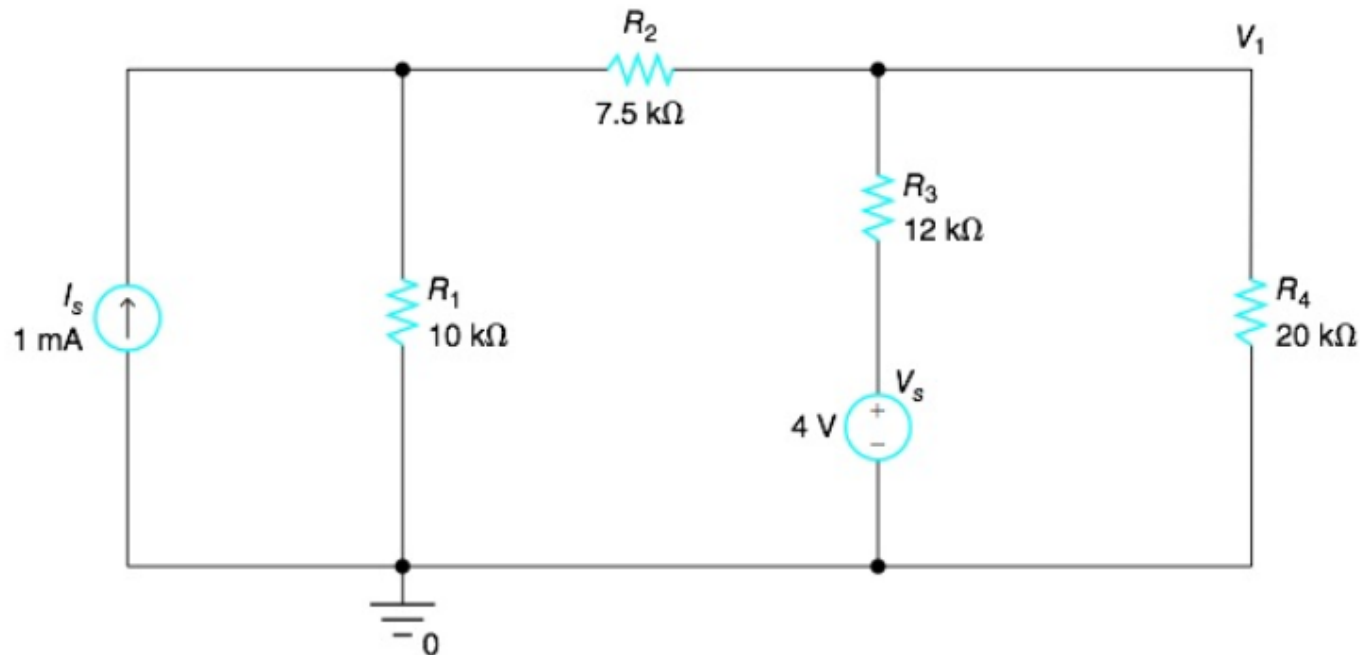- Use the superposition principle to find voltage V_1 in the circuit shown below



8 Source Transformation

- Use source transformation to find voltages V_1 and V_2 in the circuit shown below

