




University  
of Glasgow

# Electronic System Design 3


## Lecture 11.1: Low noise Amplifier Noise Analysis

Dr Duncan Bremner

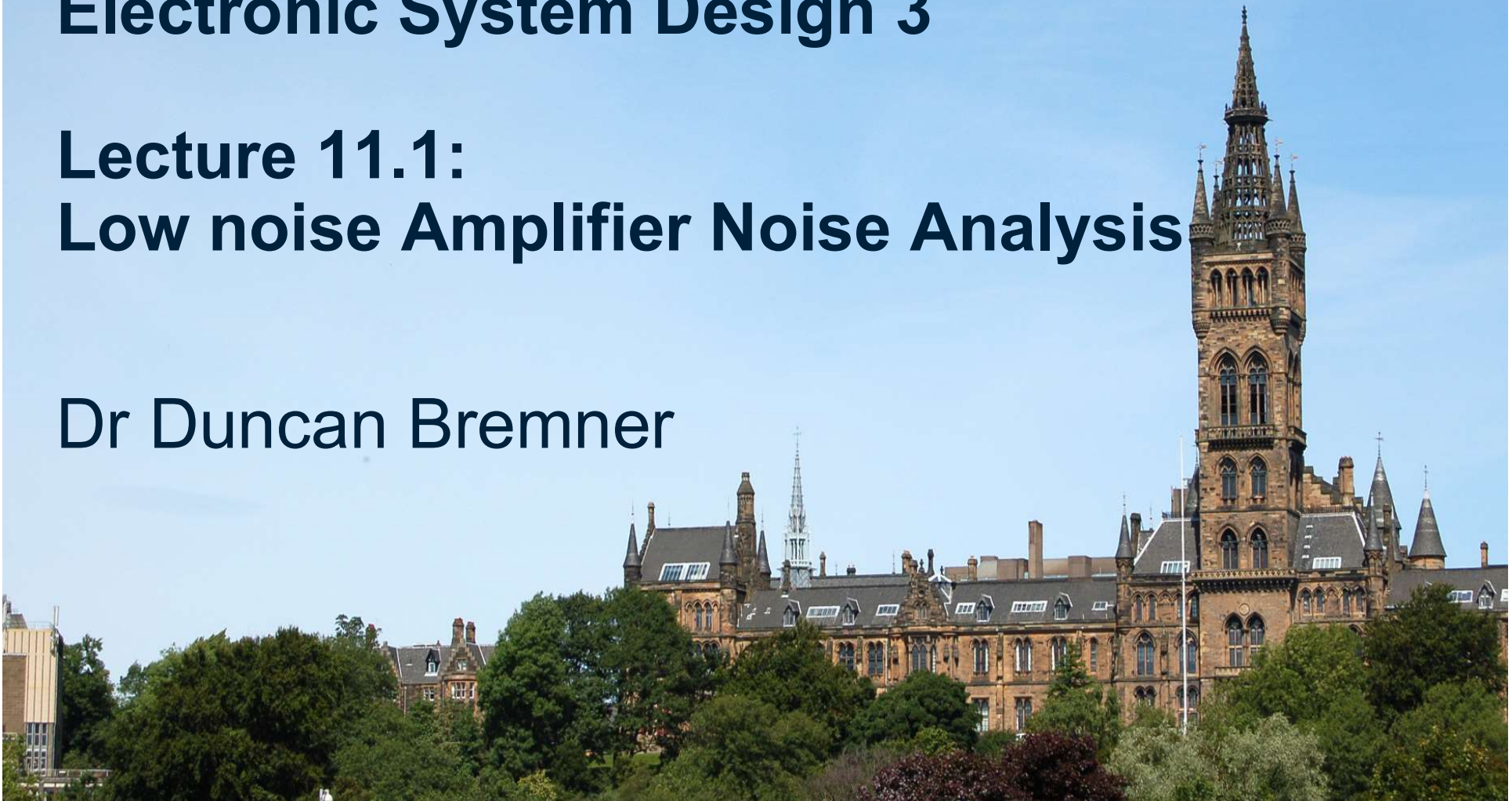

## Example 1

## Noise 3

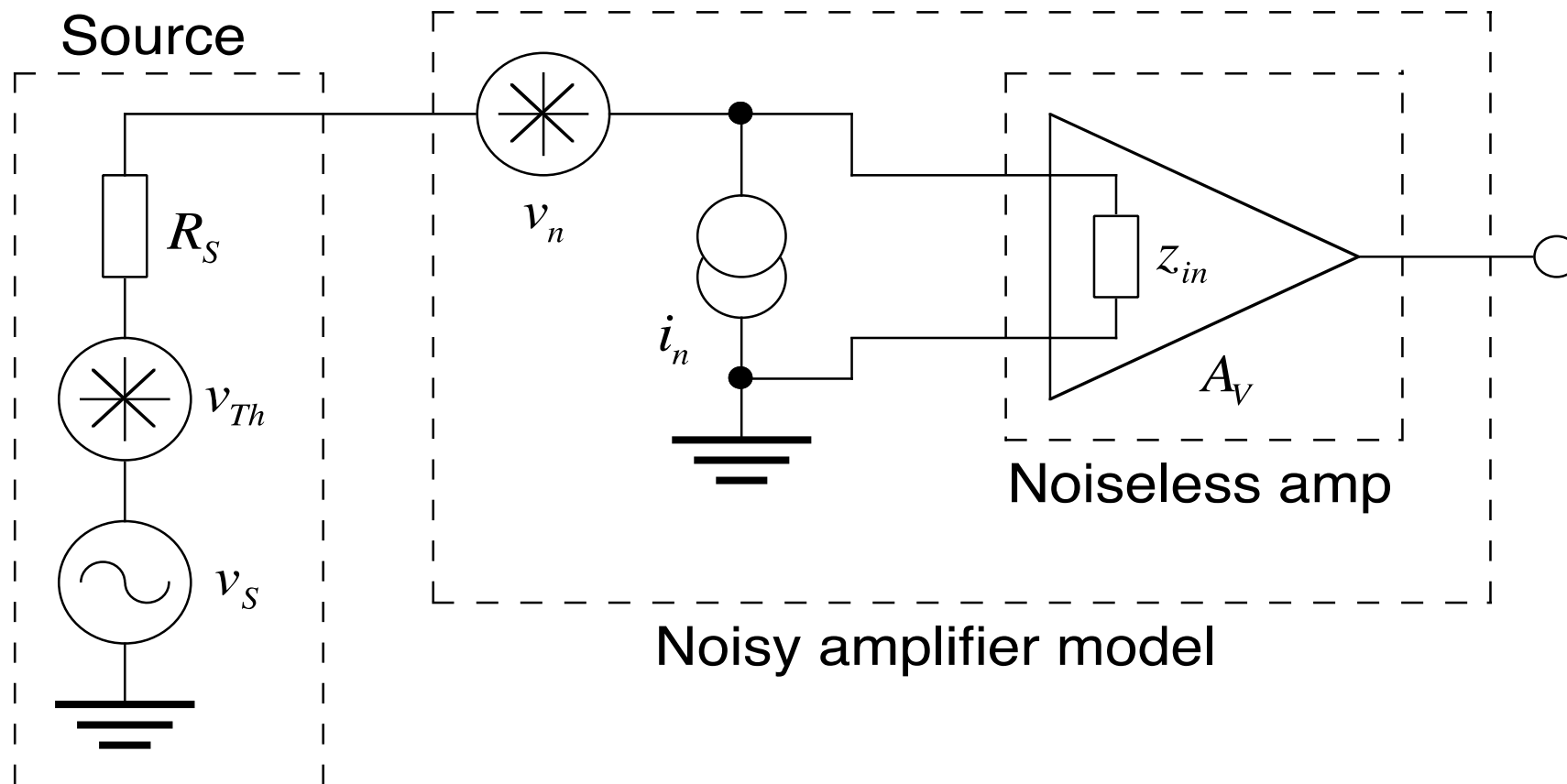

$$R_S = 10k\Omega$$

$$T = 300K$$

$$v_n = 15nV \cdot Hz^{-1/2}$$

$$i_n = 1pA \cdot Hz^{-1/2}$$

$$B = 20kHz$$

What is equivalent input noise level?

## Example 1 (2)

$$R_S = 10k\Omega; \quad T = 300K \quad \therefore v_{Th} = \sqrt{4k_B T R} = 12.9nV \cdot Hz^{-1/2}$$

$$\begin{aligned} v_{ni}^2 &= v_{Th}^2 + v_n^2 + i_n^2 |R_S|^2 \\ &= (12.9nV \cdot Hz^{-1/2})^2 + (15nV \cdot Hz^{-1/2})^2 + (1pA \cdot Hz^{-1/2})^2 \cdot (10k\Omega)^2 \\ \Rightarrow v_{ni} &= \sqrt{0.491fV^2 Hz^{-1}} = 22.2nV \cdot Hz^{-1/2} \end{aligned}$$

Multiply noise spectral density by the  $\sqrt{\text{bandwidth}}$  to get total noise

$$V_{total} = 22nV \cdot Hz^{-1/2} \cdot \sqrt{20kHz} = 3.13\mu V$$



How much worse is this than thermal noise?

Noise figure (NF) is the ratio of equivalent input power density to the thermal noise of the source. Usually expressed in dB


**A perfect amplifier adds no noise** to the signal:  $NF = 1 = 0\text{dB}$ :  
NF is always positive in dB (i.e. total noise > thermal noise)

$$\text{Noise Figure} = 20 \cdot \log_{10} \frac{v_{ni}}{v_{Th}}$$

$$\text{Noise Figure} = 20 \cdot \log_{10} \frac{22.2\text{nV} \cdot \text{Hz}^{-1/2}}{12.9\text{nV} \cdot \text{Hz}^{-1/2}} = 4.7\text{dB}$$



## Example 2: Low noise design

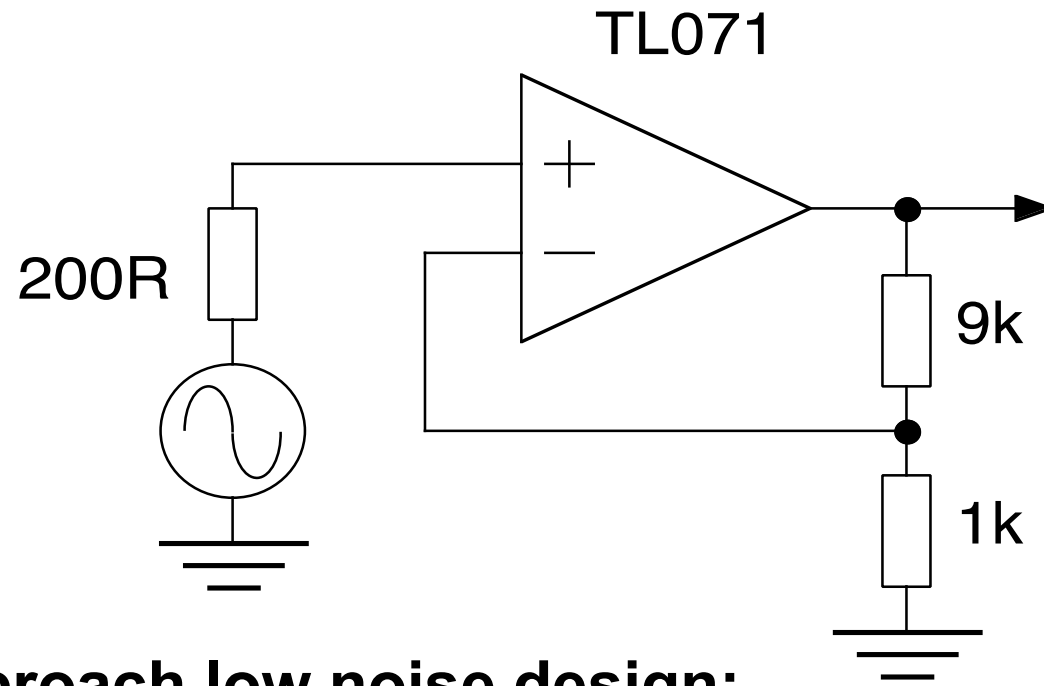

### How to approach low noise design:

1. Analyse circuit
2. Identify main sources of noise
3. Design a better amplifier




## Circuit analysis

$$\text{TL071: } v_n = 18nV \cdot \text{Hz}^{-1/2}; \quad i_n = 10fA \cdot \text{Hz}^{-1/2}$$

Input noise current density flows into both inputs

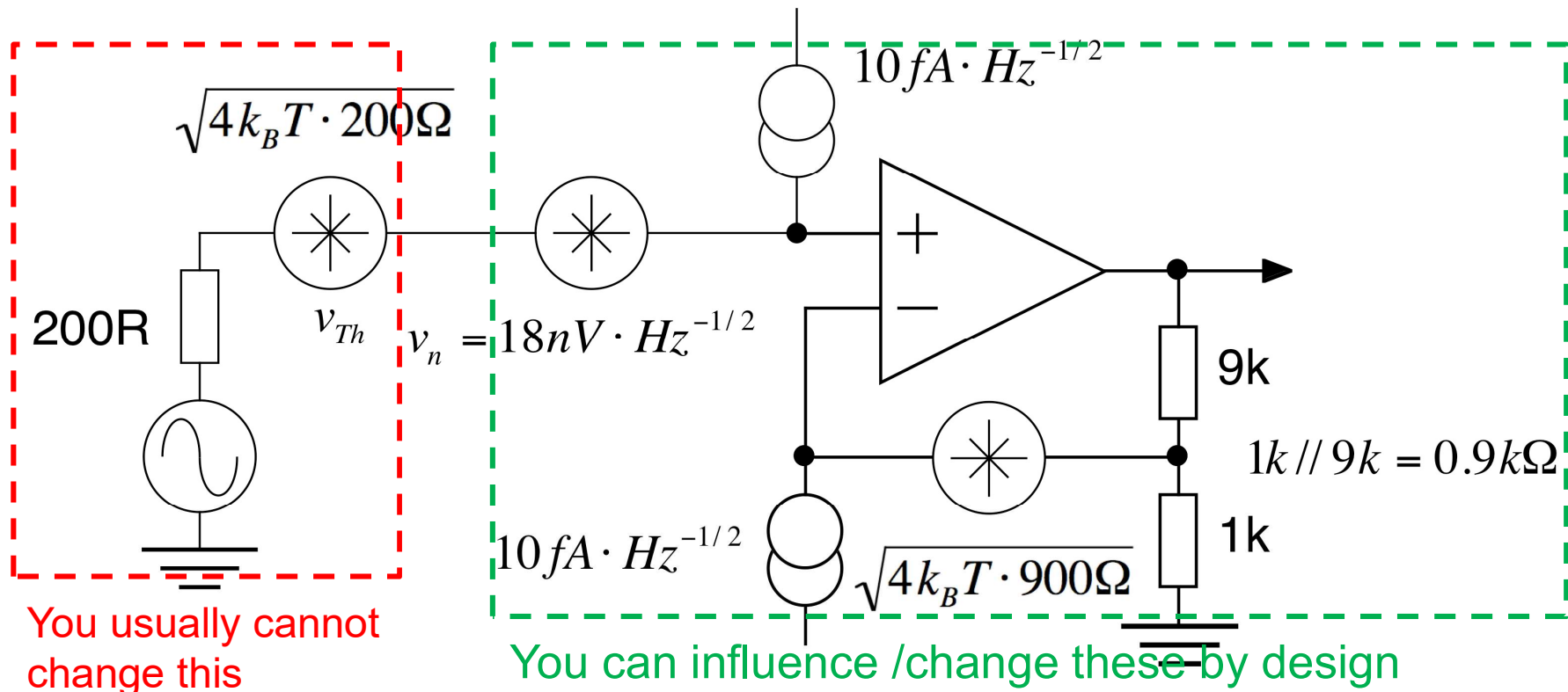
Derive noisy amplifier model equivalent circuit:






## Design 2 (3)

Analysing feedback network:

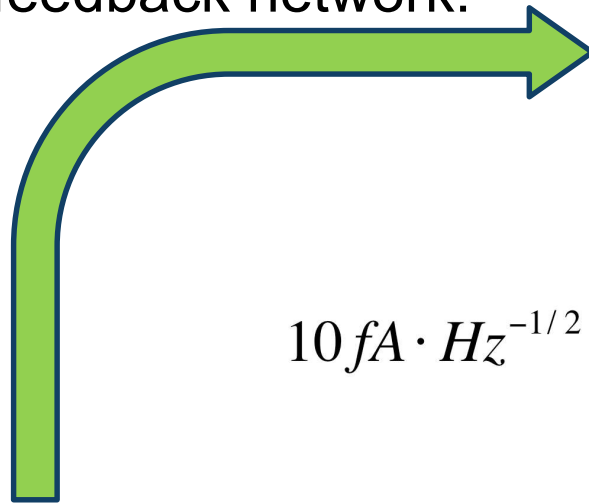

$$10 \text{ fA} \cdot \text{Hz}^{-1/2}$$

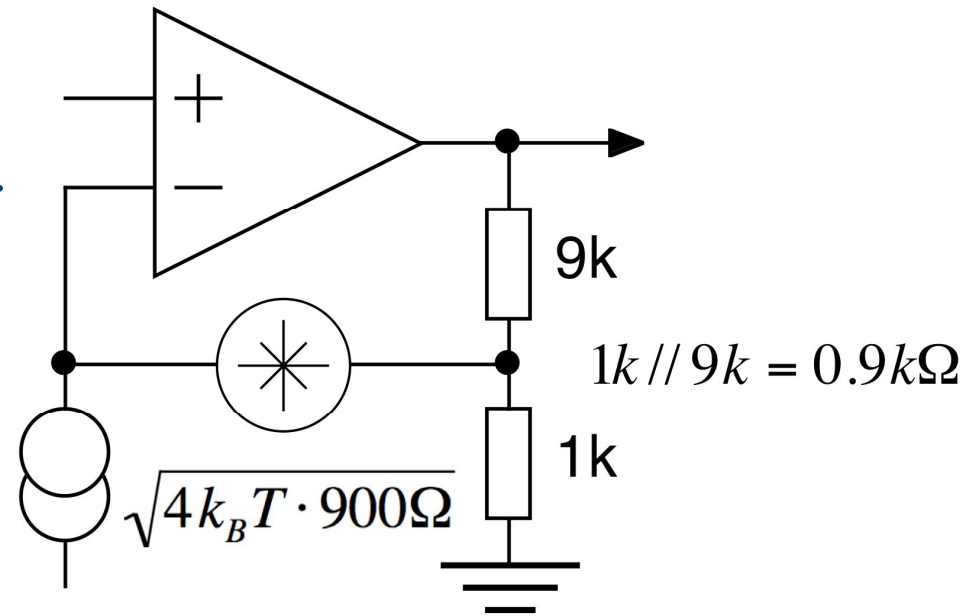

Noise voltage at inverting input

= Johnson noise in resistors + noise current x impedance

$$v_n(-) = \sqrt{(i_n \cdot 0.9 \text{ k}\Omega)^2 + \left(\sqrt{4k_B T \cdot 0.9 \text{ k}\Omega}\right)^2}$$

$$= \sqrt{\left(9 \cdot 10^{-3} \text{ nV} \cdot \text{Hz}^{-1/2}\right)^2 + \left(3.86 \text{ nV} \cdot \text{Hz}^{-1/2}\right)^2}$$




Noise current is negligible:

$$v_n(-) = 3.86 \text{ nV} \cdot \text{Hz}^{-1/2}$$




Feedback makes 2 inputs equal:

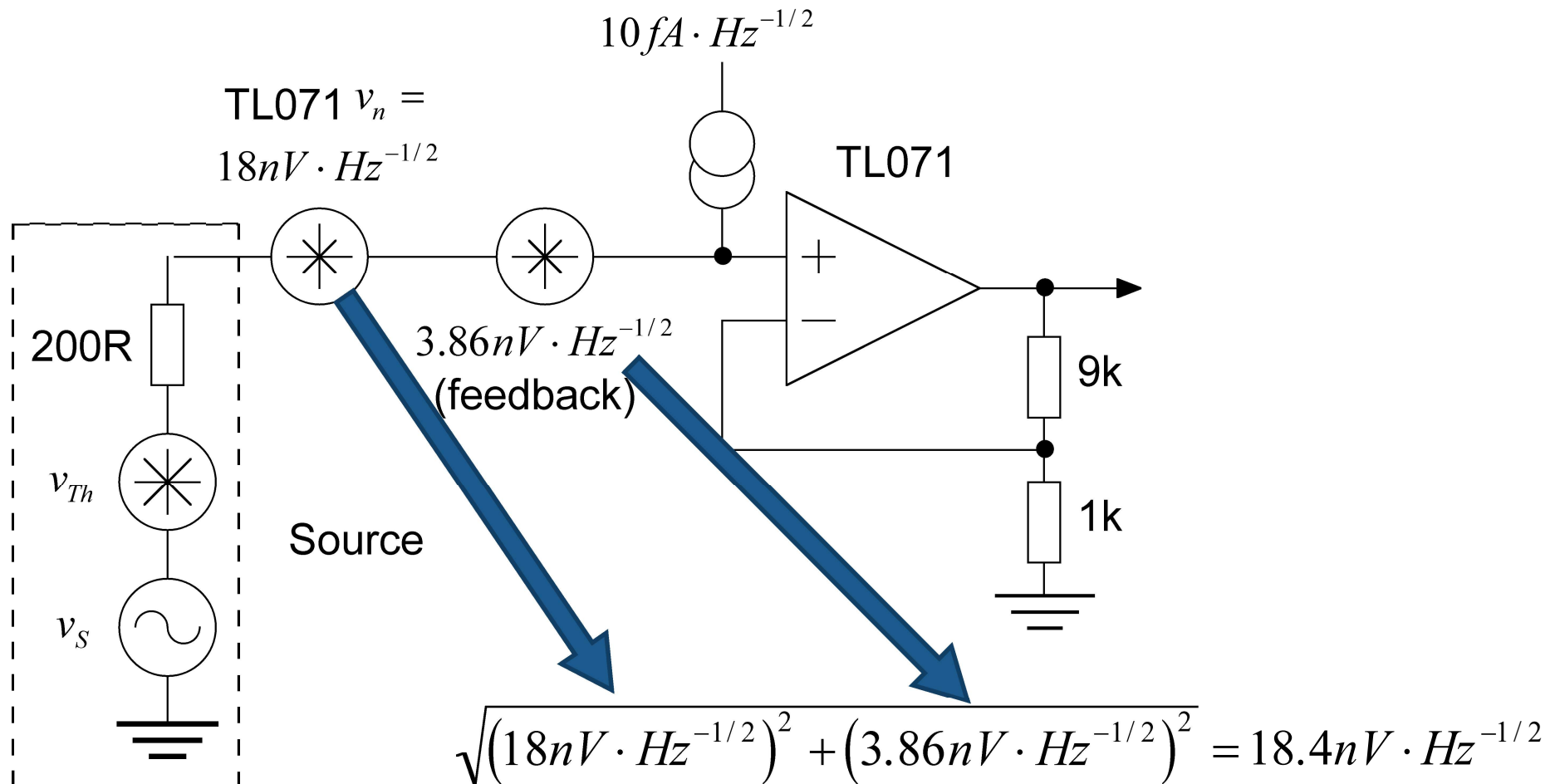Feedback network noise adds to input voltage noise:





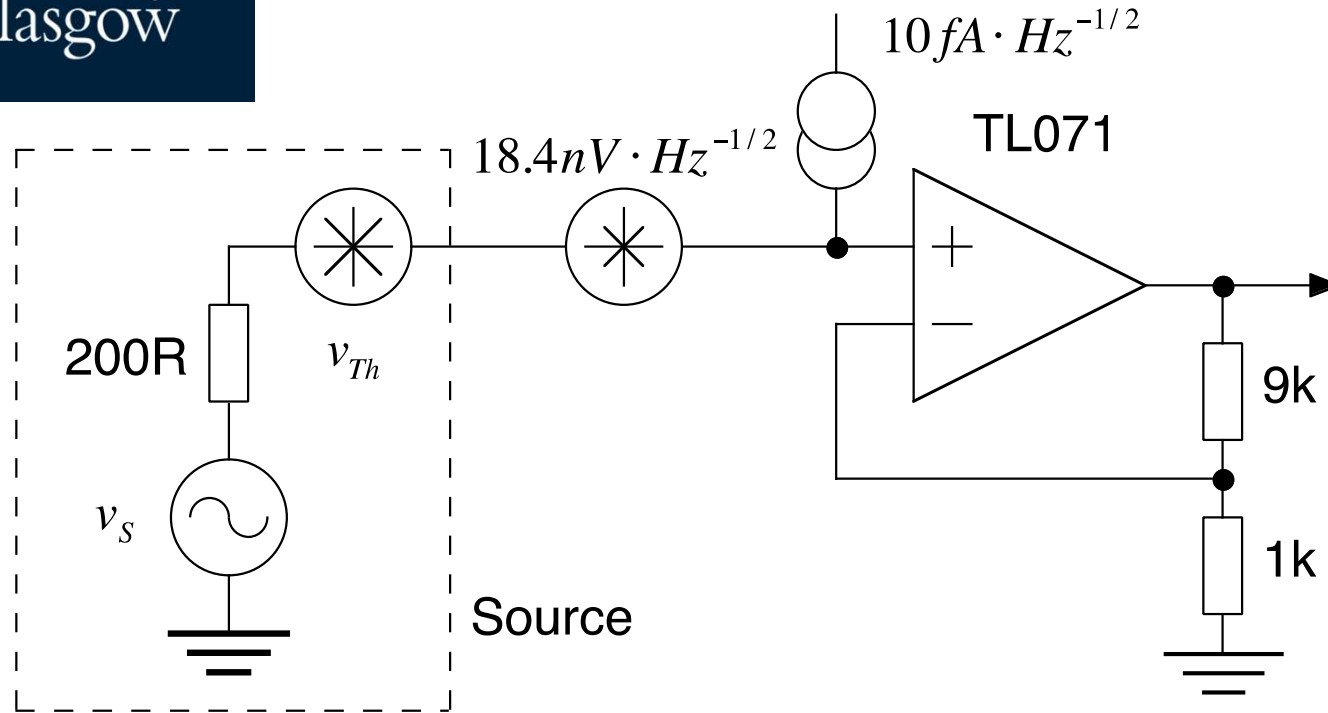

Now in the same form as the standard model

$$v_n = 18.4 nV \cdot Hz^{-1/2} \quad i_n = 10 fA \cdot Hz^{-1/2} \quad v_{Th} = \sqrt{4k_B T R} = 1.82 nV \cdot Hz^{-1/2}$$

$$v_{ni} = \sqrt{v_{Th}^2 + v_n^2 + i_n^2 R_S} = \sqrt{3.3 \cdot 10^{-18} + 338 \cdot 10^{-16} + 4 \cdot 10^{-24}} = 18.5 nV \cdot Hz^{-1/2}$$



University  
of Glasgow

Thank you  
谢谢

INSPIRING  
PEOPLE