

$$V_{RN} = 200 \angle 0^\circ \text{ V}$$

$$V_{YN} = 200 \angle -120^\circ \text{ V}$$

$$V_{BN} = 200 \angle 120^\circ \text{ V}$$

The key thing is
the 120° phase
shifts!

$$\begin{aligned} V_{RY} &= 200 - 200 \angle -120^\circ \\ &= 200 (1 + 0.5 + j0.866) = 200 (1.5 + j0.866) \\ &= \sqrt{3} 200 \angle 30^\circ = 346.4 \angle 30^\circ \text{ V} \end{aligned}$$


Note: Always give your final answer in phasor form. Always complete the calculation!

We do not need to do all the maths for V_{BR} and V_{YB} , just remember that the 120° phase shifts.


$$V_{BR} = 346.4 \angle 120^\circ \text{ V}$$

$$V_{YB} = 346.4 \angle -90^\circ \text{ V}$$

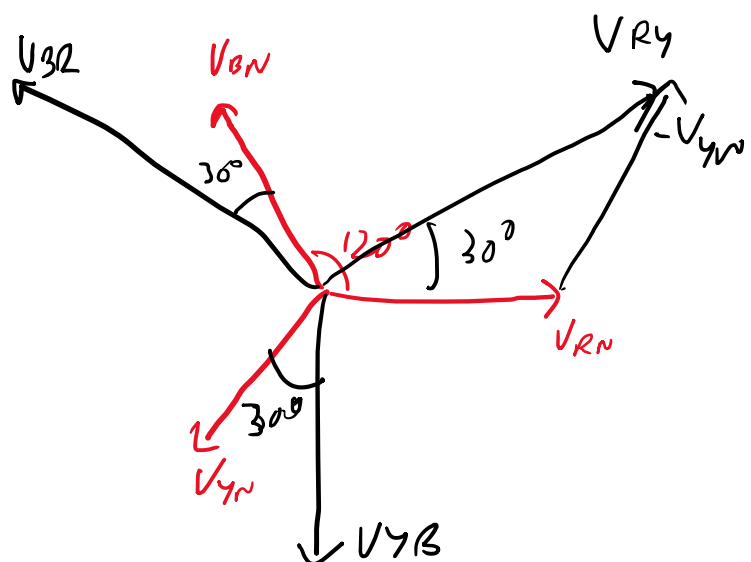It is always a good idea to draw a phasor diagram.



2

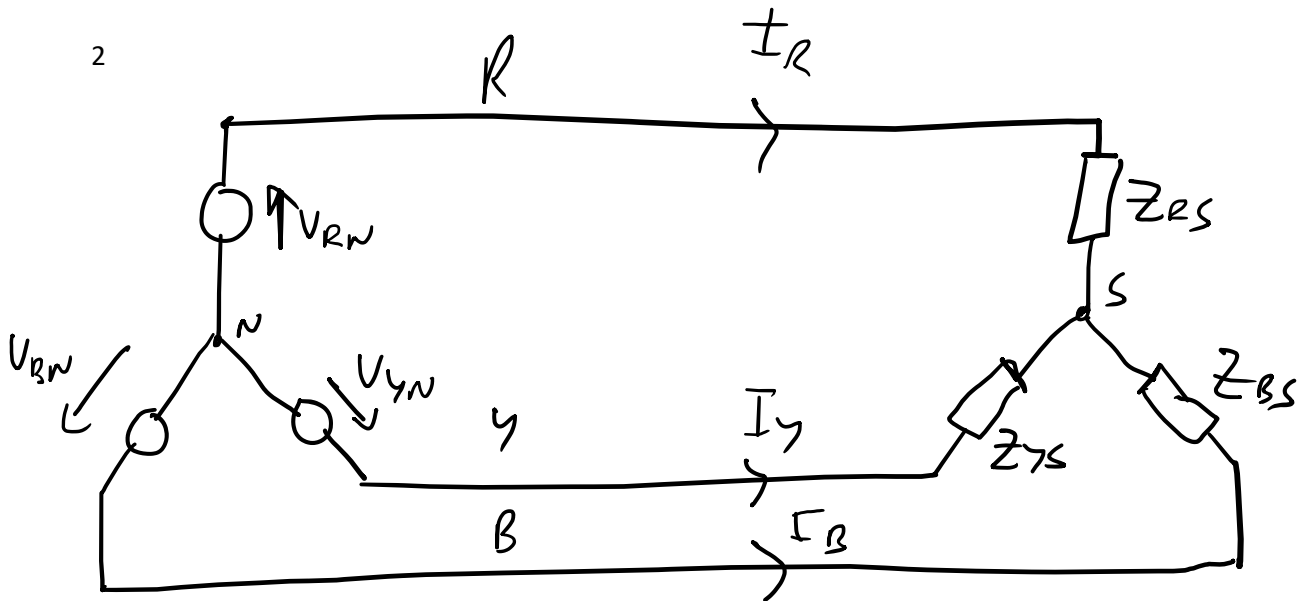

$$V_{ph} = 240V \quad \therefore V_{RN} = 240 \angle 0^\circ V$$

Since it is balanced V_{RN} must be dropped across Z_{RS} .

$$I_R = \frac{V_{RN}}{Z_{RS}} = \frac{240}{12} = 20 \angle 0^\circ A$$

Since there must be a 120° phase shift between R, Y and B:

$$I_Y = 20 \angle -120^\circ A \quad I_B = 20 \angle 120^\circ A$$

We can now find the power dissipated in each resistor:

$$P_R = I^2 R = 20^2 \times 12 = 4.8 \text{ kW}$$

So the total power is:

$$P_T = 3 \times P_R = \underline{14.4 \text{ kW}}$$

3. This is similar to Q2 except that the loads now have an inductive element

$$\begin{aligned}V_{ph} &= 10 \text{ kV} \quad \text{so} \quad V_{RN} = 10000 \angle 0^\circ \text{ V} \\V_{YN} &= 10000 \angle -120^\circ \text{ V} \\V_{BN} &= 10000 \angle 120^\circ \text{ V}\end{aligned}$$

$$Z_{RS} = 10 + j20 \Omega$$

$$\begin{aligned}\text{So: } I_R &= \frac{V_{RN}}{Z_{RS}} = \frac{10000 \angle 0^\circ}{10 + j20} = \frac{10000 \angle 0^\circ}{22.36 \angle 63.43^\circ} \\&= 447.3 \angle -63.43^\circ \text{ A}\end{aligned}$$


$$\begin{aligned}\therefore I_Y &= 447.3 \angle -63.43 - 120^\circ = 447.3 \angle -183.43^\circ \\&= 447.3 \angle 176.57^\circ \text{ A}\end{aligned}$$

$$I_B = 447.3 \angle 56.57^\circ \text{ A}$$

We can calculate the power per phase by considering the magnitude of the current and the resistance (real part of impedance).

$$P_r = 447.3^2 \times 10 = 2 \text{ MW}$$
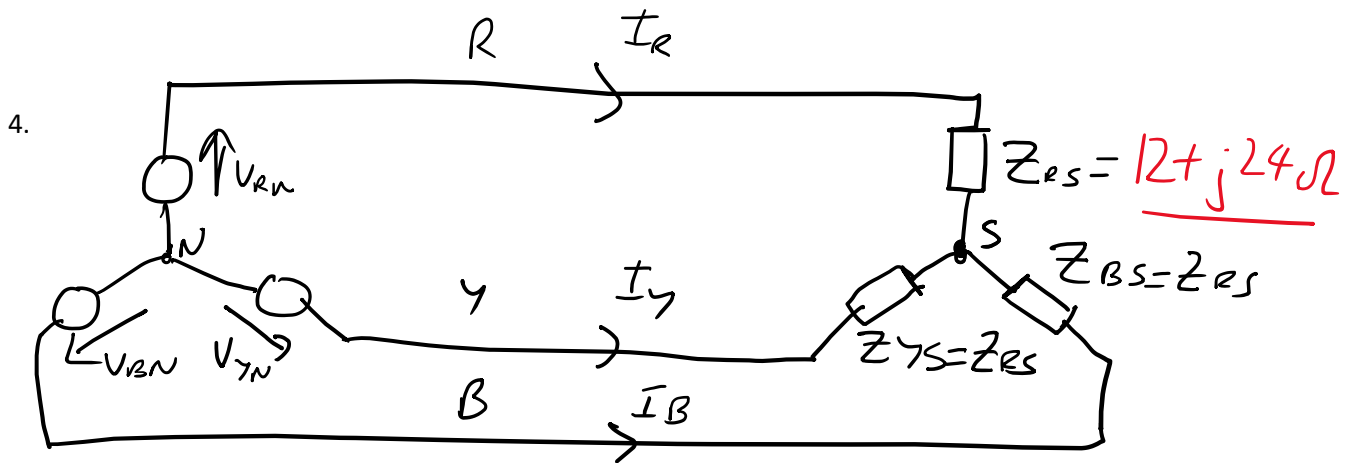
$$P_T = 3 \times P_r = \underline{6 \text{ MW}}$$



First calculate the reactance:

$$\begin{aligned}
 X_L &= 2\pi fL \\
 &= 2\pi \times 60 \times 63.7 \times 10^{-3} \\
 &= 24 \Omega
 \end{aligned}$$

$$\text{So } Z_{RS} = 12 + j24 \Omega = 26.8 \angle 63.43^\circ \Omega$$

Line voltage $= \sqrt{3}$ Phase Voltage with 30° phase shift.

$$\text{So! } V_{RY} = \sqrt{3} \times 10000 \angle 30^\circ = 17320 \angle 30^\circ \text{ V}$$

$$V_{BR} = 17320 \angle (30 + 120)^\circ = 17320 \angle 150^\circ \text{ V}$$

$$V_{YB} = 17320 \angle (30 - 120)^\circ = 17320 \angle -90^\circ \text{ V}$$

To find I_R :

$$I_R = \frac{V_{RN}}{Z_{RS}} = \frac{10000 \angle 0^\circ}{26.8 \angle 63.43^\circ} = 373 \angle -63.43^\circ \text{ A}$$

$$I_B = 373 \angle -63.43 + 120^\circ = 373 \angle 56.57^\circ \text{ A}$$

$$I_Y = 373 \angle -63.43 - 120^\circ = 373 \angle 176.57^\circ \text{ A}$$


To find total power:

$$P_R = 373^2 \times 12 = 1.67 \text{ MW}$$

$$\text{So: } P_T = 3 \times P_R = \underline{5 \text{ MW}}$$

5. Solving Y load balanced 3-phase problems with a single phase equivalent circuit is a good idea.

Draw a diagram:

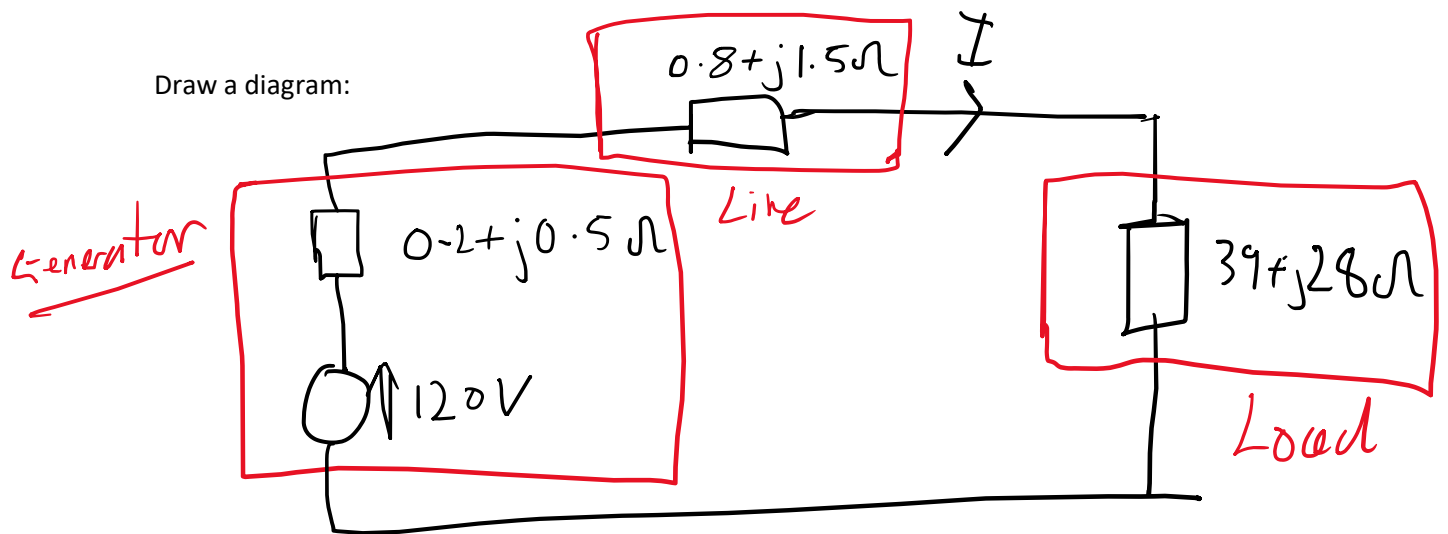

$$I = \frac{120 \angle 0^\circ}{0.2 + j0.5 + 0.8 + j1.5 + 39 + j28} = \frac{120 \angle 0^\circ}{40 + j30}$$
$$= \frac{120 \angle 0^\circ}{50 \angle 36.9^\circ} = 2.4 \angle -36.9^\circ \text{ A}$$

So we can now work out the line currents:

$$I_R = 2.4 \angle -36.9^\circ \text{ A}$$

$$I_Y = 2.4 \angle -156.9^\circ \text{ A}$$

$$I_B = 2.4 \angle 83.1^\circ \text{ A}$$

We can find Voltage across the loads:

$$\begin{aligned} V_{RL} &= I_R \times Z_{RS} = 2.4 \angle -36.9^\circ \times (39 + j28) \\ &= 2.4 \angle -36.9^\circ \times 48 \angle 35.7^\circ \\ &= 115.2 \angle -1.2^\circ \text{ V} \end{aligned}$$

$$V_{YL} = 115.2 \angle -121.2^\circ \text{ V}$$

$$V_{BL} = 115.2 \angle 118.8^\circ \text{ V}$$

Line voltages = $\sqrt{3}$ phase voltage with 30 degree phase shift.

$$V_{RY(Load)} = \sqrt{3} \times 115.2 \angle -1.2 + 30^\circ = 200 \angle 28.8^\circ \text{ V}$$

$$V_{BR(Load)} = 200 \angle 148.8^\circ \text{ V}$$

$$V_{YB(Load)} = 200 \angle -91.2^\circ \text{ V}$$

6. This question relates to a load which is a 3-phase motor. The first thing you should do is calculate the power in Watts.

$$100 \text{ HP} = 100 \times 746 = 74600 \text{ W} \\ = 74.6 \text{ kW}$$

You should note that the motor (load) is in a delta configuration.

You can write down for total power that:

$$P_T = \sqrt{3} I_{\text{Line}} V_{\text{Line}} \quad \therefore I_{\text{Line}} = \frac{74600}{460 \times \sqrt{3}} = 93.63 \text{ A}$$

Note this is the magnitude of the current. You cannot find the phase from the information given.



To find the phase current we need to realise that in a delta configuration the line and phase currents are different:

$$I_{\text{ph}} = \frac{I_{\text{Line}}}{\sqrt{3}} = \frac{93.63}{\sqrt{3}} = \underline{54 \text{ A}}$$

Alternatively, you can work this out from a single phase:

$$P = 3 I V, \quad \therefore I = \frac{74600}{3 \times 460} = \underline{\underline{54 \text{ A}}}$$

7.

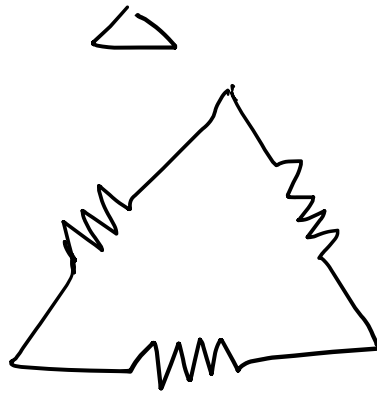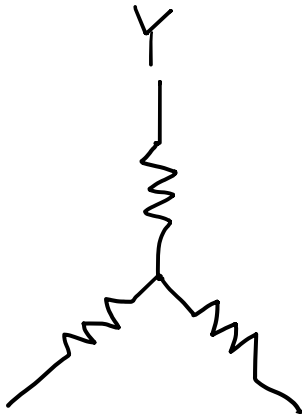

Each resistor must dissipate 5 kW. In a delta configuration each resistor sees to full line voltage so:

$$R = \frac{V_L^2}{P} = \frac{480^2}{5000} = 46.08 \Omega$$

In a Y connection each resistor sees the phase voltage:

$$R = \frac{V_{PH}^2}{P} = \frac{\left(\frac{480}{\sqrt{3}}\right)^2}{5000} = \frac{277^2}{5000} = 15.36 \Omega$$