



## Bias Current Problem

1. What is the required Value of  $R_x$  to cancel the effect of  $I_b$  at the output?
2. If  $I_b = 120nA$  and  $R_x = 200k$ , what is the Voltage error present at the output?