

# UESTC 3003: Electronic System Design

## *Static Errors*

### Lecture 2.1: Revision of Op Amps

Dr Duncan Bremner

**WORLD  
CHANGING  
GLASGOW**



# System Engineering : Signal Conditioning



- In **Electronic System Design** we will consider how to provide the best possible input signals to the system. This means signals that are:-
  - **Accurate:** providing the most accurate signal to the system
  - **Clean:** providing the system with the cleanest, lowest noise signal
  - **Immune:** (from disturbance): signals remain accurate and clean when there is interference
- Our course will explore how to deal with low level signals and condition them for the system to use (probably in a digital process)


"Pray, Mr. Babbage, if you put into the machine wrong figures, will the right answers come out?" ... I am not able rightly to apprehend the kind of confusion of ideas that could provoke such a question.

— [Charles Babbage](#), *Passages from the Life of a Philosopher*

Source Wikipedia
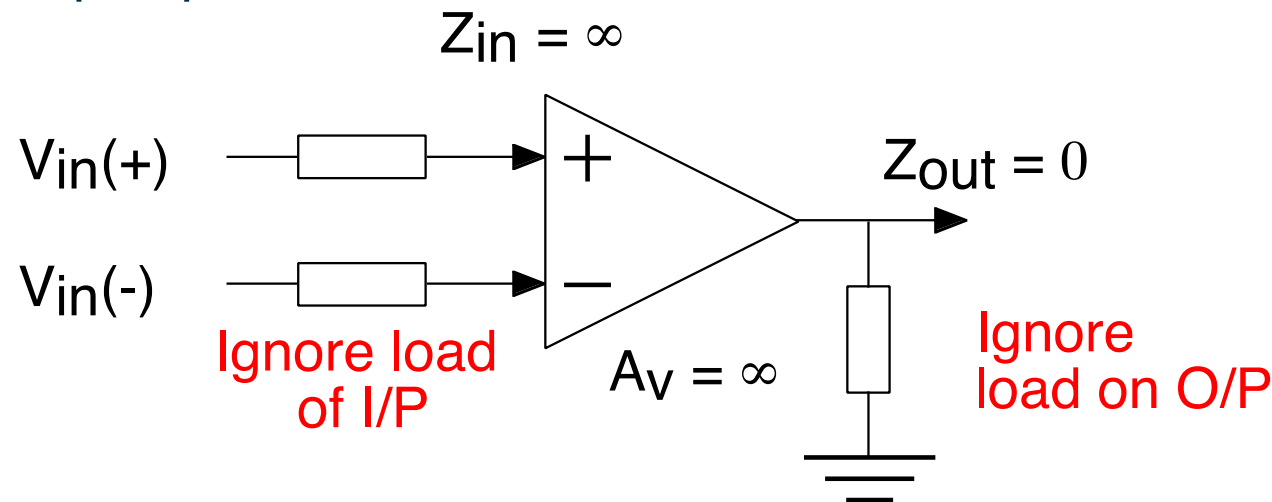
# Opamps Revision


- Analogue design simplest using opamps
- Start with perfect opamp



Virtual Earth


$$V_{OUT} = \infty (V_{IN}(+) - V_{IN}(-))$$

# Perfect opamp calculations (Revision)

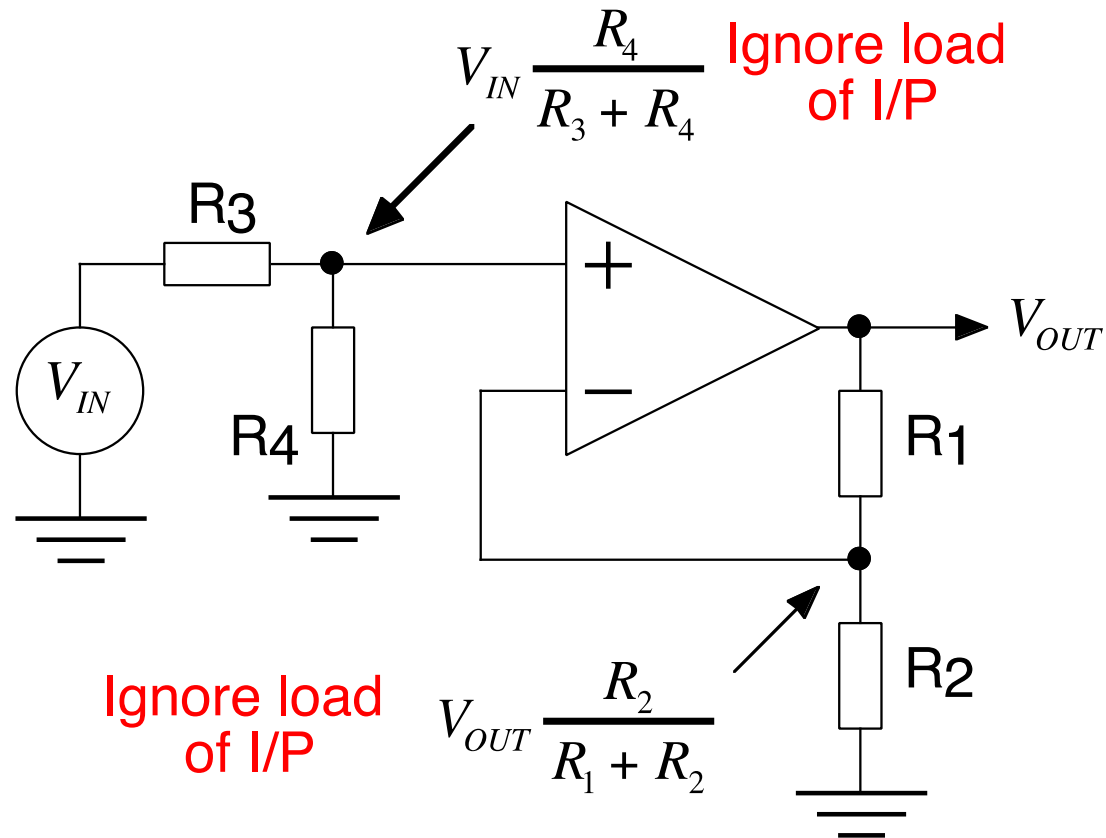



## Negative Feedback

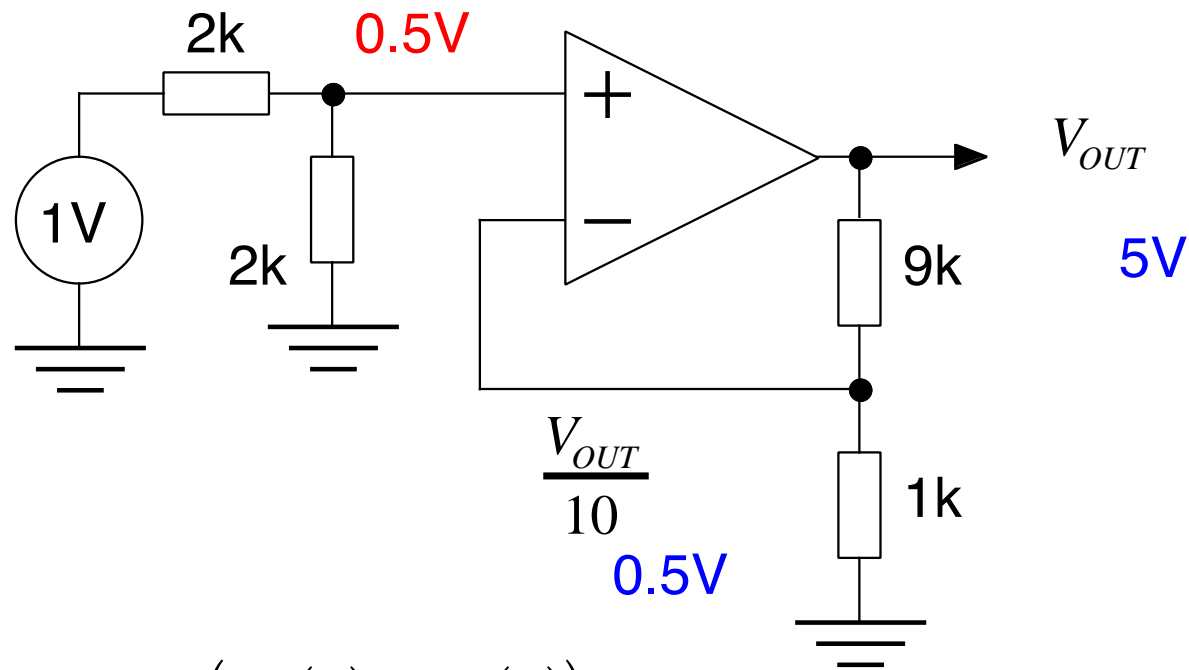


$$V_{OUT} = \infty (V_{IN}(+) - V_{IN}(-)) = \infty \cdot 0$$

# Negative Feedback

- Calculate voltage at (+), (–) inputs as a function of
  - Input voltage
  - Output voltage
- Output does **whatever it takes** to make input voltages (+) & (–) equal
- Inputs do not **directly** change anything

## Example 2: The Integrator

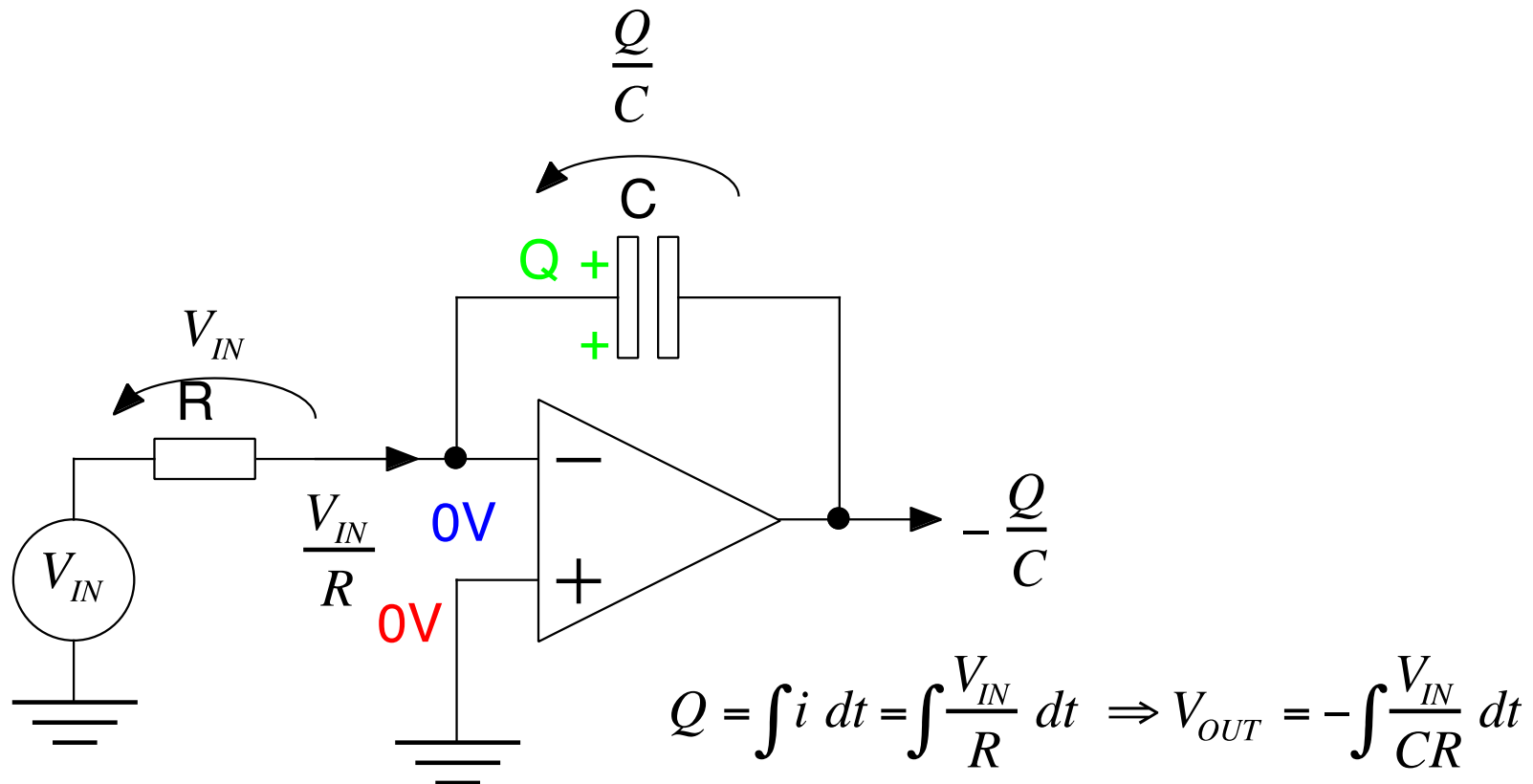

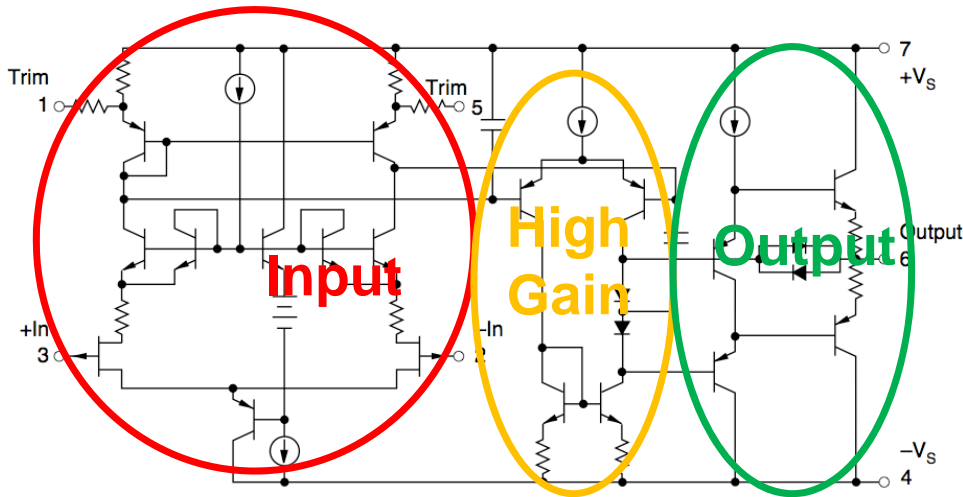
## Opamps are not perfect


- Input offset voltage
- Input currents (“Bias” and “Offset”)
- Speed
  - Gain-Bandwidth product
  - Slew Rate
- Noise
- Other
  - CMRR,  $R_{OUT}$ , PSRR, Gain, Power.....



⇒ Compare (standardized)  
datasheet parametrics  
... ( $V_{os}$ ,  $I_b$ ,  $I_{os}$ )



## Opamps are complicated

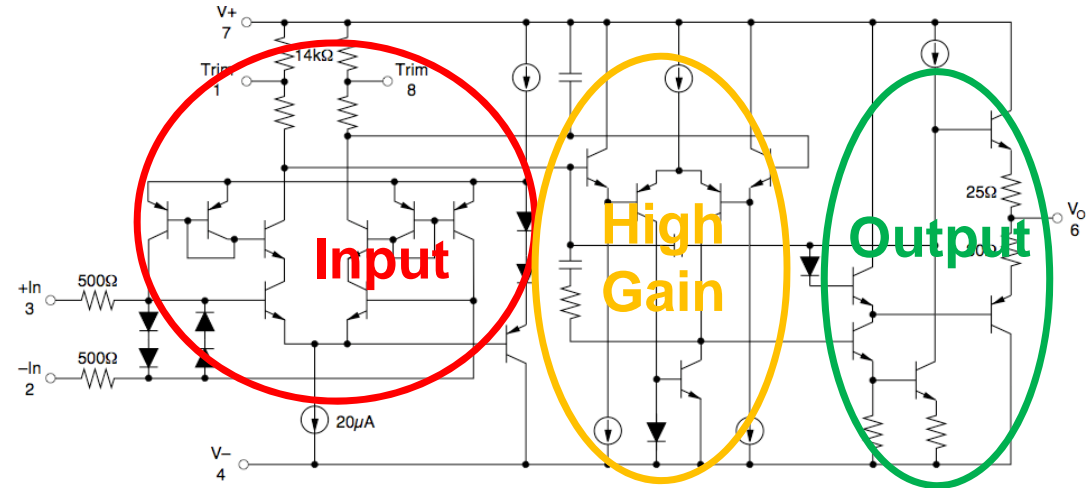

... don't try and  
compare schematics;  
leave that to experts!

# Perfect opamp calculations are easy... *(but real opamps are more difficult...)*

## Method:


- Opamps are not perfect:

Form a **model** of an imperfect opamp which is a perfect opamp  
**PLUS** additional (ideal) voltage and current sources

- Calculations still (relatively) easy (perfect opamp plus linear components)
- Source values become optimisation parameters for system
- Different circuits can be compared using standard parameters
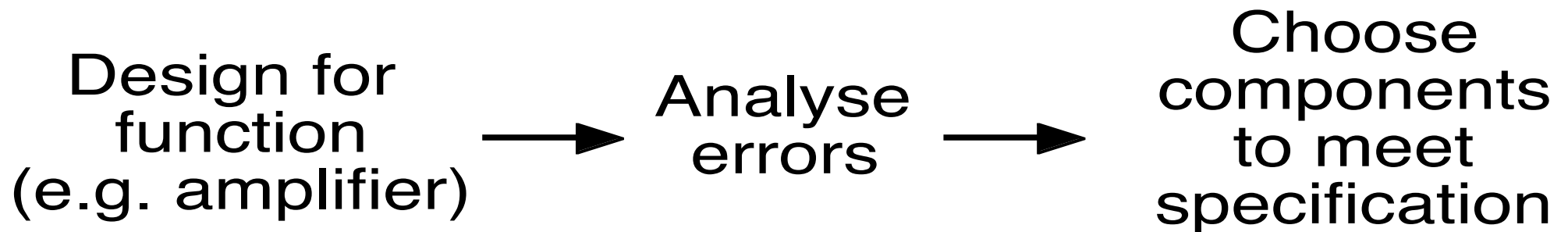
## System Design = Choice

- No opamp is perfect
- Choice of hundreds of different OpAmps
- Pennies (4p for a dual) -> £371 each
  - RS sell a reduced selection of the best opamps in a limited range of grades (4777)



## Tools to help you...

- You **cannot** get a computer to do the design for you...
- ...but you **can** get it to check if the circuit operates the way YOU wanted it to
- **Simulated Circuit Programme with Integrated Circuit Emphasis (**SPICE**)**
- many different variants derived from UC Berkeley :
- PSPICE, HSPICE, ....
- We will use LTSpice or Orcad/PSpice
- - **It is a free download** from Linear Technology Inc (Mac & PC)
- - It consists of Schematic Capture, Simulator, and Waveform engine
- It is one of the simplest SPICE versions I have found
- <http://www.linear.com/designtools/software/#LTspice>



University  
of Glasgow

Thank you  
谢谢

INSPIRING  
PEOPLE

#UofGWorldChangers



@UofGlasgow