




University
of Glasgow

Electronic System Design 3

Lecture 5.1: Figure of Merit

Static Errors

Dr Duncan Bremner

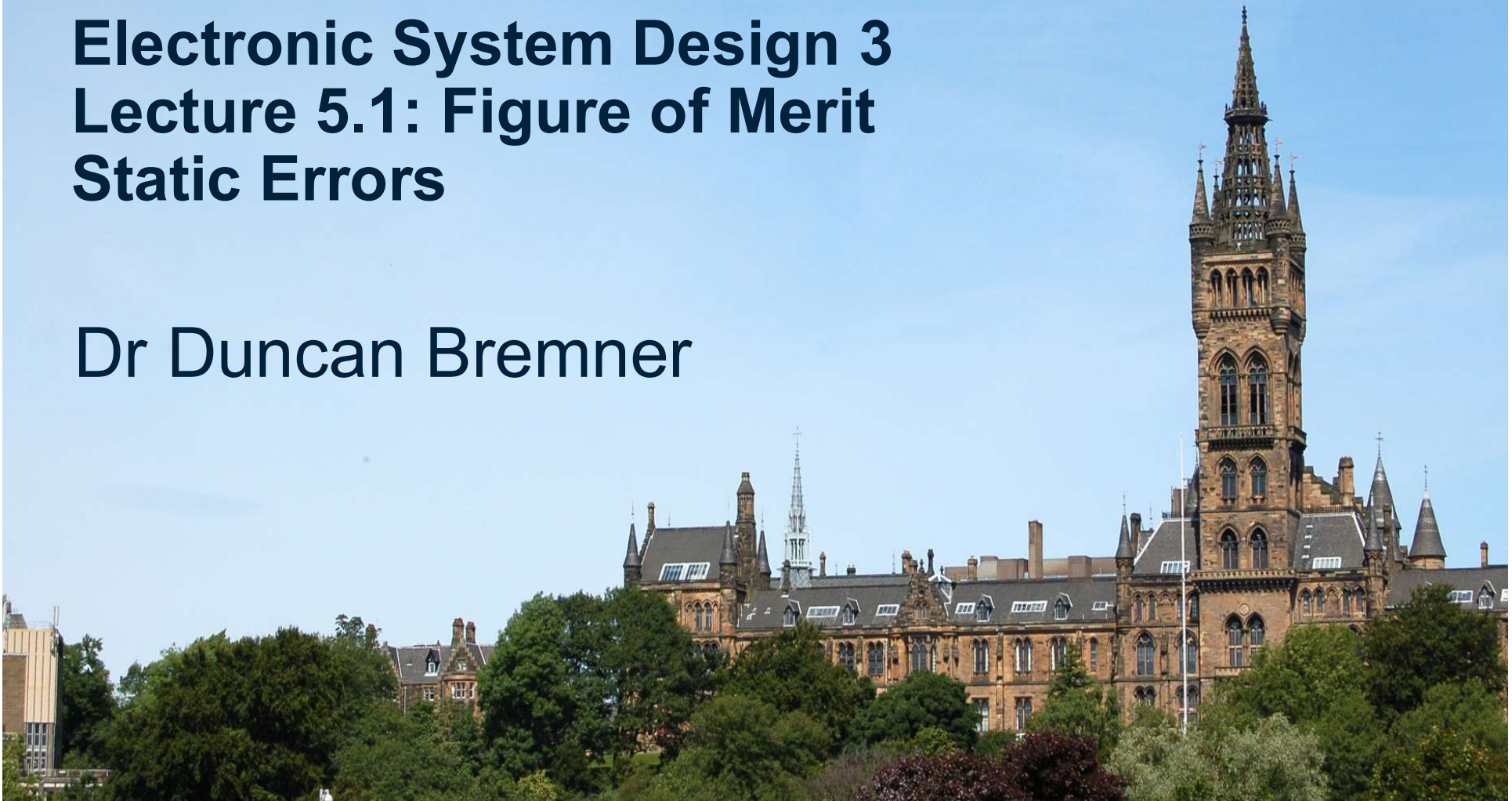

Design example 2: Figures of merit

Last example: Single number (V_{OS}) dominant.

Often many numbers contribute:

Define a **Figure of merit** for the component


Figure of merit is a function of all significant contributions of the component to the total system error.

Figure of merit changes **monotonically** with the overall error due to the component

The total error contributed by the component is clearly a good choice



Example 2: Integrate-and-Hold

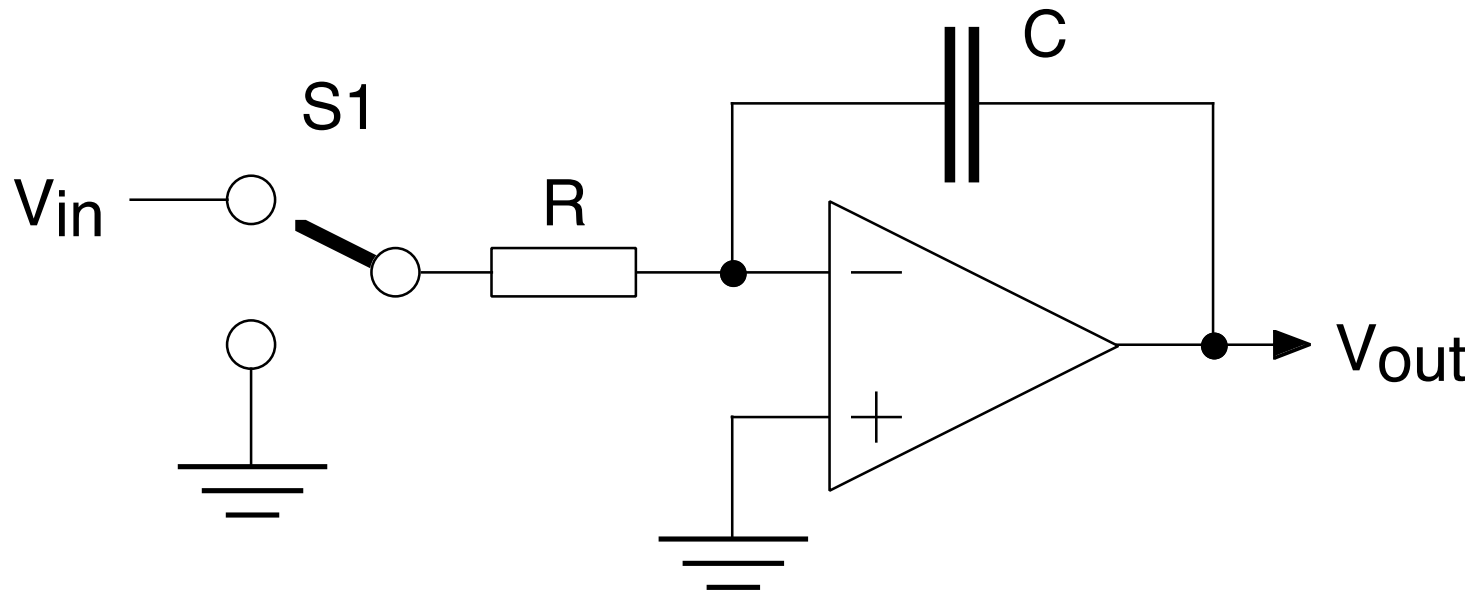


If S1 connects to V_{in} circuit is an integrator $V_{out} = -\int \frac{V_{in}}{RC} dt$

If S1 connects to 0V circuit is a memory $V_{out} = \text{constant}$



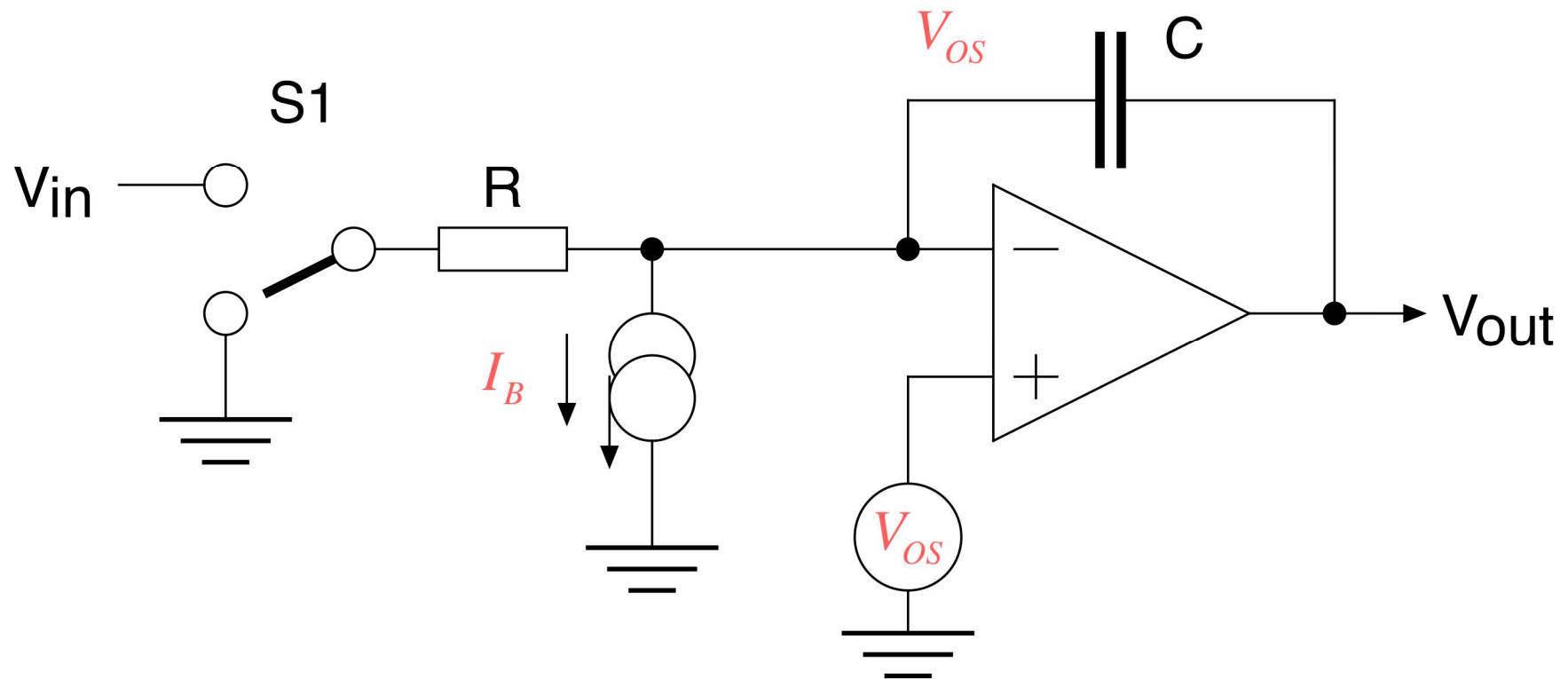Important parameter is drift during "Memory"



$$\left| \frac{dV_{out}}{dt} \right| = \frac{1}{C} \frac{dQ}{dt} = \frac{1}{C} \left(I_B + \frac{V_{OS}}{R} \right)$$

Timeconstant is fixed: $\tau = RC \quad \therefore$ one free parameter (R)

$$\left| \frac{dV_{\text{out}}}{dt} \right| = \frac{1}{C} \left(I_B + \frac{V_{OS}}{R} \right) = \frac{1}{\tau} (I_B R + V_{OS})$$

Optimisation: make R as small as possible




Practical limits on R:

If R too small,
Input Voltage range
is too small

Also:

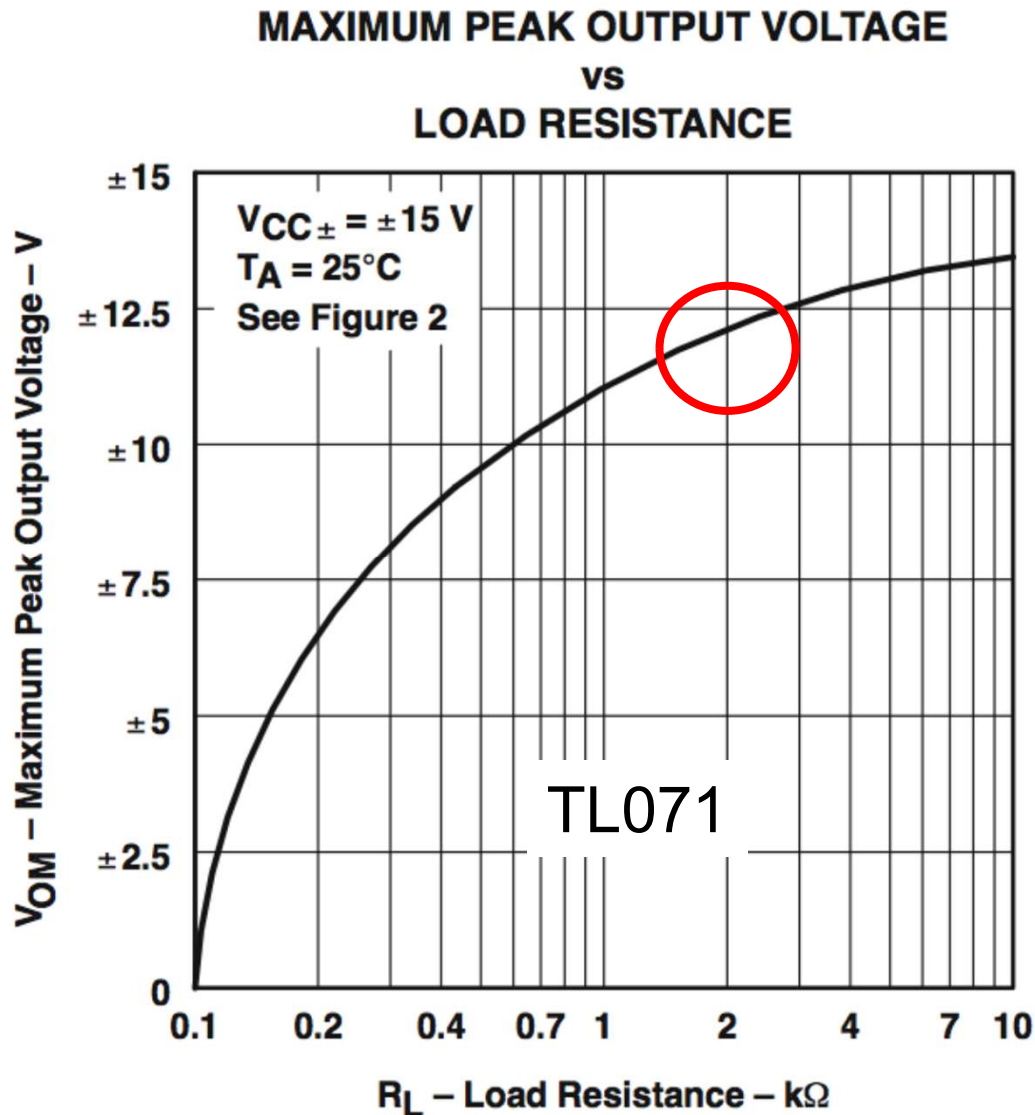
- Supply current
- Power dissipation
- Thermal drift
- V across PCB
- Available C values



$$R \geq 2k\Omega$$


Error Analysis (4)

Naïve circuit ($\tau=10s$)

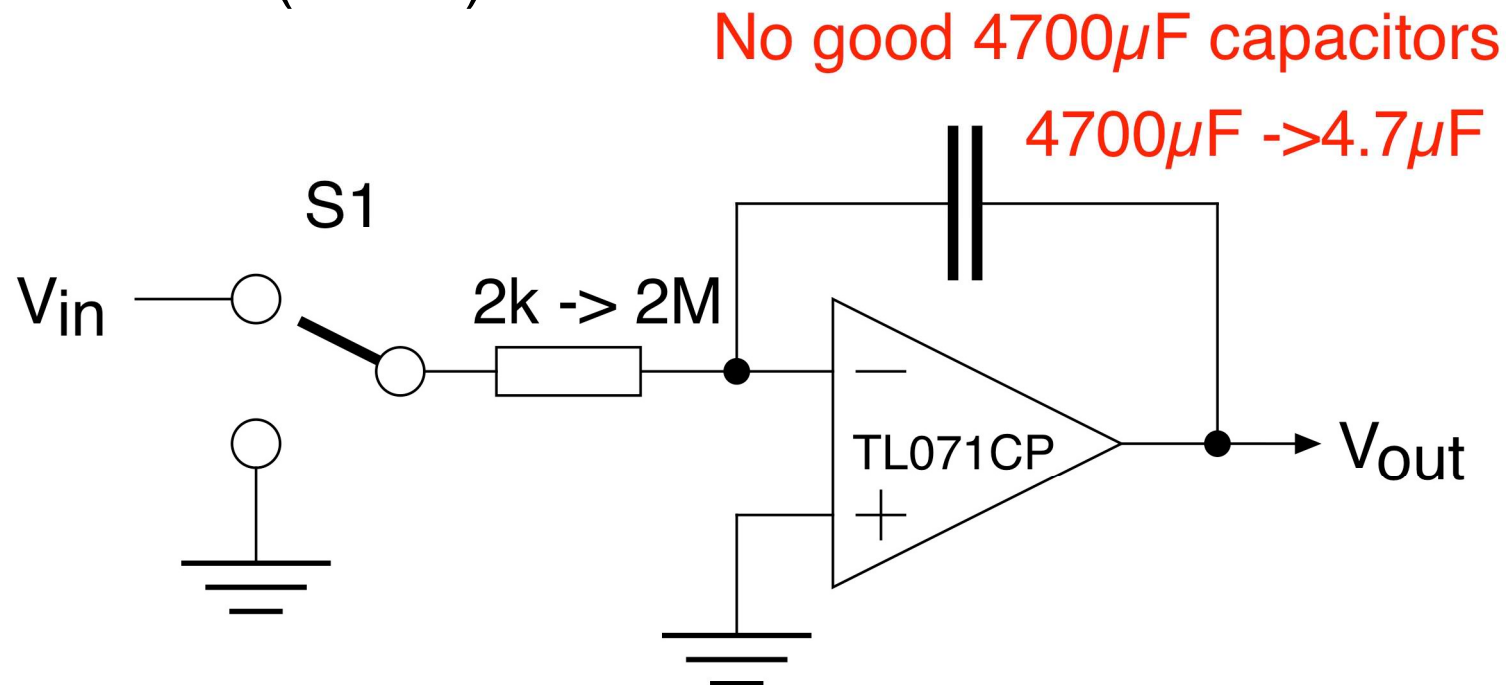


$$\left| \frac{dV_{\text{out}}}{dt} \right| = \frac{1}{\tau} (I_B R + V_{OS}) = \frac{1}{10s} \cdot (200 pA \cdot 2 M\Omega + 10 mV) = 1.04 mV \cdot s^{-1}$$

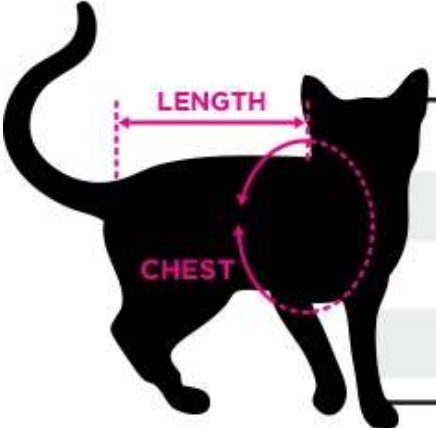How large is a 4700 μ F Polypropylene Capacitor?



	INCHES/POUNDS			CENTIMETERS/KILOGRAMS		
	SMALL	MEDIUM	LARGE	SMALL	MEDIUM	LARGE
CHEST	11-14 in	14-17 in	17-20 in	28-36 cm	36-43 cm	43-51 cm
LENGTH	10-13 in	13-16 in	13-16 in	26-33 cm	33-41 cm	33-41 cm
APPROX. WEIGHT	4-8 lbs	8-12 lbs	12-16 lbs	2-4 kg	4-6 kg	6-8 kg

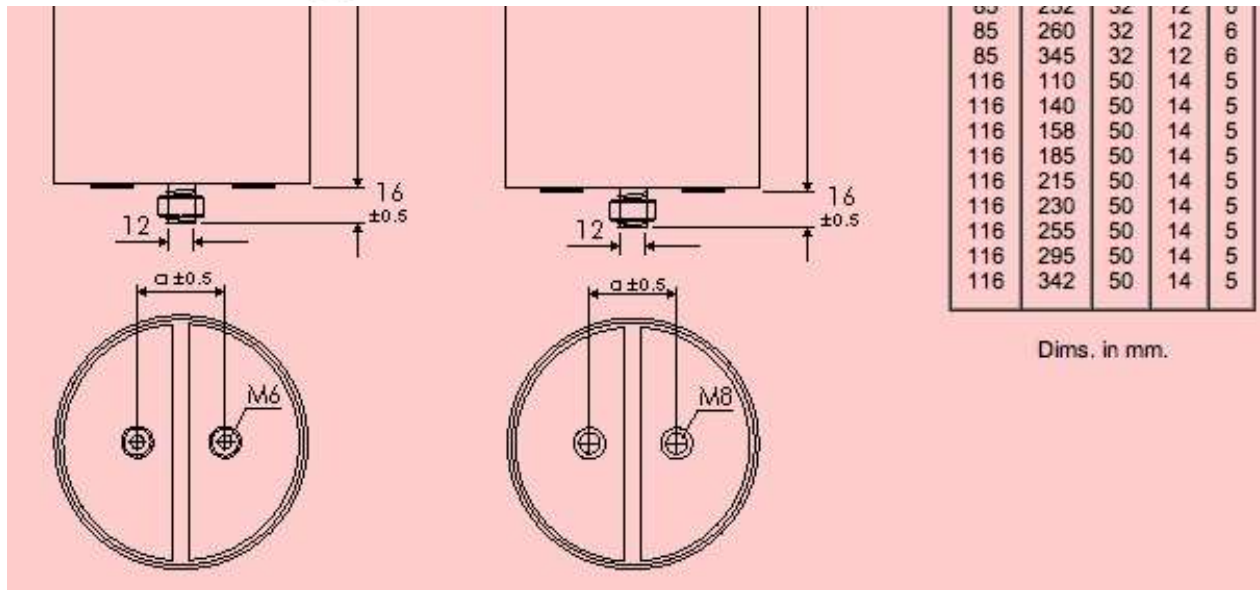

↑
This one

← This one

(Wima DC-LINK MKP 6 HP 4920 μ F 600V)



University
of Glasgow

Thank you
谢谢

INSPIRING
PEOPLE