



University  
of Glasgow

# Electronic System Design 3

## Lecture 6.2: Designing Grounds

Dr Duncan Bremner






# Designing ground

Think where the current will flow.

Put all signals onto a line with ~ no current flowing

=>Route currents separately

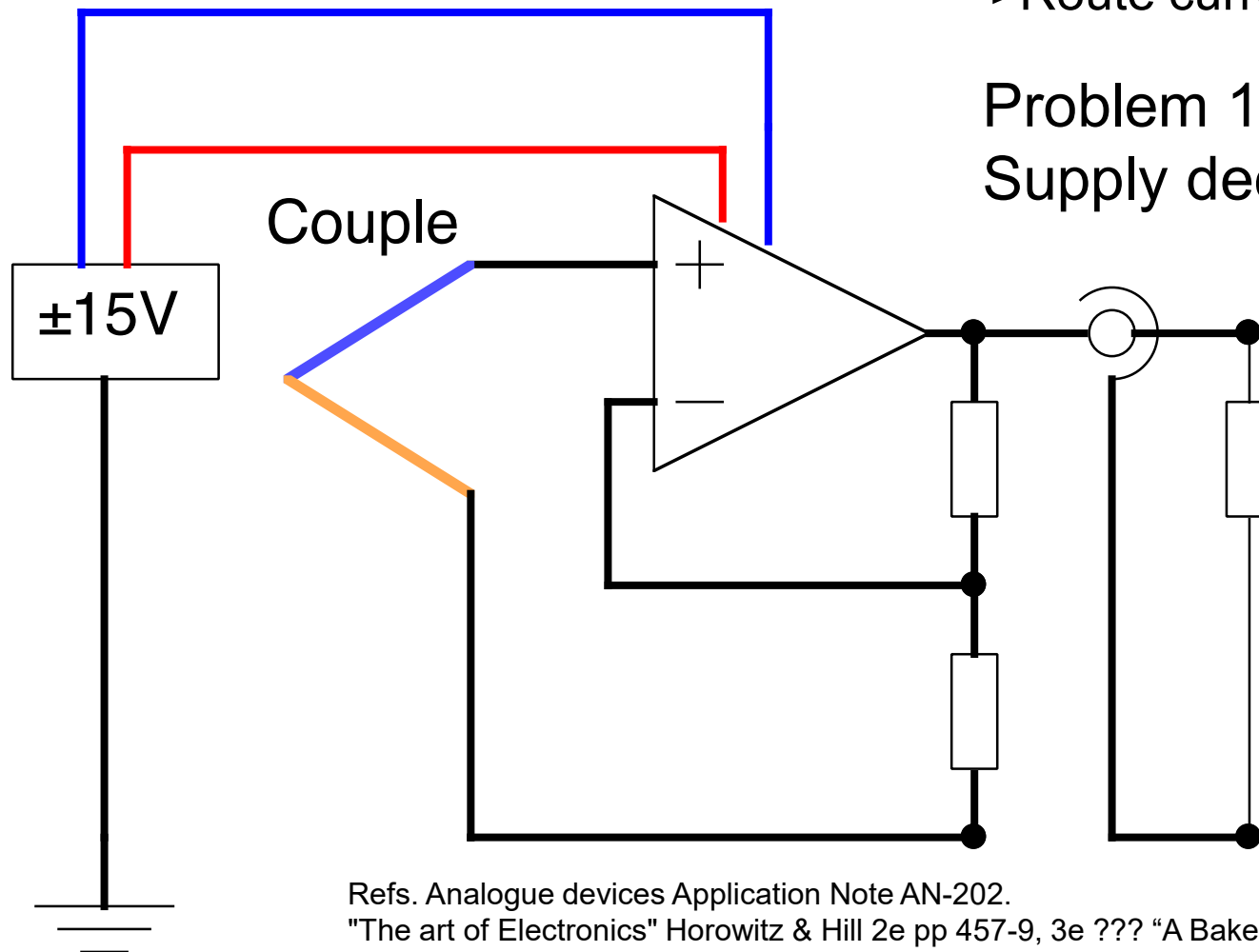

Problem 1:  
Supply decoupling


Refs. Analogue devices Application Note AN-202.

"The art of Electronics" Horowitz & Hill 2e pp 457-9, 3e ??? "A Baker's Dozen" Chapter 11


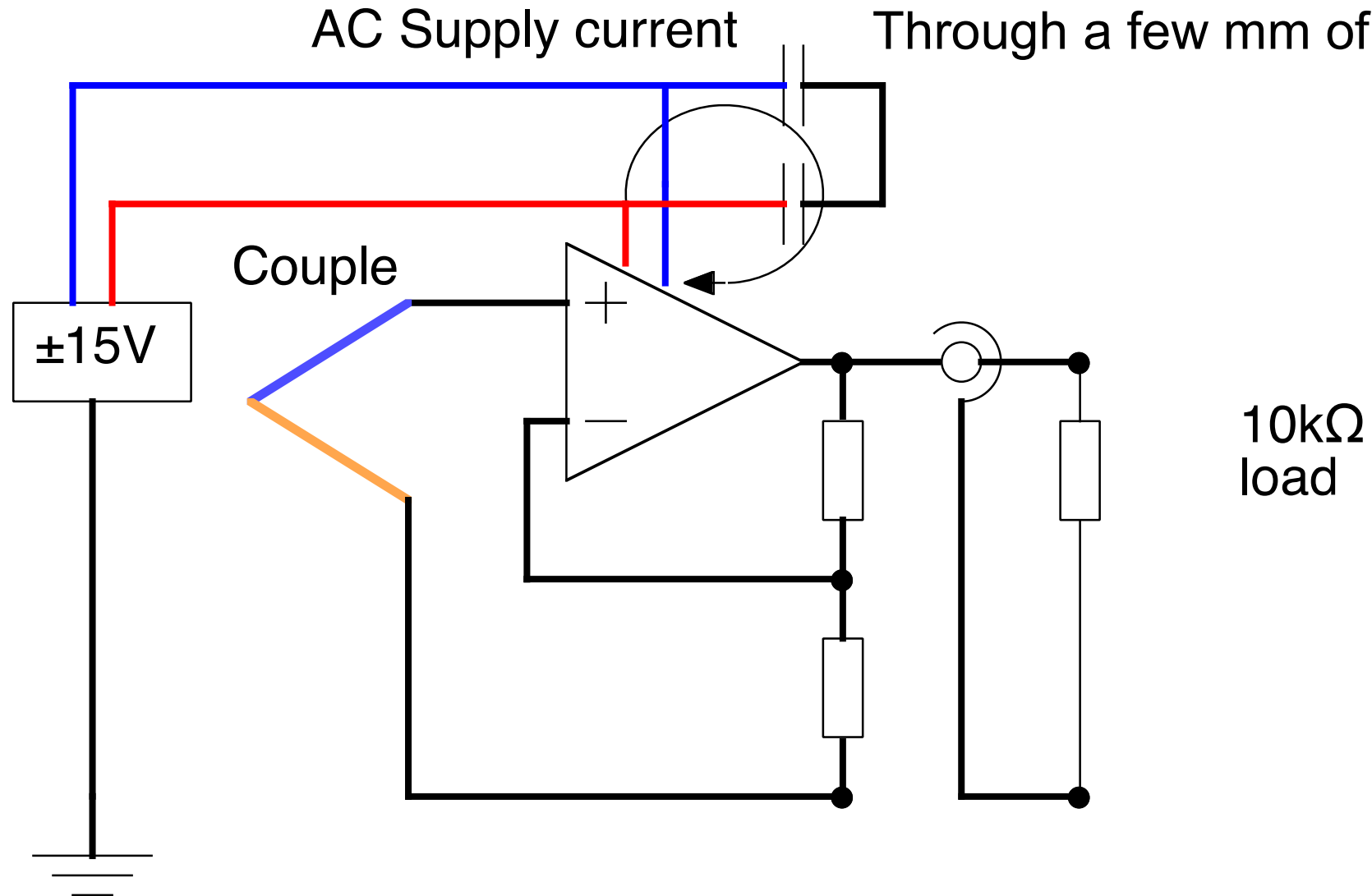
## Designing Ground (2)

Current only goes  
Through a few mm of wire





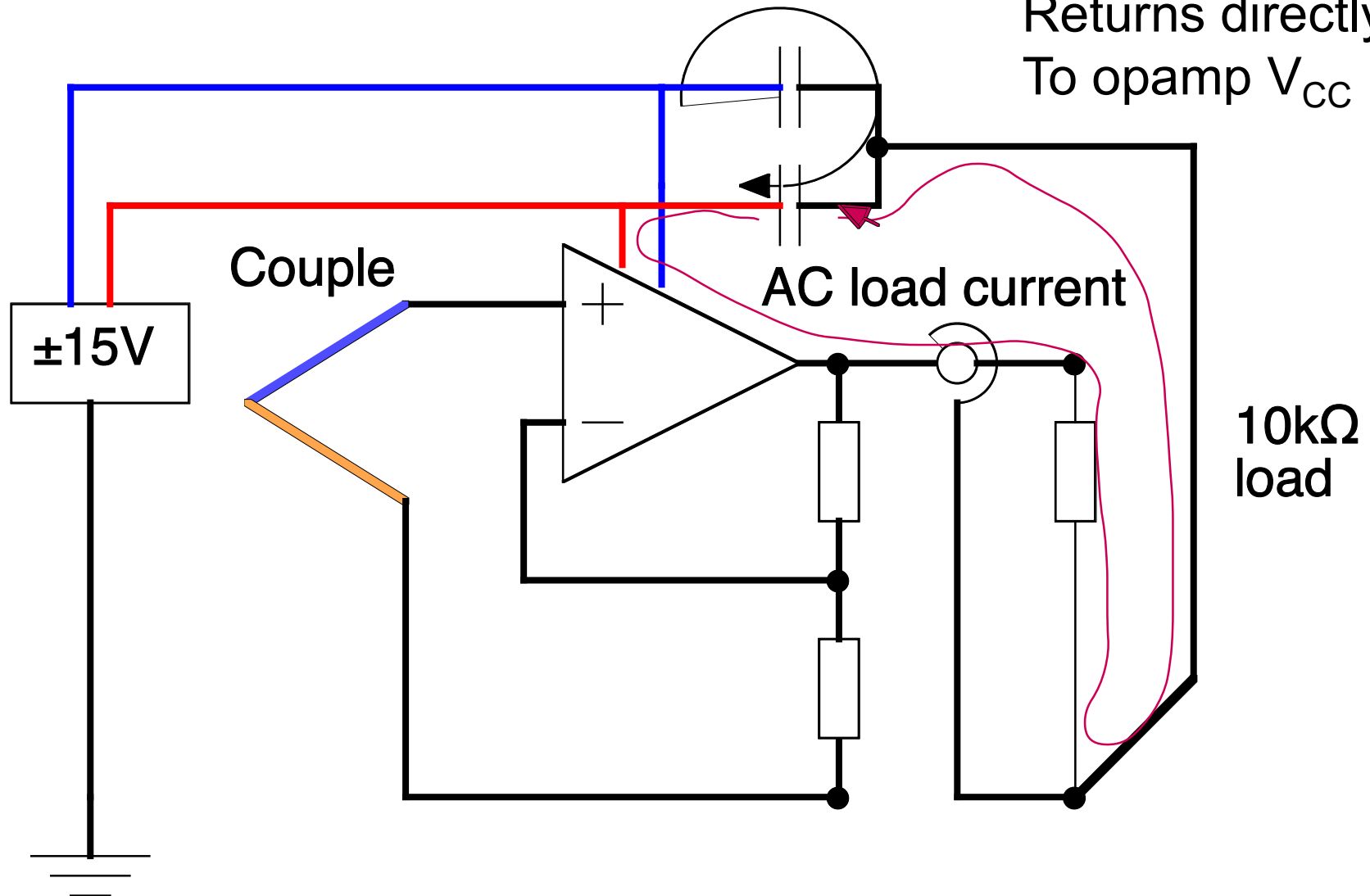
## Designing ground (3)

AC Supply current


Load current  
Returns directly  
To opamp  $V_{CC}$





## Designing Ground (4)


Connect cold end of load directly to PSU

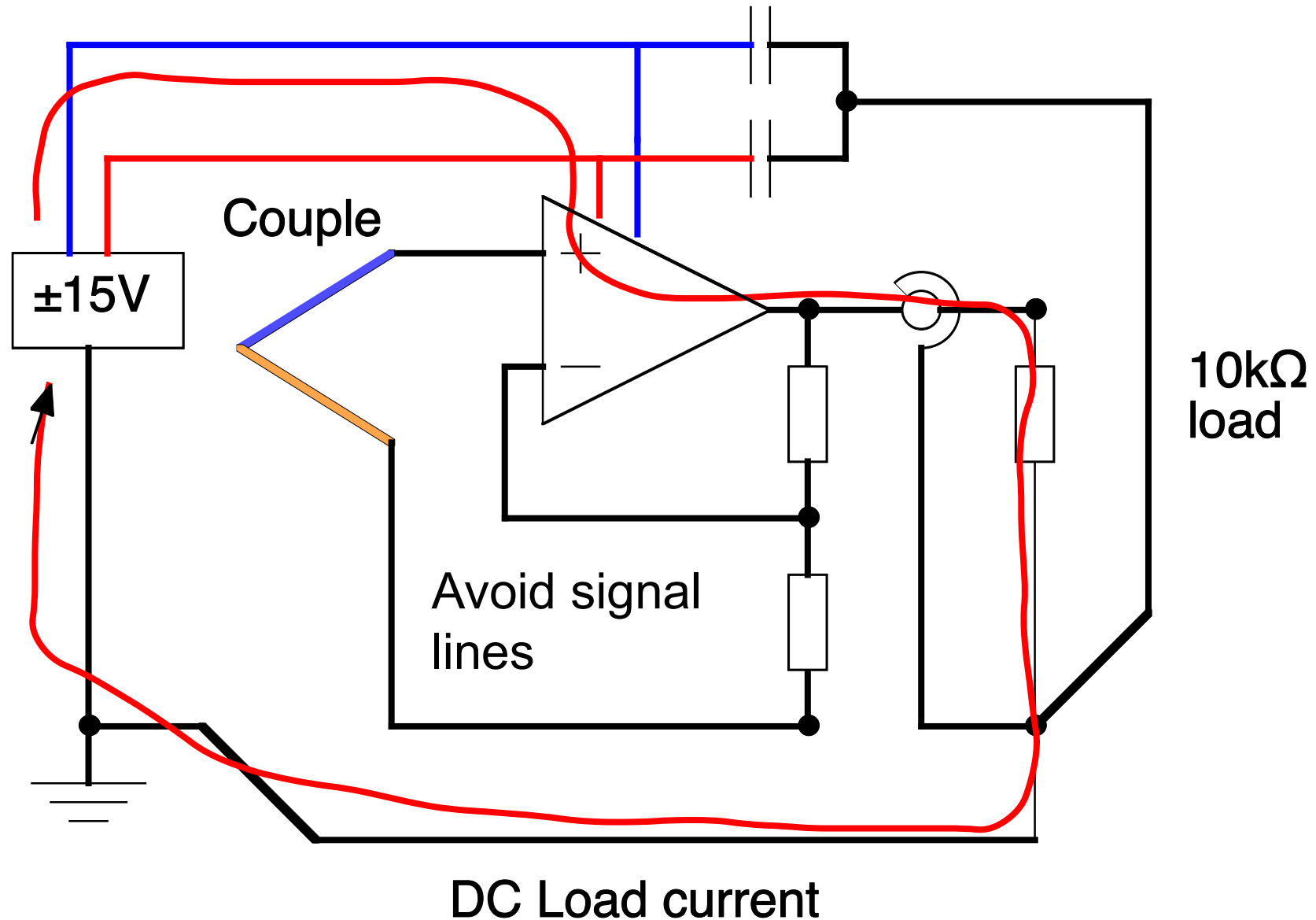




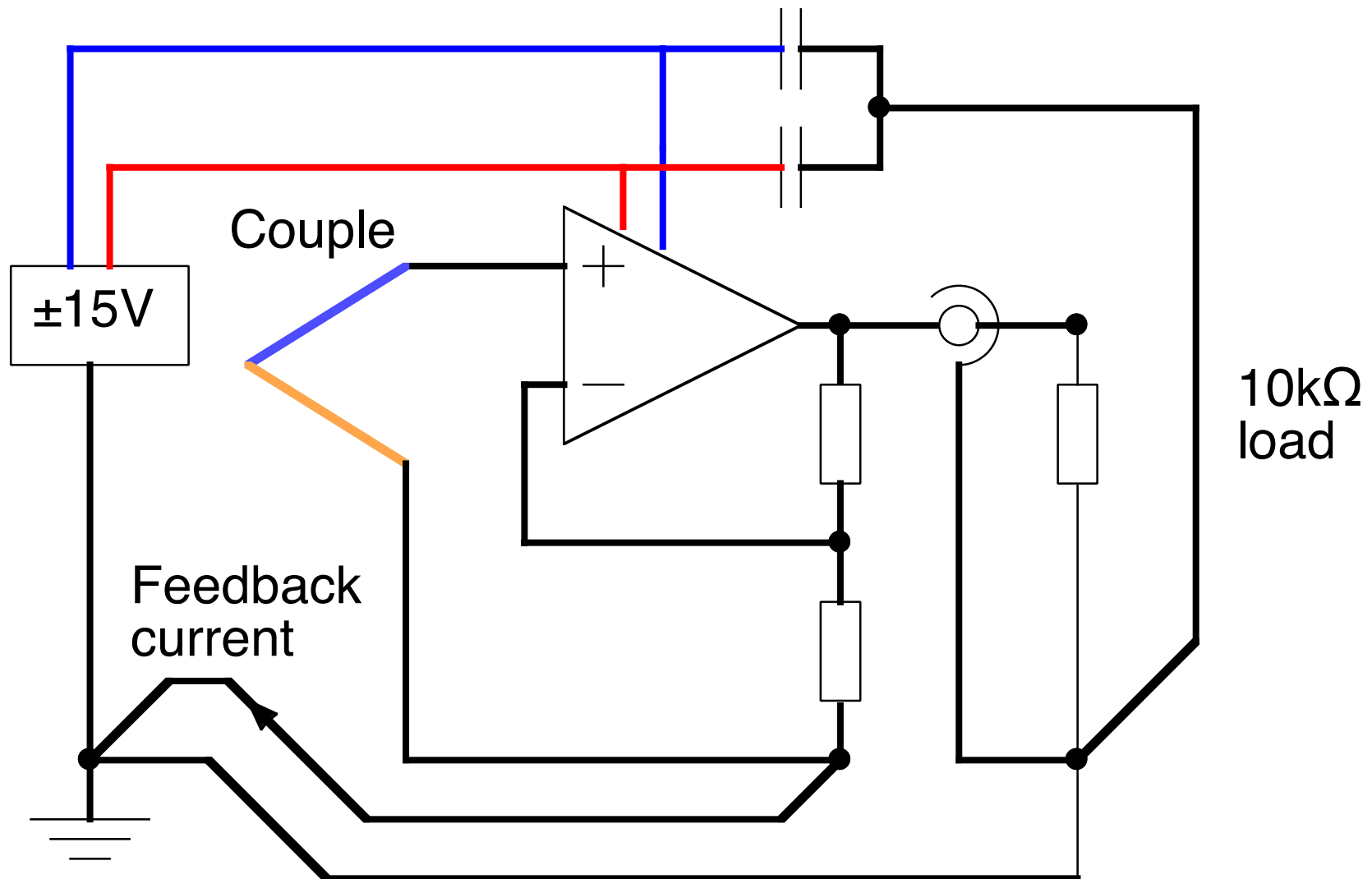
## Designing ground (5)

Connect small, known current paths separately to PSU



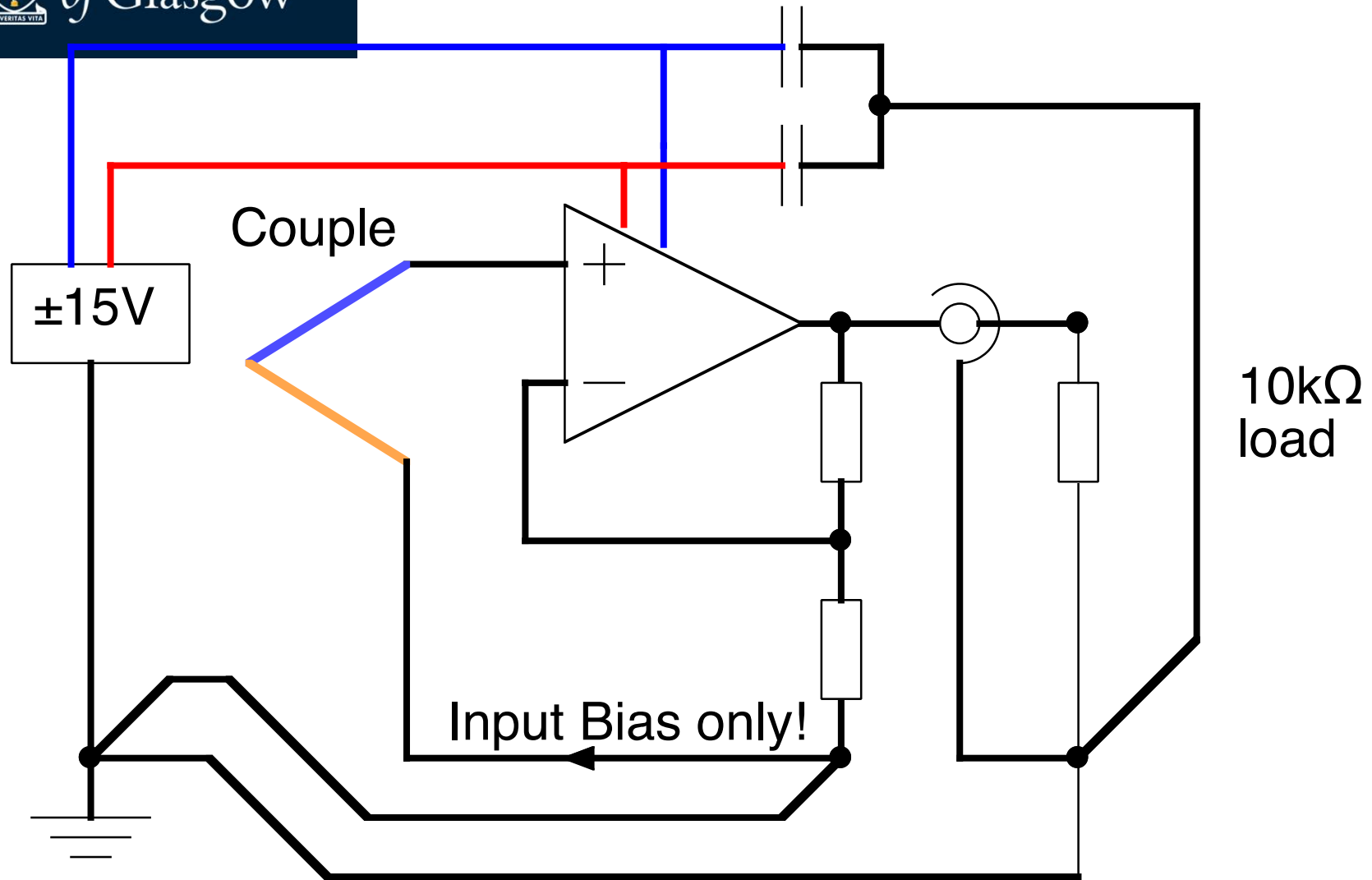


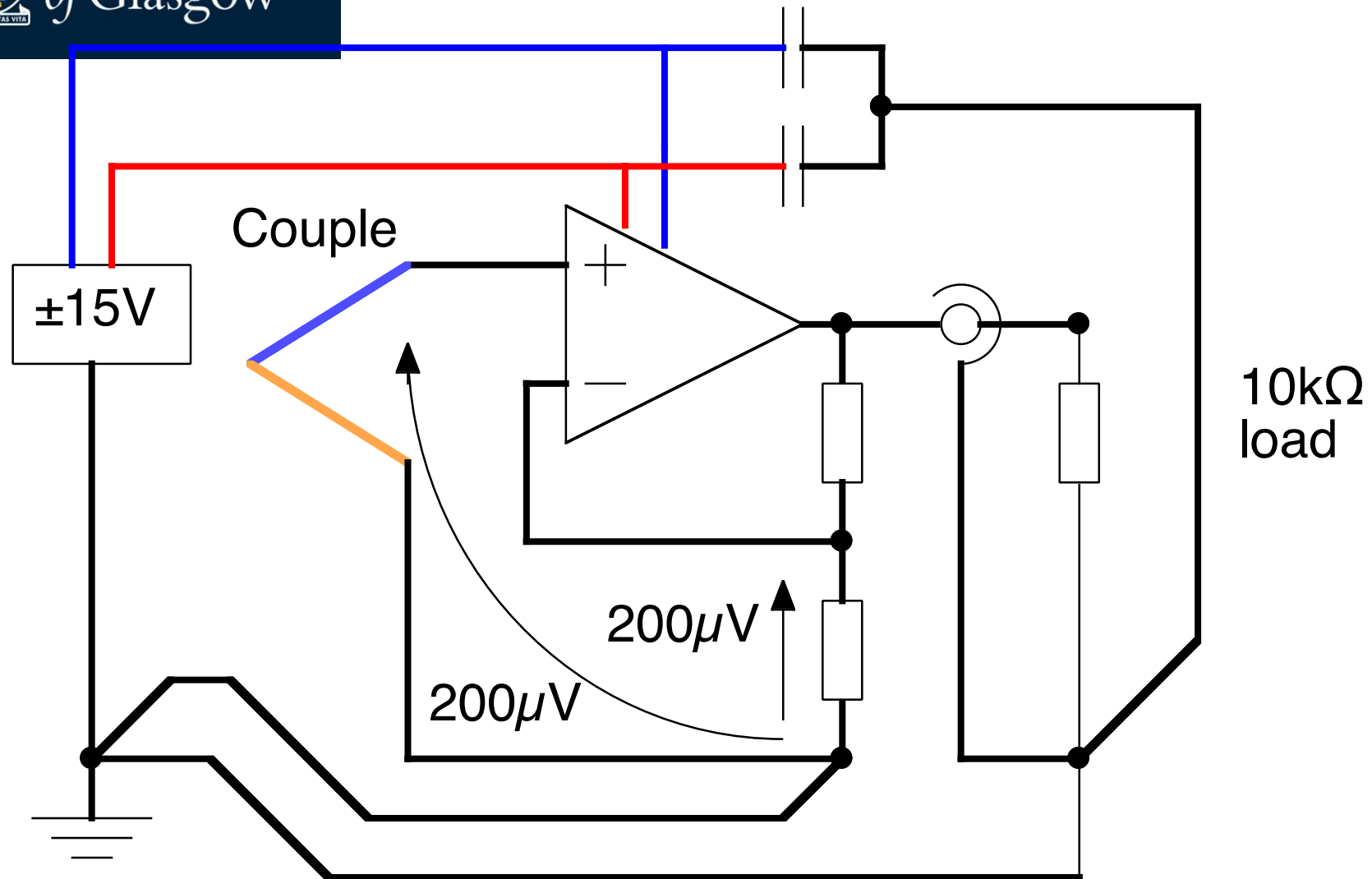Success! Thermocouple is at same voltage as bottom of Feedback resistors. Error is  $I_B \times 0.1\Omega \sim 0.1\text{nV}!!!$



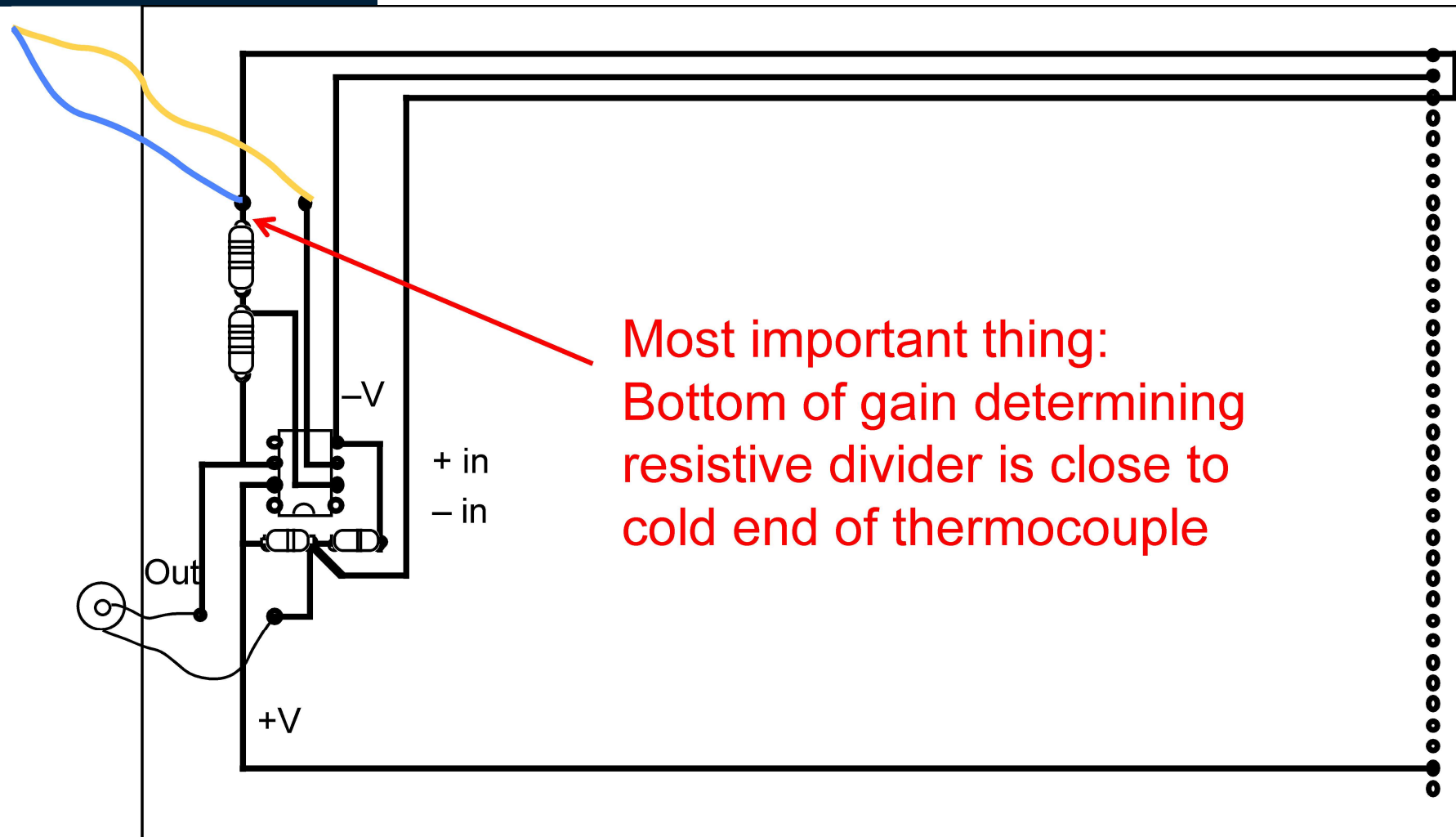Voltage across lower R is same as Voltage across couple  
**This** is the voltage which is amplified







### Summary:

- Decouple supply currents close to the IC first
- Bring "Decoupling" grounds together and route separately to PSU
- Decouple Logic **Close to chip**
- Keep "logic ground" separate from others and route separately to PSU
- Design "Signal" ground so that no currents flow through connections of low voltage

"Signal Ground" is a signal which is  $\sim 0V$ ,

**not** "The ground for the signals"



## Designing Ground (9)

Good thing about this method:

- System **manufacturing** cost is unchanged

Bad things about this method:

- System **design** cost is (much) higher
- Full analysis is complicated (coupling, radiation...)
- Complex ICs may not give adequate access to signals
- Only appropriate to small systems / sub-systems
- Incompatible with most layout tools (they only 'know' about a single ground connection...)

Generally this method is a help, but not a complete solution



University  
of Glasgow

## Common-Mode Rejection

Problem with previous circuit is that ground is a signal level...

And a sewer for random stray currents


Use **PLAN B**

Measure the **difference** between the two leads and let 'em vary  
With respect to "Ground" however they like


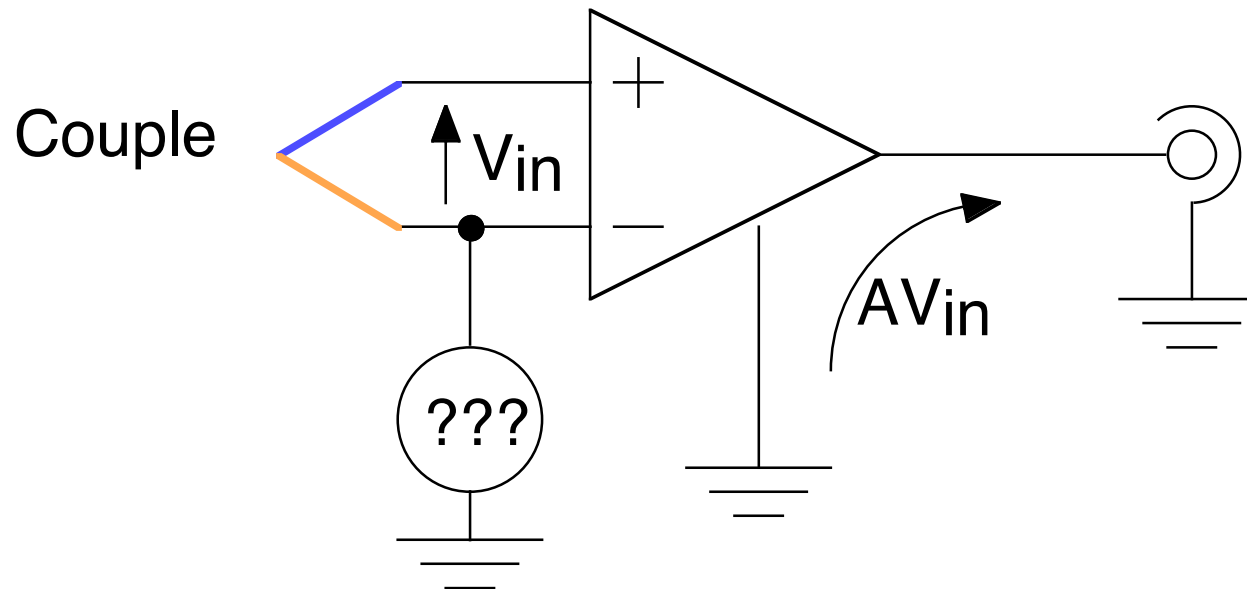
## Common-Mode Rejection (2)

Component “X” = **Instrumentation Amplifier**



- Component X
- Has a big gain (O/P is big, so no more problems)
  - Doesn't care what ground potential “???” Is  
= **Common-mode rejection**
  - Produces an output voltage with respect to an explicit third (output ground) input



University  
of Glasgow

Thank you  
谢谢

INSPIRING  
PEOPLE