

# UESTC 3003: Electronic System Design

*Static Errors*

## Lecture 2.2: OpAmp Imperfections

Dr Duncan Bremner

WORLD  
CHANGING  
GLASGOW



- Imperfections in opamp modelled as Perfect Opamp + sources
- Performance of system is measured against a specification
- ESD3 is concerned with the methods used to connect the two to produce a design which can be proven to meet specification

**CHEAPLY.**

# System Engineering : Signal Conditioning



- In **Electronic System Design** we will consider how to provide the best possible input signals to the system. This means signals that are:-
  - **Accurate:** providing the most accurate signal to the system
  - **Clean:** providing the system with the cleanest, lowest noise signal
  - **Immune:** (from disturbance): signals remain accurate and clean when there is interference
- Our course will explore how to deal with low level signals and condition them for the system to use (probably in a digital process)

"Pray, Mr. Babbage, if you put into the machine wrong figures, will the right answers come out?" ... I am not able rightly to apprehend the kind of confusion of ideas that could provoke such a question.

— [Charles Babbage](#), *Passages from the Life of a Philosopher*

Source Wikipedia

# Imperfect Opamps

• Perfect Opamp:  $\longrightarrow V_{OUT} = \infty(V_{IN}(+) - V_{IN}(-))$

• Imperfect Opamp<sup>1</sup>

- Current flows in inputs

**Bias**

**Offset**

- Slow

**Bandwidth**

**Slew Rate**

**Phase margin**

- O/P has finite impedance (but reduced by feedback)

- Input voltage error

**Offset**

**Common-Mode rejection**

**Power Supply rejection**

**Drift (Time / Temperature)**

*For a more detailed analysis read:*

*“Opamps for Everyone” Chapter 11*

<sup>1</sup>“Users Guide to Applying and Measuring Operational Amplifier Specifications” Ray Stata  
Analog Devices Application Note AN-356

# How to design with imperfect components...

- Specify (sub)system
  - Function (e.g. Gain of +10)
  - External connections (e.g. source voltage range, impedance...)
  - Performance (e.g. scale and offset error, bandwidth, power dissipation..)

## 1. Naïve design for basic function

- Full design including choice of opamp, component values...
- **Hint:** Start with cheap components then work upwards

## 2. Analyse circuit for sources of error

- Identify dominant errors
- Remove/reduce the dominant errors


## 3. Optimise your design...

- Best performance....
- Minimum cost



• **Specification and Analysis** are the keys to good design.

## NE5532: Where is the input stage ?

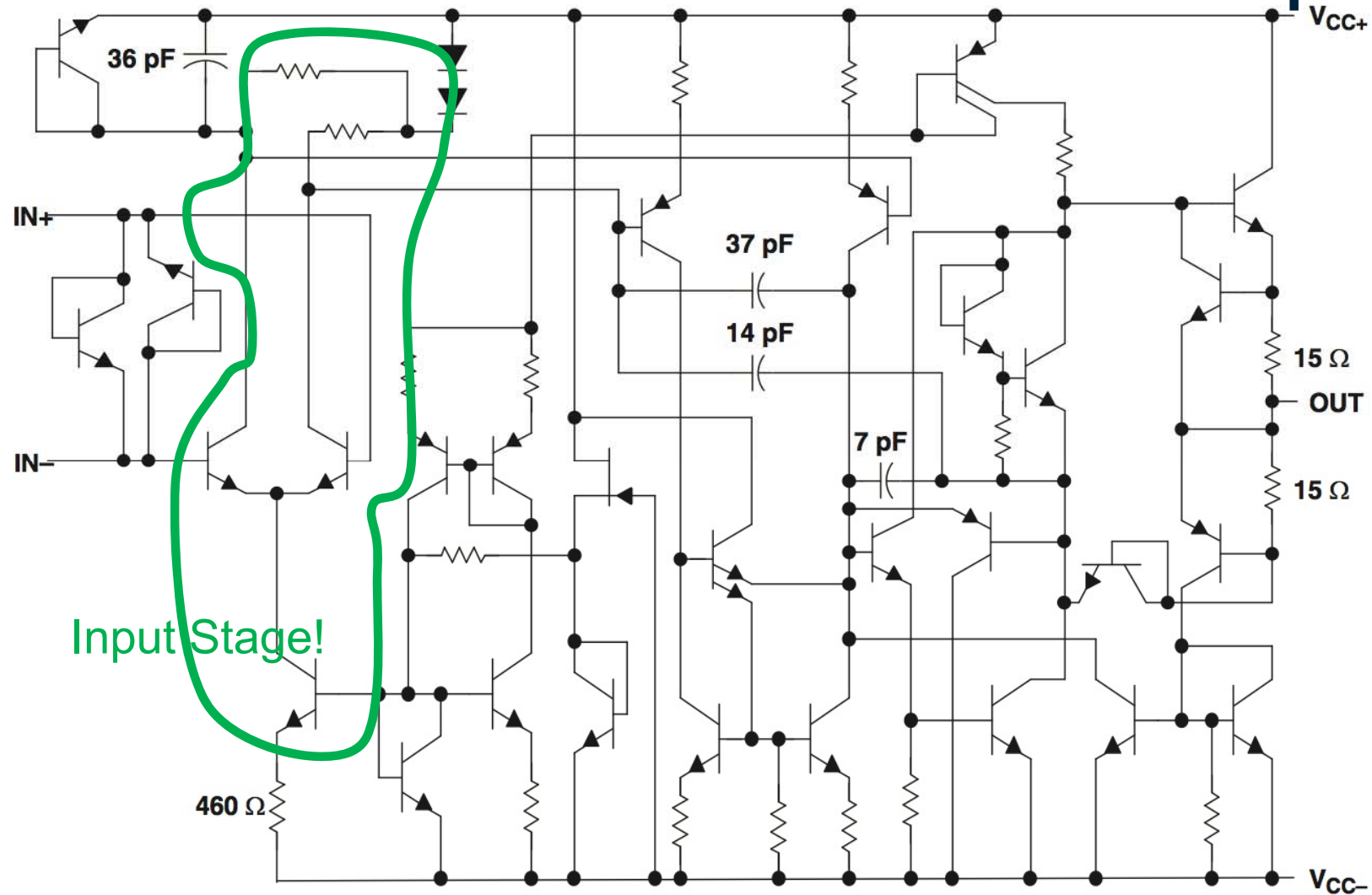

Component values shown are nominal.






# Input Stage

$$Q1 \equiv Q2$$

$$V_{BE1} = V_{BE2} \therefore I_{C1} = I_{C2}$$

$$I_{C1}/\beta_1 = I_{C2}/\beta_2$$

In(+) = In(-)  
(virtual earth)

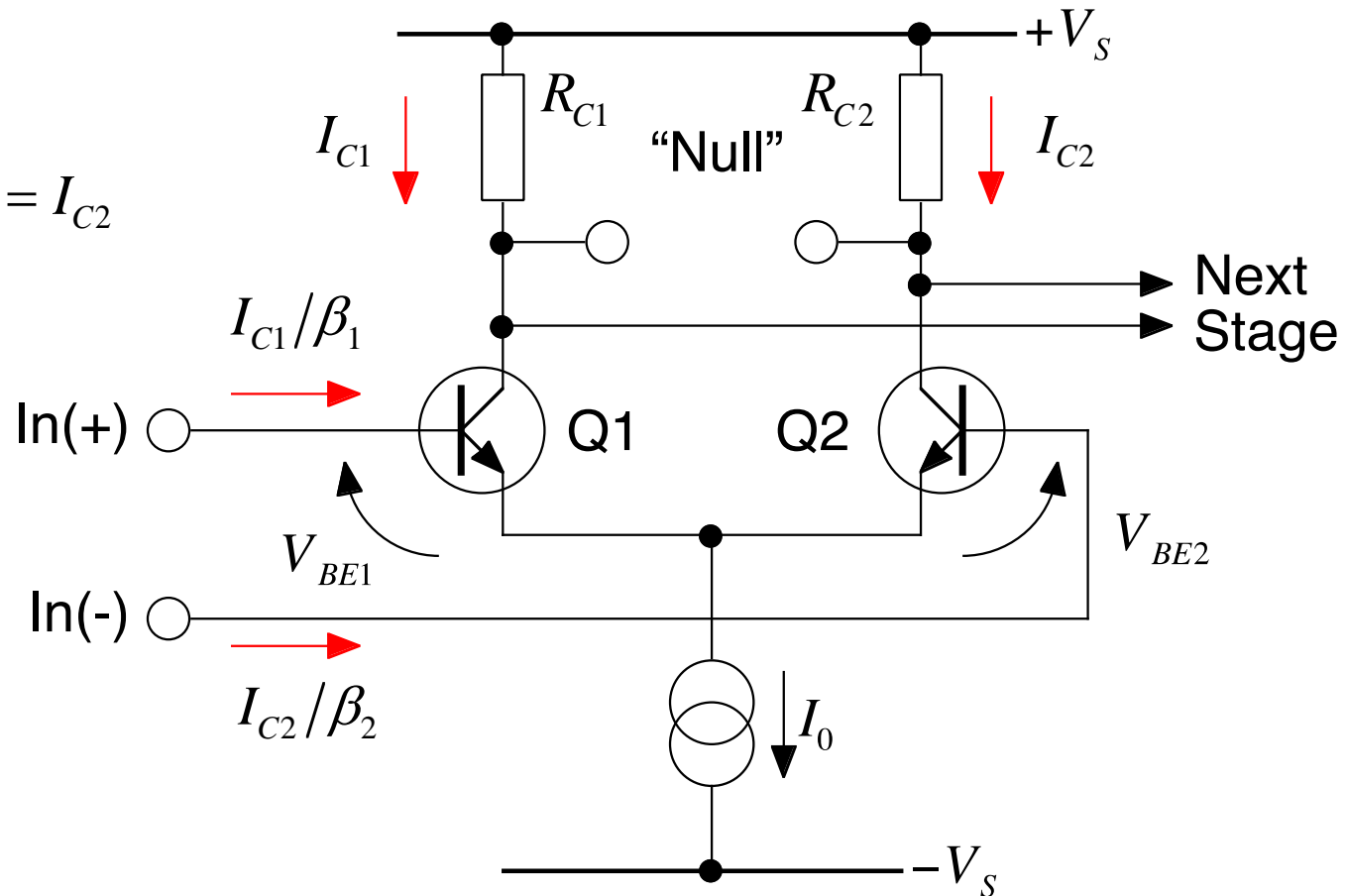


See, for example

"The Monolithic Operational Amplifier: A Tutorial Study"

National Semiconductor Application Note AN-A

## Input Stage

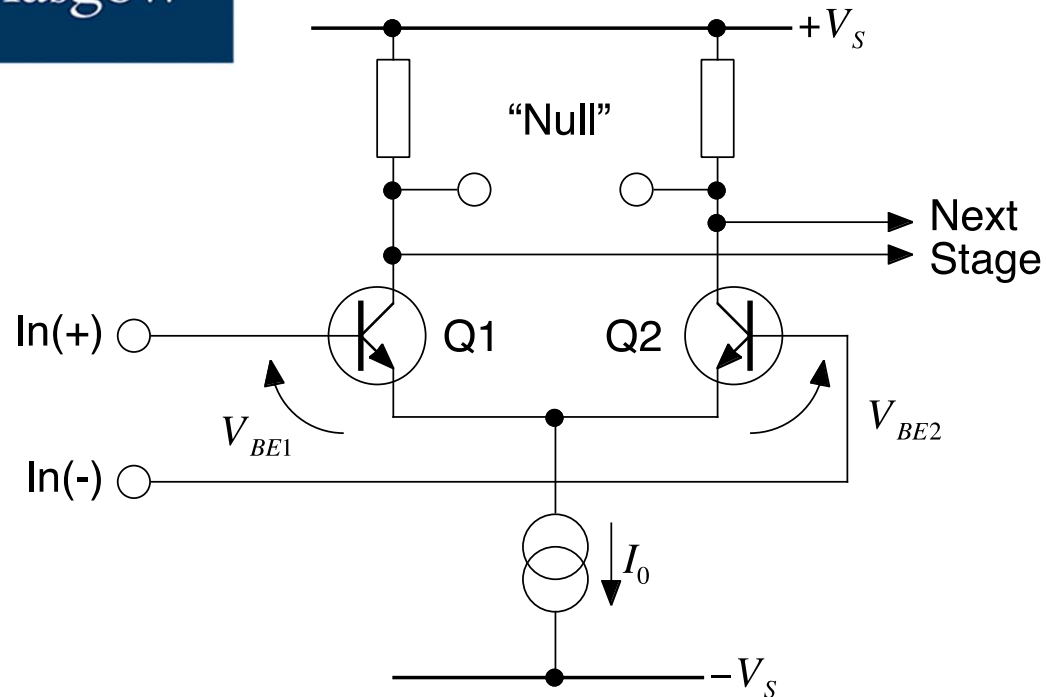

Because of constant current  
“tail” total collector current is  
constant

Because of matched  
components and virtual  
earth principle both input  
currents are equal

Input currents are equal and independent of input voltage if negative feedback  
present; Constant input current


$$Z_{IN} \approx \infty; \quad i_{IN} \neq 0$$


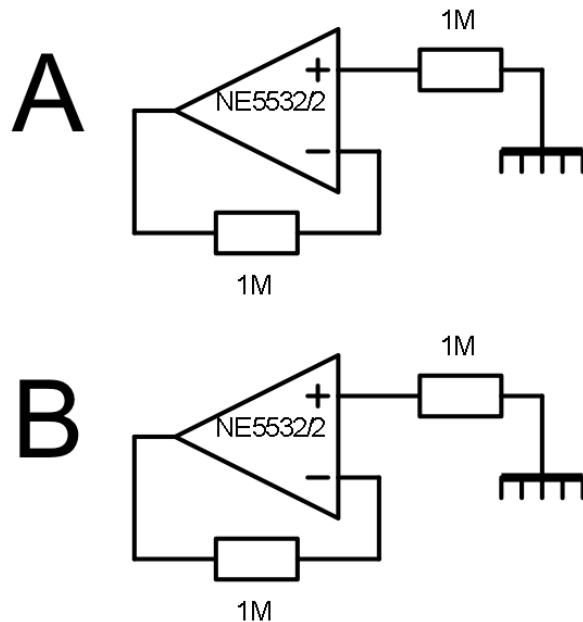
## Intellectual Experiment...

NE5532 has two opamps in one package

Put  $1\text{M}\Omega$  in series with inputs to measure current...




Input current (nA)	Noninverting	Inverting
Chip 1 Amplifier A	Wait!!!	
Chip 1 Amplifier B		
Chip 2 Amplifier A		
Chip 2 Amplifier B		

For a perfect opamp input current = 0 so no voltage across  $1\text{M}\Omega$  resistors



University  
of Glasgow

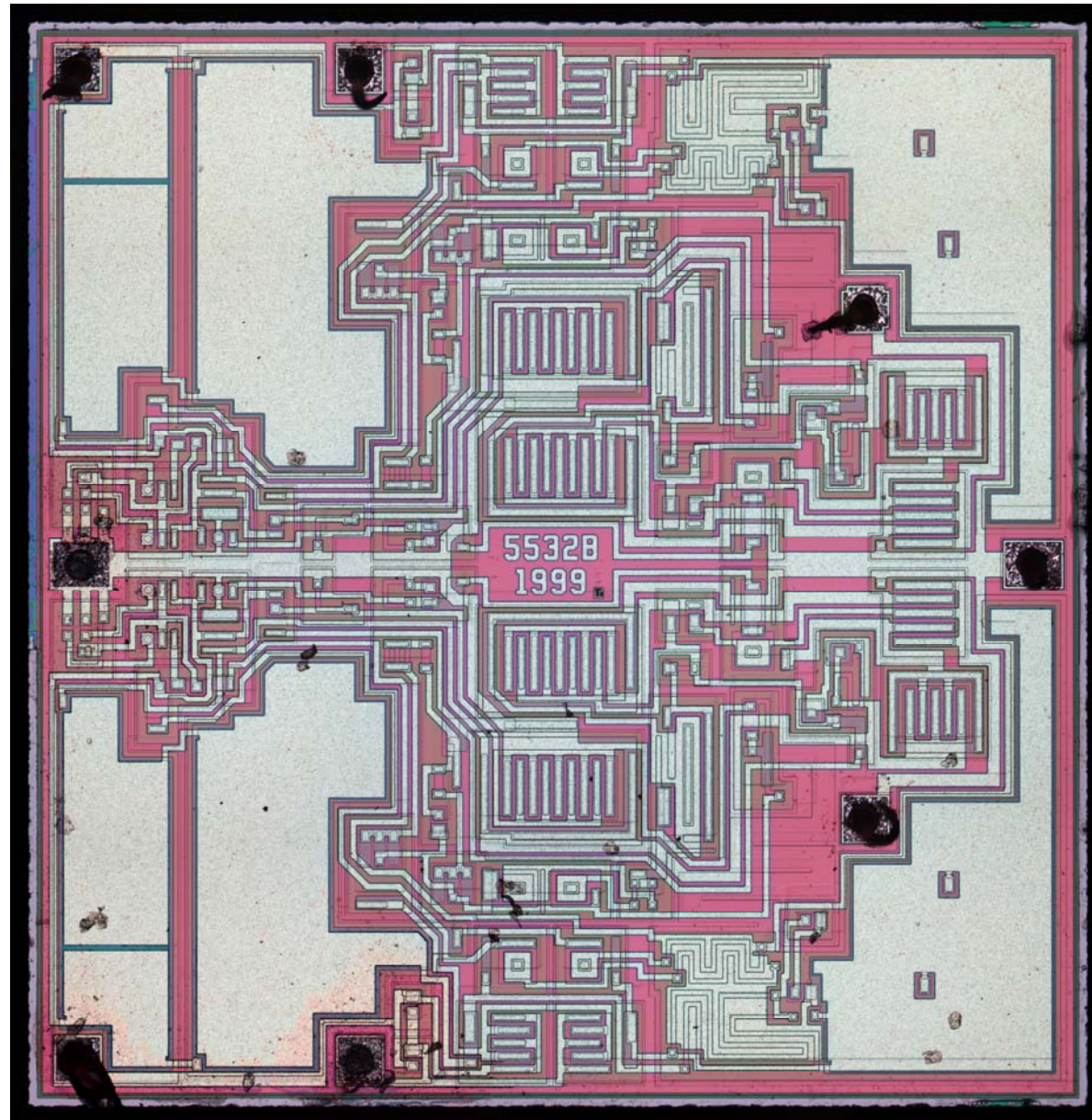

**What is  
inside the  
NE 5532?**





University  
of Glasgow

What is  
inside the  
NE 5532?

Input  
Stage 'A'

Input  
Stage 'B'

(2)A In +

(6)B In -

(3)B In -

(5)B In +

(1)Out A

(7)Out B


(8)Vcc

(4)Vee

Amplifier A

Amplifier B


5532B  
1999

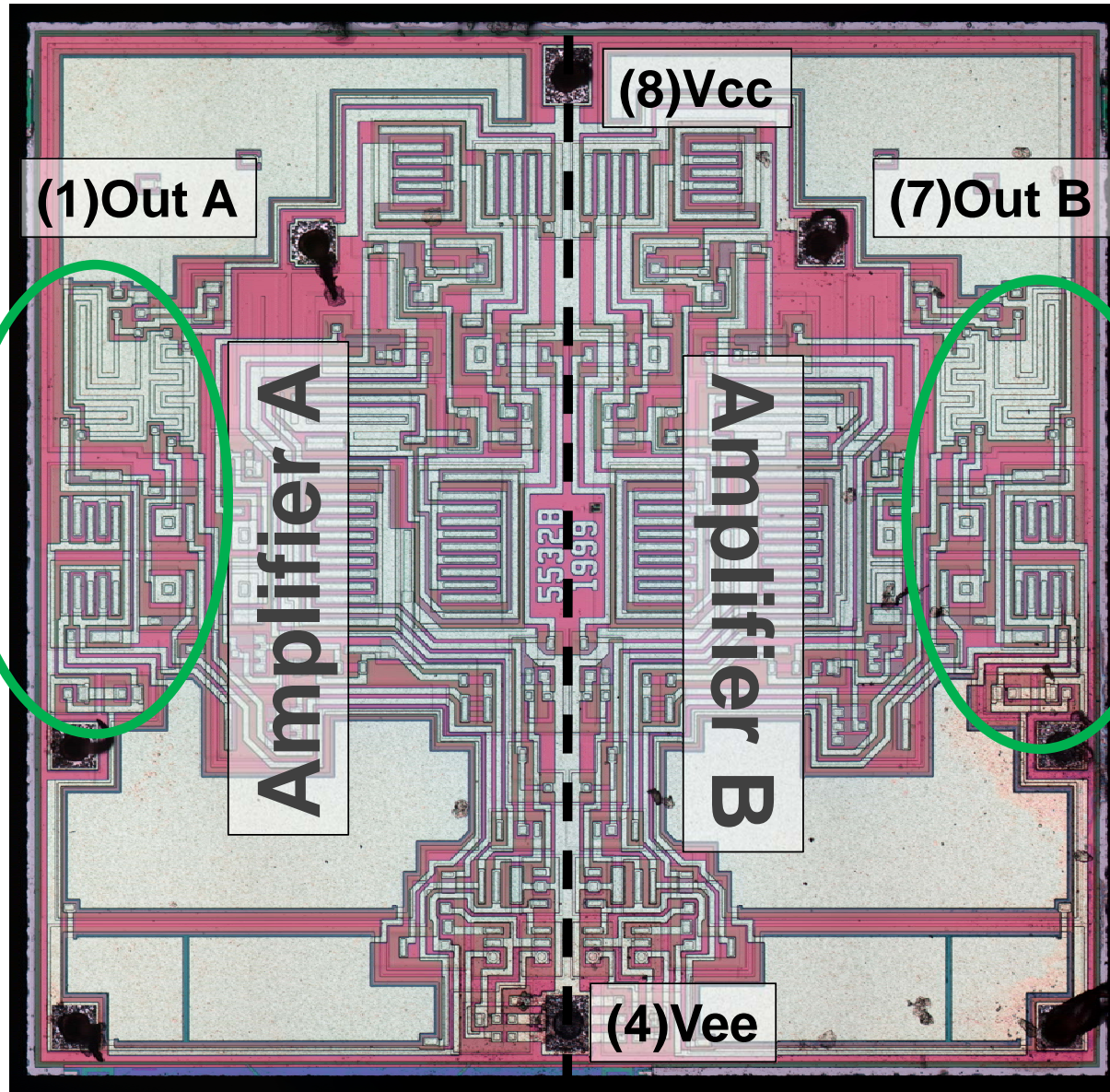
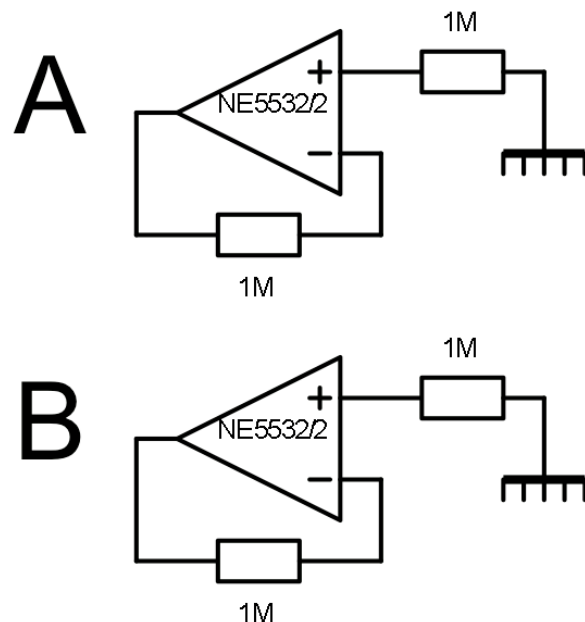
## Back to our Experiment...

NE5532 has two opamps in one package

Put  $1\text{M}\Omega$  in series with inputs to measure current...



For a perfect opamp input current = 0 so no voltage across  $1\text{M}\Omega$  resistors

Input current (nA)	Noninverting	Inverting
Chip 1 Amplifier A	180nA	190nA
Chip 1 Amplifier B	230nA	210nA
Chip 2 Amplifier A	350nA	370nA
Chip 2 Amplifier B	420nA	430nA

- Matching is good between inputs
- Matching is good between amplifiers on the same chip
- Matching is bad between chips

# Input Errors (1)

- If transistors are identical

- Differential current depends on difference in inputs

<Virtual Earth>

- Input currents (1,2) are equal = **Input Bias Current,  $I_B$**

- Collector resistors are equal

- Differential O/P Voltage = 0 for Differential I/P Voltage = 0

(Use multiple stages of differential gain then subtract currents)

$$I_{C1} + I_{C2} \approx I_0 \text{ for all } \text{In}(\pm)$$

- Emitter is connected to a constant current source

$$\Rightarrow \frac{\partial I_B}{\partial V_{IN}} = 0; \quad R_{IN} = \infty$$


$I_B$  is constant with input voltage

Even ants look different  
if you look closely!


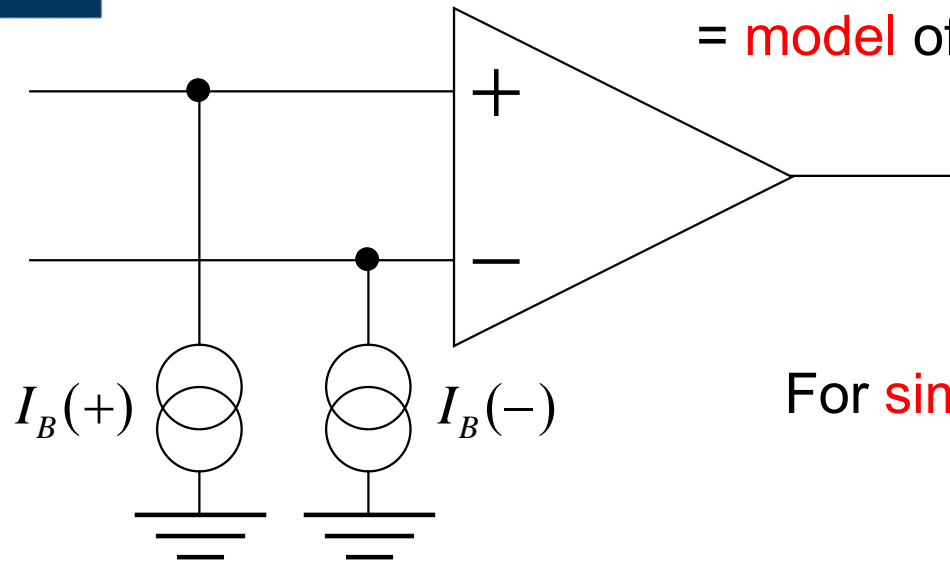
# Imperfect Opamp model (so far)

Perfect Opamp + Current sources  
= **model** of a real opamp



$$I_B(+)\approx I_B(-)$$

For **simple** opamp. (Not always)

$$I_B\equiv\frac{I_B(+)+I_B(-)}{2}\text{ (i.e. the average current)}$$

**Min 10fA**

1pA (MOSFET)

Typical

100pA (JFET)

**Max ~10μA**

10nA(Bipolar)





University  
of Glasgow

Thank you  
谢谢

INSPIRING  
PEOPLE

#UofGWorldChangers



@UofGlasgow