
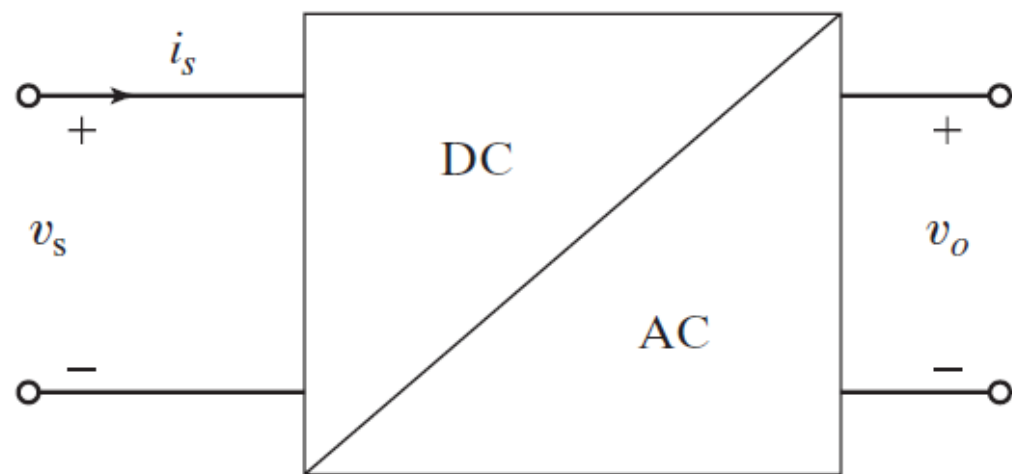


DC-AC Inverters – Fundamental Concepts

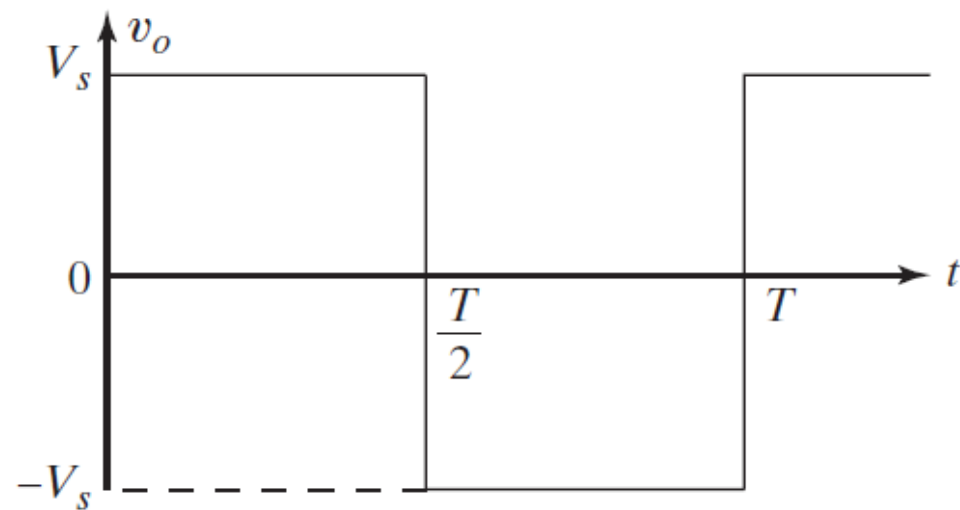
- DC-AC Converters are known as inverters
- Role is to convert a DC signal to AC
- Ideally, output should be sinusoidal.
 - In reality, they are non-sinusoidal and contain harmonics
 - This is fine for low and medium power applications
- Divided into two main types
 - Single Phase
 - Three Phase
- Semiconductor devices typically used



(a) Block diagram




(b) Output voltage

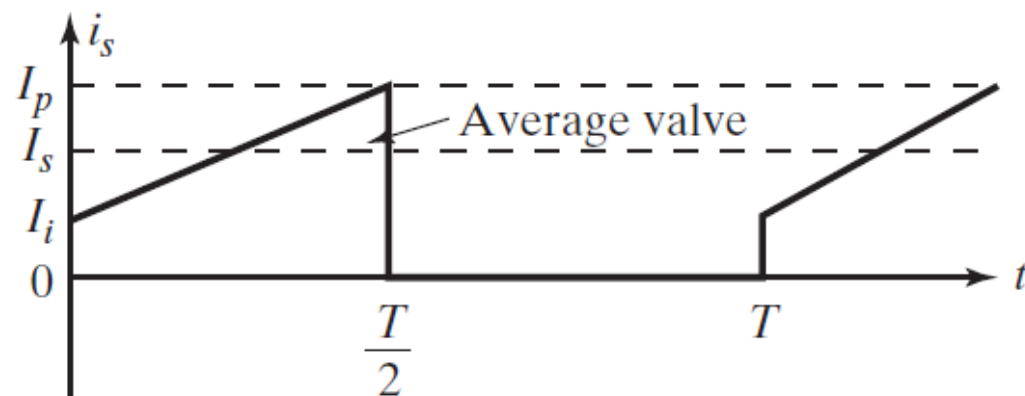

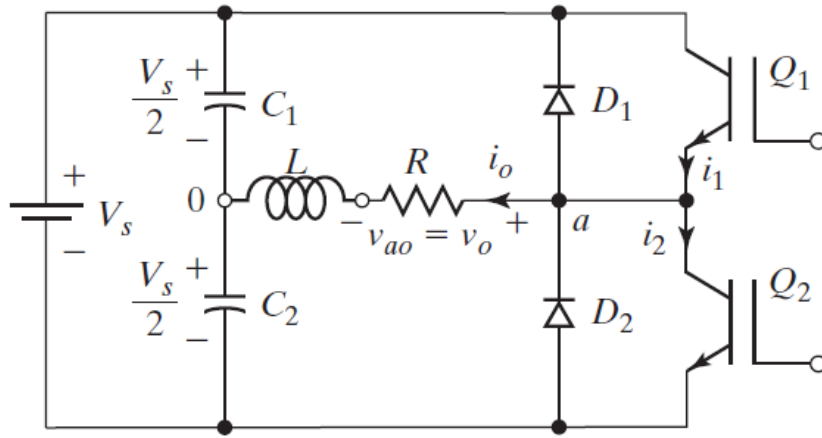
(c) Input current

Important Performance Parameters


- Power Output: $I_o V_o \cos\theta = I_o^2 R$, where I_o and V_o are the rms load voltage and current. θ is the angle of the load impedance.
- Input Power of Inverter: $P_s = I_s V_s$, where I_s and V_s are the average i/p current and voltage.
- Total Harmonic Distortion: $\frac{1}{V_{o1}} \left(\sum_0^\infty V_{on}^2 \right)^{1/2}$, where V_{o1} is rms value of fundamental component and V_{on} is rms value of nth harmonic component.



(a) Circuit

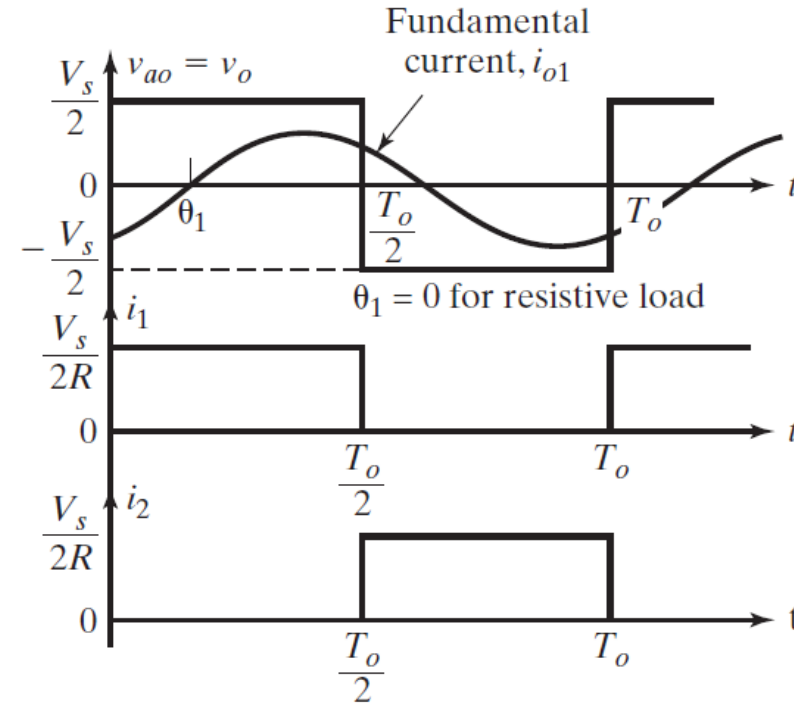

(b) Waveforms with resistive load

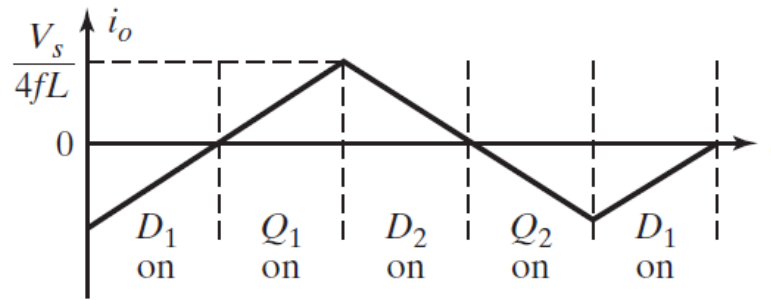

(c) Load current with highly inductive load

Parameter Equations

The root-mean-square (rms) output voltage can be found from

$$V_o = \left(\frac{2}{T_0} \int_0^{T_0/2} \frac{V_s^2}{4} dt \right)^{1/2} = \frac{V_s}{2}$$

The instantaneous output voltage can be expressed in Fourier series as

$$v_o = \frac{a_0}{2} + \sum_{n=1}^{\infty} (a_n \cos(n\omega t) + b_n \sin(n\omega t))$$

Due to the quarter-wave symmetry along the x -axis, both a_0 and a_n are zero. We get b_n as

$$b_n = \frac{1}{\pi} \left[\int_{-\pi/2}^0 \frac{-V_s}{2} \sin(n\omega t) d(\omega t) + \int_0^{\pi/2} \frac{V_s}{2} \sin(n\omega t) d(\omega t) \right] = \frac{2V_s}{n\pi}$$

which gives the instantaneous output voltage v_o as

$$\begin{aligned} v_o &= \sum_{n=1,3,5,\dots}^{\infty} \frac{2V_s}{n\pi} \sin n\omega t \\ &= 0 \quad \text{for } n = 2, 4, \dots \end{aligned} \qquad V_{o1} = \frac{2V_s}{\sqrt{2}\pi} = 0.45V_s$$

Dc supply current. Assuming a lossless inverter, the average power absorbed by the load must be equal to the average power supplied by the dc source. Thus, we can write

$$\int_0^T v_s(t) i_s(t) dt = \int_0^T v_o(t) i_o(t) dt$$

where T is the period of the ac output voltage. For an inductive load and a relatively high switching frequency, the load current i_o is nearly sinusoidal; therefore, only the fundamental component of the ac output voltage provides power to the load. Because the dc supply voltage remains constant $v_s(t) = V_s$, we can write

$$\int_0^T i_s(t) dt = \frac{1}{V_s} \int_0^T \sqrt{2}V_{o1} \sin(\omega t) \sqrt{2}I_o \sin(\omega t - \theta_1) dt = TI_s$$

where V_{o1} is the fundamental rms output voltage;

I_o is the rms load current;

θ_1 is the load angle at the fundamental frequency.

Thus, the dc supply current I_s can be simplified to

$$I_s = \frac{V_{o1}}{V_s} I_o \cos(\theta_1)$$

Example

Finding the Parameters of the Single-Phase Half-Bridge Inverter

The single-phase half-bridge inverter in slide 5 has a resistive load of $R = 2.4 \, \Omega$ and the dc input voltage is $V_s = 48 \, \text{V}$. Determine:

- (a) the rms output voltage at the fundamental frequency V_{01} ,
- (b) the output power P_0 ,
- (c) the average and peak currents of each transistor,
- (d) the peak reverse blocking voltage V_{BR} of each transistor,
- (e) the average supply current I_s ,
- (f) the THD,

Solutions

$V_s = 48 \text{ V}$ and $R = 2.4 \text{ } \Omega$.

a. $V_{01} = 0.45 * 48 = 21.6 \text{ V}$.

b. $V_0 = V_s/2 = 48/2 = 24 \text{ V}$. The output power $P_0 = V_0^2/R = 24^2/2.4 = 240 \text{ W}$.


c. The peak transistor current $I_p = 24/2.4 = 10 \text{ A}$. Because each transistor conducts for 50% duty cycle, the average current of each transistor is $I_Q = 0.5 * 10 = 5 \text{ A}$.

d. The peak reverse blocking voltage $V_{BR} = 2 * 24 = 48 \text{ V}$.


e. The average supply current: $I_s = P_0/V_s = 240/48 = 5 \text{ A}$.

f. $V_{01} = 0.45V_s$ and the rms harmonic voltage $V_h = 0.2176V_s$,
 $\text{THD} = 10.2176V_s/10.45V_s = 48.34$.


Single Phase Bridge Inverter

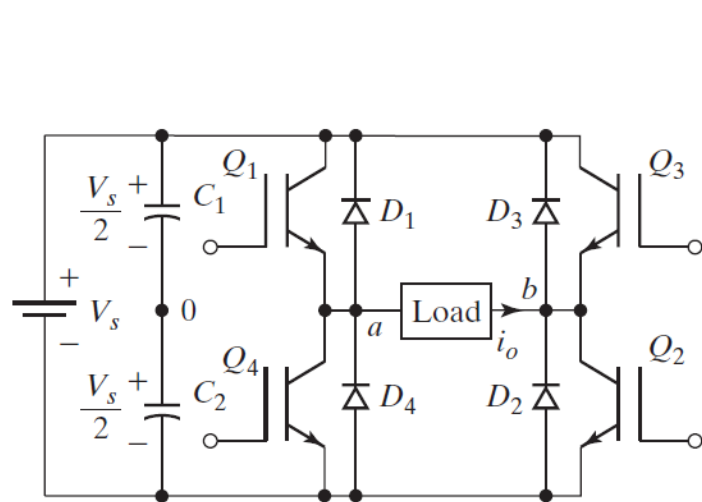

(a) Circuit

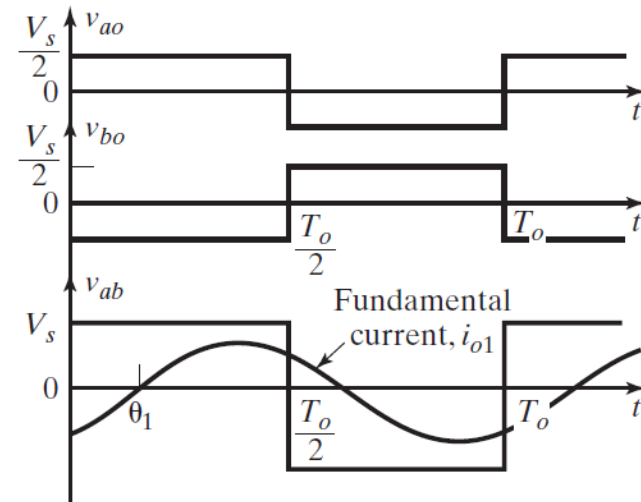

(b) Waveforms

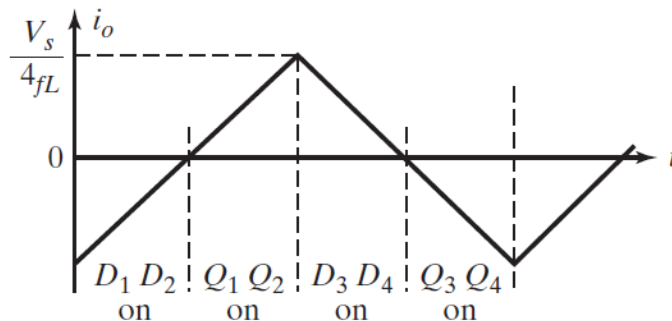

(c) Load current with highly inductive load

Switch States

Switch States for a Single-Phase Full-Bridge Voltage-Source Inverter						
State	State No.	Switch State*	v_{ao}	v_{bo}	v_o	Components Conducting
S_1 and S_2 are on and S_4 and S_3 are off	1	10	$V_S/2$	$-V_S/2$	V_S	S_1 and S_2 if $i_o > 0$ D_1 and D_2 if $i_o < 0$
S_4 and S_3 are on and S_1 and S_2 are off	2	01	$-V_S/2$	$V_S/2$	$-V_S$	D_4 and D_3 if $i_o > 0$ S_4 and S_3 if $i_o < 0$
S_1 and S_3 are on and S_4 and S_2 are off	3	11	$V_S/2$	$V_S/2$	0	S_1 and D_3 if $i_o > 0$ D_1 and S_3 if $i_o < 0$
S_4 and S_2 are on and S_1 and S_3 are off	4	00	$-V_S/2$	$-V_S/2$	0	D_4 and S_2 if $i_o > 0$ S_4 and D_2 if $i_o < 0$
$S_1, S_2, S_3,$ and S_4 are all off	5	off	$-V_S/2$ $V_S/2$	$V_S/2$ $-V_S/2$	$-V_S$ V_S	D_4 and D_3 if $i_o > 0$ D_1 and D_2 if $i_o < 0$

Parameter Equations

The rms output voltage can be found from


$$V_o = \left(\frac{2}{T_0} \int_0^{T_0/2} V_s^2 dt \right)^{1/2} = V_s$$

$$v_o = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_s}{n\pi} \sin n\omega t$$

$$V_{o1} = \frac{4V_s}{\sqrt{2}\pi} = 0.90V_s$$

$$i_0 = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_s}{n\pi \sqrt{R^2 + (n\omega L)^2}} \sin(n\omega t - \theta_n)$$

where $\theta_n = \tan^{-1}(n\omega L/R)$.


$$v_s(t)i_s(t) = v_o(t)i_o(t)$$

$$i_s(t) = \frac{1}{V_s} \sqrt{2}V_{o1} \sin(\omega t) \sqrt{2}I_o \sin(\omega t - \theta_1)$$

$$i_s(t) = \frac{V_{o1}}{V_s} I_o \cos(\theta_1) - \frac{V_{o1}}{V_s} I_o \cos(2\omega t - \theta_1)$$