



POWER ENGINEERING

#02 SINGLE-PHASE AC POWER SYSTEMS

Semester 1 – 2021/2022



电子科技大学
University of Electronic Science and Technology of China

Outline

- ❑ **RLC Components**
- ❑ **AC Voltage/Current Source**
 - Instantaneous Voltage/Current
 - Average and RMS Voltage/Current
- ❑ **AC Power**
 - Instantaneous Power
 - Average Power
- ❑ **Power Factor**
- ❑ **Voltage/Current Phasors and Phasor Diagram**
- ❑ **Component Impedance**
- ❑ **Power Triangle**
 - Apparent Power
 - Real Power
 - Reactive Power
- ❑ **Power Efficiency**

A SIMPLE ELECTRICAL POWER SYSTEM

Electrical Generator



Electrical
Transformer



Electrical Loads



lighting heating motors

- ❑ Each **component** can be represented by **an equivalent circuit** made up of a combination of simple electrical components: **voltage source, resistance, inductance and capacitance**
- ❑ With the equivalent circuit we can determine component voltages and currents, and then from this determine **POWER** related properties such as **Real Power, Apparent Power, System Efficiency and Power Factor**


BASIC PASSIVE ELEMENTS LCR



resistance (**R**) / conductance (**G**)
unit: ohm (Ω) / siemens (S)
Energy Dissipation Element !!!



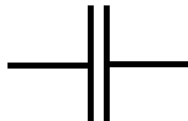inductance (**L**)
unit: henry (H)
Energy Storage Element




capacitance (**C**)
unit: farad (F)
Energy Storage Element

Voltage-Current Relationship in Time Domain


	DC	AC
Resistor Ohm's Law	$V = RI$	$v(t) = Ri(t)$
Inductor		$v(t) = L \frac{di(t)}{dt}$
Capacitor		$v(t) = \frac{1}{C} \int i(t) dt$

Behaviors of LCR in time domain


STEADY-STATE AC CIRCUIT

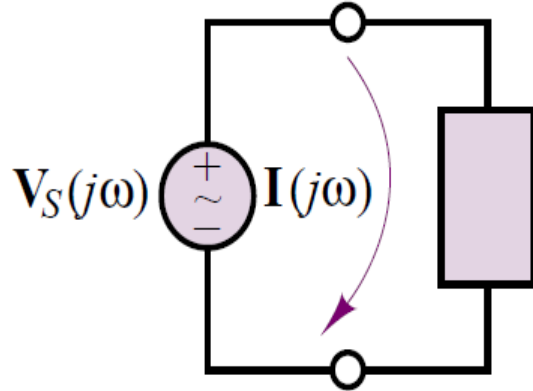

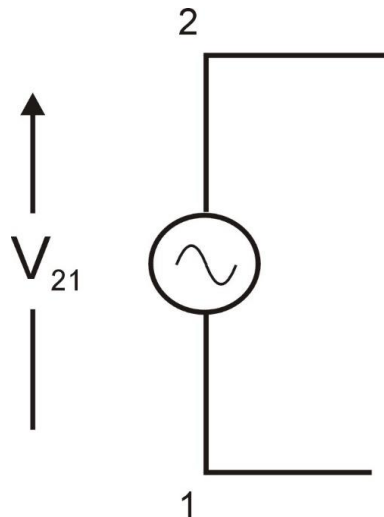- Circuit in ***Steady State***;
- ***Excitation Source V_s or I is a sinusoidal function with constant amplitude and constant frequency.***
- ***DC Circuit*** is a special case of **steady-state AC Circuit** in the case of frequency $\omega=0$



Ideal Voltage Source

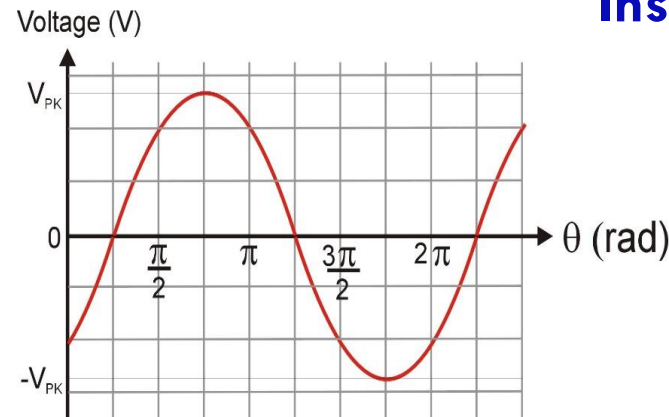

Instantaneous voltage

$$v(\theta) = V_{PK} \sin\left(\theta - \frac{\pi}{4}\right)$$


$$v(t) = V_{PK} \sin\left(\omega t - \frac{\pi}{4}\right)$$

AVERAGE VALUE

A general periodic function $y(t)$, with period T , has an **average** or **mean value** Y_{av} given by:

$$Y_{av} = \frac{1}{T} \int_0^T y(t) dt$$

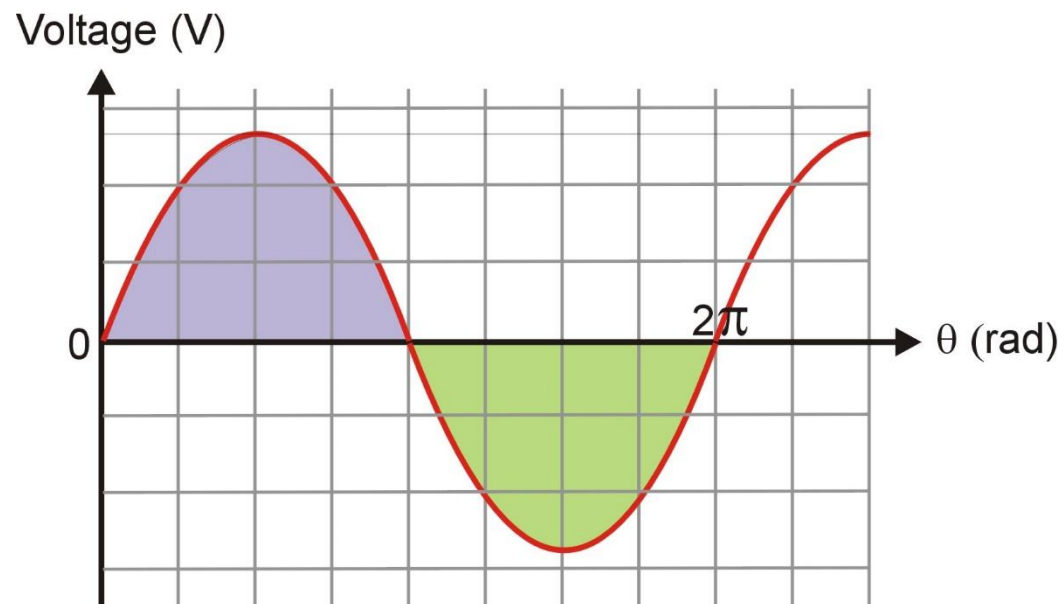The mean value of a sine or cosine function is **0**.



$$V_{av} = \frac{1}{2\pi} \int_0^{2\pi} V_{pk} \sin \theta d\theta$$

$$V_{av} = \frac{V_{pk}}{2\pi} [-\cos \theta]_0^{2\pi}$$


$$V_{av} = \frac{V_{pk}}{2\pi} [-1 + 1]$$

$$V_{av} = 0$$

EFFECTIVE OR RMS VALUE

The **Root Mean Square (RMS)** or **Effective value** of a general periodic function $y(t)$, with period T , has an effective value:
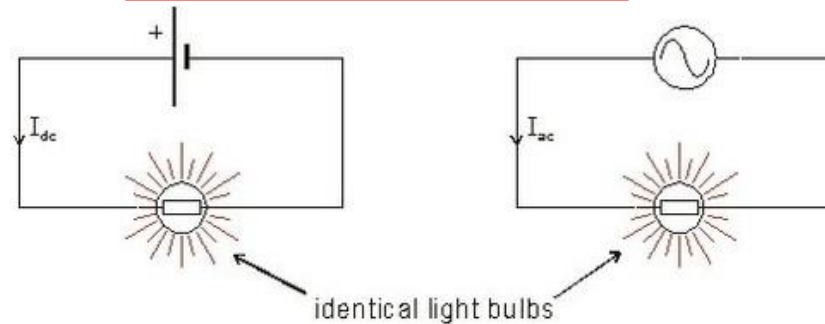
$$Y_{rms} = \sqrt{\frac{1}{T} \int_0^T y(t)^2 dt}$$



The mean value of sine/cosine is **0**, can not be used to measure the power of an AC circuit. The RMS value is also referred to as the **“heating” value** since a current passing through a pure resistor results in power being dissipated. RMS value of the AC current I_{ac} is **equivalent** to the DC current I_{dc} passing through a resistor, to produce same heat !!!

RMS VALUE & POWER DISSIPATION

Power Dissipation in resistors

$$P_{dc} = \frac{V_{dc}^2}{R} = I_{dc}^2 R$$

$$P_{av} = \frac{1}{T} \int_0^T v(t)i(t)dt = \frac{1}{T} \int_0^T \frac{v(t)^2}{R} dt$$

$$= \frac{1}{R} \left(\underbrace{\sqrt{\frac{1}{T} \int_0^T v(t)^2 dt}}_{rms} \right)^2 = \frac{v_{rms}^2}{R}$$

RMS
voltage



$$= R \left(\underbrace{\sqrt{\frac{1}{T} \int_0^T i(t)^2 dt}}_{rms} \right)^2 = i_{rms}^2 R$$

RMS
Current



Instantaneous Power

$$p(t) = v(t)i(t)$$

Average Power

$$P_{av} = \frac{1}{T} \int_0^T p(t)dt = \frac{1}{T} \int_0^T v(t)i(t)dt$$

$$v_{rms} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt}$$

$$i_{rms} = \sqrt{\frac{1}{T} \int_0^T i(t)^2 dt}$$

RMS VALUE OF A SINUSOIDAL WAVEFORM

$$V_{rms} = \sqrt{\left[\frac{1}{\tau} \int_0^{\tau} v^2(\theta) d\theta \right]} = \sqrt{\left[\frac{1}{2\pi} \int_0^{2\pi} V_{pk}^2 \sin^2 \theta d\theta \right]}$$


$$= \sqrt{\left[\frac{V_{pk}^2}{2\pi} \int_0^{2\pi} \left[\frac{1}{2} (1 - \cos 2\theta) \right] d\theta \right]}$$

$$V_{rms} = \sqrt{\left[\frac{V_{pk}^2}{2\pi} \left[\frac{1}{2} \left(\theta - \frac{1}{2} \sin 2\theta \right) \right]_0^{2\pi} \right]} = \sqrt{\left[\frac{V_{pk}^2}{2\pi} \left[\frac{2\pi}{2} - 0 - 0 + 0 \right] \right]} = \frac{|V_{pk}|}{\sqrt{2}}$$


$$V_{rms} = \frac{|V_{pk}|}{\sqrt{2}}$$

Resistance (Power Dissipation > 0)

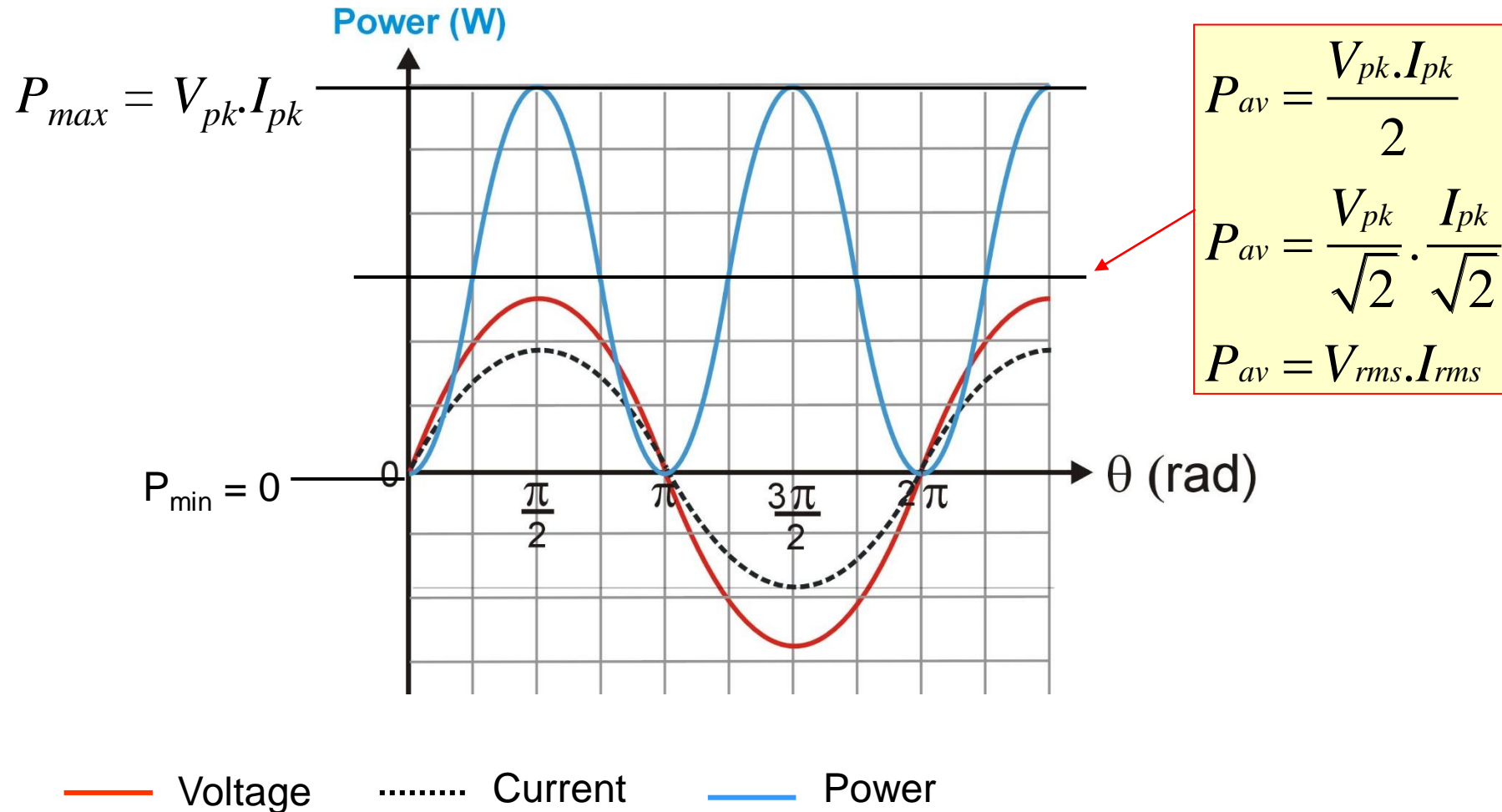Instantaneous Power: $p(t) = v(t) \times i(t)$




Inductance (Power Dissipation = 0)

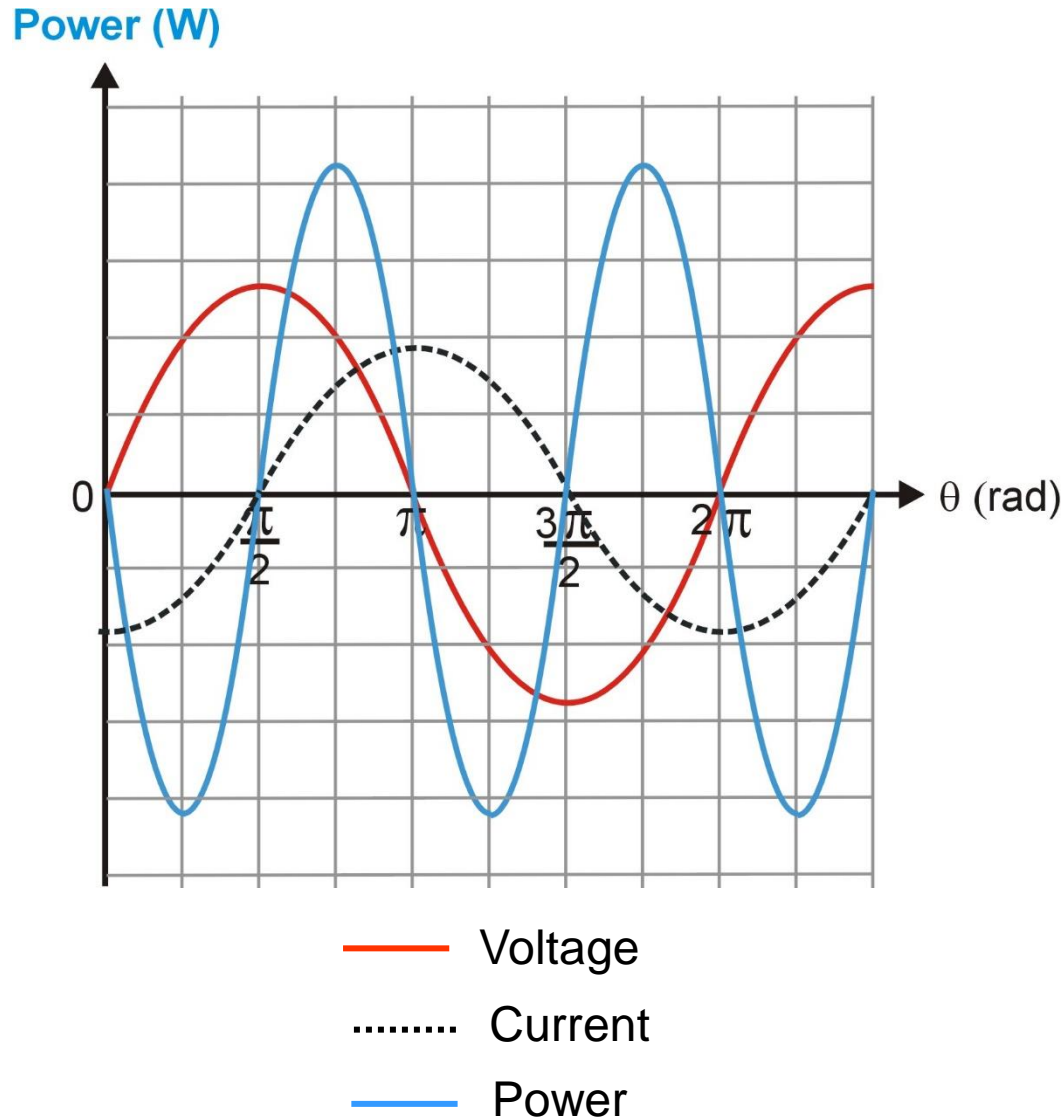

$$P_{av} = 0$$

The power simply oscillates between the inductor and the supply at **twice the supply frequency**

Capacitance (Power Dissipation = 0)

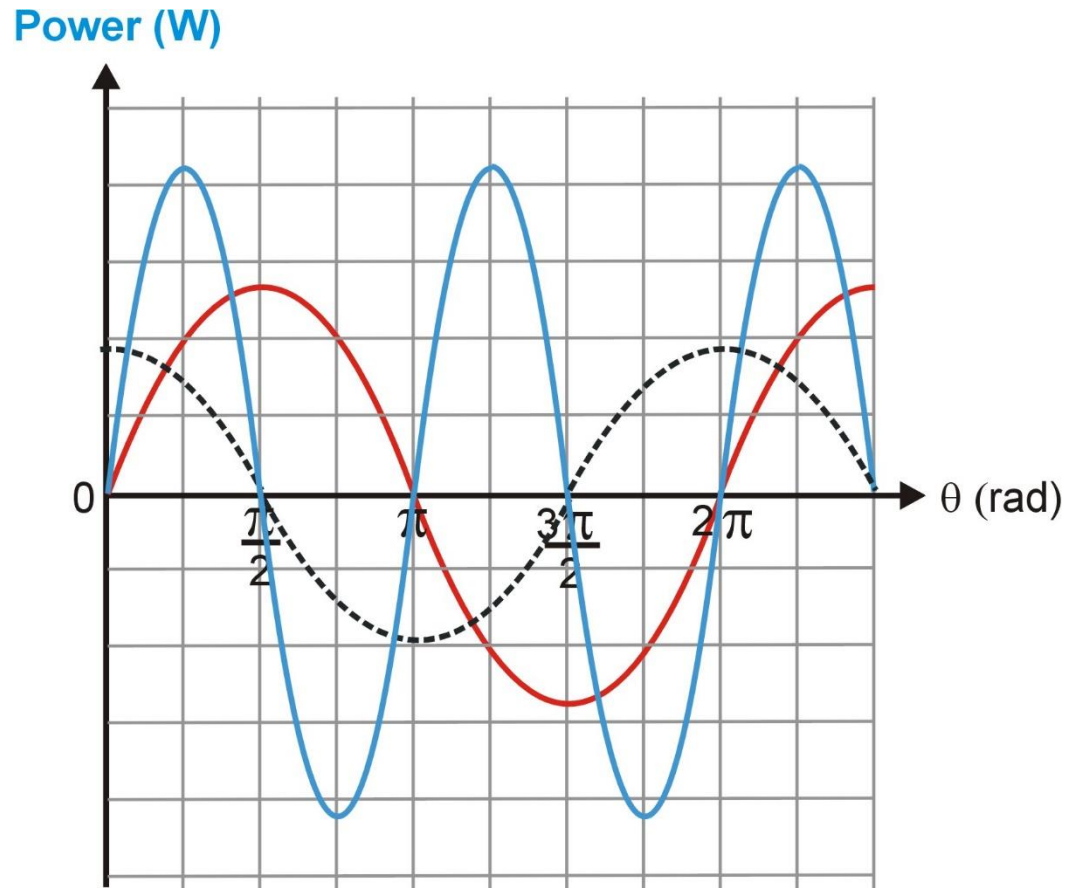


— Voltage
..... Current
— Power

$$P_{av} = 0$$

The power simply oscillates between the capacitor and the supply at **twice the supply frequency**

Complex Load (combination of R, L and C)

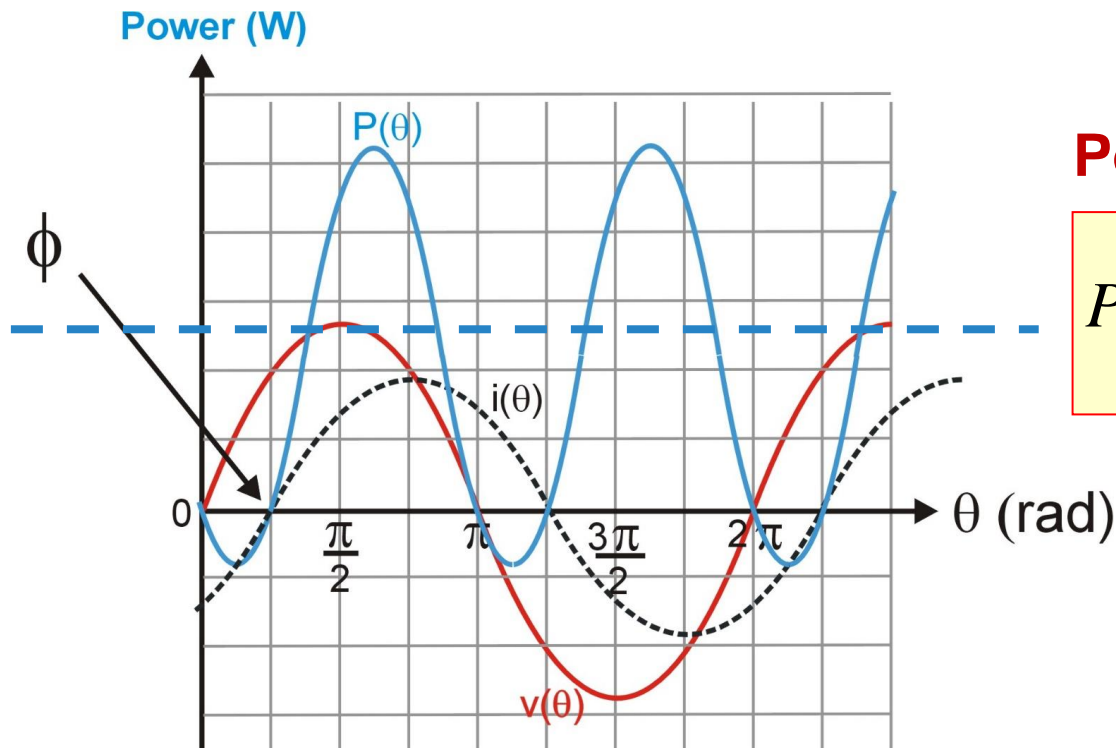A general expression for average power where the current lags (or leads) the voltage by **angle ϕ**



Power Dissipation

$$P_{av} = \frac{1}{\tau} \int_0^{\tau} v(\theta) \cdot i(\theta - \phi) d\theta$$

Complex Load (combination of R, L and C)

$$\begin{aligned} P_{av} &= \frac{1}{\pi} \int_0^{\pi} (V_{pk} \cdot \sin \theta) \cdot (I_{pk} \cdot \sin(\theta - \phi)) d\theta \\ &= \frac{V_{pk} \cdot I_{pk}}{\pi} \left[\int_0^{\pi} (\sin^2 \theta \cdot \cos \phi - \sin \theta \cdot \cos \theta \cdot \sin \phi) d\theta \right] \\ &= \underbrace{\left[\frac{V_{pk} \cdot I_{pk} \cdot \cos \phi}{\pi} \int_0^{\pi} \sin^2 \theta d\theta \right]}_{V_{rms} \cdot I_{rms} \cdot \cos \phi} - \underbrace{\left[\frac{V_{pk} \cdot I_{pk} \cdot \sin \phi}{\pi} \int_0^{\pi} (\sin \theta \cdot \cos \theta) d\theta \right]}_{=0} \\ &= V_{rms} \cdot I_{rms} \cdot \cos \phi \end{aligned}$$

Power Dissipation

$$P_{av} = V_{rms} \cdot I_{rms} \cdot \cos \phi$$

POWER FACTOR

The average power dissipated by an AC load is dependent on the cosine of the angle of the impedance, the term $\cos \phi$ is referred to as the power factor (**pf**).:



$$\text{pf} = \cos \phi$$

Note: The **power factor** is equal to **0** for a purely inductive or capacitive load; and is equal to **1** for a purely resistive load; in every other case,

$$0 < \text{pf} < 1$$

Power factor is **dimensionless**, a measure of how effectively the load draws the real power.

An Example

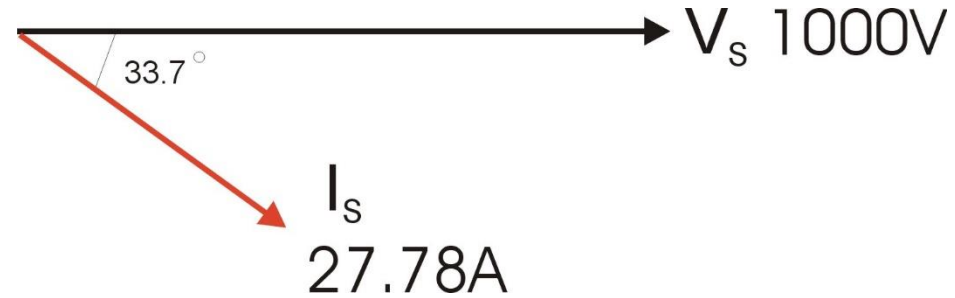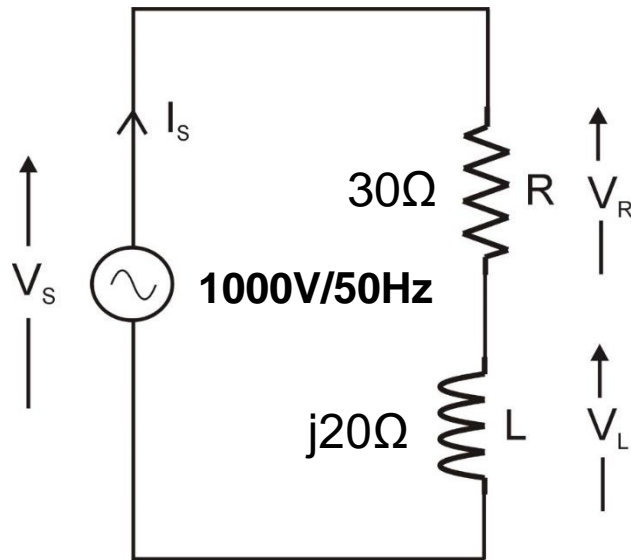

$$I_s = \frac{V_s}{(30 + j20)\Omega} = \frac{1000\angle 0^\circ}{36.1\angle 33.7^\circ}$$
$$= 27.78\angle -33.7^\circ$$

$$P_{av} = V_{rms} \cdot I_{rms} \cdot \cos \phi = I_{rms}^2 R$$


$$P_{av} = 1000 \times 27.78 \times \cos(33.7^\circ)$$

$$P_{av} = 23112W$$

$$\text{pf} = \cos(33.7^\circ) \approx 0.832$$

COMPLEX OHM'S LAW

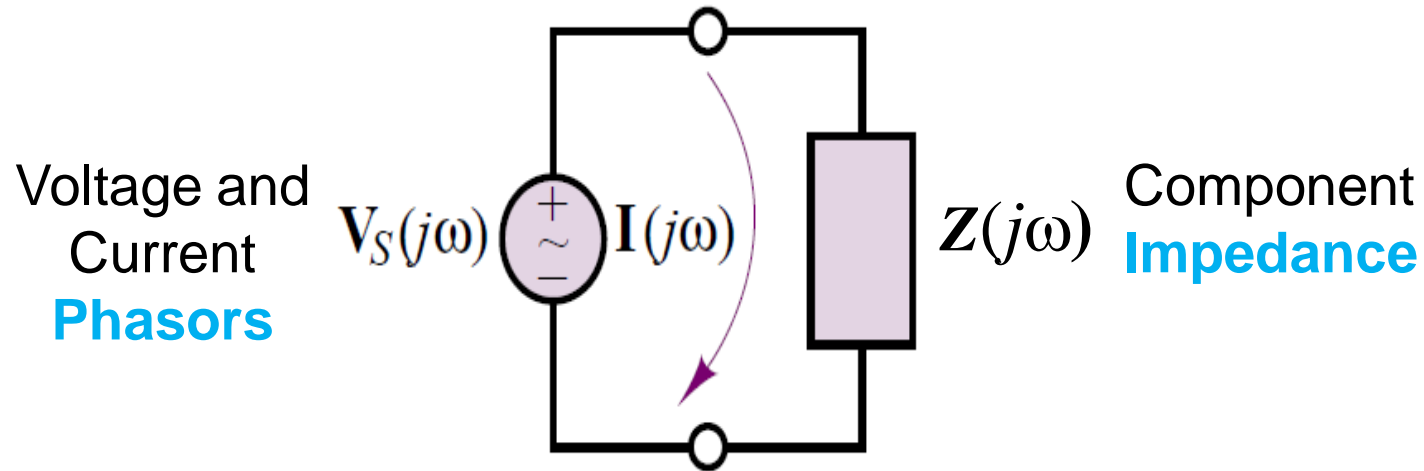Phasor and **Impedance** are introduced to simplify AC circuit analysis, without complicated calculus (differential equations) of trigonometric function.



$$Z(j\omega) = \frac{V_S(j\omega)}{I(j\omega)}$$

PHASOR

Phasor is only used to express **sinusoidal voltage** or **current** variables with complex number for mathematical convenience. **No Real Physical Significance.**

Any sinusoidal signal may be represented in one of two ways:

□ Instantaneous form in the time domain:


$$v(t) = V_m \cos(\omega t + \varphi_1); \quad i(t) = I_m \cos(\omega t + \varphi_2)$$

□ Phasor form:

$$\mathbf{V}(j\omega) = \frac{V_m}{\sqrt{2}} e^{j\varphi_1} = \underbrace{\frac{V_m}{\sqrt{2}}}_{\text{RMS value}} \angle \varphi_1; \quad \mathbf{I}(j\omega) = \frac{I_m}{\sqrt{2}} e^{j\varphi_2} = \underbrace{\frac{I_m}{\sqrt{2}}}_{\text{RMS value}} \angle \varphi_2$$

Note: $j\omega$ in the notation $\mathbf{V}(j\omega)$, indicating $e^{j\omega t}$ dependence of the phasor.

PHASOR DIAGRAM

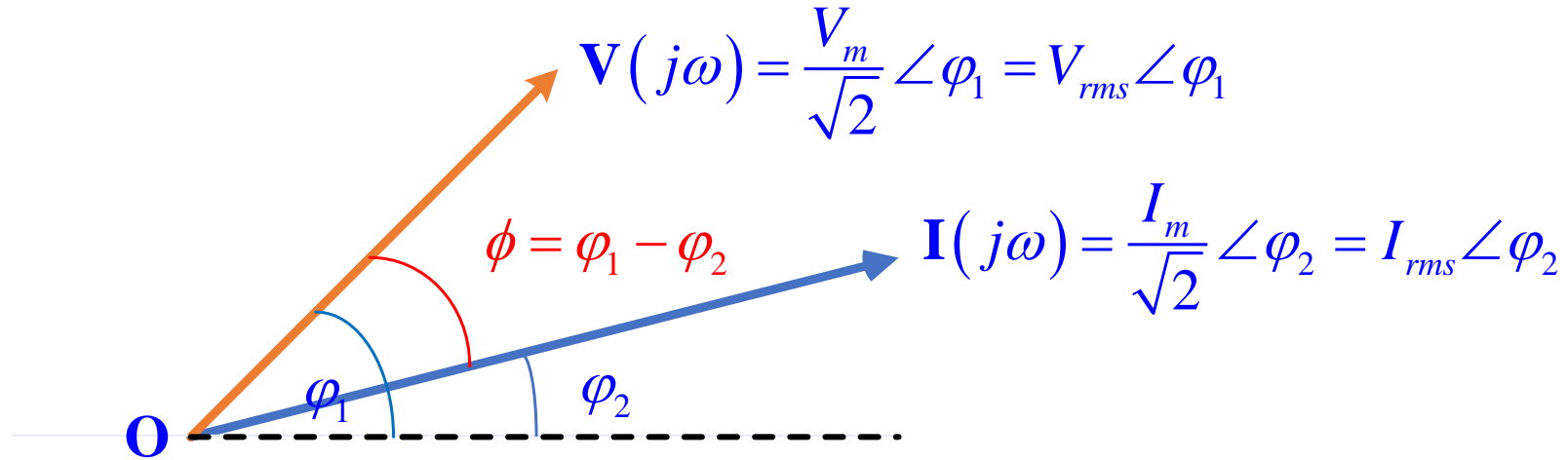

IMPEDANCE


$$\mathbf{Z}(j\omega) = \frac{\mathbf{V}(j\omega)}{\mathbf{I}(j\omega)} = \frac{V_{rms}}{I_{rms}} \angle \phi = R + jX = |Z|(\cos \phi + j \sin \phi)$$

IMPEDANCE

Component	Voltage/Current Phase Relationship	Complex Impedance (Cartesian)	Complex Impedance (Polar)
Resistance	Voltage and Current are in phase	$Z_R = R + j0$	$Z_R = R \angle 0^\circ$
Inductance	Current lags the Voltage by 90°	$Z_L = 0 + j\omega L$	$Z_L = \omega L \angle 90^\circ$
Capacitance	Current leads the Voltage by 90°	$Z_C = 0 - j/(\omega C)$	$Z_C = \frac{1}{\omega C} \angle -90^\circ$

Note: The REACTANCE of an Inductance $X_L = \omega L$
The REACTANCE of a capacitance $X_C = 1/(\omega C)$

An EXAMPLE OF AC CIRCUIT ANALYSIS

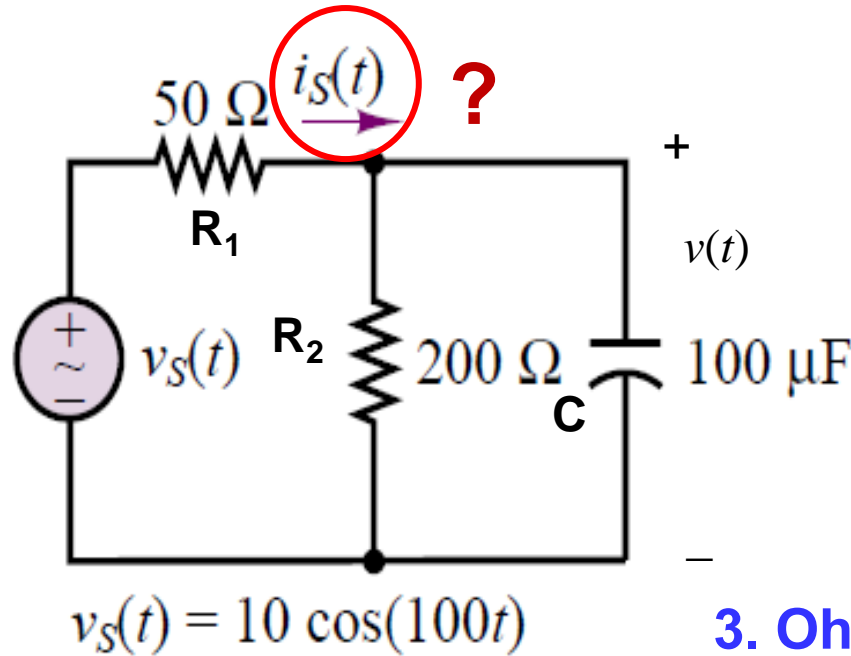

2. Impedance

$$Z_{R1} = 50\Omega$$

$$Z_{R2} = 200\Omega$$

$$Z_C = \frac{1}{j\omega C} = -j100\Omega$$

1. Source Phasor

$$v_S(t) = 10 \cos(100t)$$

$$\omega = 100 \text{ rad/t}$$

Time
Domain

$$\mathbf{V}_S(j\omega) = \left(10 / \sqrt{2}\right) \angle 0^\circ$$

3. Ohm's Law

$$\mathbf{I}_S = \frac{\mathbf{V}_S}{Z_{R1} + Z_{R2} \parallel Z_C} = \frac{\mathbf{V}_S}{R_1 + \frac{R_2}{1 + j\omega C R_2}}$$


$$= \left(0.083 / \sqrt{2}\right) \angle 0.727 \text{ A}$$

4. Instantaneous value

$$i_s(t) = 0.083 \cos(100t + 0.727) \text{ A}$$

A PRACTICE QUESTION

Determine the values of V_R and V_L

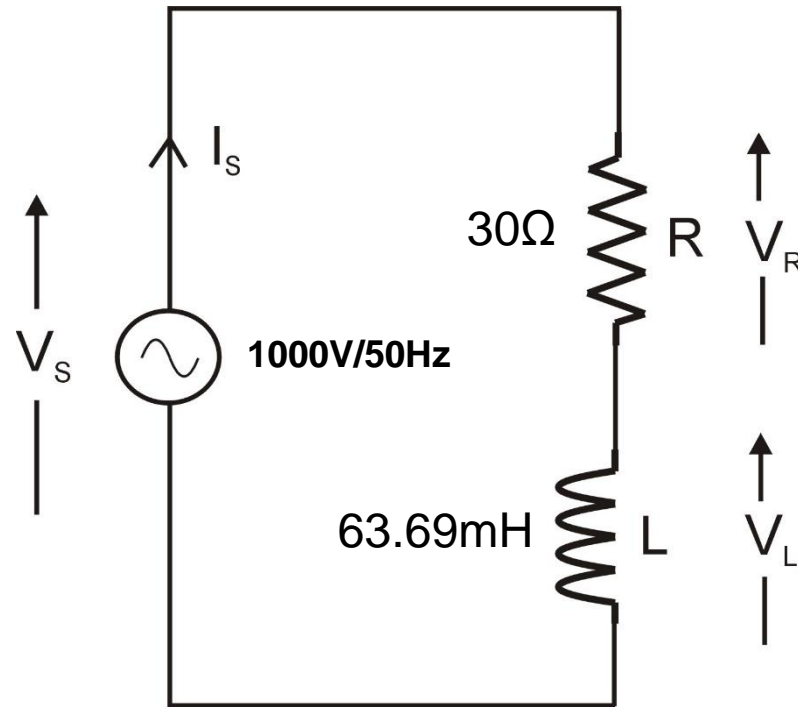

Note: 1000V is RMS voltage!

POWER TRIANGLE

$$\mathbf{S} = \tilde{\mathbf{V}}\tilde{\mathbf{I}}^* \quad \text{Complex Power} \quad * \text{ Conjugate}$$

$$\begin{aligned}\mathbf{S} &= V_{rms} I_{rms} \cos \phi + j V_{rms} I_{rms} \sin \phi \\ &= P + jQ\end{aligned}$$

Apparent power :


$$S = \sqrt{P^2 + Q^2} = V_{rms} I_{rms}$$

Real (average) power :


$$P = P_{av} = V_{rms} I_{rms} \cos \phi = S \cos \phi$$

Reactive power :

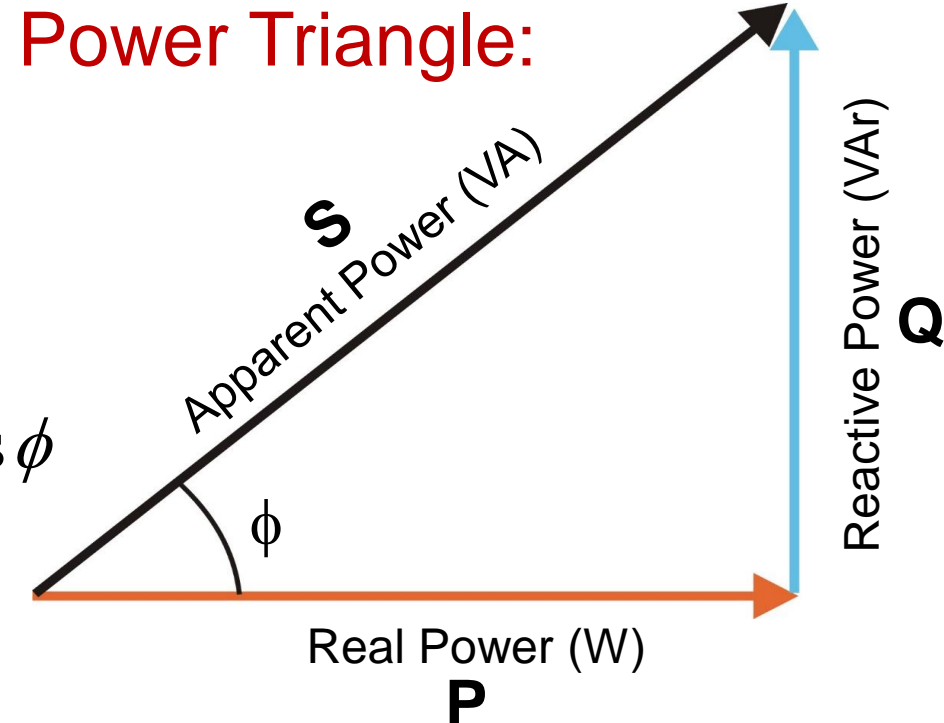
$$Q = V_{rms} I_{rms} \sin \phi = S \sin \phi$$




INDUCTIVE LOAD

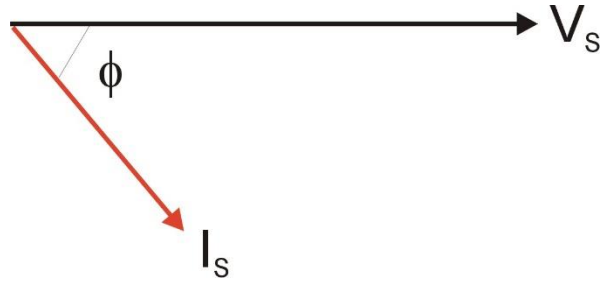

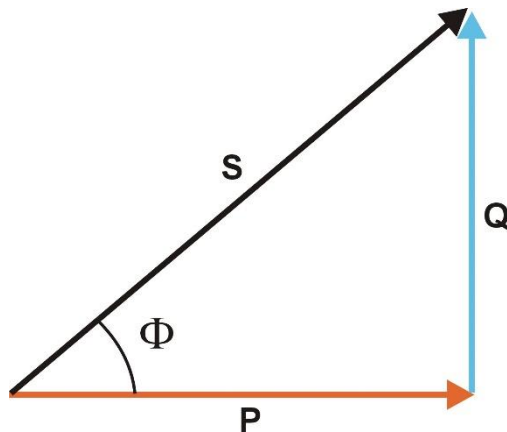
If the Current **LAGs** the voltage by angle ϕ (indicating that the load is inductive + resistive) then Reactive Power (Q) is deemed to be Positive and is termed **ABSORBING VAR's**




CAPACITIVE LOAD

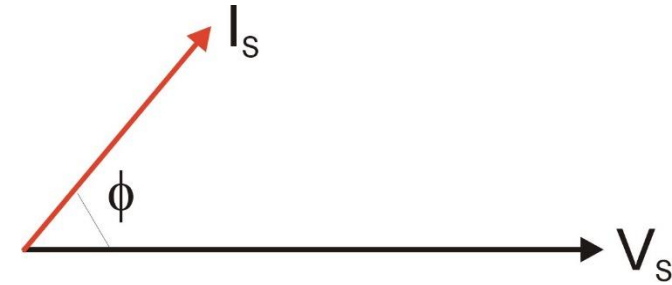

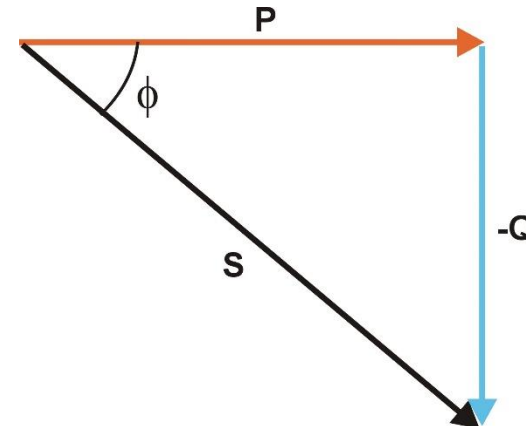If the Current **LEADS** the voltage by angle ϕ (indicating that the load is capacitive + resistive) then Reactive Power (Q) is deemed to be Negative and is termed **GENERATING VAR's**



POWER EFFICIENCY IN EPS

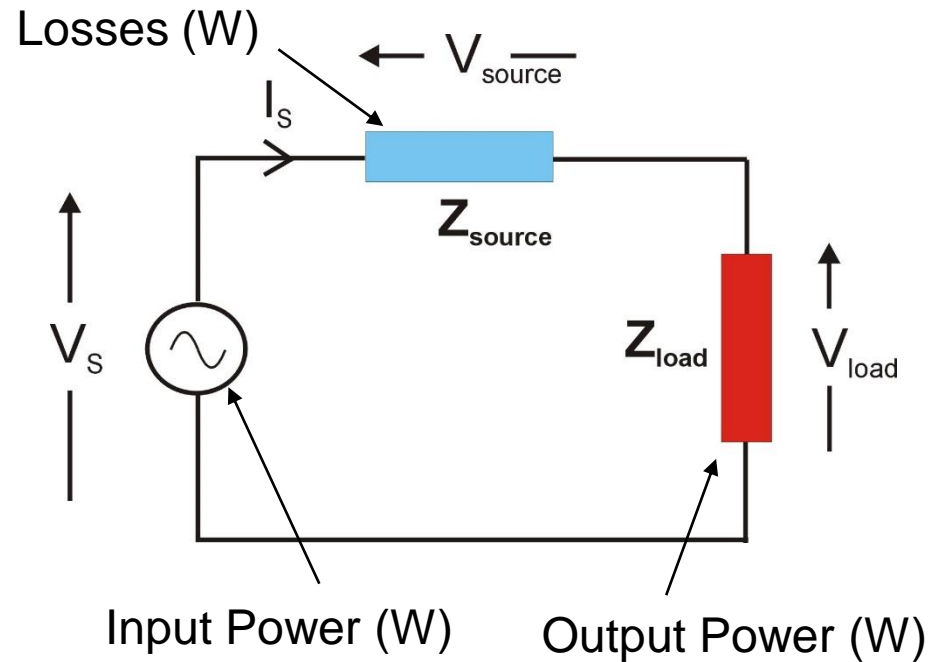


$$\begin{aligned}\text{Efficiency} &= \frac{\text{Output Power (W)}}{\text{Input Power (W)}} \times 100\% \\ &= \frac{\text{Output Power (W)}}{\text{Output Power (W)} + \text{Losses (W)}} \times 100\%\end{aligned}$$

Note that Input & Output Power are **REAL Powers (W)**

AN EXAMPLE

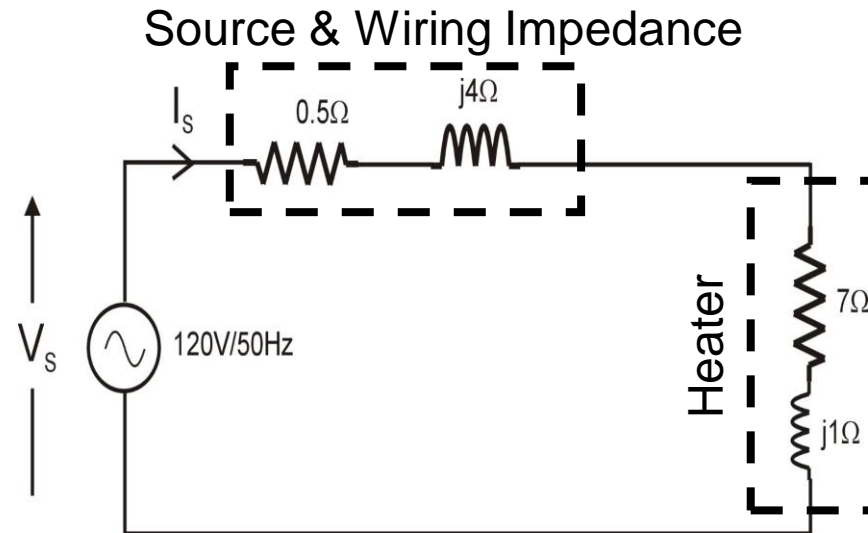The heating system for a remote monitoring station consists of a diesel generator which outputs 120V/50Hz connected to a Heater:



1. The **total circuit impedance Z_T**
2. The supply current I_s
3. A phasor diagram indicating V_s and I_s
4. **Apparent Power, Real Power, Reactive Power and Power Factor** at the power supply
5. The Heater output power
6. **Power Efficiency** of the heating system

Consider:

$$V = V_{rms} \angle \theta_V$$

Where θ_V is the phase angle of the voltage, and

$$I = I_{rms} \angle \theta_I$$

Where θ_I is the phase angle of the current.

We could say that:

$$S = VI = V_{rms} \angle \theta_V \times I_{rms} \angle \theta_I = V_{rms} I_{rms} \angle (\theta_V + \theta_I)$$

Let's now do the same calculation with the complex conjugate of I (I^*)

$$S = VI^* = V_{rms} \angle \theta_V \times I_{rms} \angle -\theta_I = V_{rms} I_{rms} \angle (\theta_V - \theta_I)$$



Which is correct ?

P is the real part of S, which is $S \cdot \cos(\theta)$, where θ is the difference in phase angle between V and I ($\theta_V - \theta_I$).


1. $S = VI^*$ will give the correct real part.
2. $S = VI$ will give the wrong real part.
 - Therefore to calculate the correct Real Power we must use $S = VI^*$. [You could use the complex conjugate of V but it is convention to use I^*]

Hence, when we calculate Q we use I^* and the angle in the power triangle will be positive for a load which has inductive reactance. (The opposite to the power factor angle)

SOLUTION TO EXAMPLE QUESTION

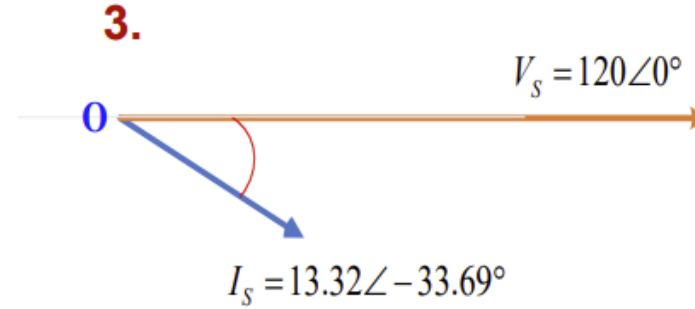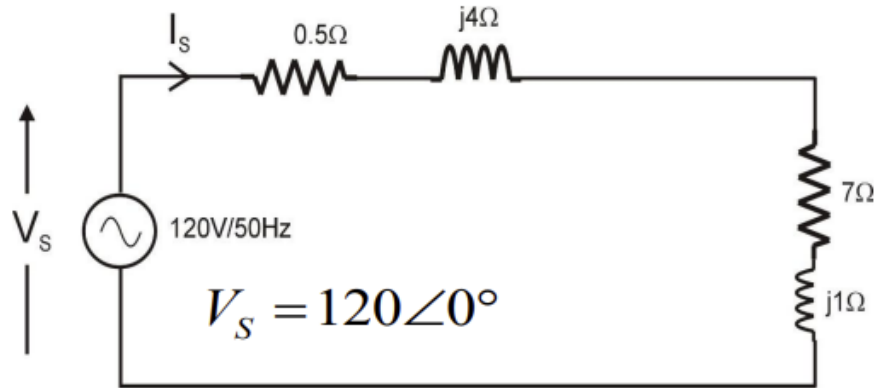

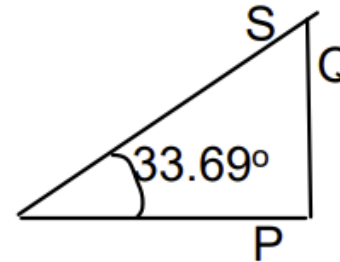1. $Z_T = (0.5 + j4 + 7 + j1)\Omega = 7.5\Omega + j5\Omega = 9.01\angle 33.69^\circ$
2. $I_S = V_S / Z_T = 120\angle 0^\circ / 9.01\angle 33.69^\circ = 13.32\angle -33.69^\circ$
4. $S = V_{S_{rms}} \times I_{S_{rms}}^* = 120 \times 13.32 \approx 1598 \text{ VA}$
 $P = S \cos(33.69^\circ) = I_S^2 \times 0.832 = 1329.6 \text{ W}$
 $Q = S \sin(33.69^\circ) = I_S^2 \times 0.555 = 98.42 \text{ Var}$
5. $P_{out} = I_S^2 \times 7 \approx 1242 \text{ W}$
6. $\eta = P_{out} / P = 93.4\%$





#02 Single-Phase AC Power Systems