



University  
of Glasgow

# Electronic System Design 3


## Lecture 11.3: Photodiode Transimpedance Amplifier (TIA)

Dr Duncan Bremner





### Current amplifier (photodiode amp)

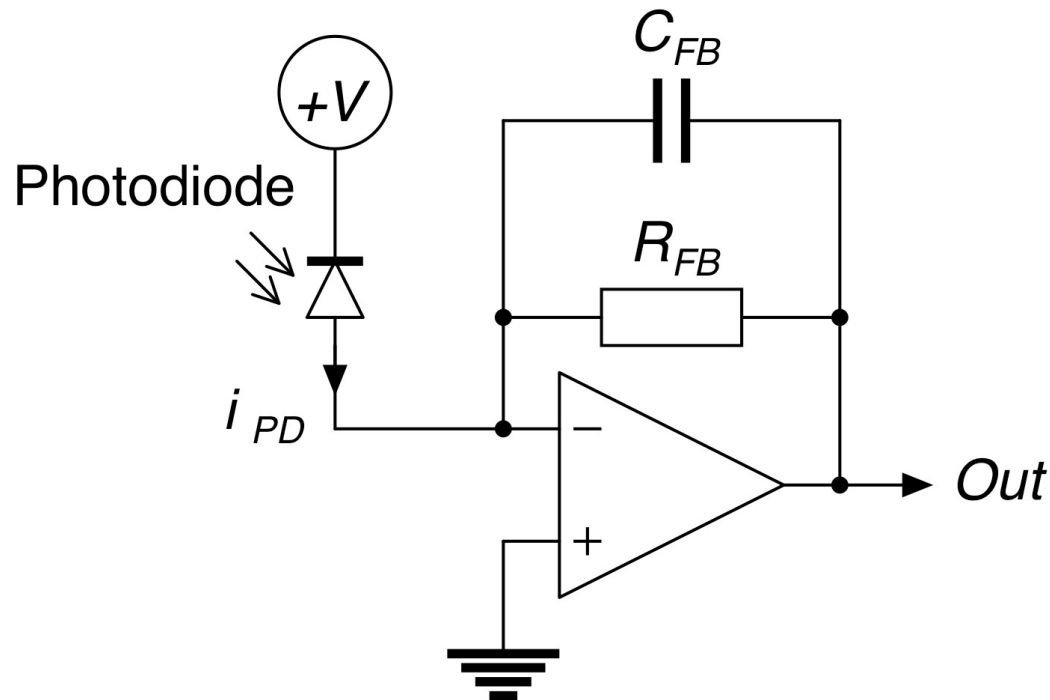

Notes:


- Photodiode is  $\approx$  constant current source
- $C_{FB}$  is **necessary** for stability: use 1pF  $\infty$  (Ignore for this analysis)
- Photodiode has full shot noise



Re-draw to include all  
noise sources


## Design 3 (2)

( $R_{FB}$  thermal)

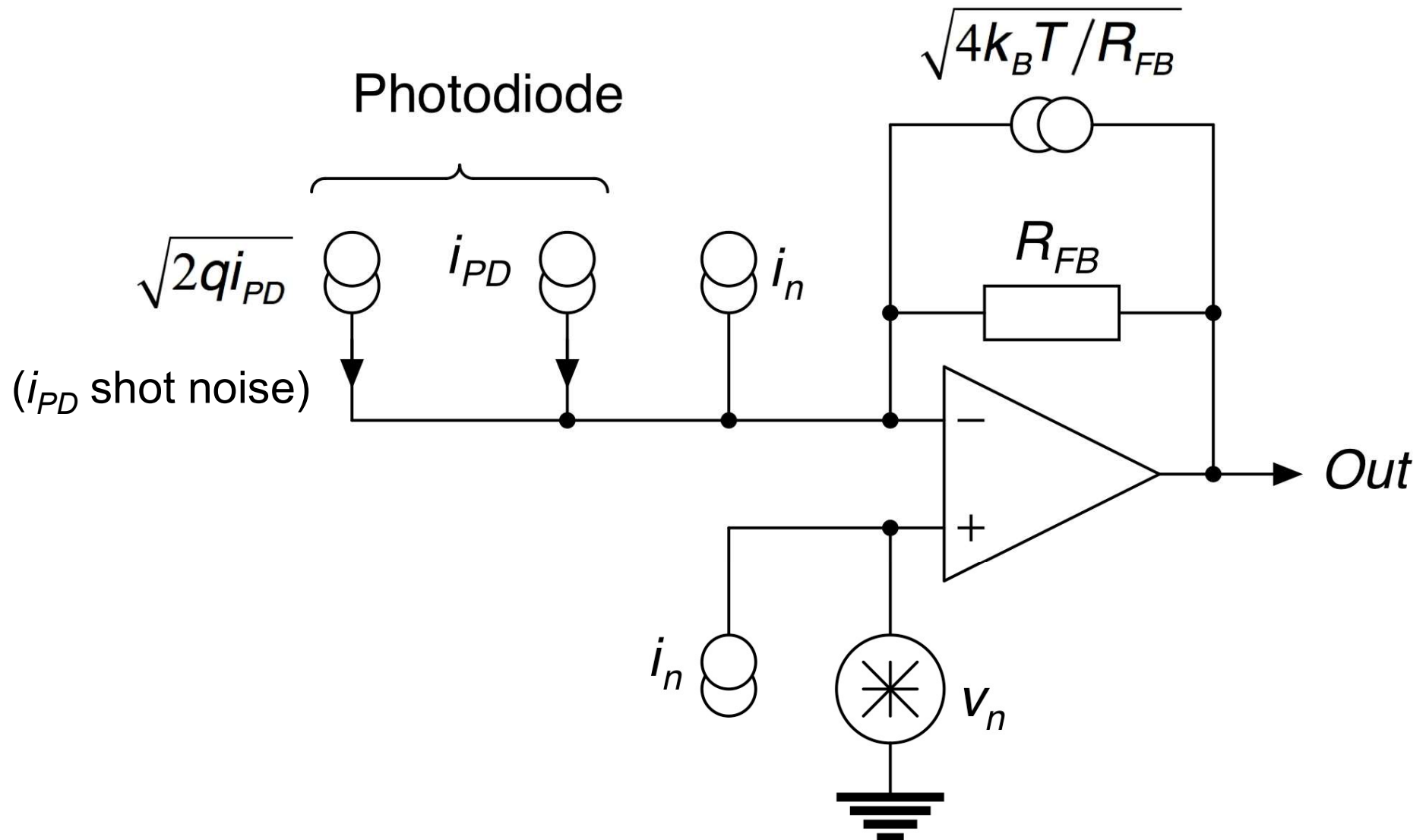


Re-draw to include all  
noise sources

## Design 3 (2)

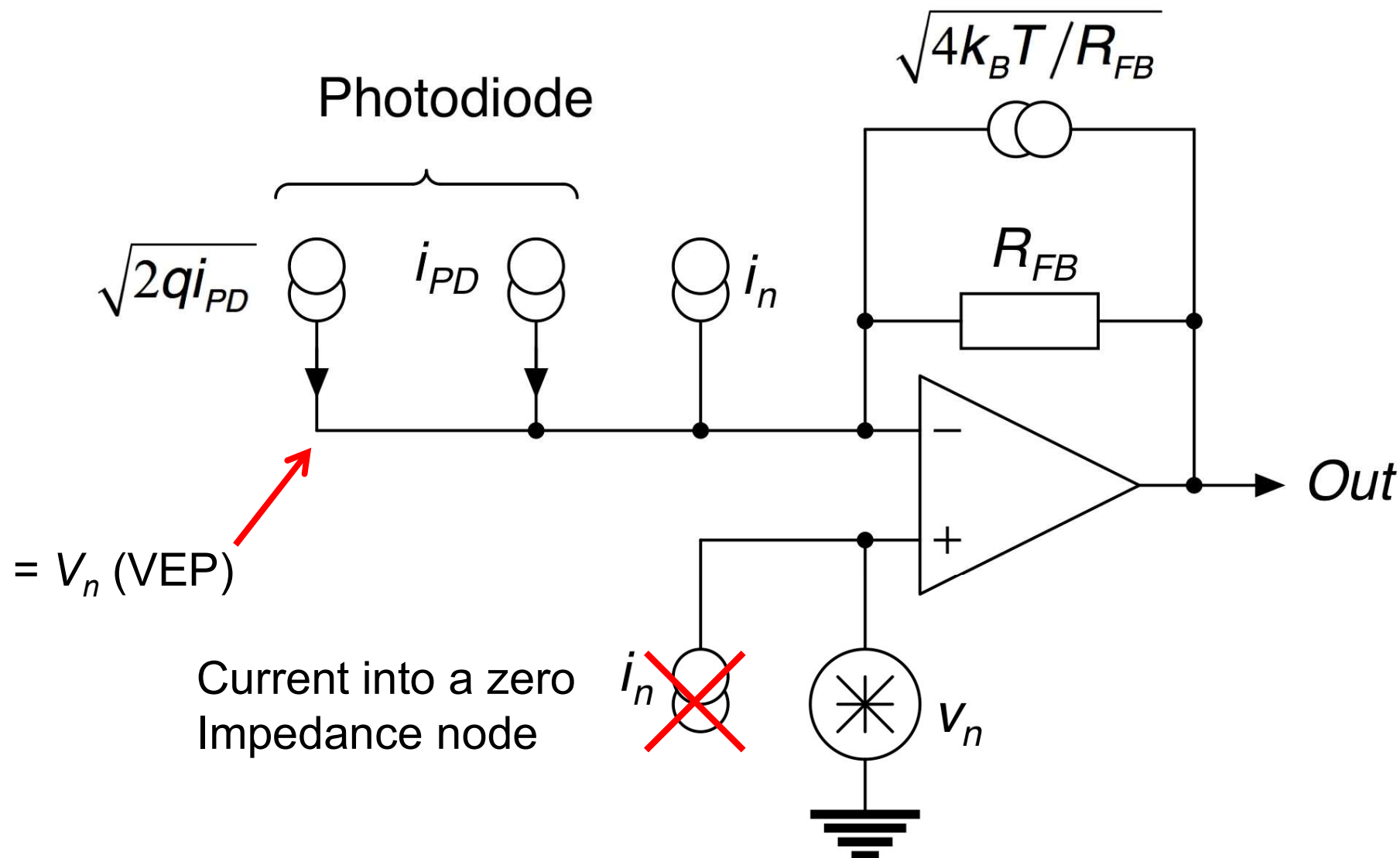

Re-draw to include all  
noise sources

## Design 3 (2)

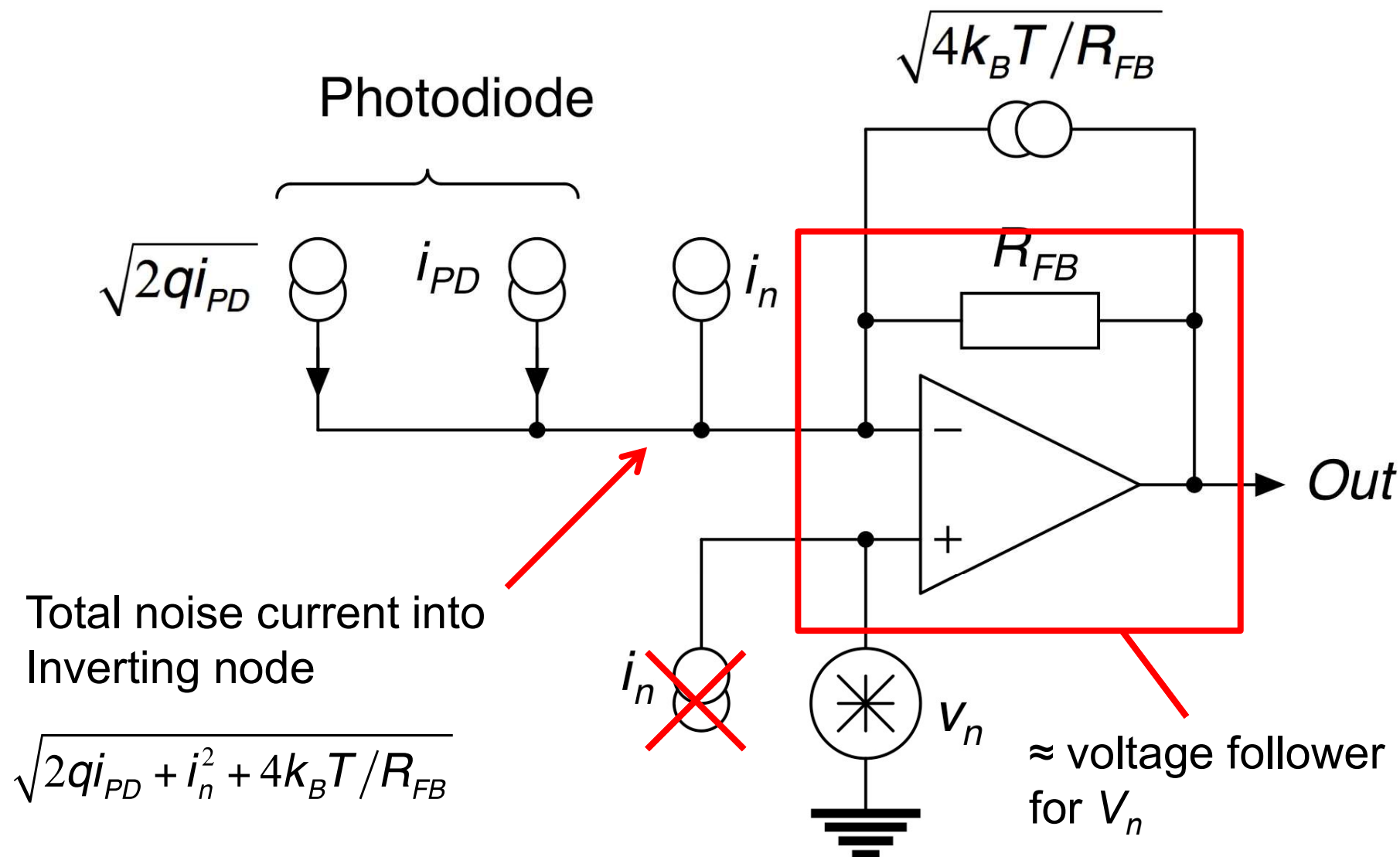



Hence total noise RTI is total current noise through  $R_{FB} + v_n / R_{FB}$   
Added as uncorrelated noise sources:

$$i_n(RTI) = \sqrt{\frac{v_n^2}{R_{FB}^2} + 2qi_{PD} + i_n^2 + \frac{4k_B T}{R_{FB}}}$$

As the shot noise is the fundamental limit for the measurement of photodiode current, for low noise we require that

$$2qi_{PD} \gg \frac{v_n^2}{R_{FB}^2} + i_n^2 + \frac{4k_B T}{R_{FB}}$$

Amplifier noise

Resistor noise

$$\text{Hence } R_{FB} \gg \frac{4k_B T}{2qi_{PD}}$$

$$\text{For } i_{PD} = 100\text{nA}; \text{ then } R_{FB} \gg 510\text{k}\Omega$$

# Noise Analysis: Summary

Convert detailed circuit to noisy amplifier model

Uncorrelated noise sources add as sum of squares  $v_{tot} = \sqrt{v_1^2 + v_2^2 + \dots + v_n^2}$

**Largest** source will dominate :  $\sqrt{2^2 + 1^2} = 2.23$       -> Intuition!

Voltage = noise spectral density  $\cdot \sqrt{\text{bandwidth}}$

Noise Figure =  $20 \cdot \log_{10} \frac{v_{ni}}{v_{Th}}$





University  
of Glasgow

Thank you  
谢谢

INSPIRING  
PEOPLE