



Circuit Analysis and Design

Academic year 2019/2020 – Semester 1 – Presentation 7


Masood Ur-Rehman, Qammer H. Abbasi, Guodong Zhao

[masood.urrehman](mailto:masood.urrehman@glasgow.ac.uk), [qammer.abbasi](mailto:qammer.abbasi@glasgow.ac.uk), [guodong.zhao](mailto:guodong.zhao@glasgow.ac.uk)@glasgow.ac.uk

“A good student never steal or cheat”

Agenda

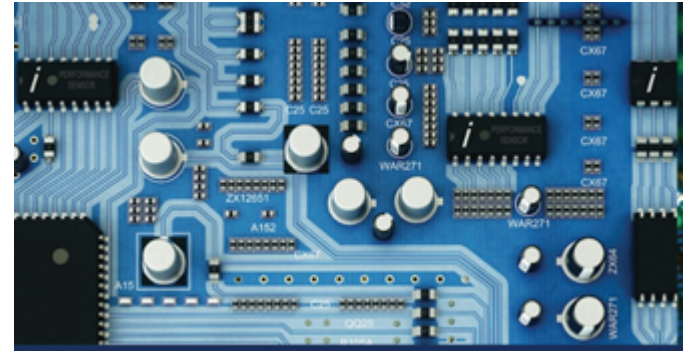- **Introduction**
- **Superposition principle**
- **Source transformations**
- **Summary**



Introduction


- The theorems are superposition principle, source transformation, Thévenin's theorem, Norton's theorem, and maximum power transfer.
- If a circuit contains more than one source, the circuit can be analyzed by summing the response from each source with all other sources deactivated. This is called the superposition principle.
- A voltage source with a series resistor is interchangeable with a current source in parallel to a resistor : **source transformation**.
- According to Thévenin's theorem, a given circuit is equivalent to a voltage source V_{th} and a series resistor R_{th} between terminals a and b .
- According to Norton's theorem, a given circuit is equivalent to a current source I_n and a parallel resistor R_n between terminals a and b .
- The load resistance R_L that maximizes the power delivered to the load is given by the Thévenin equivalent resistance R_{th} .

Superposition Principle

- Suppose that a circuit has N independent sources with $N \geq 2$.
- Create N circuits from the original circuit with only one independent source by deactivating the other $N-1$ independent sources.
- Deactivating a current source is to open-circuit it and deactivating a voltage source is to short-circuit it.
- The unknown voltages and currents of the original circuit can be found by adding the voltages and currents from the N circuits with one independent source: [superposition principle](#).
- The superposition principle reveals the contribution of each source to the voltages and currents in the circuit.
- It makes it easier to interpret the response of the circuit because we can trace the sources of the response.

Superposition Principle

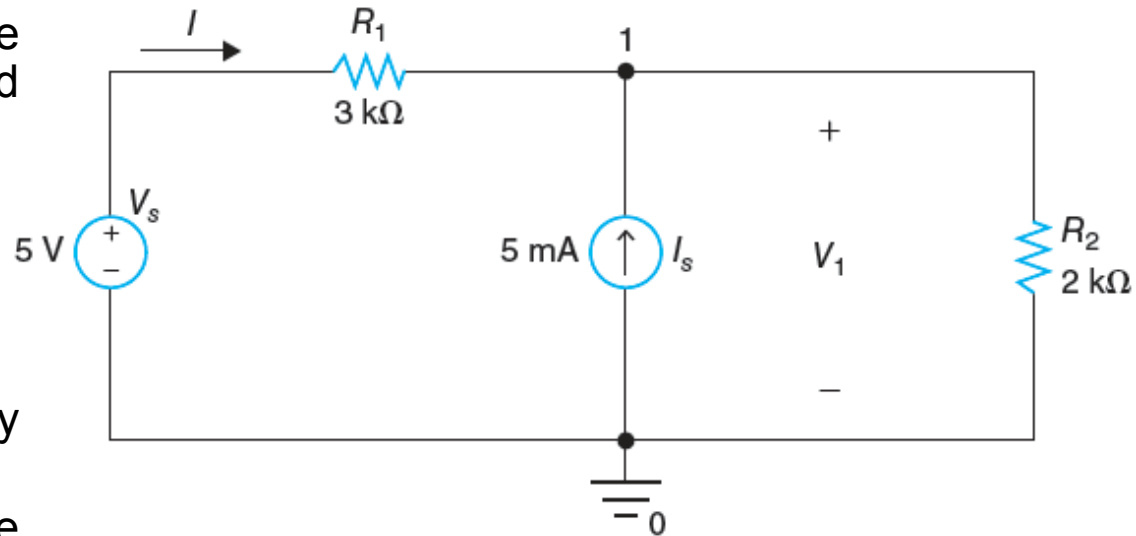- Consider a circuit with a voltage source V_s , a current source I_s , and two resistors R_1 and R_2 .




Finding V_1 and I using superposition principle?

- Deactivate the current source by removing it from the circuit.
- The circuit contains only one independent source V_s .
- Applying the voltage divider rule,


$$V_{11} = V_s \times R_2 / (R_1 + R_2) = 5 \times 2 / 5 = 2\text{ V}$$
- The contribution of the voltage source to the voltage across R_2 is 2 V .
- Applying Ohm's law,
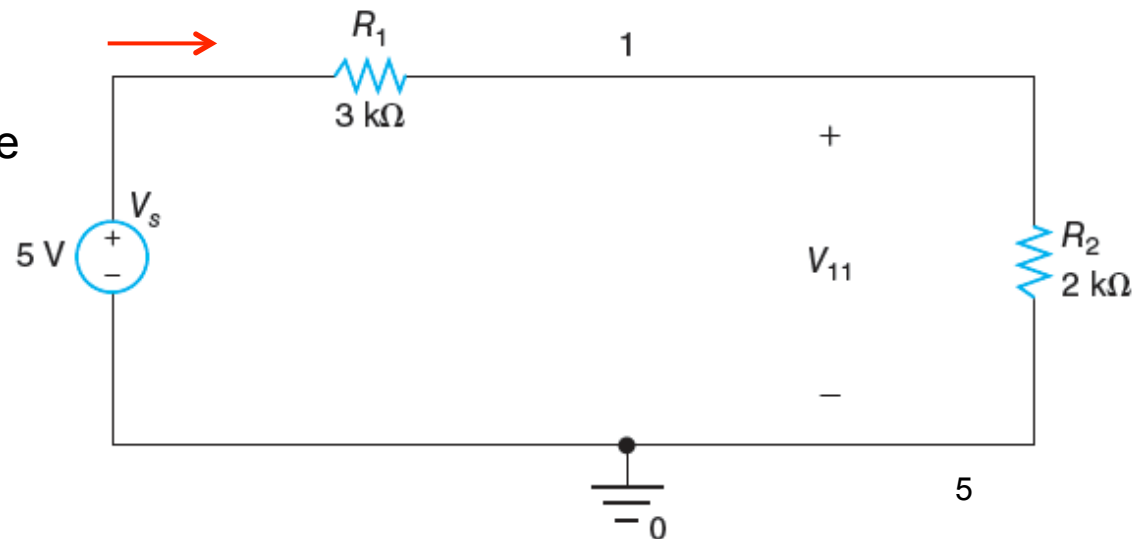
$$I_a = V_s / (R_1 + R_2) = 5 / 5\text{ k} = 1\text{ mA}$$





Superposition Principle

- Deactivate the voltage source by short-circuiting.
- The circuit contains only one independent source I_s .
- Applying the current divider rule, we obtain the current through R_2 :
$$I_2 = I_s \times R_1 / (R_1 + R_2) = 5\text{m} \times 3/5 = 3\text{ mA}$$
- The voltage across R_2 is given by $V_{12} = R_2 I_2 = 2000 \times 0.003 = 6\text{ V}$
- The contribution of the current source to the voltage across R_2 is 6 V.
- Applying KCL $\rightarrow I_b = -(I_s - I_2) = -2\text{ mA}$
- The voltage across R_2 is given by the sum of V_{11} and $V_{12} \rightarrow$
$$V = V_{11} + V_{12} = 2\text{ V} + 6\text{ V} = 8\text{ V}$$
- The current I is the sum of I_a and $I_b \rightarrow$
$$I = I_a + I_b = -1\text{ mA}$$

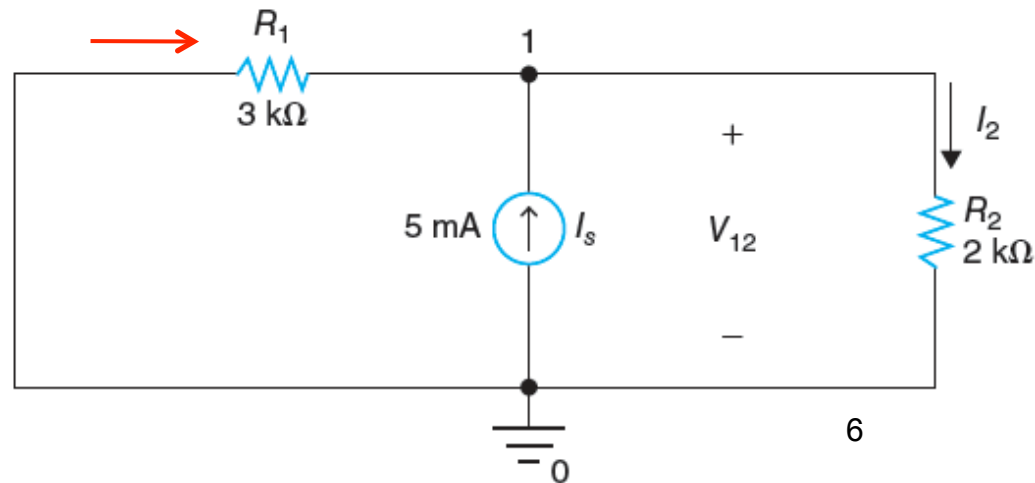

EXAMPLE 4.1

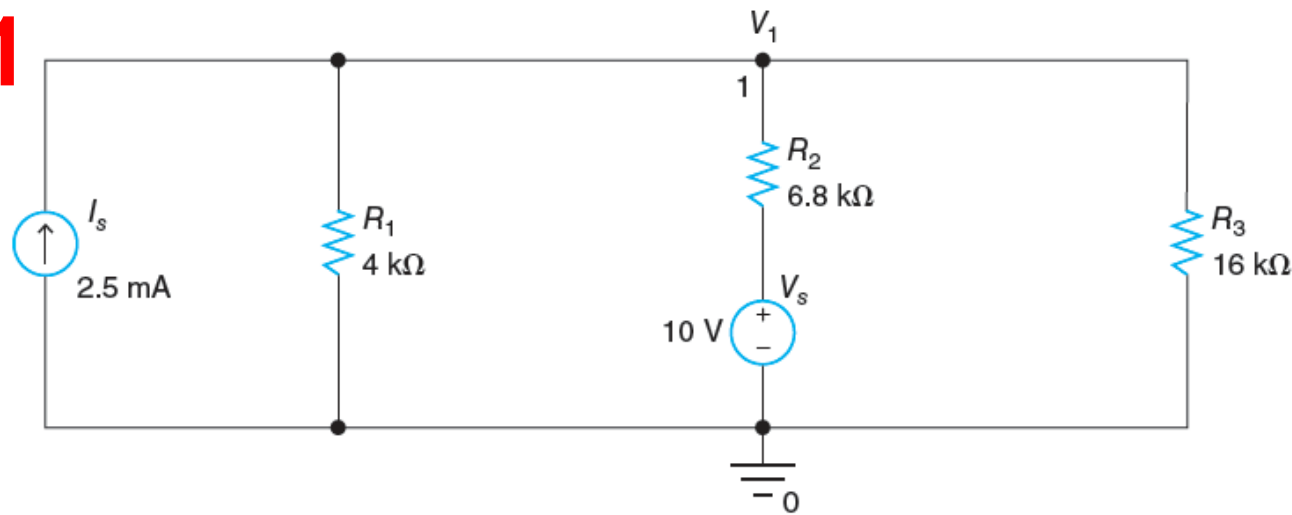


- Use superposition principle to find V_1 in the circuit.
- When the current source is deactivated, the circuit reduces to .
- $R_a = R_1 \parallel R_3 = 4 \times 16 / 20 \text{ k}\Omega = 3.2 \text{ k}\Omega$


- Voltage divider rule:


$$V_{11} = V_s \times R_a / (R_2 + R_a)$$

$$V_{11} = 10 \times 3.2 / 10 = 3.2 \text{ V}$$

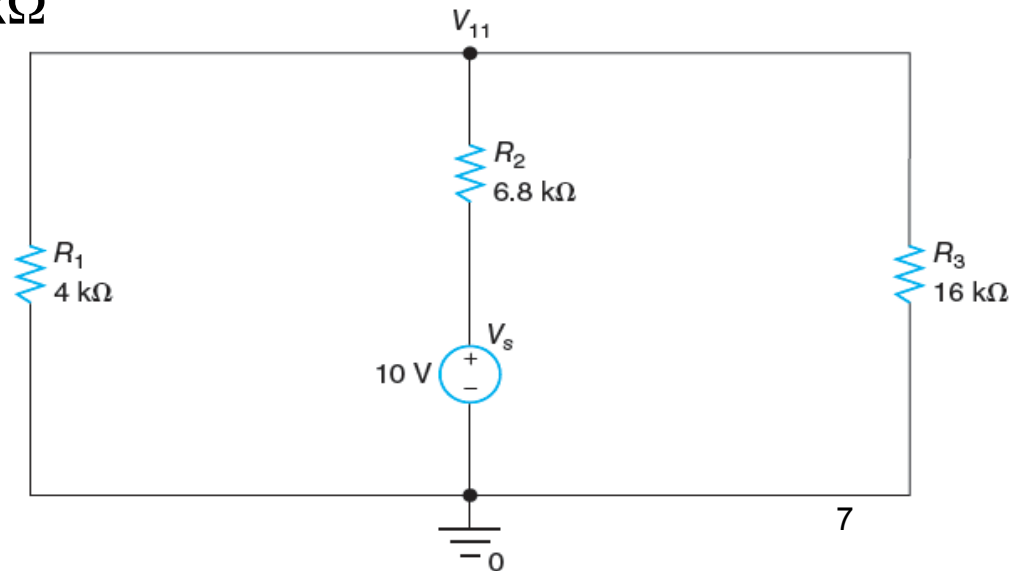



EXAMPLE 4.1

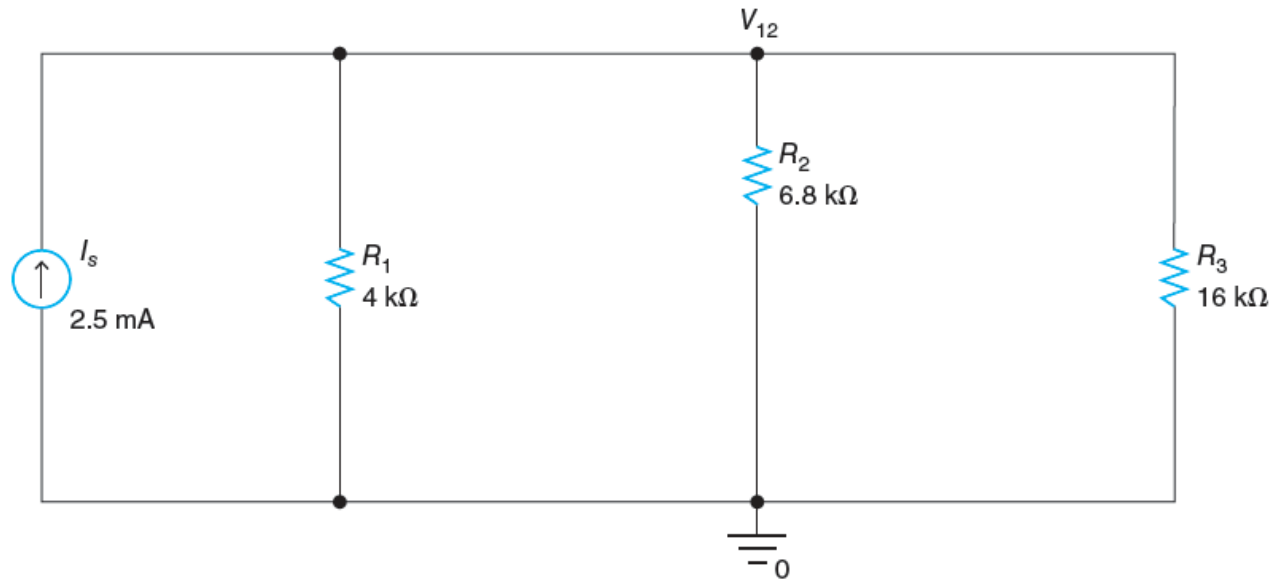

- When the voltage source is deactivated, the circuit reduces to .
- $R_a = R_1 \parallel R_3 = 4 \times 16 / 20 \text{ k}\Omega = 3.2 \text{ k}\Omega$
- $R_b = R_a \parallel R_2 = 3.2 \times 6.8 / 10 = 2.176 \text{ k}\Omega$
- Ohm's law $\rightarrow V_{12} = R_b \times I_s = 2.176 \times 2.5 = 5.44 \text{ V}$
- The voltage V_1 is the sum of V_{11} and V_{12} :
 $V_1 = V_{11} + V_{12} = 3.2 \text{ V} + 5.44 \text{ V} = 8.64 \text{ V}$

EXAMPLE 4.2

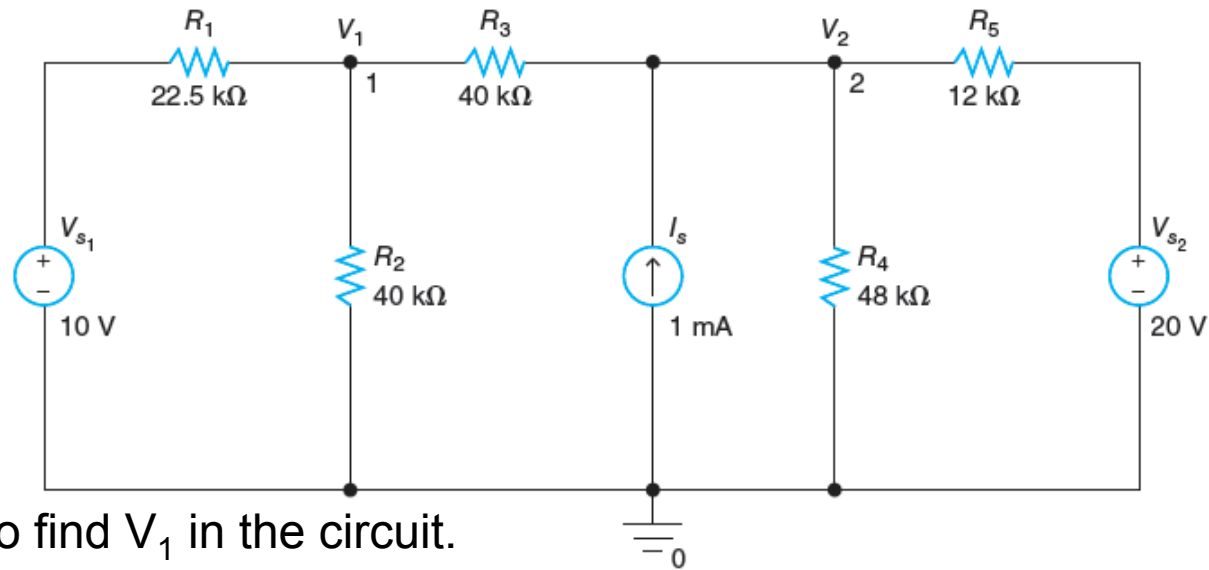

- Use superposition principle to find V_1 in the circuit.
- When I_s and V_{s2} are deactivated, the circuit reduces to .


- $R_a = R_4 \parallel R_5 = 48 \times 12 / (48 + 12) = 9.6 \text{ k}\Omega$

$$R_b = R_3 + R_a = 49.6 \text{ k}\Omega$$


$$R_c = R_2 \parallel R_b = 40 \times 49.6 / (40 + 49.6) = 22.1429 \text{ k}\Omega$$


- Voltage divider rule:

$$V_{11} = V_{s1} \times R_c / (R_1 + R_c) = 4.96 \text{ V}$$

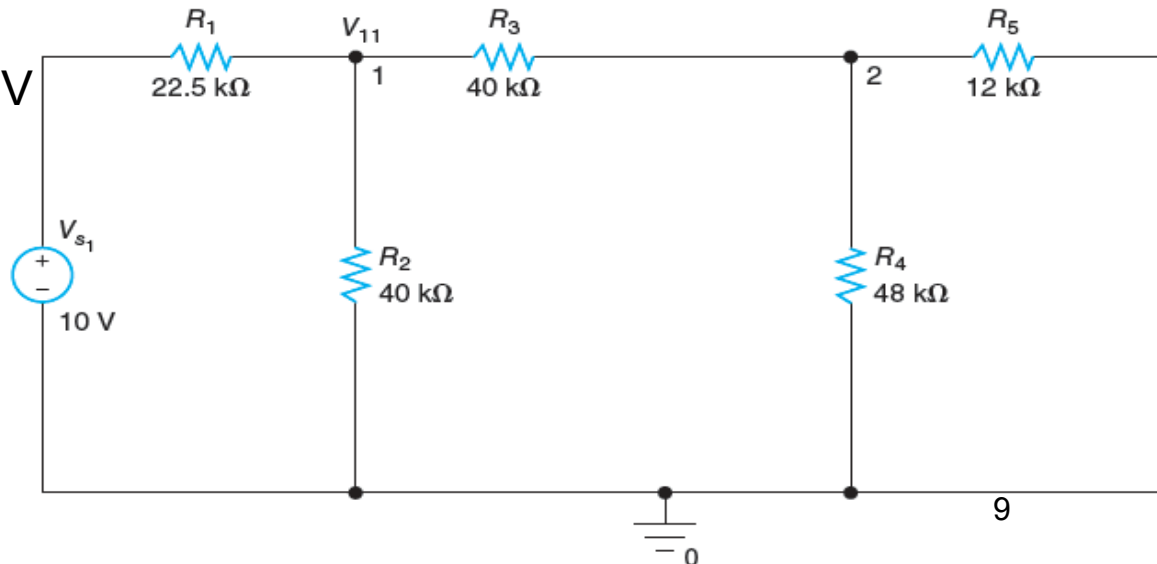



EXAMPLE 4.2

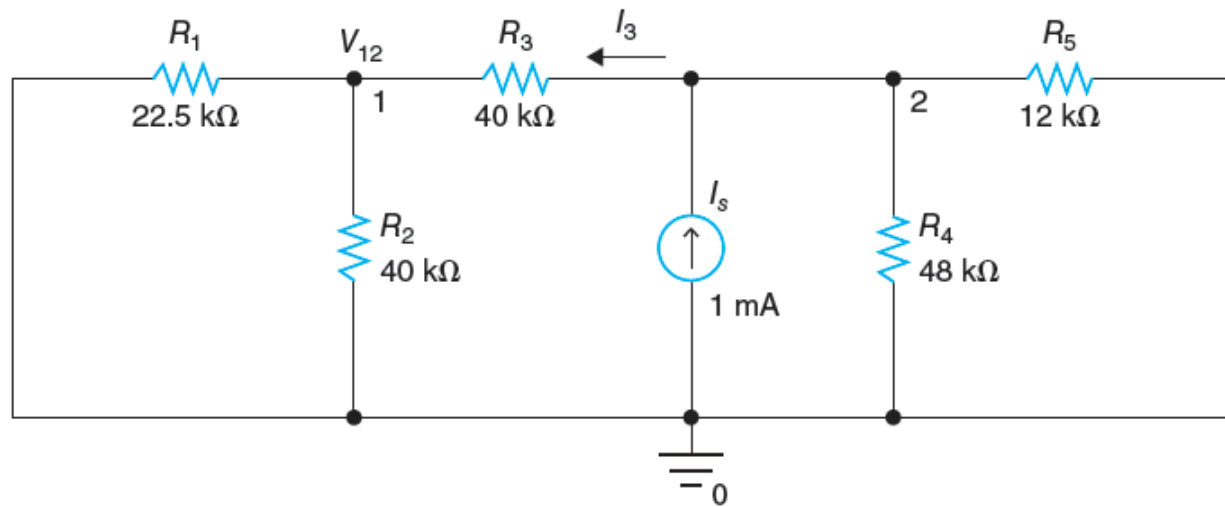


- When V_{s1} and V_{s2} are deactivated, the circuit reduces to .
- $R_a = R_4 \parallel R_5 = 48 \times 12 / (48 + 12) = 9.6 \text{ k}\Omega$
 $R_d = R_1 \parallel R_2 = 22.5 \times 40 / (22.5 + 40) = 14.4 \text{ k}\Omega$
 $R_e = R_3 + R_d = 54.4 \text{ k}\Omega$
- Current divider rule:
 $I_3 = I_s \times R_a / (R_a + R_e) = 0.15 \text{ mA}$
- Ohm's law:
 $V_{12} = R_d I_3 = 2.16 \text{ V}$


EXAMPLE 4.2

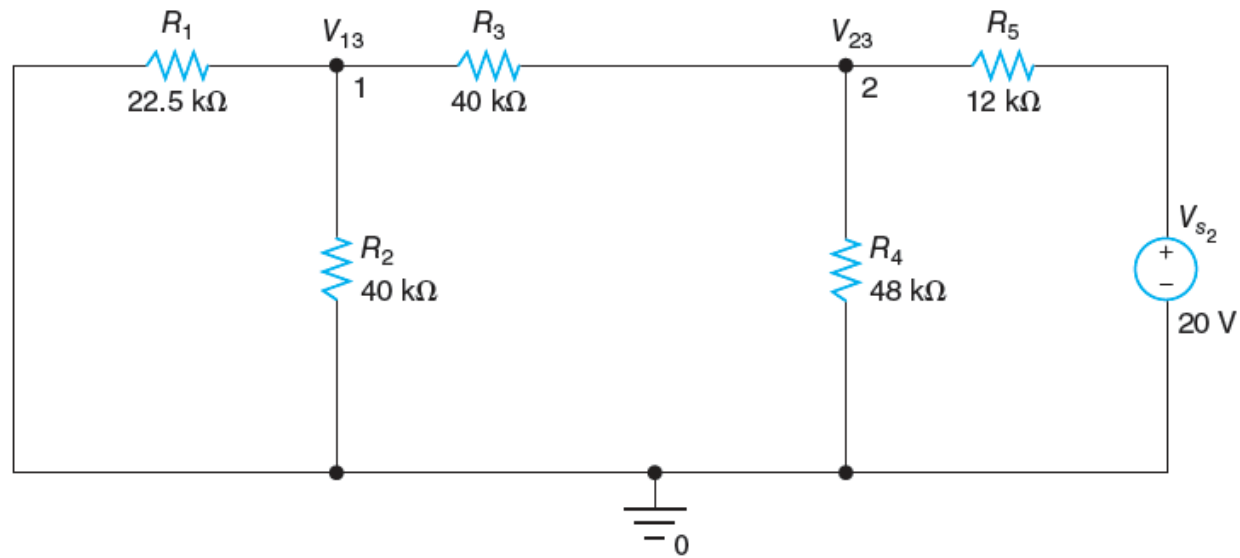

- When V_{s1} and I_s are deactivated, the circuit reduces to .
- $R_d = R_1 \parallel R_2 = 22.5 \times 40 / (22.5 + 40) = 14.4 \text{ k}\Omega$
 $R_e = R_3 + R_d = 54.4 \text{ k}\Omega$
 $R_f = R_4 \parallel R_e = 48 \times 54.4 / (48 + 54.4) = 25.5 \text{ k}\Omega$
- Voltage divider rule:
 $V_{23} = V_{s2} \times R_f / (R_5 + R_f) = 13.6 \text{ V}$
 $V_{13} = V_{23} \times R_d / (R_3 + R_d) = 3.6 \text{ V}$
- The voltage V_1 is given by
 $V_1 = V_{11} + V_{12} + V_{13} = 4.96 \text{ V} + 2.16 \text{ V} + 3.6 \text{ V} = 10.72 \text{ V}$

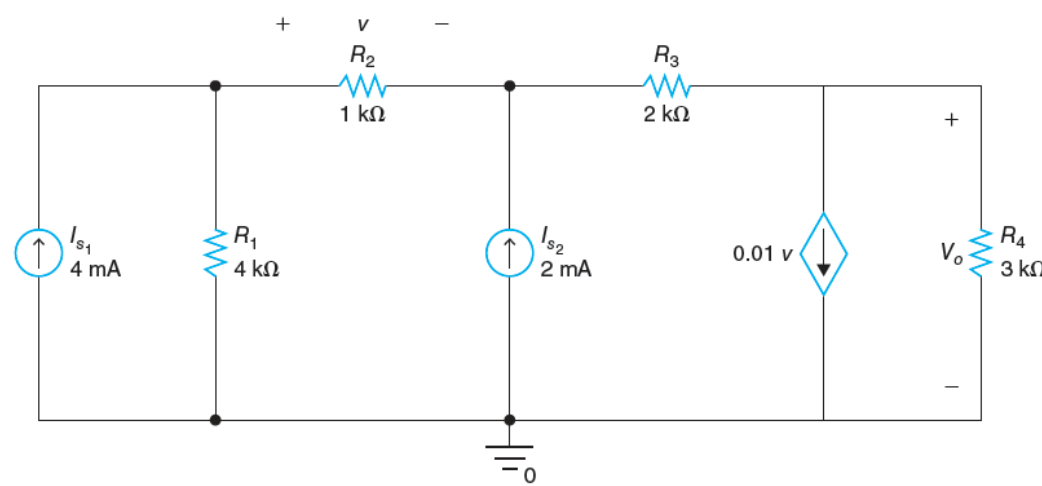EXAMPLE 4.3

- Use superposition principle to find V_o in the circuit.
- When I_{s2} is deactivated, the circuit reduces to .



- $v = (V_{11} - V_{o1}) \times R_2 / (R_2 + R_3) = (V_{11} - V_{o1}) / 3$


- Node 1 $\rightarrow -0.004 + \frac{V_{11}}{4000} + \frac{V_{11} - V_{o1}}{3000} = 0$ Multiply by 12000 $\rightarrow 7V_{11} - 4V_{o1} = 48$ (1)

- Node 2 $\rightarrow \frac{V_{o1} - V_{11}}{3000} + \frac{V_{o1}}{3000} + 0.01 \frac{V_{11} - V_{o1}}{3} = 0$ Multiply 3000 $\rightarrow -8V_{o1} + 9V_{11} = 0 \Rightarrow$


$$V_{11} = (8/9)V_{o1} \text{ (2),}$$

$$(2) \rightarrow (1): (7 \times 8/9) V_{o1} - 4V_{o1} = 48 \Rightarrow$$

$$(20/9) V_{o1} = 48 \Rightarrow V_{o1} = 48 \times 9/20 = 21.6V$$

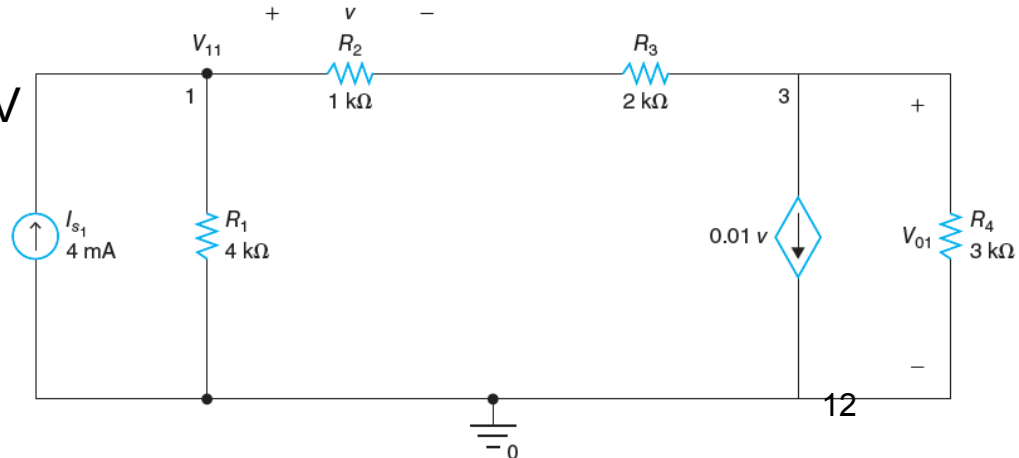


EXAMPLE 4.3

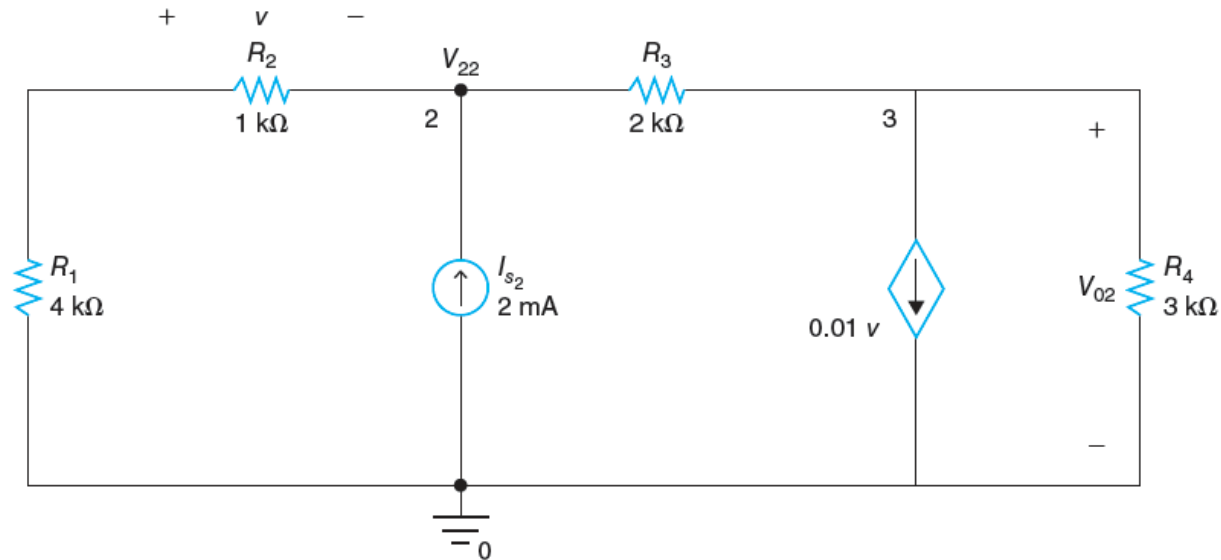

- When I_{s1} is deactivated, the circuit reduces to the one shown in Figure 4.15.
- $v = (-V_{22}) \times R_2 / (R_1 + R_2) = (-V_{22})/5$
- Node 2: $\frac{V_{22}}{5000} - 0.002 + \frac{V_{22} - V_{02}}{2000} = 0$ Multiply by 10000: $7V_{22} - 5V_{02} = 20$ (3)
- Node 3: $\frac{V_{02} - V_{22}}{2000} + \frac{V_{02}}{3000} + 0.01 \frac{-V_{22}}{5} = 0$ Multiply 6000: $3V_{02} - 3V_{22} + 2V_{02} - 12V_{22} = 0$,
- $V_{22} = (1/3)V_{02}$ (4), Substitute Equation (4) into Equation (3) \rightarrow
 $(7/3)V_{02} - 5V_{02} = 20 \Rightarrow (-8/3)V_{02} = 20 \Rightarrow V_{02} = -60/8 = -7.5 \text{ V}$
- $V_0 = V_{01} + V_{02} = 21.6 \text{ V} - 7.5 \text{ V} = 14.1 \text{ V}$

Source Transformation

- A circuit consisting of a voltage source with voltage V_s and a series resistor with resistance R_s , is equivalent to a circuit consisting of a current source with current V_s/R_s and a parallel resistor with resistance R_s .
- Equivalence means that the circuits have the same open-circuit voltage across a and b , the same short-circuit current through a and b , and the same resistance looking into the circuit from a and b after deactivating the source.
- A circuit consisting of a current source with current I_s and a parallel resistor with resistance R_s is equivalent to a circuit consisting of a voltage source with voltage $I_s R_s$ and a series resistor with resistance R_s .

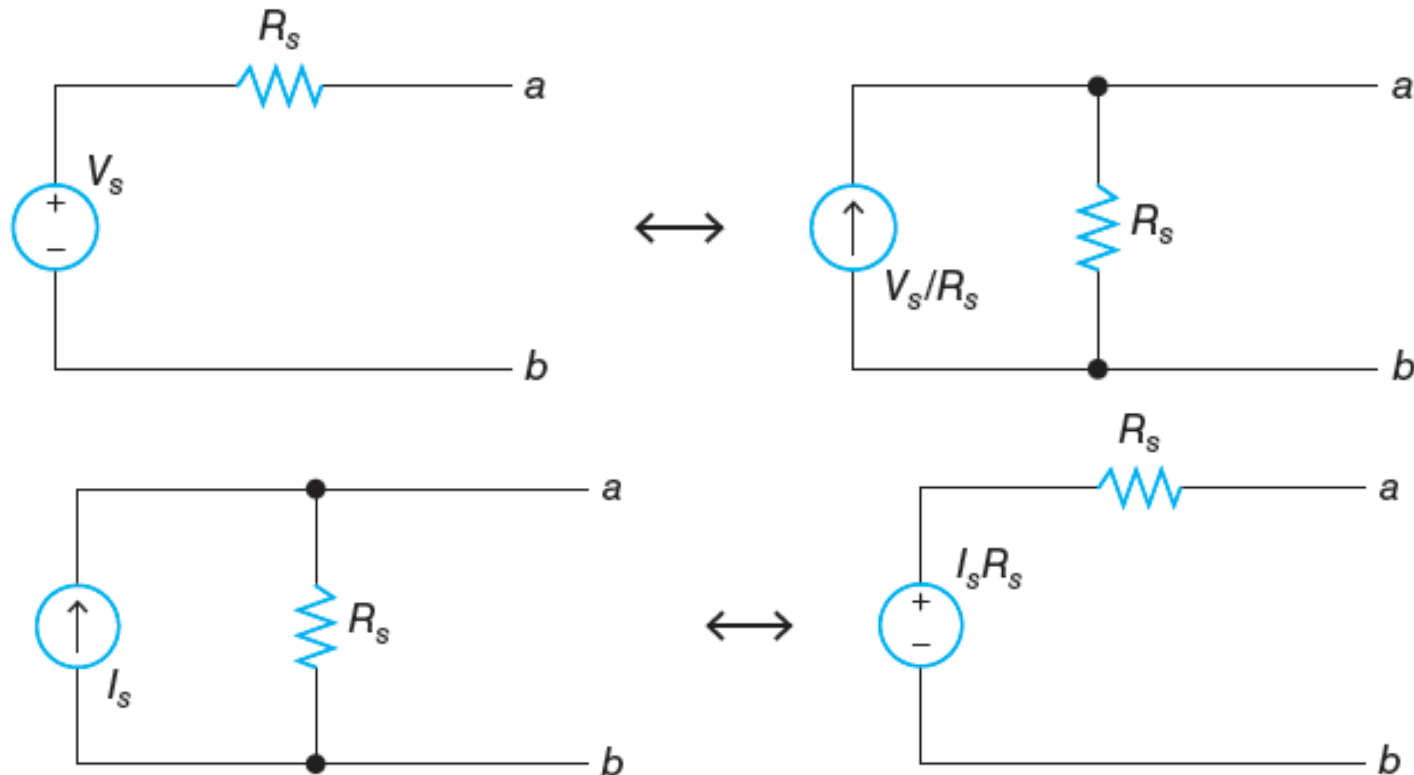

Source Transformation

- The source transformations apply to dependent sources as well. Figures 4.19 and 4.20 show the equivalence of a voltage source and a series resistor, and a current source and a parallel resistor.

FIGURE 4.19

A dependent voltage source and a series resistor are equivalent to a dependent current source and a parallel resistor.

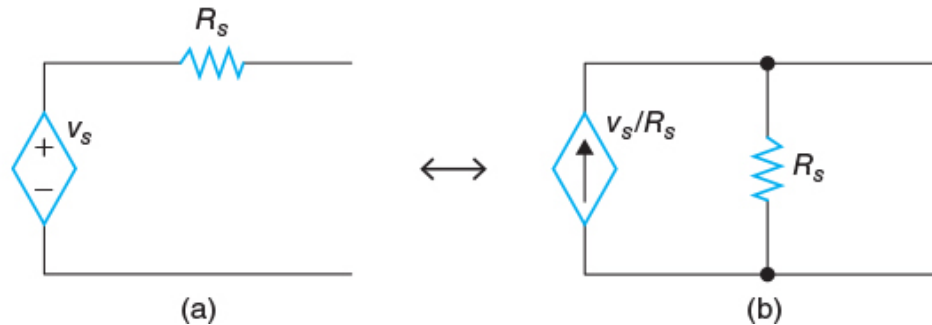



FIGURE 4.20

A dependent current source and a parallel resistor are equivalent to a dependent voltage source and a series resistor.




Source Transformation

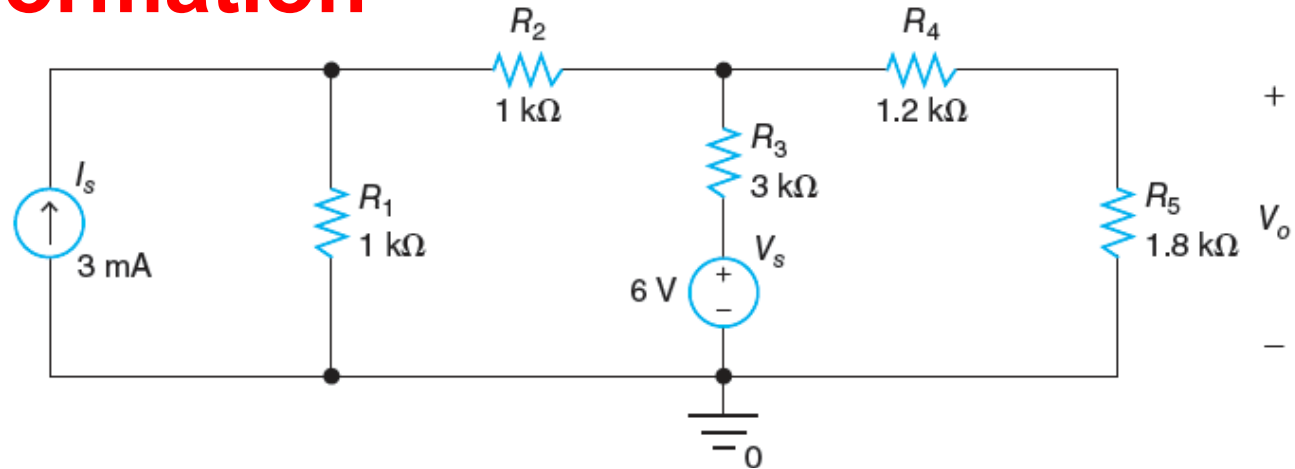
- We are interested in finding V_o using source transformation.



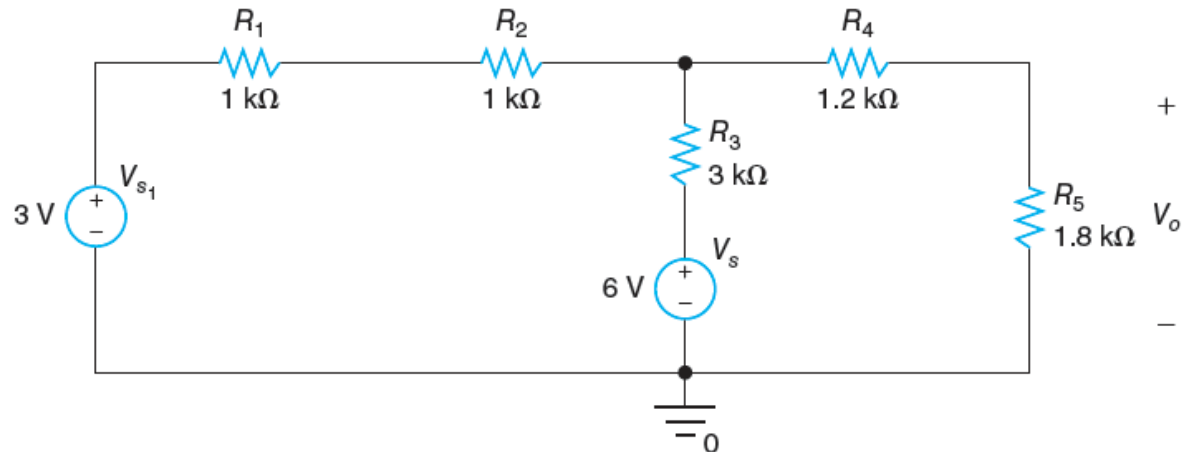
- I_s and R_1 can be transformed to a voltage source V_{s1} and a series resistor R_1 .
Let $R_a = R_1 + R_2 = 2\text{ k}\Omega$.



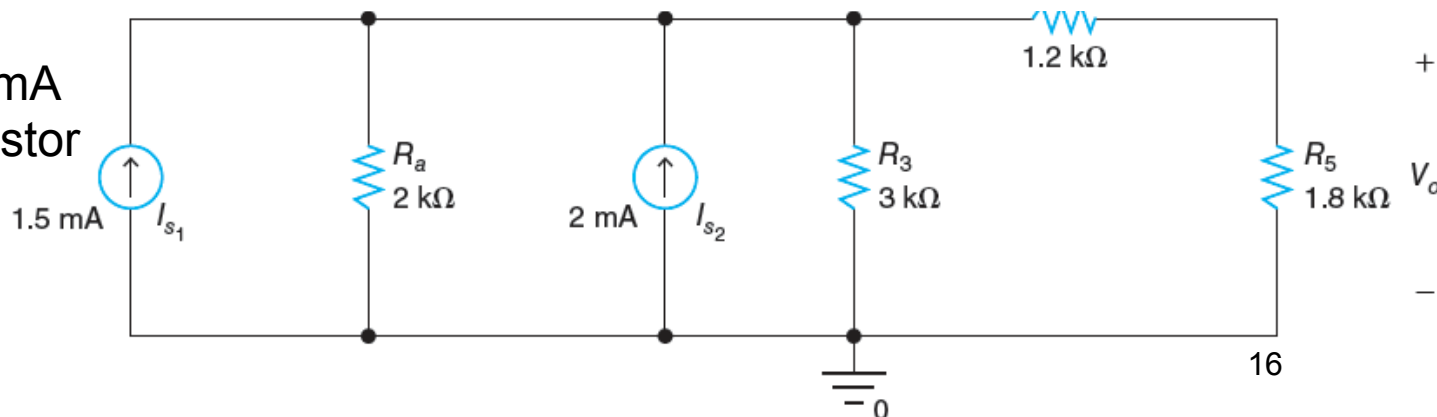
- V_{s1} and R_a can be transformed to a current source $I_{s1} = V_{s1}/R_a = 1.5\text{ mA}$ and a parallel resistor R_a .



Source Transformation

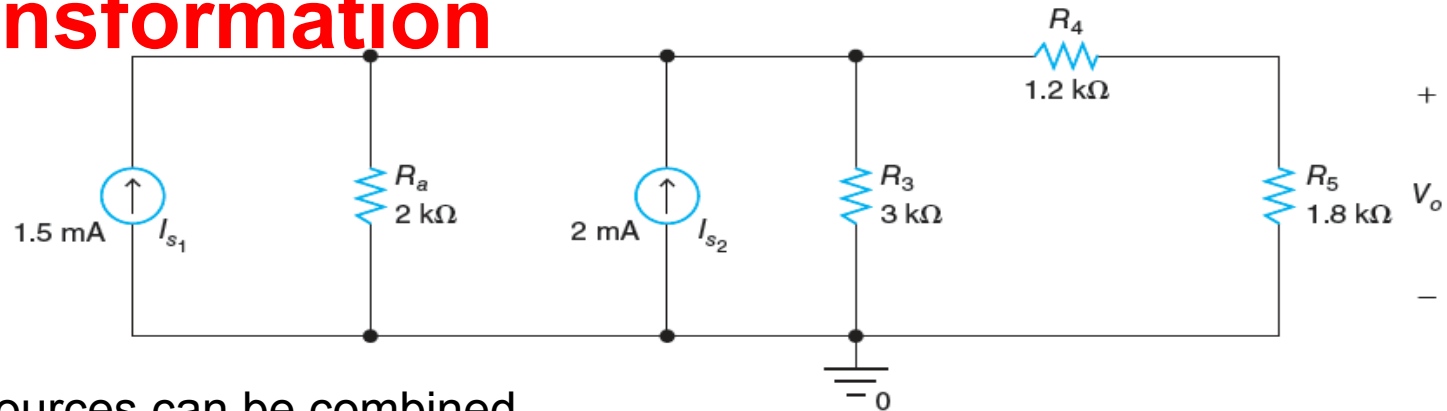

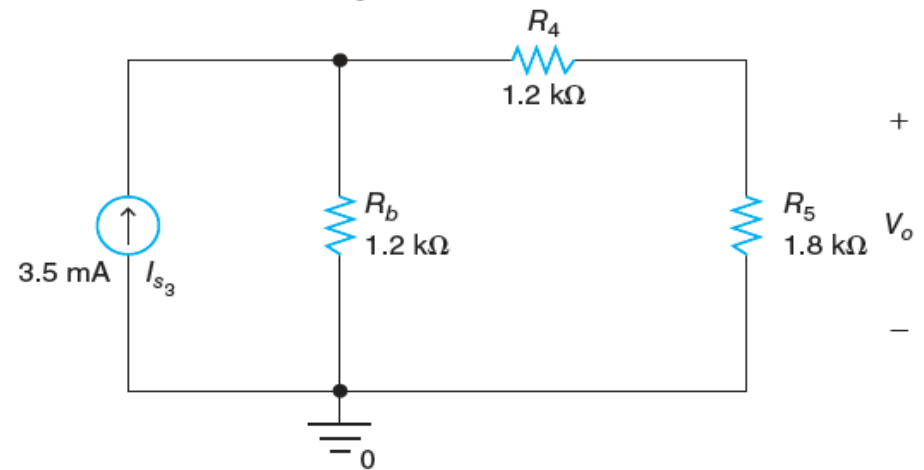- The two current sources can be combined into one current source with current $I_{s3} = I_{s1} + I_{s2} = 3.5\text{ mA}$, and parallel resistors R_a and R_3 can be combined into an equivalent resistor with resistance $R_b = R_a \parallel R_3 = 1.2\text{ k}\Omega$.




- I_{s3} and R_b can be transformed to a voltage source with voltage $V_{s2} = R_b I_{s3} = 4.2\text{ V}$ and a series resistor R_b .

- According to the voltage divider rule, we obtain


$$V_o = V_{s2} \times R_5 / (R_b + R_4 + R_5)$$
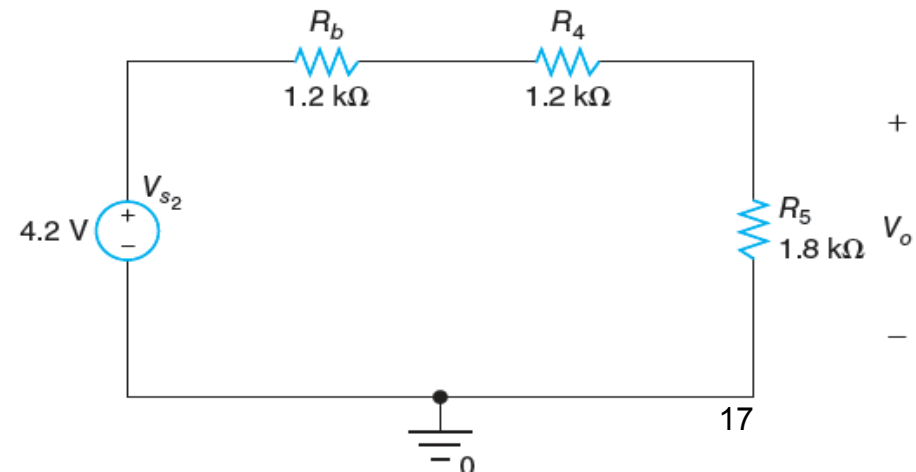
$$= 4.2\text{ V} \times 1.8 / (1.2 + 1.2 + 1.8) = 1.8\text{ V}$$




Source Transformation

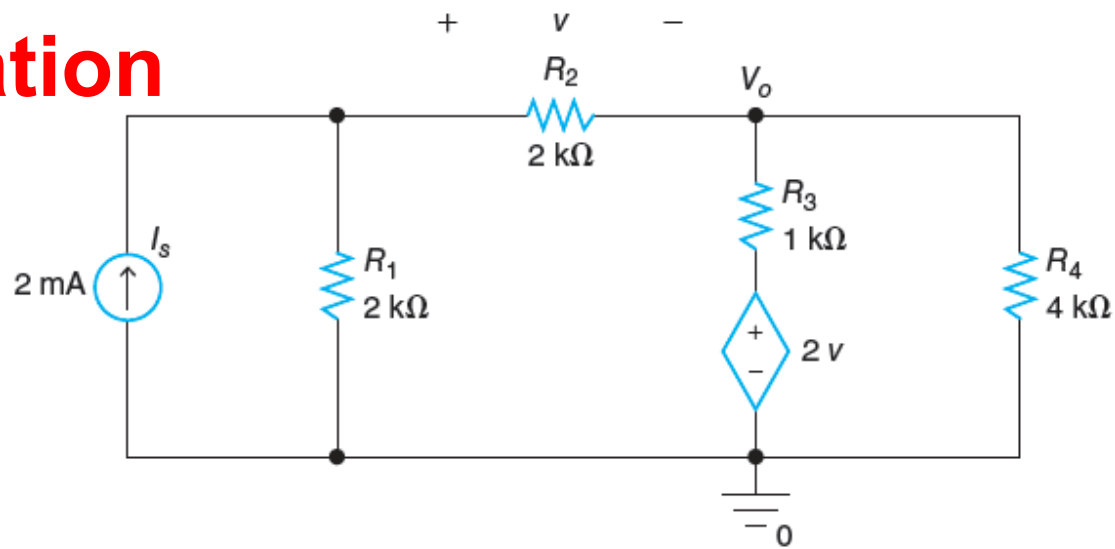
- We are interested in finding V_o in the circuit.



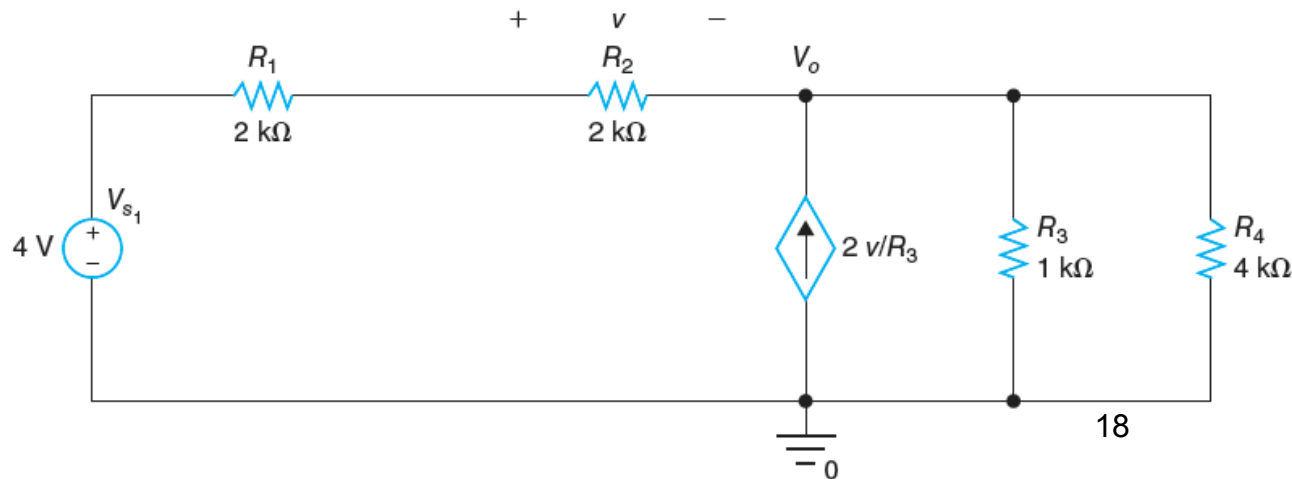- I_s and R_1 are transformed to V_{s1} with voltage 4 V and a series resistor R_1
- The voltage source 2 V and series resistor R_3 can be transformed to a current source with current $2\text{ V}/R_3$ and a parallel resistor R_3 .
- Let R_a be the equivalent resistance of the parallel connection of R_3 and R_4 . Then, we have $R_a = R_3 \parallel R_4 = 0.8\text{ k}\Omega$.



Source Transformation

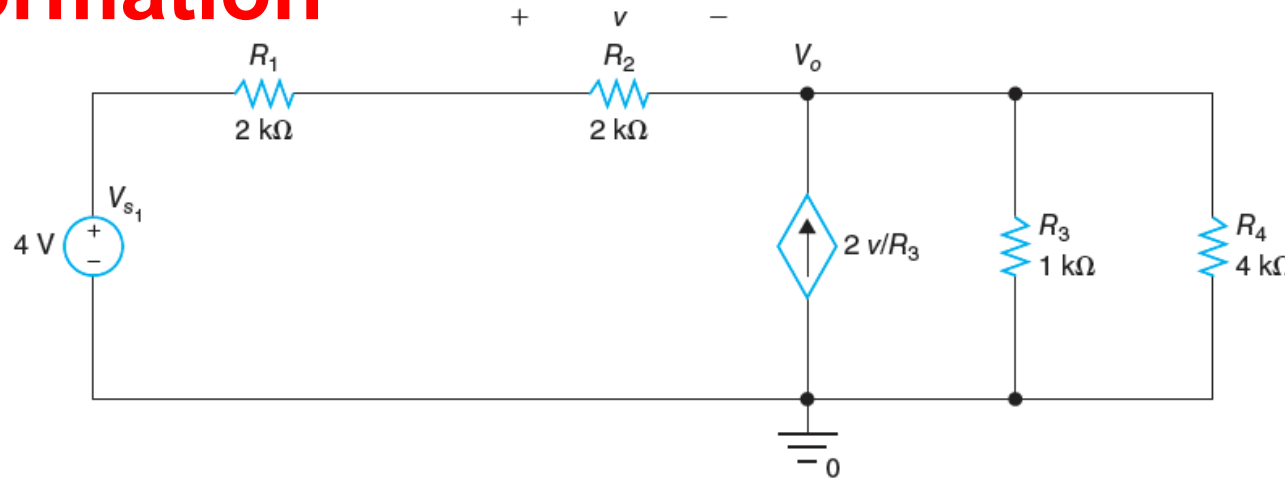

- The current source with current $2v/R_3$ and a parallel resistor R_a can be transformed to a voltage source with voltage $2vR_a/R_3$ and a series resistor R_a .
- Collecting the voltage drops around the mesh, we obtain


$$-4 + 2000i + 2000i + 800i + 2(2000i)800/1000 = 0$$

$$i = 4/8000 = 0.5 \text{ mA}$$

- The voltage V_o is given by


$$V_o = V_s - 2000i - 2000i$$

$$V_o = 4 \text{ V} - 1 \text{ V} - 1 \text{ V} = 2 \text{ V}$$

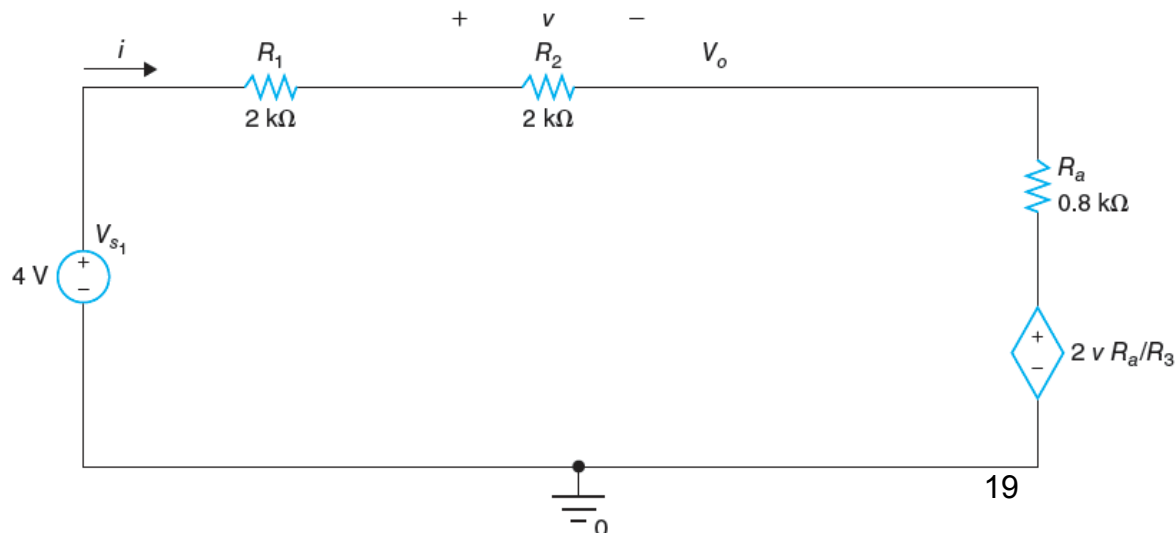


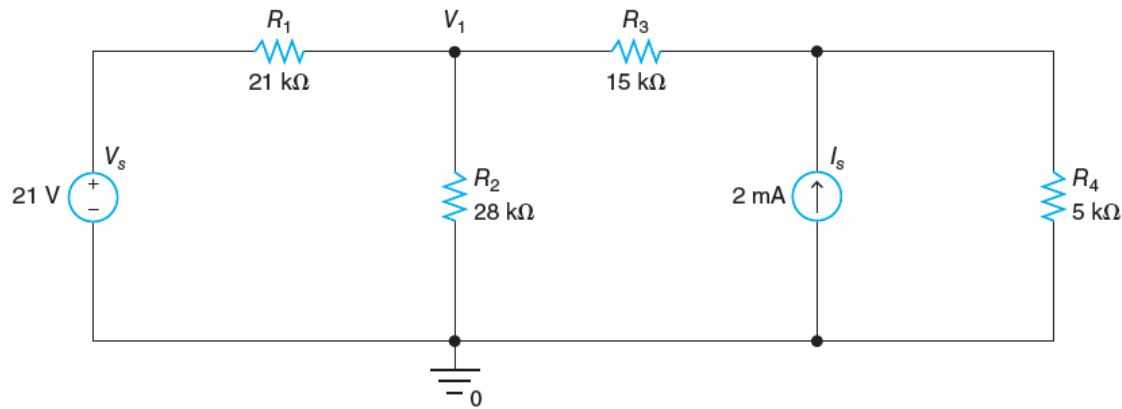EXAMPLE 4.4


- Use source transformation to find V_1 in the circuit.



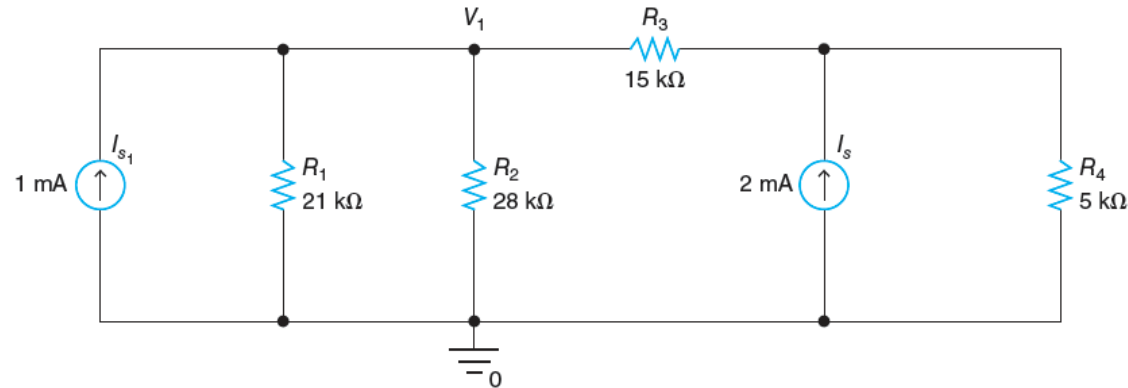- V_s and R_1 are transformed to $I_{s1} = V_s/R_1 = 1\text{ mA}$ and R_1 .




- Let $R_a = R_1 \parallel R_2 = 12\text{ k}\Omega$. Then, the parallel connection of R_1 and R_2 can be replaced by R_a .

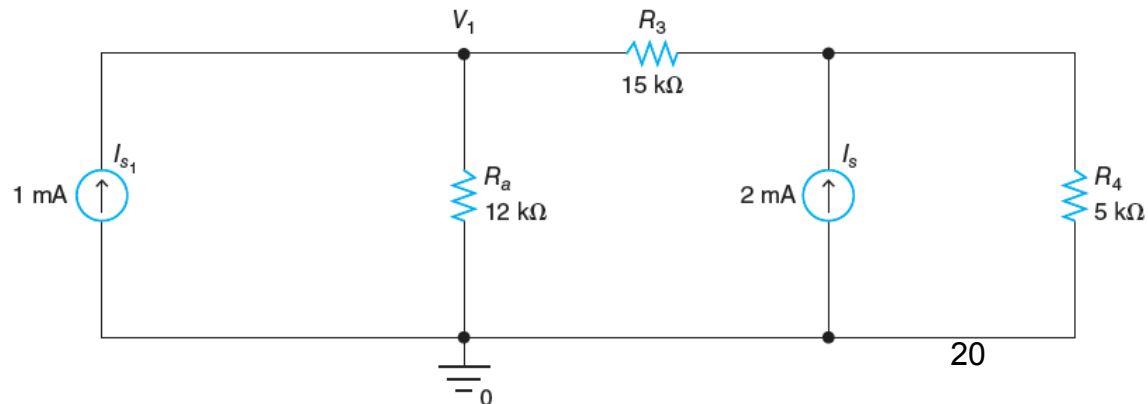


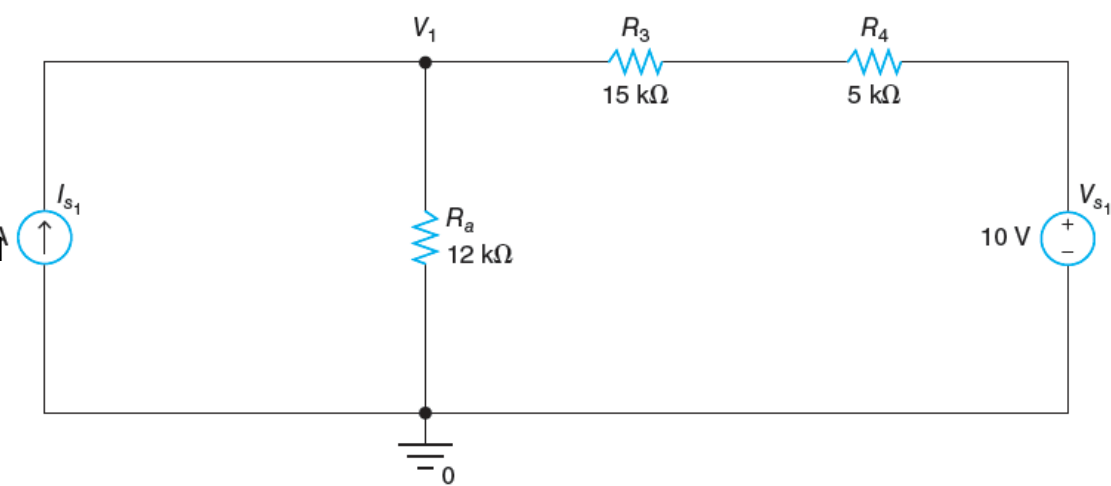EXAMPLE 4.4


- I_s and R_4 are transformed to V_{s1}
 $= R_4 I_s = 10 \text{ V}$ and R_4 .



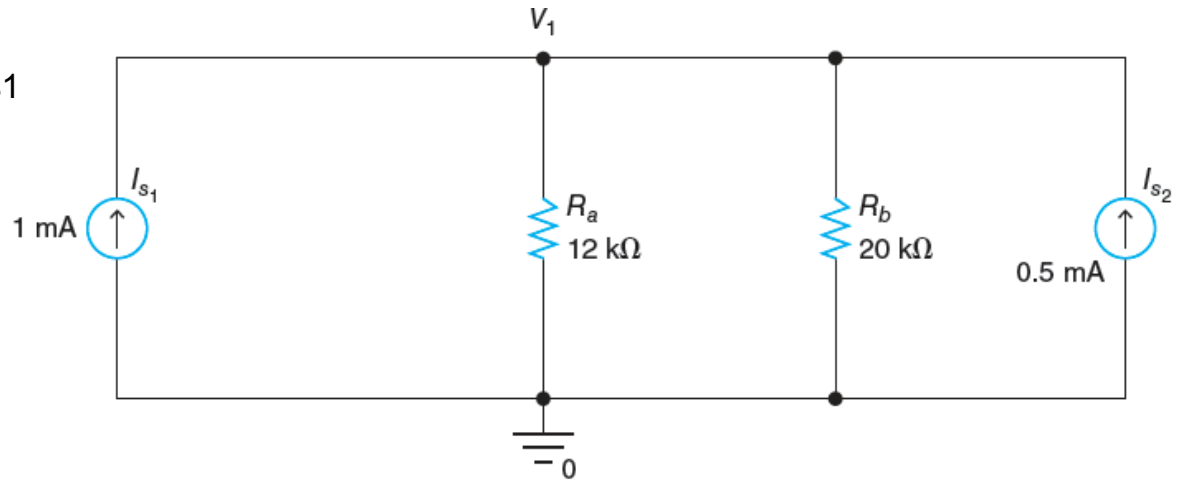
- Let $R_b = R_3 + R_4 = 20 \text{ k}\Omega$. V_{s1} and R_b are transformed to $I_{s2} = V_{s1}/R_b = 0.5 \text{ mA}$ and R_b in parallel.




- $R_c = R_a \parallel R_b = 7.5 \text{ k}\Omega$,
 $I_{s3} = I_{s1} + I_{s2} = 1.5 \text{ mA}$
- $V_1 = R_c I_{s3} = 11.25 \text{ V}$

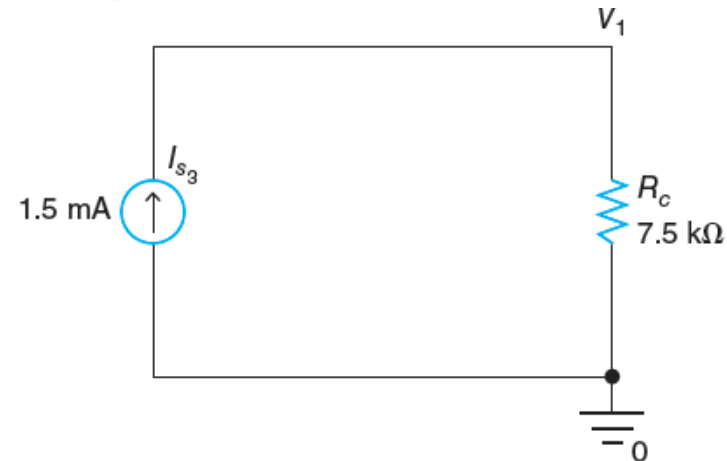

EXAMPLE 4.5

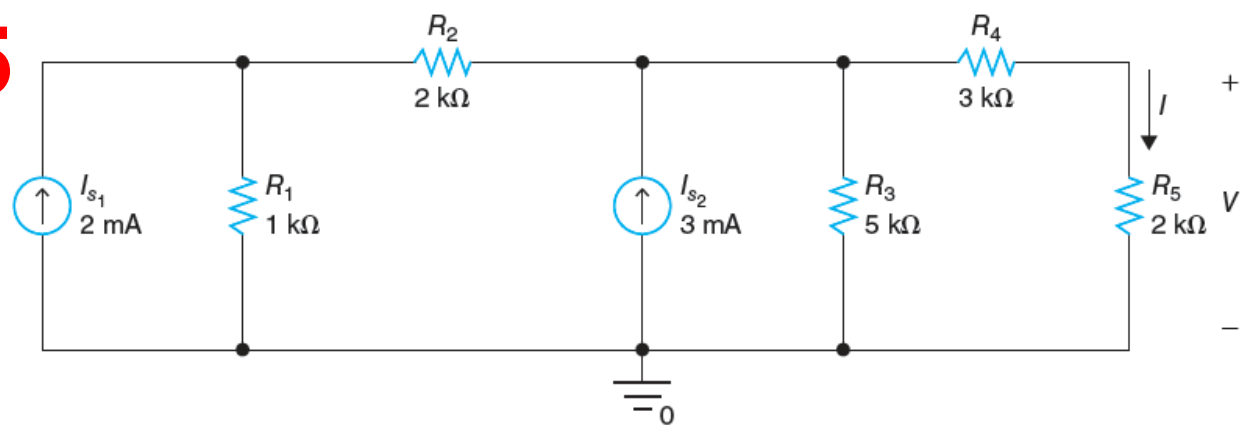


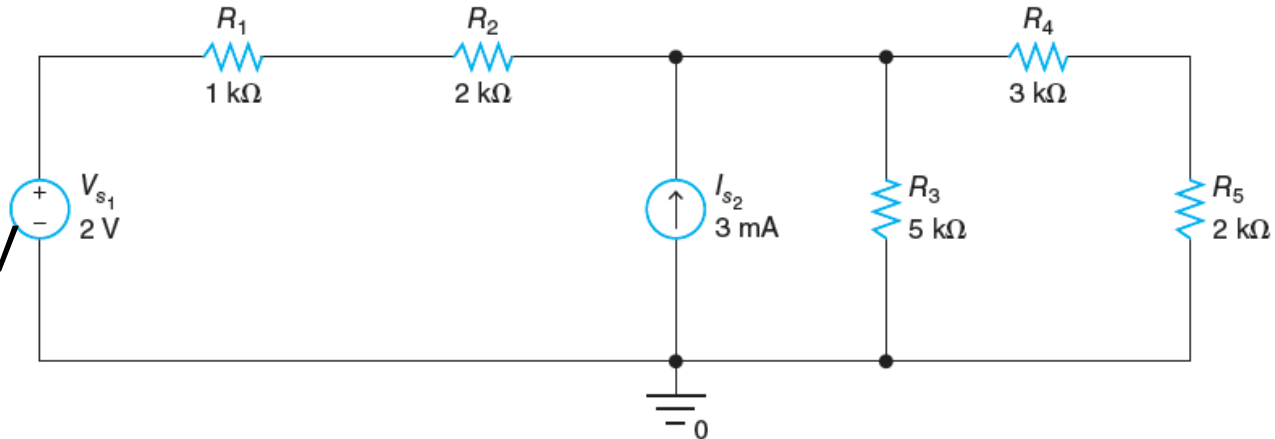- Use source transformation to find V and I for the circuit.






- Transform I_{s1} and R_1 to $V_{s1} = R_1 I_{s1} = 2\text{ V}$ and R_1 .

- $R_6 = R_1 + R_2 = 3\text{ k}\Omega$.

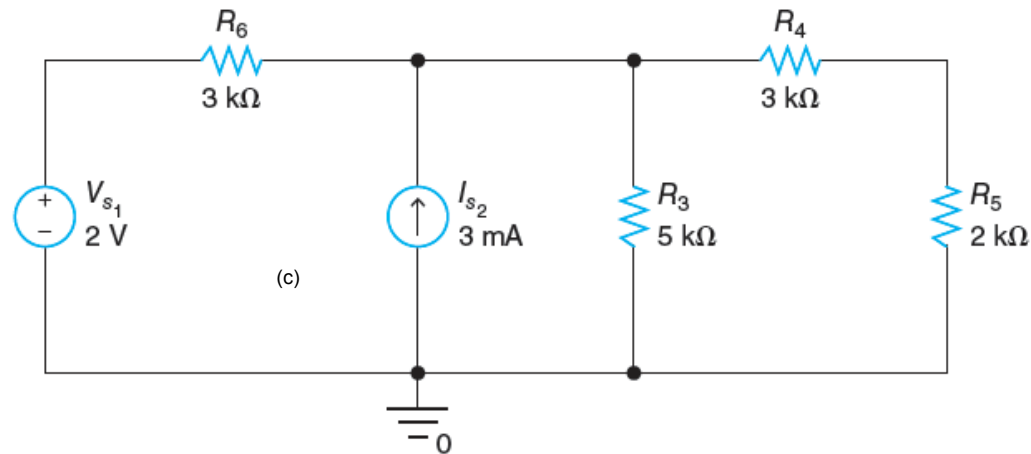




EXAMPLE 4.5

- Transform V_{s1} and R_6 to $I_{s3} = V_{s1}/R_6 = 2/3 \text{ mA}$ and R_6 .
- $R_7 = R_3 \parallel R_6 = 15/8 \text{ k}\Omega$,
 $I_{s4} = I_{s2} + I_{s3} = 11/3 \text{ mA}$.
- Transform I_{s4} and R_7 to $V_{s2} = R_7 I_{s4} = 55/8 \text{ V}$ and R_7 .
- $I = V_{s2}/(R_7 + R_4 + R_5) = 1 \text{ mA}$
- $V = R_5 I = 2 \text{ V}$

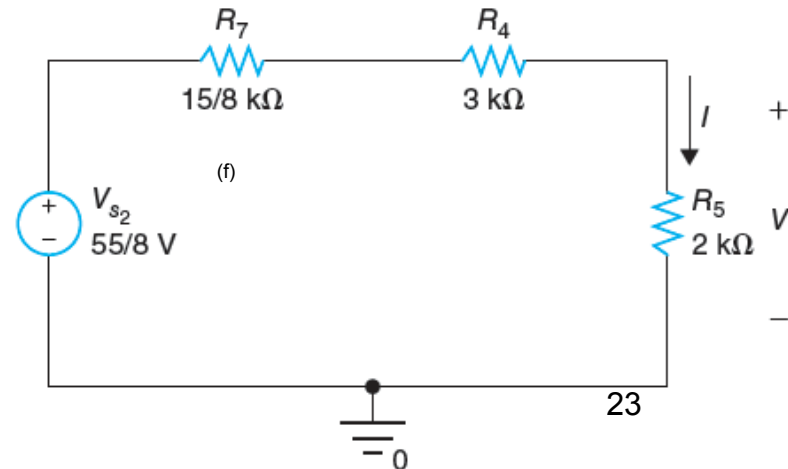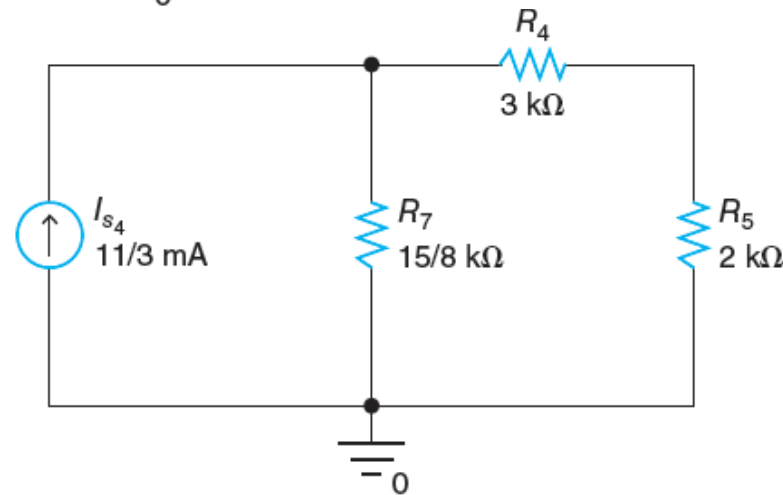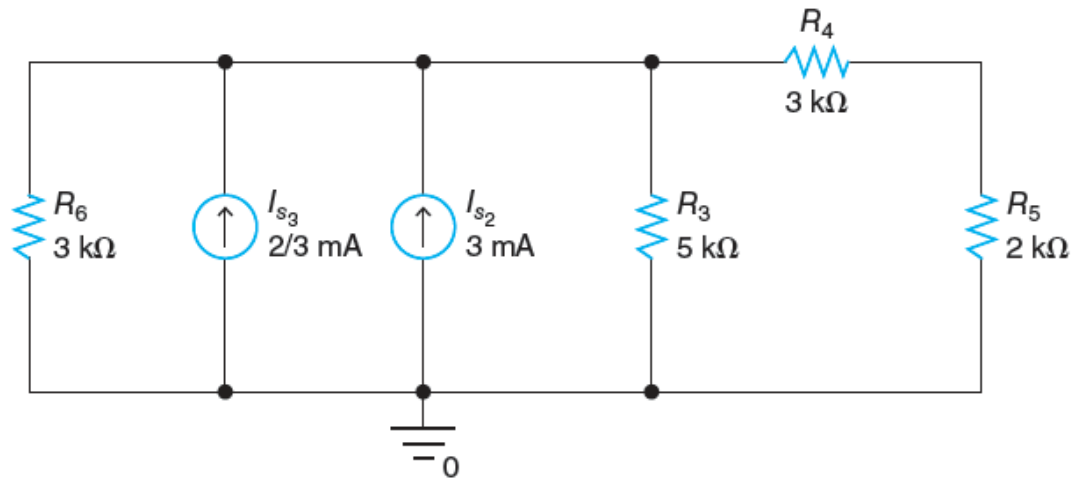


EXAMPLE 4.6

- Use source transformation to find V_1 .
- Transform the current source and R_3 to a voltage source with voltage $0.005\text{V} \times 1000 = 5\text{V}$ and R_3 .
- $R_4 = R_2 + R_3 = 4\text{ k}\Omega$
- Transform current source 5V and R_4 to voltage source with current $5\text{V}/R_4 = 0.00125\text{A}$ and R_4 .

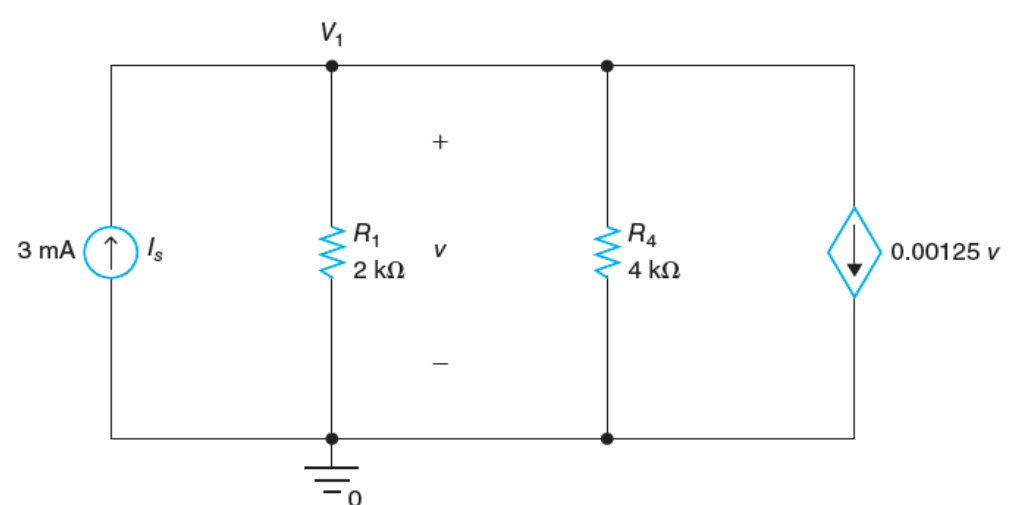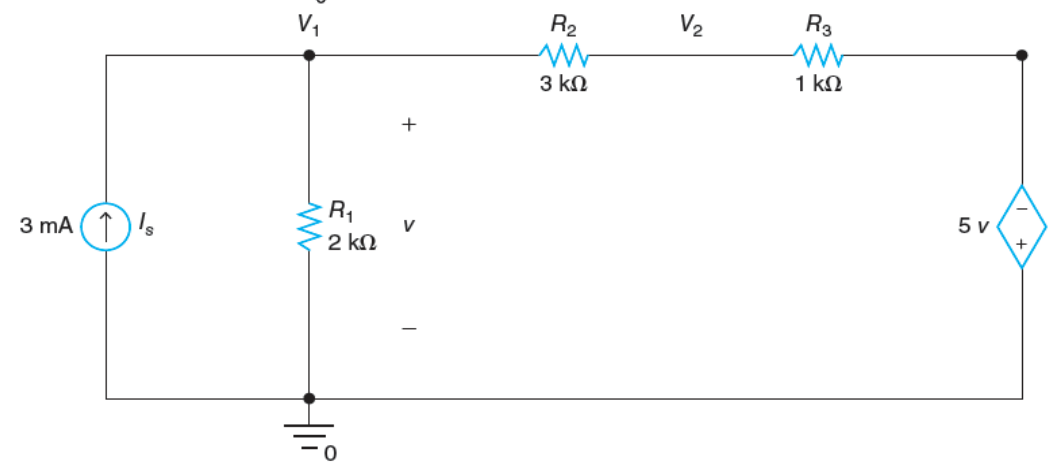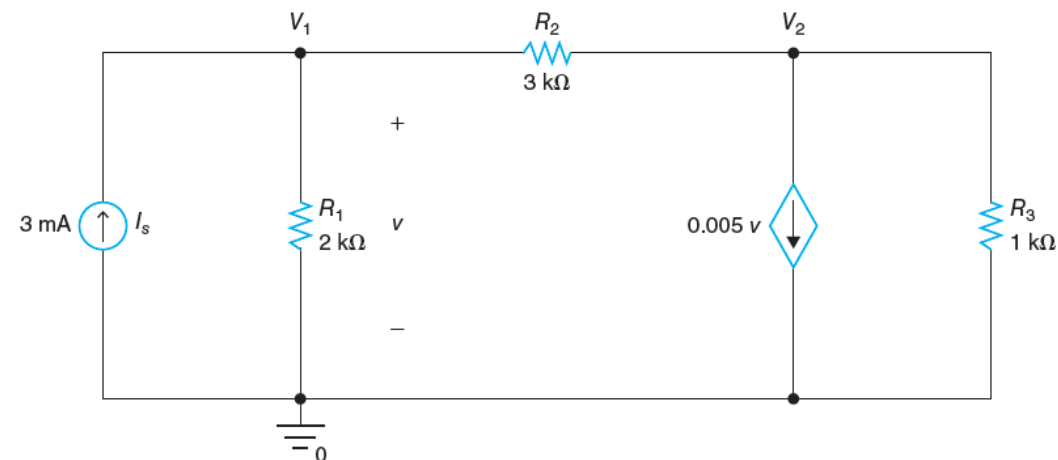

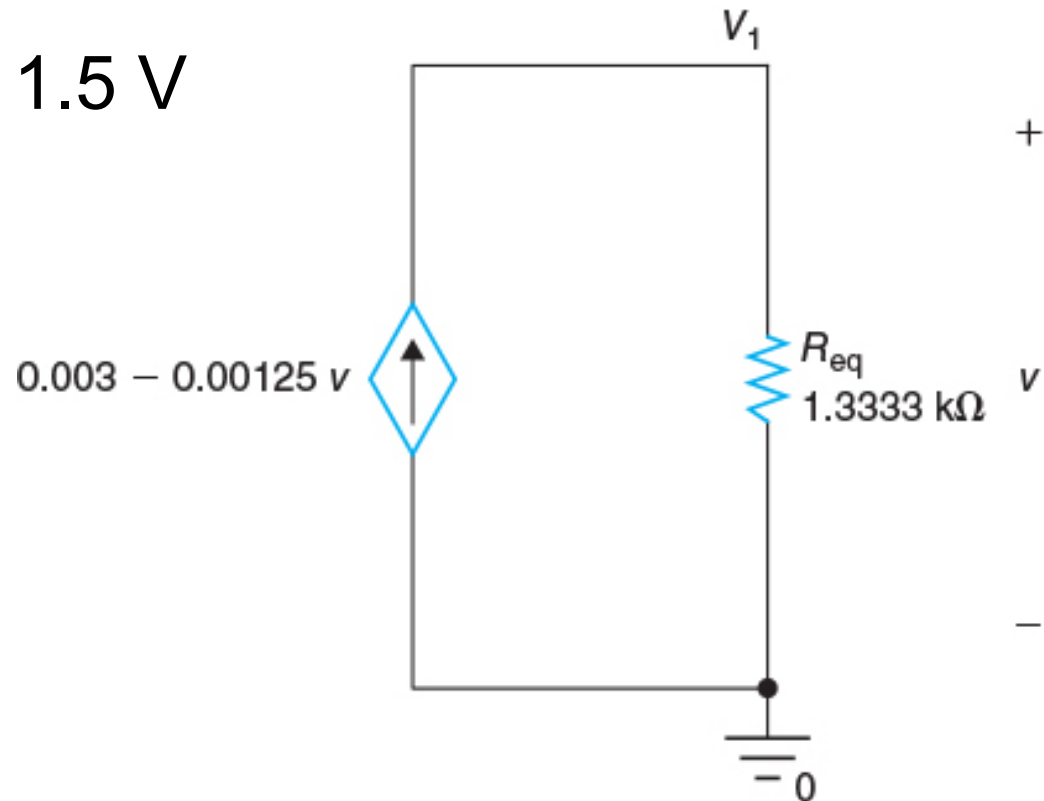EXAMPLE 4.6

- $R_{eq} = R_1 \parallel R_4 = 1.3333 \text{ k}\Omega$
- Add the currents to get $0.003 - 0.00125v$.
- $v = (0.003 - 0.00125v) \times 1333.3333 = 4 - 1.6667v$
- $v = V_1 = 4/2.66667 \text{ V} = 1.5 \text{ V}$



Summary

- Superposition principle
- Source transformations
- What will we study in next lecture.