

UESTC 3003: Electronic System Design

Static Errors


Lecture 2.4: Bias Current Blues(2)

Dr Duncan Bremner

WORLD
CHANGING
GLASGOW



A Cool Fix (If currents are **Equal**)

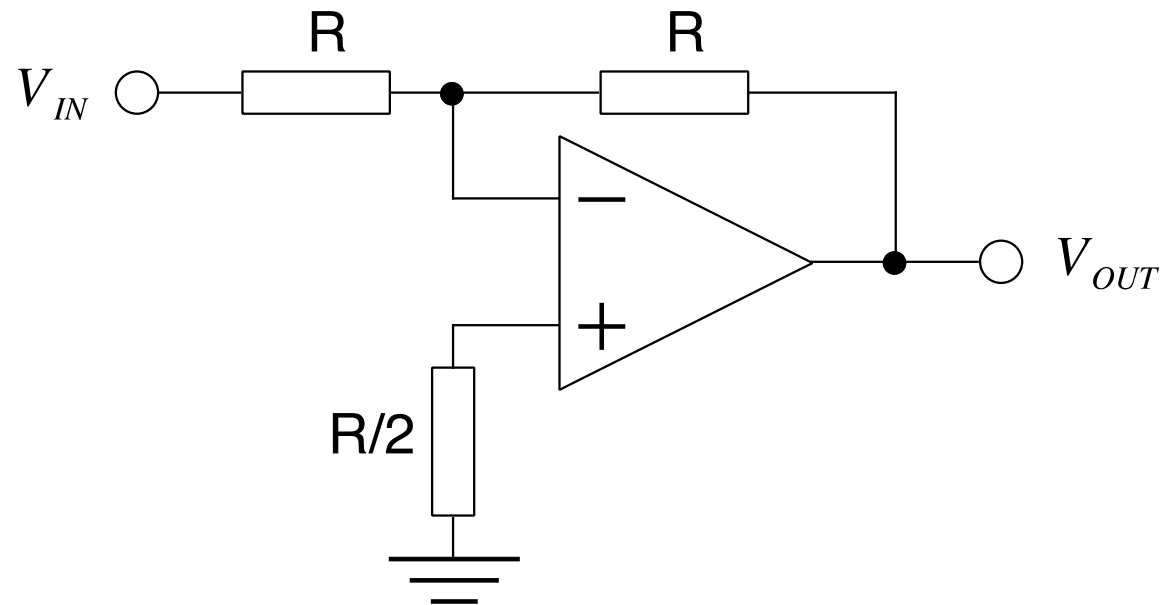


Make **DC** resistances equal at both inputs

(NOTE: Take care if there are inductors or capacitors about!)




Compensating for Equal Bias Currents

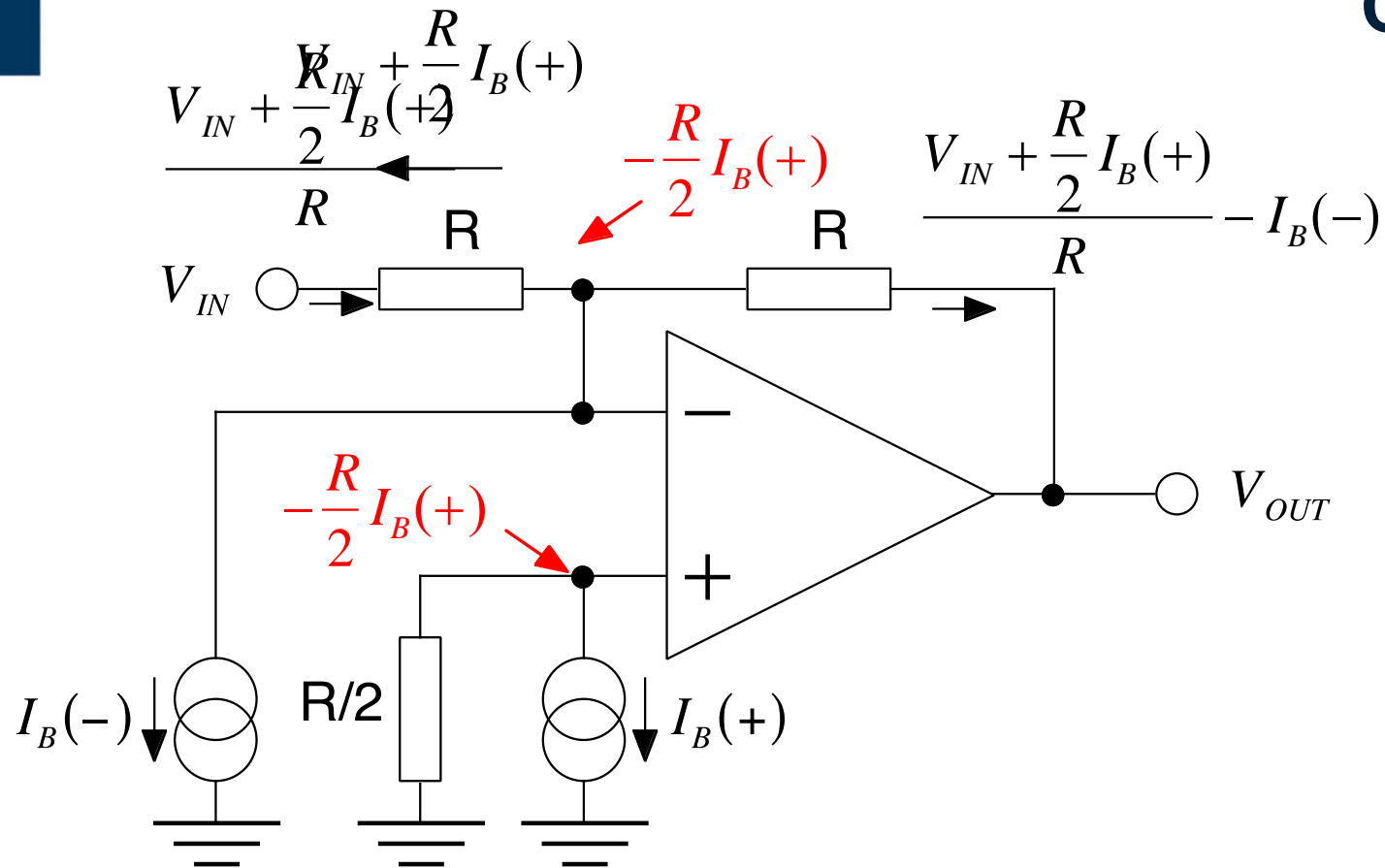

$$V_{OUT} = -\frac{R}{2}I_B(+)-V_{IN}-\frac{R}{2}I_B(+)+RI_B(-) = -V_{IN}+R(I_B(-)-I_B(+))$$

Equal Bias Currents and Gain

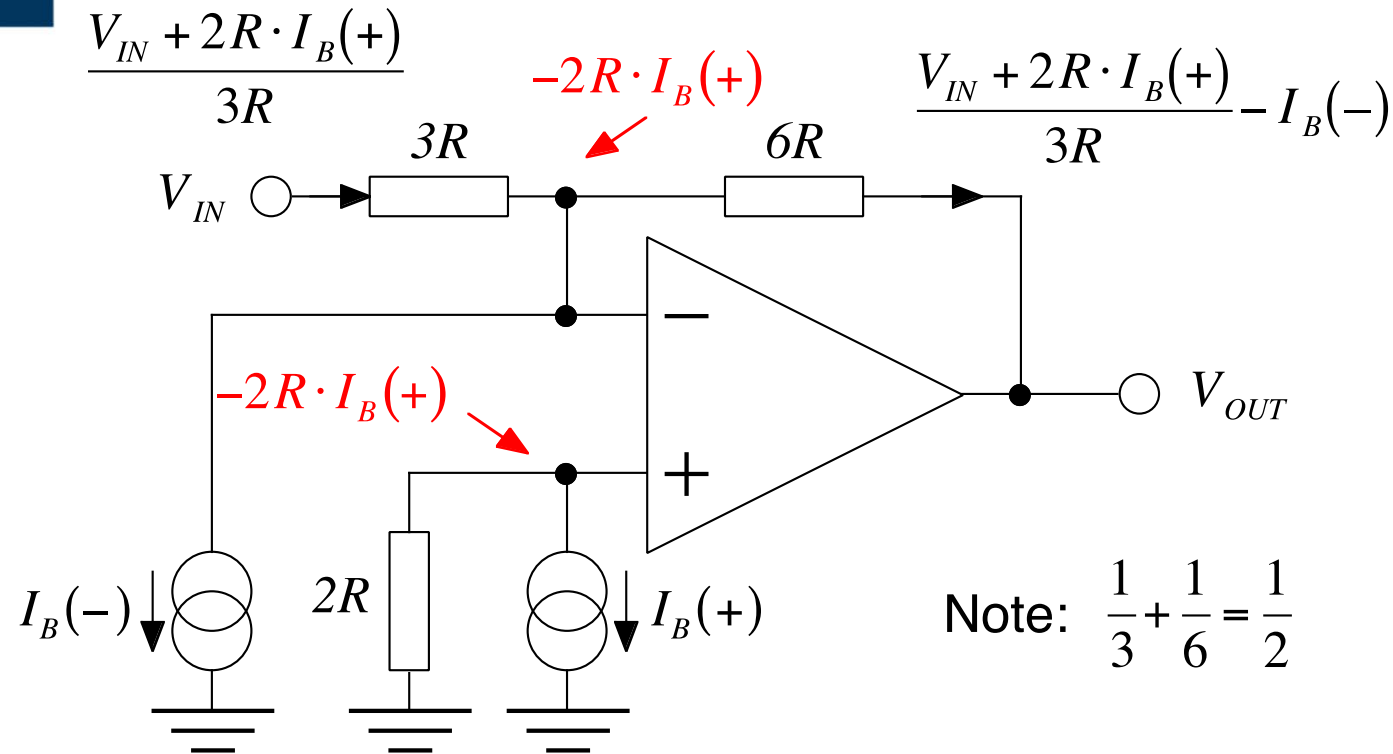

$$V_{OUT} = -2R \cdot I_B(+)-\frac{6RV_{IN}}{3R}-\frac{6R \cdot 2R \cdot I_B(+)}{3R}+6R \cdot I_B(-)$$


$$=-2V_{IN}-6R \cdot I_B(+)+6R \cdot I_B(-)=-2V_{IN}+6R(I_B(-)-I_B(+))$$



Equal Bias Currents


Equal source impedances compensate
for bias current *in general*

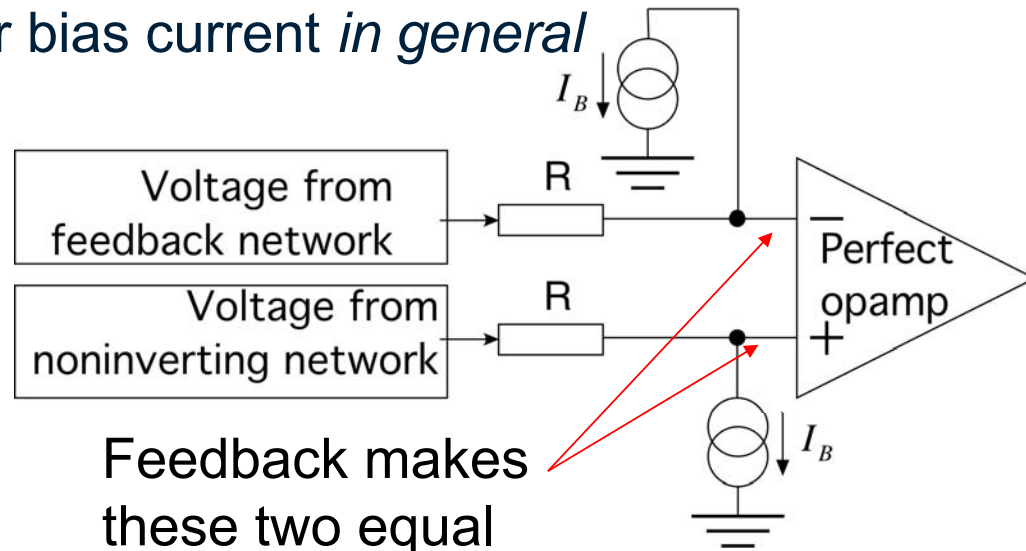R is the Thevenin
Equivalent source
resistance of the
associated network




So Voltage from FB network
Still equals the voltage from
the noninverting network

Is equivalent to

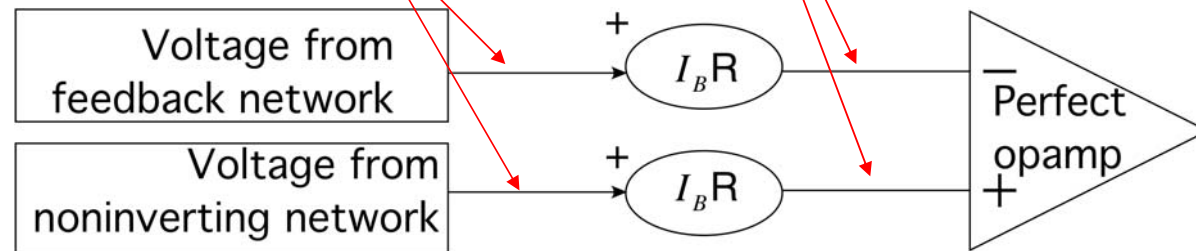

Noninverting

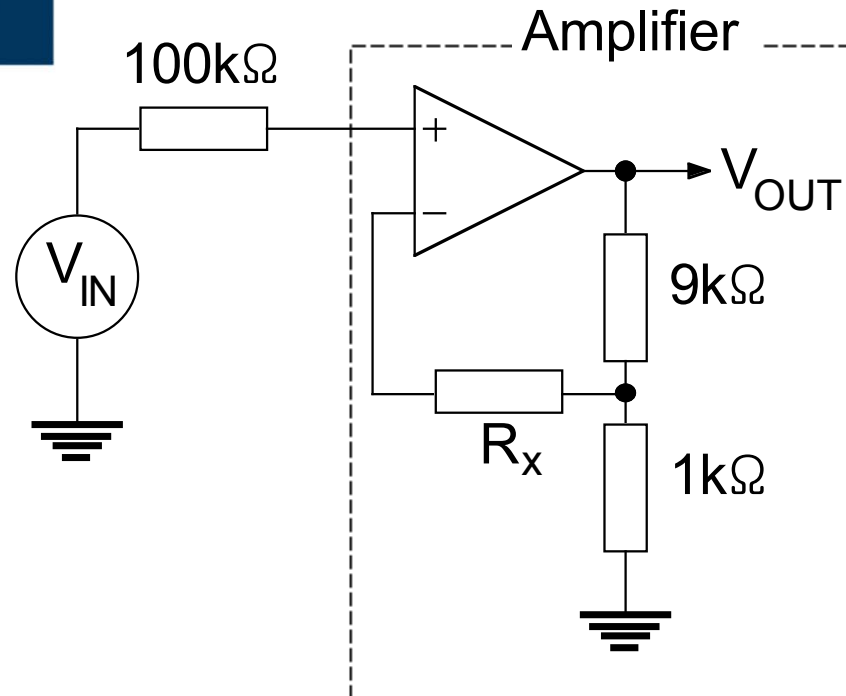

What is the required
Value of R_x ?

$$\text{Need } 1\text{k} \parallel 9\text{k} + R_x = 100\text{k}\Omega \quad R_x = 100\text{k}\Omega - 0.9\text{k}\Omega = 99.1\text{k}\Omega$$

Exercise: Show that this works! [Use $I_b(+) = I_b(-) = 150\text{nA}$]

Thank you
谢谢

INSPIRING
PEOPLE

#UofGWorldChangers



@UofGlasgow